

Embedding SHT2x in 5V Supply


Sample Scheme, ESD Protection and Material List

The new digital SHT2x humidity and temperature sensor series integrates multi-functionality on a small footprint. Due to the underlying physics of the highly integrated on-chip CMOS circuitry the supply voltage of the SHT2x is restricted to 2.2 - 3.6V. This application note provides sample schemes for embedding the SHT2x with I²C-bus (Chapter 0) and embedding of SHT2x with PWM interface (Chapter 0) into 5V power supply environment.

I²C Interface


Sample schemes

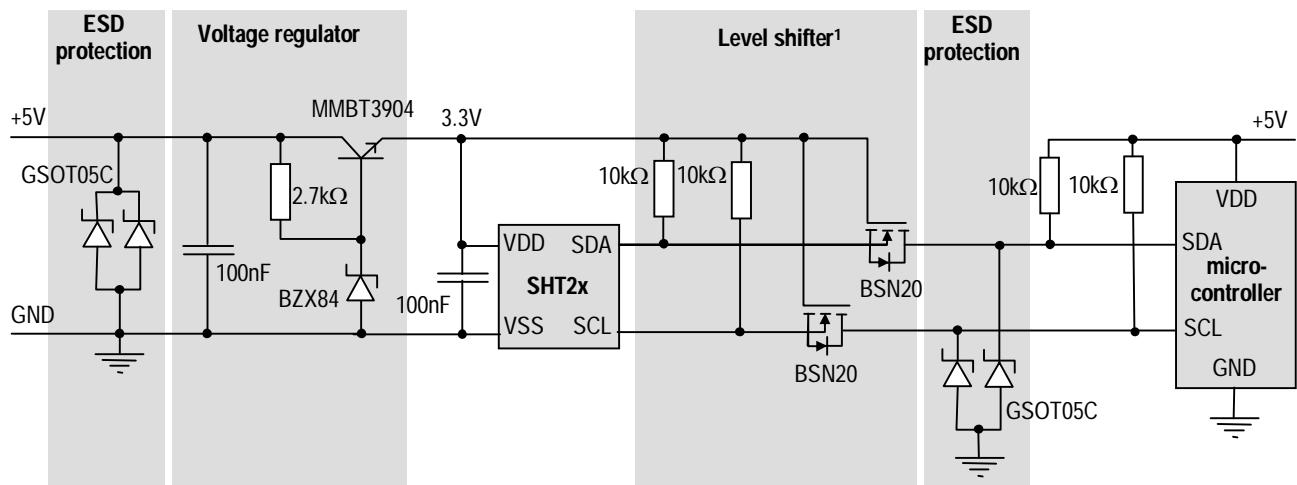Level shifter based on FET: Low cost implementation of SHT2x by voltage regulator, optional ESD protection and bi-directional FET level shifter for I²C-bus.



For more details on bidirectional level shifter for I²C-bus please refer to US 5,689,196 and Application Note AN97055 by NXP: <http://www.standardics.nxp.com/support/documents/i2c/pdf/an97055.pdf>

Level shifter based on IC:

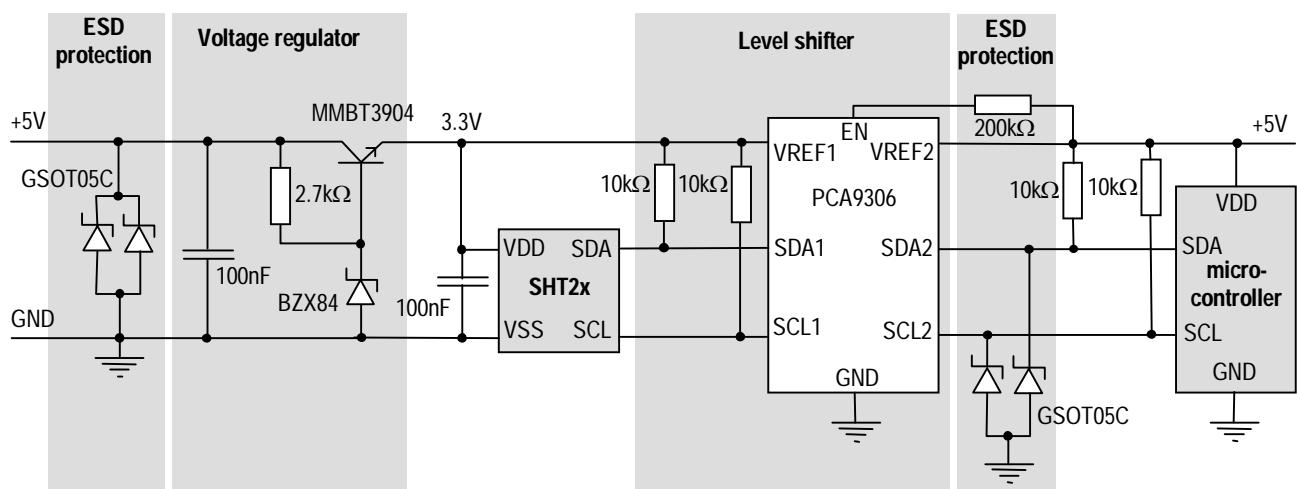

Bill of material


Component	Type	FET level shifter SDA & SCL, ESD protection	FET level shifter SDA & SCL, without ESD protection	IC level shifter SDA & SCL, ESD protection
Resistor	diverse 0603	3	3	3
Capacitor	100nF, 0603	2	2	2
Transistor	MMBT3904	1	1	1
Diodes	GSOT05C	2	0	2
Z-diode	BZX84C4V3	1	1	1
FET level shifter	BSN20	2	2	0
IC level shifter	PCA9306	0	0	1

The level shifter based on FET can be implemented at lower cost than the IC version. Please note, that the FET version is covered by patents of NXP.

PWM Interface

Following sample scheme of embedding a SHT2x device into a 5V power supply environment is optimized to save costs of external components. In comparison to the embedding with I²C protocol according to setup in Chapter 0, especially the level shifter set-up is optimized for costs. The ESD protection is recommended but not mandatory if adequate ESD precautions in production are considered.

Sample scheme – open collector output

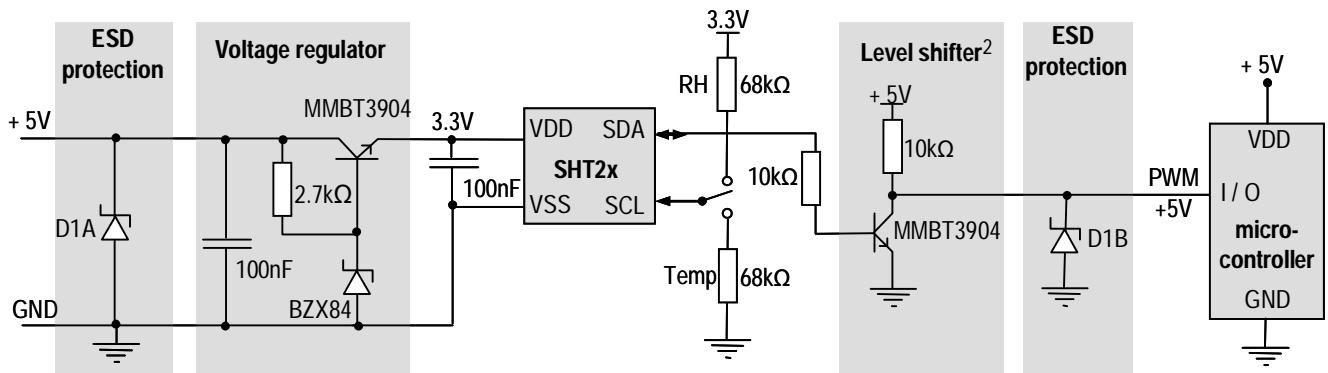

Important Notice: The level shifter transistor at the signal output does invert the PWM sensor signal.

According to the PWM interface specifications of SHT2x series, the SCL line can be drawn high for relative humidity read out or grounded for temperature read out.

Above sample scheme implements an open collector output with a bipolar transistor. If a 5V push-pull output is needed, the single line driver of type 74AHCT1G125 can be used as a level shifter instead of the transistor driver.

Bill of material

Component	Type	Transistor level shifter for SDA, ESD protection
Resistor	diverse 0603	5
Capacitor	100nF, 0603	2
Transistor	MMBT3904	2
Diodes (D1)	GSOT05C	1
Z-diode	BZX84C4V3	1

Revision History

Date	Revision	Changes
6 March 2009	1.0	Initial version (DHA)
14. July 2009	1.1	Chapter 2, PWM interface added (CLA), Sensirion CN added

Copyright © 2010 by SENSIRION.
 CMOSens® is a trademark of Sensirion
 All rights reserved

Headquarter and Sales Offices

Headquarter

SENSIRION AG
 Laubisuetistr. 50
 CH-8712 Staefa ZH
 Switzerland

Phone: + 41 (0)44 306 40 00
 Fax: + 41 (0)44 306 40 30
info@sensirion.com
<http://www.sensirion.com/>

Sales Office USA:

SENSIRION Inc.
 2801 Townsgate Rd., Suite 204
 Westlake Village, CA 91361
 USA

Phone: 805 409 4900
 Fax: 805 435 0467
michael.karst@sensirion.com
<http://www.sensirion.com/>

Sales Office Korea:

SENSIRION KOREA Co. Ltd.
 #1414, Anyang Construction Tower B/D,
 1112-1, Bisan-dong, Anyang-city
 Gyeonggi-Province
 South Korea

Phone: 031 440 9925-27
 Fax: 031 440 9927
info@sensirion.co.kr
<http://www.sensirion.co.kr>

Sales Office Japan:

SENSIRION JAPAN Co. Ltd.
 Postal Code: 108-0074
 Shinagawa Station Bldg. 7F,
 4-23-5, Takanawa, Minato-ku
 Tokyo, Japan

Phone: 03 3444 4940
 Fax: 03 3444 4939
info@sensirion.co.jp
<http://www.sensirion.co.jp>

Sales Office China:

SENSIRION CHINA Co. Ltd.
 Room 2411, Main Tower
 Jin Zhong Huan Business Building,
 Futian District, Shenzhen, PC 518048
 PR China

Phone: +86 755 8252 1501
 Fax: +86 755 8252 1580
info@sensirion.com.cn
www.sensirion.com.cn

Find your local representative at: <http://www.sensirion.com/reps>