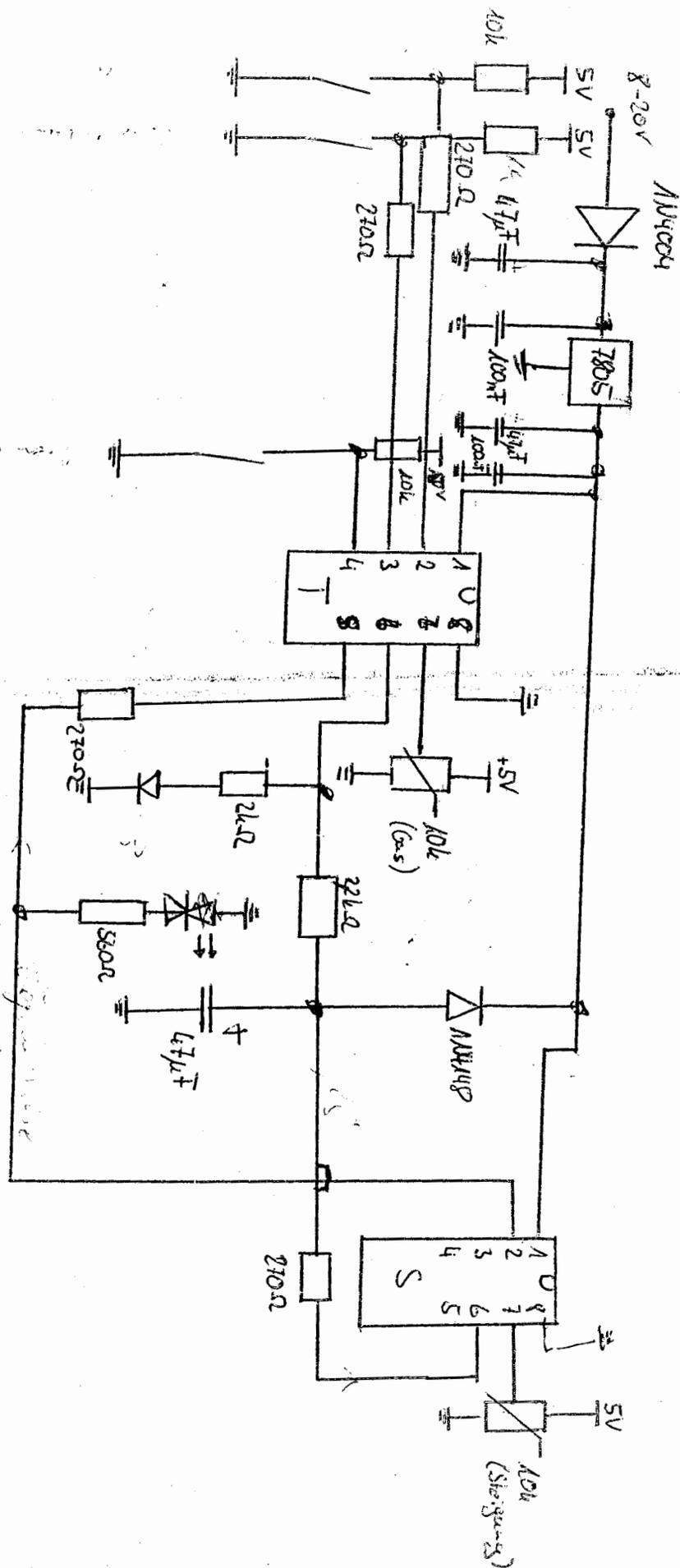


Schaltplan Temperatur



$$C = R \cdot C \approx 0,15$$

$$C = \frac{0,15}{R} = \frac{10^{-1}}{2,2 \cdot 10^3} = 0,4 \cdot 10^{-4}$$