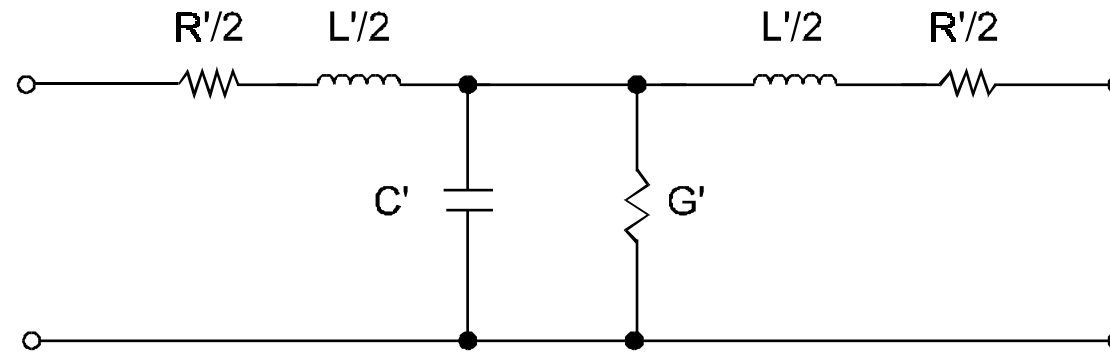


Basics and Practical Examples of Transmission



Circuit Diagram of a Transmission Line




L'	Characteristic Inductance per Unit Length	nH/cm
C'	Characteristic Capacitance per Unit Length	pF/cm
R'	Characteristic Resistance per Unit Length	Ω/cm
G'	Characteristic Conductance per Unit Length	S/cm

$$\text{Line Impedance } \vec{Z}_0 = \sqrt{\frac{j\omega L' + R'}{j\omega C' + G'}}$$



Loss-free Transmission Lines

 At high frequencies the transmission line losses on printed circuit boards in digital systems can be neglected.




With $R' \ll j\omega L'$ and $G' \ll j\omega C'$:

Line impedance	$Z_o = \sqrt{\frac{L'}{C'}}$	(real number !)
Propagation time	$\tau = \sqrt{L' \times C'}$	
Cut-off-frequency	$f_o = \frac{1}{2\pi\sqrt{L' \times C'}}$	with $L', C' \rightarrow 0 \Rightarrow f_o = \infty$



Transmission Line

 

A transmission line consists of

- a signal line which carries the signal current**
- a signal return line (mostly GND) which carries a return current of the same magnitude.**

Any DC interconnect between the GND terminals of the two circuits (e.g. safety earth) will not provide a signal return path according to the transmission line theory.

The area between the signal line and the return lines determines the capability of the circuit to radiate RF and also its immunity against EMI.

Transmission Line Theory

Rule of Thumb:

The transmission line theory has to be applied, when the rise time of the signal is shorter than twice the propagation time.

Example 1 : Twisted pair cable; $\tau = 5 \text{ ns/m}$; $t_r = 2 \text{ ns}$

$$L = \frac{t_r}{2\tau} = \frac{2 \text{ ns}}{2 \times 5 \text{ ns/m}} = 0.2 \text{ m}$$

Example 2 : Bus Line; $t = 20 \text{ ns/m}$; $t_r = 2 \text{ ns}$

$$L = \frac{t_r}{2\tau} = \frac{2 \text{ ns}}{2 \times 20 \text{ ns/m}} = 0.05 \text{ m}$$

With shorter signal lines all line reflections occur during the rise/fall time of the signal. In this case it is allowed to use the simplified capacitive load line model.







Typical Line Impedances


	L' (nH/cm)	C' (pF/cm)	Z (Ω)	τ (ns/m)
SINGLE WIRE (FAR AWAY FROM GND)	20	0.06	600	~ 4
SPACE	μ_0	ϵ_0	370	3,3
TWISTED PAIR CABLE	5-10	0.5-1	80-120	5
FLAT CABLE (ALTERNATING SIGNAL AND GND WIRE)	5-10	0.5-1	80-120	5
WIRE ON PC BOARD	5-10	0.5-1.5	70-100	~ 5
COAX CABLE	2,5	1.0	50	5
BUS LINE	5-10	10-30	20-40	10-20



   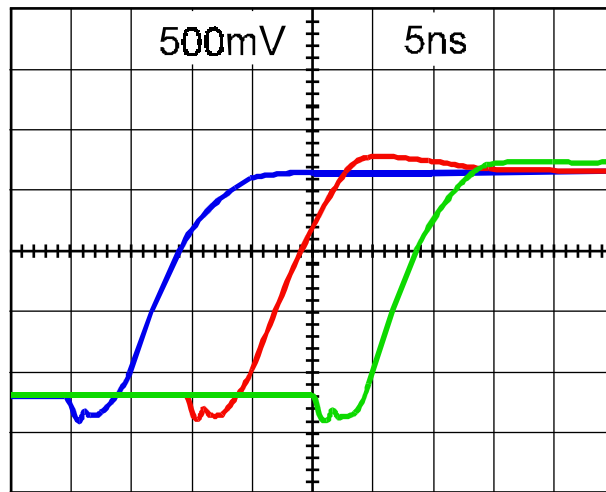
Waveforms with Transmission Lines and Capacitive Load





Analysis of Line Reflections

 

Waveforms caused by Line Reflections

 

Lattice Diagram

  

$$\rho_A = \frac{30 - 75}{30 + 75} = -0.429$$

$$\rho_B = \frac{100 - 75}{100 + 75} = 0.143$$

$$V_o = 3.70 \text{ V}$$

$$V_a = V_o \times 75 \Omega / (75 \Omega + 30 \Omega) = 2.64 \text{ V}$$

$$V_{r1} = 2.64 \text{ V} \times 0.14 = 0.37 \text{ V}$$



$$V_{r2} = 0.37 \text{ V} \times (-0.42) = -0.16 \text{ V}$$

$$V_{r3} = -0.16 \text{ V} \times 0.14 = -0.02 \text{ V}$$

$$V_{r4} = -0.02 \text{ V} \times (-0.42) = 0.009 \text{ V}$$



Bergeron Diagram

 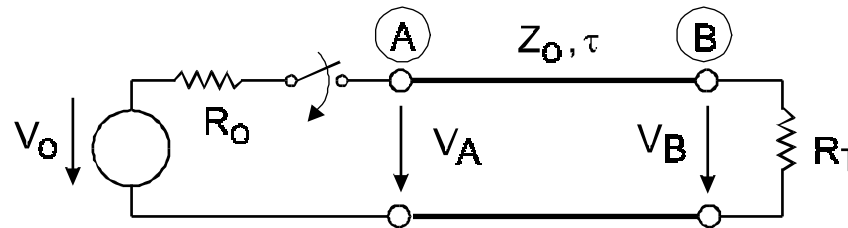





Voltage changes only after twice the propagation time. Incident wave is independent from line termination.

$$V_{A(0 < t < 2\tau)} = V_0 \times \frac{Z_0}{R_0 + Z_0}$$



Steady state condition:

$$V_{(t=\infty)} = V_0 \times \frac{R_T}{R_0 + R_T}$$







Line Reflections - Special Cases

    



- - - - - LINE START
 ———— LINE END

  

Line Reflections - Special Cases

      

Measurement of the Line Impedance

  

$$Z_0 = \frac{R_0^{*})}{V_o / V_a - 1}$$


$$\tau \times Z_0 = L'$$

$$\tau / Z_0 = C'$$


*) Note: $R_0 = 50 \Omega // 50 \Omega = 25 \Omega$

Line Reflections

Open Circuit

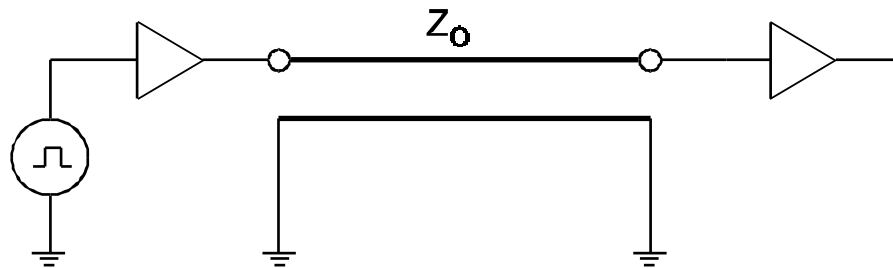


 An open circuit at the line end causes under- and overshoots which may exceed the maximum rated input voltage of the receiving circuit.



The following over- and undershoots may cross the threshold voltage of the receiver several times and may generate system errors.


Line Reflections Terminated Line

 






Line reflections are eliminated by a correct line termination.

A mismatch up to 50% is acceptable.

 Note: - Increased Power Dissipation
- High drive Capability required.





Line Termination Circuits

  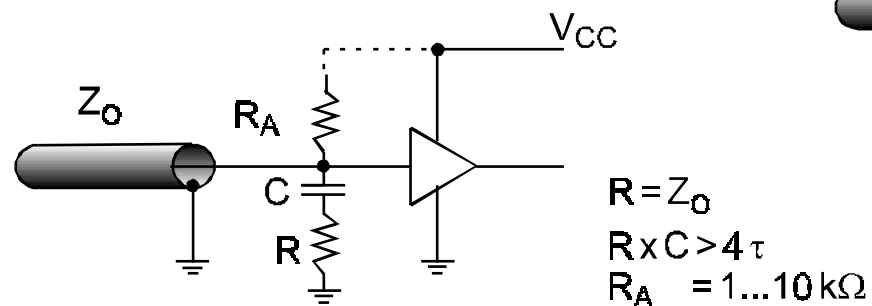 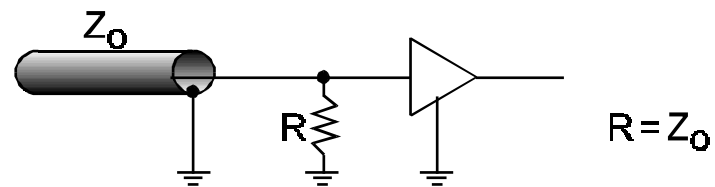

**Mismatch of 50%...100% acceptable
 (with low impedance bus lines up to
 400%).**

Line Reflections

Matching of Generator Impedance

  

Under- and overshoots are avoided by matching the output impedance of the line driver to the line impedance by means of a series resistor. Power dissipation is not increased (recommended in CMOS systems).

Note: Undefined logic levels along the transmission line for up to twice the propagation time.


Circuits with built-in serial termination (25Ω to 30Ω):

8 Bit: SN74ABT2244

16 Bit: SN74ABT162244


18 Bit: SN74ABT162501

Line Reflections Clamping Diodes

 

Clamping diodes at the end of the transmission line absorb the energy of under- and overshoots and ensure a clean signal waveform.

 Input circuits of logic ICs contain these clamping diodes.



Note: The clamping diodes of VLSI circuits are often not capable to handle the high currents generated by line reflections (parasitic transistors!). Provide additional Schottky clamping diodes!


Schottky Diode Arrays:

SN74S1050, SN74S1051, SN74S1052, SN74S1053,
SN74S1056, SN74F1056, SN74F1016, SN74F1018

Bus Termination Arrays

Released Functions :



 
SN74S1050 12-Bit Schottky Diode Array
SN74S1051 12-Bit Schottky Diode Network
SN74S1052 16-Bit Schottky Diode Array
SN74S1053 16-Bit Schottky Diode Network
SN74S1056 8-Bit Schottky Diode Array
SN74F1056 9-Bit Schottky Diode Array
SN74F1016 16-Bit Schottky Diode
R-C Bus Termination Array
SN74F1018 18-Bit Schottky Diode
R-C Bus Termination Array



Applications :

- ★ Arrays in TTL systems
- ★ Networks in CMOS systems (positive overshoots)
- ★ Small buses, e.g. Memory Arrays
- ★ System bus in personal computers

Clamping Circuit TL7726

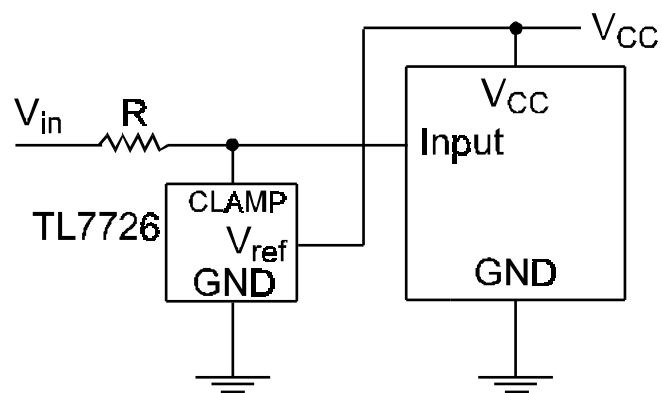  

★ The clamping circuit TL7726 protects sensitive analog and digital inputs against excessive overvoltages and by that ensures the function of the circuit.