



$$\frac{U_- - U_E}{R} + \frac{U_- - U_A}{R} = 0$$

$$U_- = \frac{U_A + U_E}{2}$$

$U_+ = U_-$ wegen virtueller Masse

$$\frac{U_+ - U_E}{R} + U_+ j\omega C = 0$$

$$U_+ (1 + j\omega RC) = U_E$$

$$\frac{U_A + U_E}{2} (1 + j\omega RC) = U_E$$

$$U_A (1 + j\omega RC) = 2U_E - U_E (1 + j\omega RC)$$

$$U_A = U_E \frac{1 - j\omega RC}{1 + j\omega RC}$$

= Allporm