

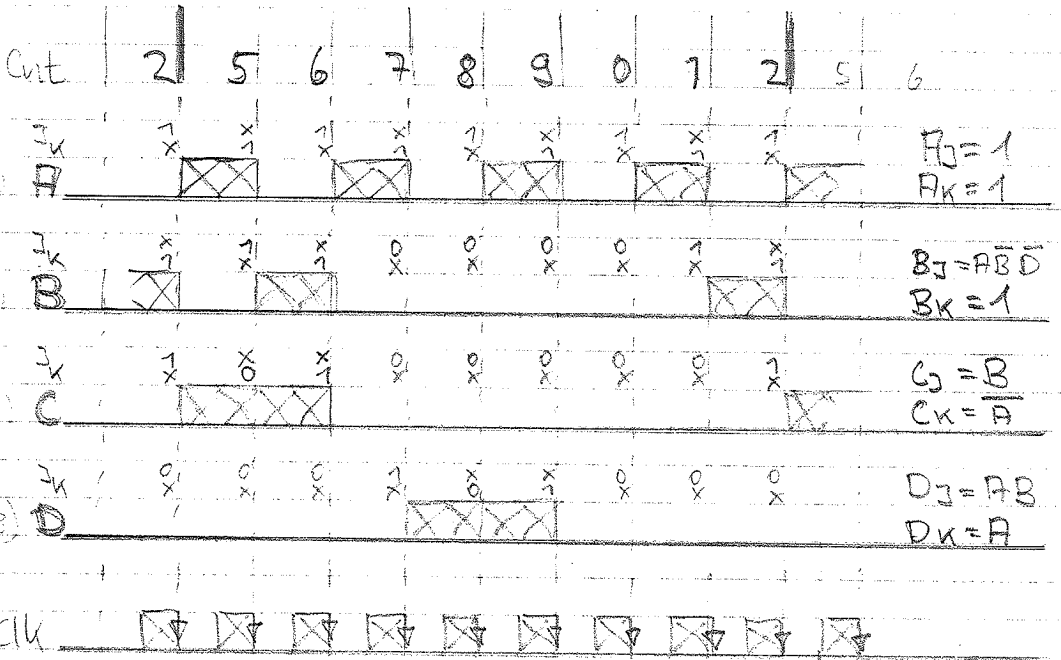
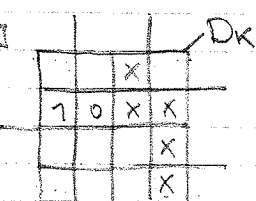
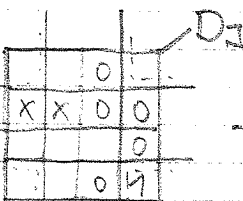
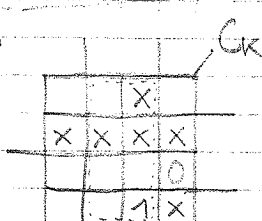
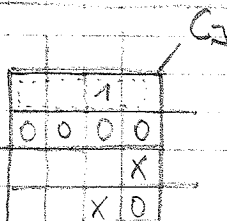
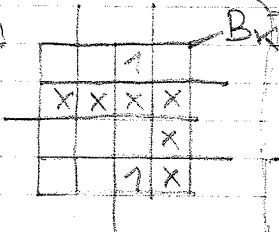


CUX

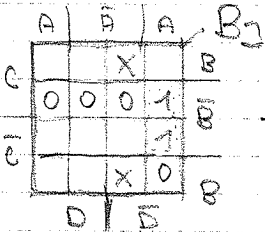

J-K-FF

| J | K | Q_{n+1} |
|---|---|------------------|
| 0 | 0 | Q_n |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $\overline{Q_n}$ |

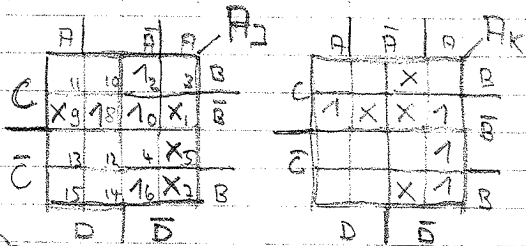

freie kanten sind dont care = X