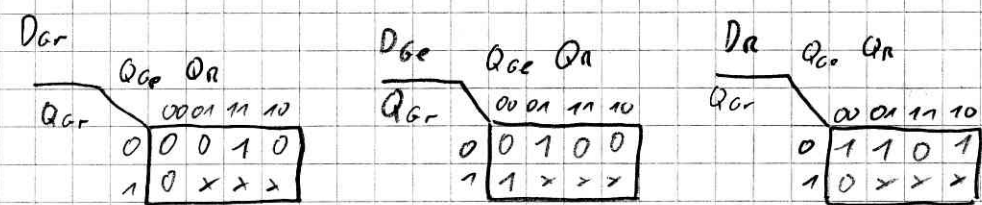



I <sub>n</sub>			I <sub>n+1</sub>					
Q <sub>Gr</sub>	Q <sub>Ge</sub>	Q <sub>R</sub>	Q <sub>Gr</sub>	Q <sub>Ge</sub>	Q <sub>R</sub>	D <sub>Gr</sub>	D <sub>Ge</sub>	D <sub>R</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	1
0	1	0	0	0	1	0	0	1
0	1	1	1	0	0	1	0	0
1	0	0	0	1	0	0	1	0
1	0	1				x	x	x
1	1	0				x	x	x
1	1	1				x	x	x



$$D_{Gr} = Q_{Ge} Q_R$$

$$D_{Ge} = Q_{Gr} \overline{Q_{Ge}} \vee \overline{Q_{Ge}} Q_R = \overline{Q_{Ge}} (Q_{Gr} \vee Q_R)$$
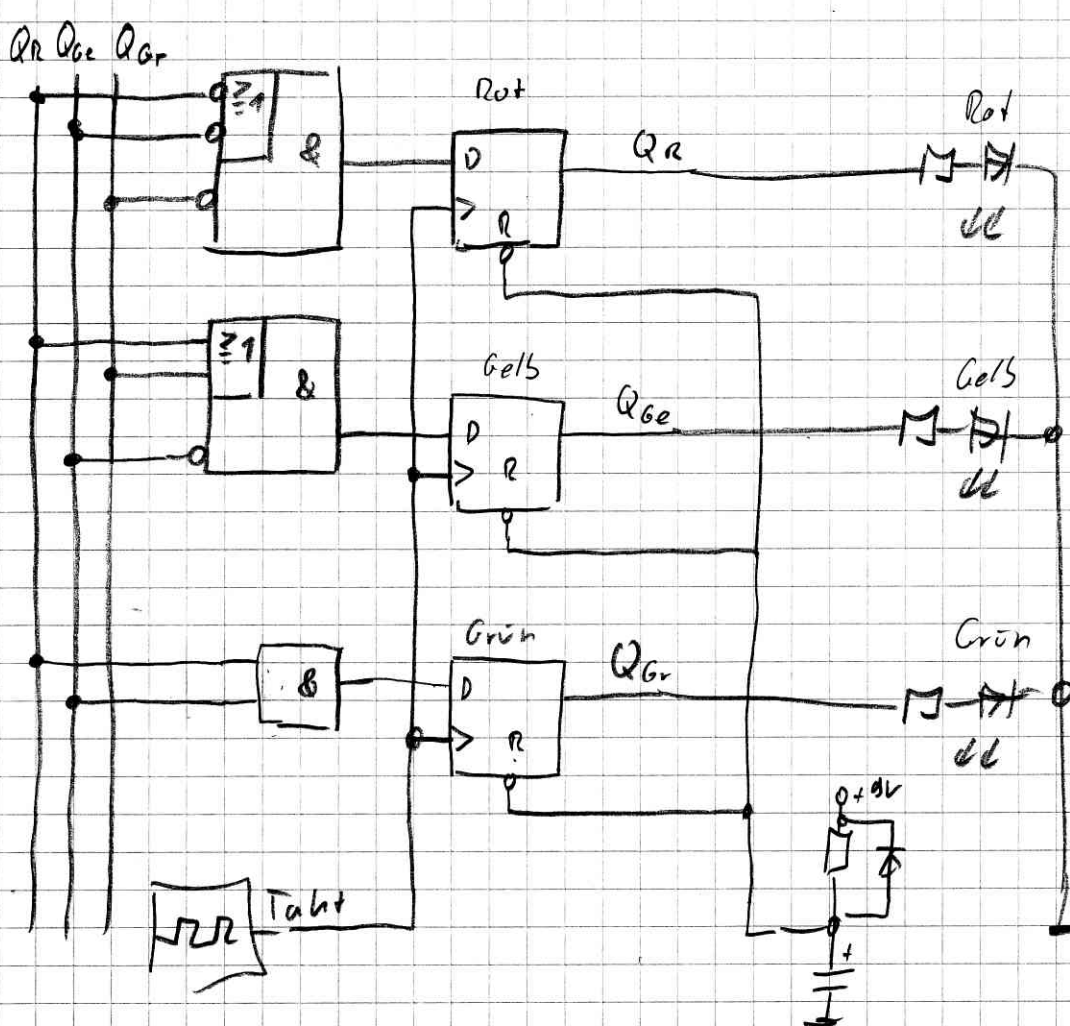
$$D_R = \overline{Q_{Gr}} \overline{Q_{Ge}} \vee \overline{Q_{Gr}} \overline{Q_R} = \overline{Q_{Gr}} (\overline{Q_{Ge}} \vee \overline{Q_R})$$



Lösung von Ganymed  
aus microcontroller.net

19.04.2009