



Figure 1 This low-dropout-voltage regulator features a noise floor of only $6 \text{ nV}/\sqrt{\text{Hz}}$, making it an ideal power source for low-noise oscillators.