

Divide by 2.5

 


Figure 2

Divide by 2.5 in Two CLBs

This circuit divides the clock by 2.5, generating 40 MHz from a 100 MHz input for example (Figure 2). Three flip-flops form a $\div 5$ circuit, and the G and H look-up tables together generate two output periods at the H output. The first output pulse is driven by the A flip-flop, the second output pulse is derived from the B AND C signal, but is delayed half an incoming clock cycle. The output stays Low while the clock is High, and stays High after B has gone Low, until the clock goes Low again. It is this latch circuit that may cause simulator problems.

Divide by 5 with 50% Output Duty Cycle

This two-CLB circuit divides the clock by five and maintains a 50/50 output duty cycle (Figure 3). Three flip-flops form a $\div 5$ circuit, and the G look-up tables generate the divided output. The first output pulse is started by the A flip-flop and terminated by the B flip-flop, when the clock is Low. It is this latch circuit that may cause simulator problems.

Divide by 5

 


Figure 3

Divide by 3 with 50% Output Duty Cycle

This one-CLB circuit divides the clock by three, and maintains a 50/50 output duty cycle (Figure 4). The two flip-flops form a $\div 3$ circuit, and the G look-up tables generate the divided output. The first output pulse is started by the A flip-flop and terminated by B flip-flop, when the clock is Low. It is this latch circuit that may cause simulator problems. Σ

Divide by 3

 


Figure 4