

PASSIVE LOSSLESS SNUBBERS FOR HIGH FREQUENCY PWM CONVERTERS

Sam Ben-Yaakov and Gregory Ivensky

**Power Electronics Laboratory
Department of Electrical and Computer Engineering
Ben-Gurion University of the Negev**

**P. O. Box 653, Beer-Sheva 84105, ISRAEL
Tel: +972-7-646-1561; Fax: +972-7-647-2949**

Email: sby@ee.bgu.ac.il

March 1999

OUTLINE

Chapter 1. Introduction

- 1. Seminar objectives**
- 2. Hard versus soft switching**
- 3. Diode reverse recovery**
- 4. IGBT behavior under hard switching**
- 5. Why soft switching?**
- 6. Soft switching terminology**
- 7. Soft switching by passive lossless snubbers**
- 8. Simulation tools**

Chapter 2. Passive lossless snubbers perspective

- 1. Passive lossless snubber approaches**
- 2. Snubbers evolution**
- 3. The switched inductor (SIM) model**
- 4. Basic switching cell of common PWM converters**
- 5. Fundamental principles**
- 6. Practical aspects**

Chapter 3. Basics of resonant networks

- 1. Reset of resonant elements**
- 2. Resonant networks - the vehicle of snubbing and energy circulation**
- 3. Basic resonant network parameters**
- 4. Ideal LC-network with ideal diode fed by a voltage source V_s**
- 5. Some trivial cases and practical aspects**
- 6. Resonant inductor design**

Chapter 4. Switch turn-off lossless snubbers

- 1. The 'one way' capacitor. Versions 1 and 2 (SNB1 & SNB2)**
- 2. Switch turn-off lossless snubber (SNB3)**
- 3. Applying snubber SNB3 in a flyback converter**
- 4. Applying snubber SNB3 in a forward converter**
- 5. A switch turn-off lossless snubber for a boost converter (SNB4)**

Chapter 5. Switch turn-on and diode turn-off snubbers

- 1. Flyback reset snubber. Versions 1 and 2 (SNB5 & SNB6).
Practical aspects**
- 2. Low stress turn-on snubber (SNB7). Experimental results.
Implementation in APFC**
- 3. RMS current of the snubber inductor in a boost converter
implemented in APFC**

Chapter 6. Turn-on and turn-off single switch snubbers

- 1. Generic LCC 'turn off' & 'turn on' snubber topology**
- 2. Boost converter with LCC snubber: D type 'on' and S type
'off' (SNB8)**
- 3. Some additional recent turn-on & turn-off passive lossless
LCC snubbers (SNB9 - SNB12)**
- 4. LCC snubbers with improved reset (SNB13)**
- 5. Boost converter with LLC-type snubber (SNB14)**

- 6. Buck converter with LC-type snubber (SNB15)**
- 7. Turn-on, turn-off and turn-on - turn-off snubbers. Can parasitic elements be used?**

Chapter 7. Rectifier diodes lossless snubbers

- 1. Phase shifted PWM (PSPWM) converters**
- 2. Residual issues in PSPWM**
 - 2.1. Circulating current. Lossless output snubbers SNB16 & SNB17**
 - 2.2. Rectifier's diodes reverse recovery. Possible remedy-saturable reactor. Snubber SNB18**
- 3. Experimental PSPWM converter**
- 4. Improved magnetic snubber for rectifier diodes in DC/DC converters (SNB19)**

Chapter 8. Combining snubber and power supply functions

- 1. Turn-off snubber with energy recovery back to the input or into a local power supply (SNB20)**
- 2. A local power supply with turn off snubber features**
- 3. Application of proposed power supply in a boost APFC**

Conclusions

References



Chapter 1

INTRODUCTION

SEMINAR OBJECTIVES

- To demonstrate the use and benefits of passive lossless snubbers in modern high frequency power electronics design.
- Relevant topologies
- Soft switching
- Parasitic effects
- Limitation - pros & cons

HARD VERSUS SOFT SWITCHING

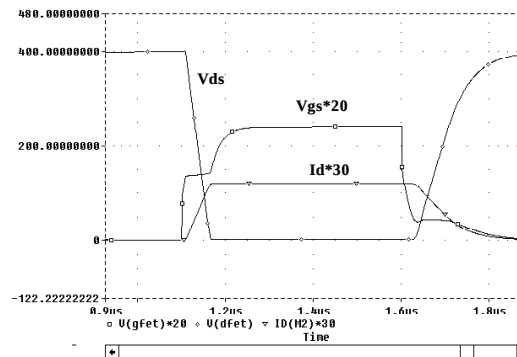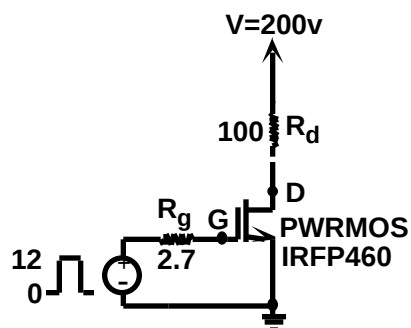


MOSFET switching stage

Switching waveforms
(simulation)


- Switching losses are proportional to switching frequency



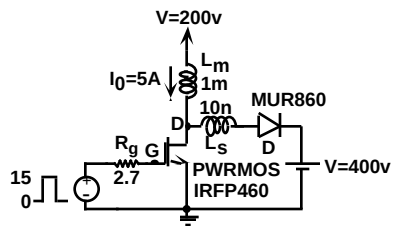Modern simulators include switching behavior




Hard switched boost stage

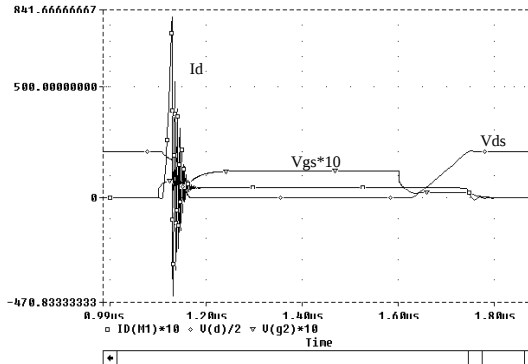

**Basic waveforms
(simulation)**


- * **Diode reverse current and parasitic oscillations**
- * **Natural 'softening' at 'turn off'**
 - 'Turn On' more troublesome in MOSFETS
 - 'Turn On' & 'Turn off' problematic for IGBT -> ZCS

Diode Reverse Recovery [25, 39]

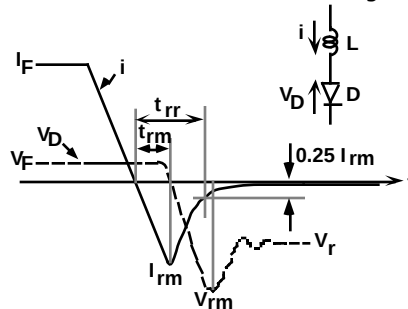


- **Low voltage drop on diode in reverse recovery period**
- $\frac{di}{dt} = \frac{V}{L}$
- **High reverse currents**
- **High reverse voltage**
- **Parasitic oscillations**

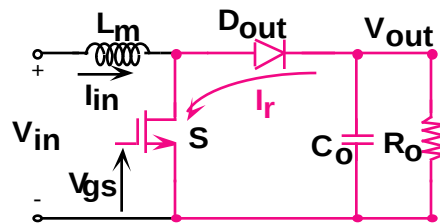The reverse recovery problem in Boost topology




- Short circuit against V_{out}
- Occurs in all topologies

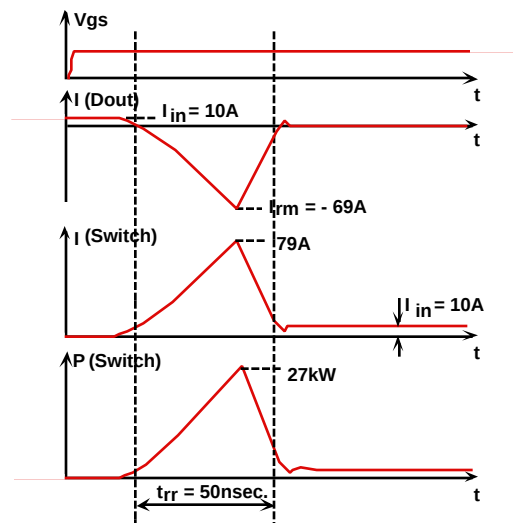The reverse recovery problem in Boost topology




- High reverse currents
- High losses
- EMI emission

Dependence on L

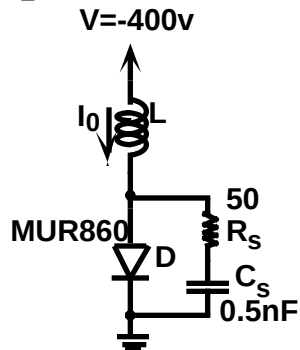

Diode switching circuit - reverse recovery

Dependence on L - Simulation

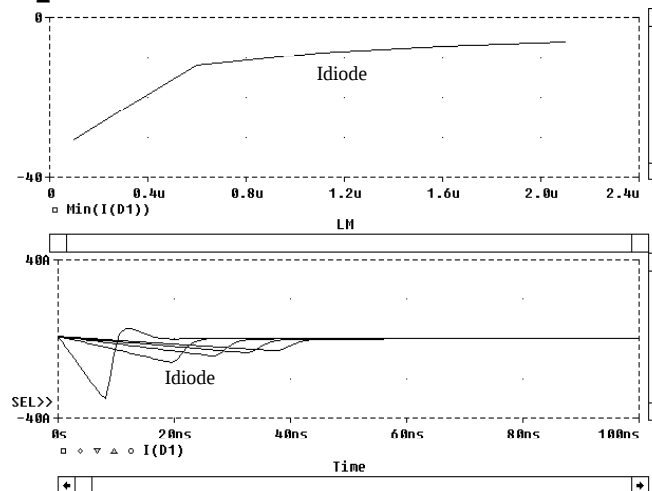

Diode reverse recovery switching waveforms

- 👁 **Very high reverse currents**
- 👁 **A function of series inductance**
- 👁 **Detrimental effect in isolated and non isolated converters**
- 👁 **Becomes very important in high switching frequency**

Trapped Energy as L becomes Larger


Assume: t_{rm} constant

Peak reverse current : $I_{rm} = \frac{V}{L} t_{rm}$


Trapped energy $E = \frac{1}{2} (I_{rm})^2 L = \frac{(V t_{rm})^2}{2L}$

- Trapped energy decreases as L becomes larger
- Adding inductance ---> Advantageous

Center Tap Rectifier

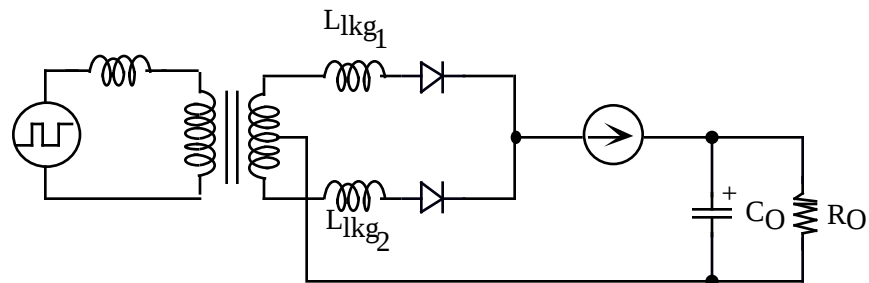

Leakage inductance at secondary

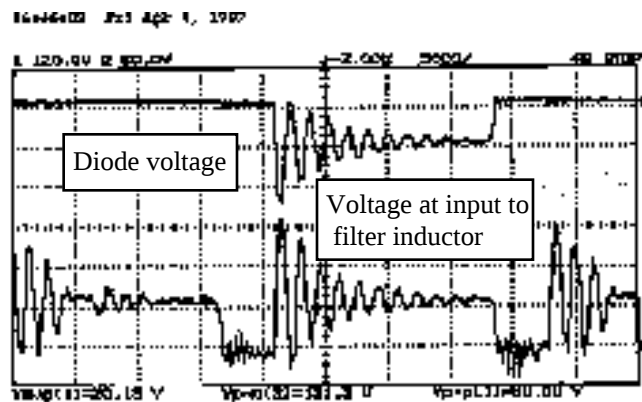


Experimental waveforms (no diode snubber)

- Greatly influenced by transformer leakage
- Forces the use of high voltage diodes


IGBT BEHAVIOR UNDER HARD SWITCHING

[5, 16, 20, 21, 38]

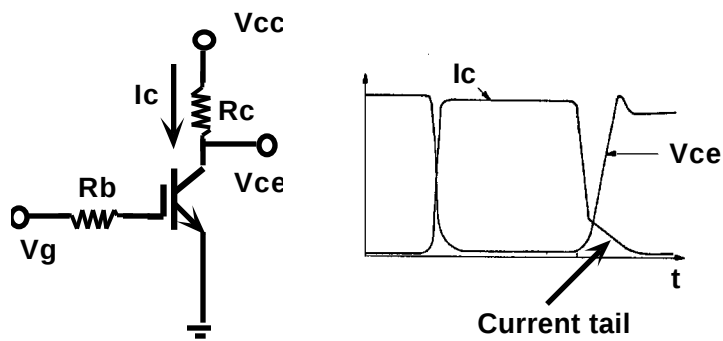


- * **Current tail due to stored minority carriers**
- * **Switching losses increase linearly with switching frequency**
- * **Switching frequency limit is at about 25 kHz**


Why Soft Switching ?

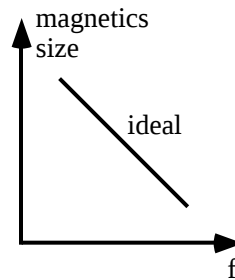

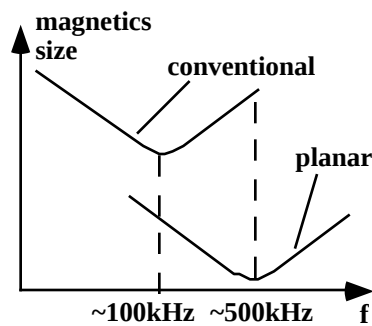Ideal Size/Switching frequency relationships




Practical size realization

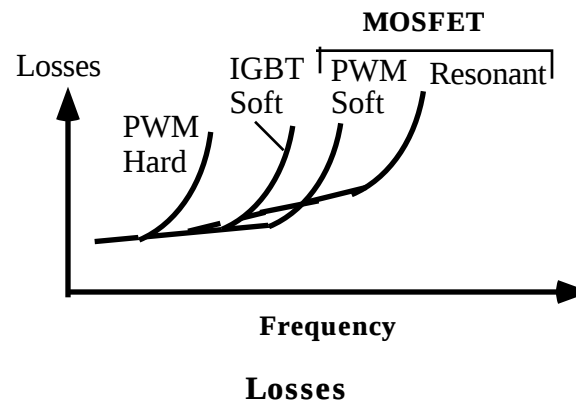

👁 Conflicting constraints

/ Soft switching helps to reduce EMI emission ???

SOFT SWITCHING TERMINOLOGY

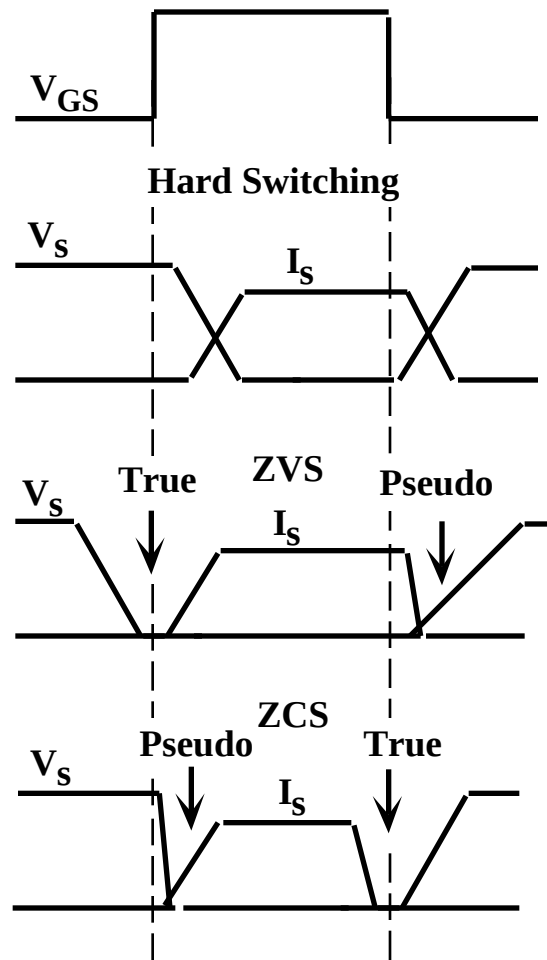


'True' soft switching calls for external active circuitry



'Pseudo' soft switching by lossless snubbers

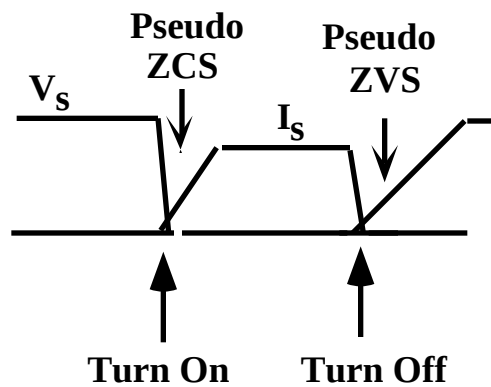Soft Switching by Passive Lossless Snubbers



- For MOSFETs -> OK
- For IGBTs -> ZCS at 'turn off' might be more desirable (current tail)
- This can not be accomplished with a Passive Snubber unless operating in constant 'off' time (quasi-resonant)

SIMULATION TOOLS

- 4 **Modern device models account for switching behavior**
 - * **Old Models DO NOT account for switching behavior**
 - * **Difficult to account for PCB parasitics**
 - * **Simulation of switching losses is still unreliable**
- P **Cycle-by-Cycle simulation**
 - 4 **Can faithfully describe the basic switching phenomena**
 - 4 **Very useful tool to examine snubber operation**
- P **Average Simulation [3]**
 - 4 **Can account for snubber effect on dynamics**
 - 4 **Can be used to design the feedback loop**

**MODEL MUR860 D (IS=783U RS=30M N=4.82 BV=600
IBV=10U
+ CJO=330P VJ=.75 M=.333 TT=79.2N)
* Motorola 600 Volt 8 Amp 55M us Si Diode 02-24-1994**


**.MODEL DN5406 D (IS=2.68P RS=7.31M N=1.17 BV=900
IBV=10U
+ CJO=124P VJ=.6 M=.333 TT=14.4U)
* Motorola 600 Volt 3 Amp 15 us Si Diode 11-23-1990**

- **Parameters can be changed to test various aspects, e.g.TT for reverse recovery**

```
.SUBCKT IRF150 10 20 30
*   TERMINALS: D G S
M1 1 2 3 3 DMOS L=1U W=1U
RG 20 2 5.35
RD 10 1 4.3M
RDS 1 3 635K
CGD 4 1 2.75N
RCG 4 1 10MEG
MCG 4 5 2 2 SW L=1U W=1U
ECG 5 2 2 1 1
DGD 2 6 DCGD
MDG 6 7 1 1 SW L=1U W=1U
EDG 7 1 1 2 1
DDS 3 1 DSUB
LS 30 3 7.5N
.MODEL DMOS NMOS (LEVEL=3 VMAX=1.6MEG THETA=265.6M
VTO=3.3
+ KP=9 RS=8.12M IS=2.01P CGSO=2.65M)
.MODEL SW NMOS (LEVEL=3 VTO=0 KP=.45)
.MODEL DCGD D (CJO=2.75N M=.5 VJ=.41)
.MODEL DSUB D (IS=2.01P RS=5.20M VJ=.8 M=.4 CJO=2.60N
TT=720N)
.ENDS
*   IR 100 Volt 28 Amp 45M Ohm N-Channel Power MOSFET 11-20-
1990
```

Chapter 2

PASSIVE LOSSLESS SNUBBERS PERSPECTIVE

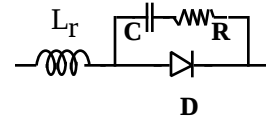

RC SNUBBERS - Diode RC snubber

LOSSES $P_{d(\min)} = \left\{ \frac{(2 V_o)^2 C}{2} \right\} f_s$; $P_{d(lkg)} = \left\{ \frac{(I_{pkr})^2 L_{lkg}}{2} \right\} f_s$

$P_{d(\min)}$ = minimum losses

V_o = output voltage

C = snubber capacitor

I_{pkr} = peak reverse current

f_s = switching frequency

L_{lkg} = leakage inductance



Resistor dissipation may reach 10's of Watts

PASSIVE LOSSLESS SNUBBER APPROACHES

1. Snubbing in multiple switch configuration (e.g. half bridge)
2. Auxiliary (dual) switch snubbers [4, 15, 33, 37]
3. Snubbers in single switch configuration (references given below)

No. # 1: Most effective

- Few extra components => economical

No. # 2: Effective but costly

- Calls for extra switches and drives
- Diminishing return

No. # 3: Good compromise

- Only passive elements needed
- Proven to improve efficiency
- Potentially lowers EMI emission

* This seminar will concentrate on single switch and diode snubbers for PWM converters

Snubbers Evolution


- SCR (1): RC snubbers - high losses
- SCR (2): Lossless Snubbers - help to turn off devices
- PWM (1): RC Snubbers - high losses
- PWM (2): Quasi Resonant - high stresses and conduction losses
- PWM (3): Auxiliary Switch - complex
- PWM (4): Lossless Snubbers -optimal (as of now)




Passive Lossless Snubbers are comparable in performance to the Dual Switch approaches but are less expensive !

The Switched Inductor (SIM) Model

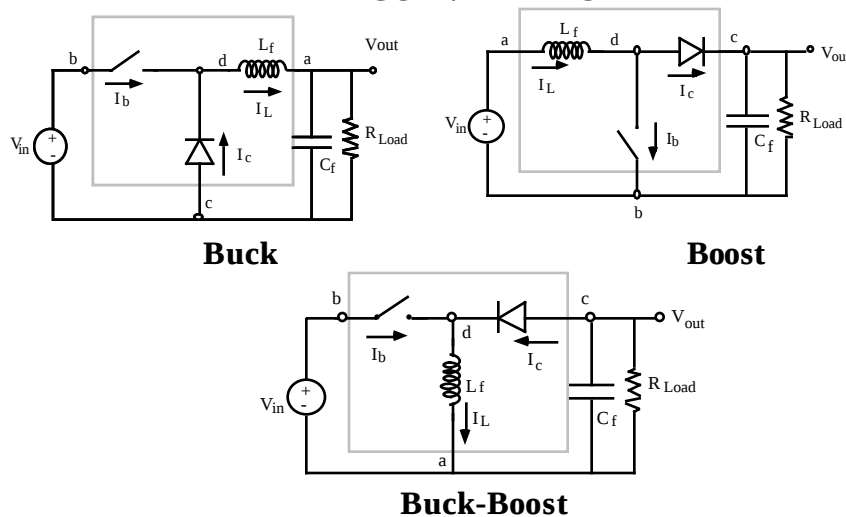BASIC SWITCHING CELL OF COMMON PWM CONVERTERS



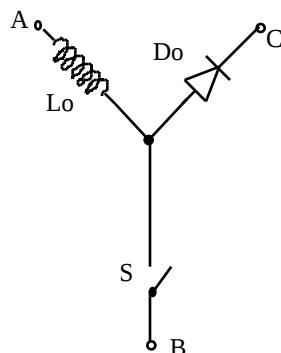
BASIC SWITCHING CELL OF COMMON PWM CONVERTERS




Topology	V_{in}	V_o	Topology	V_{AB}	V_{CB}
Buck	V_{CB}	V_{CA}	Buck	$V_{in} - V_o$	V_{in}
Boost	V_{AB}	V_{CB}	Boost	V_{in}	V_o
Buck-Boost	V_{AB}	$-V_{CA}$	Buck-Boost	V_{in}	$V_{in} + V_o$

Fundamental Principles

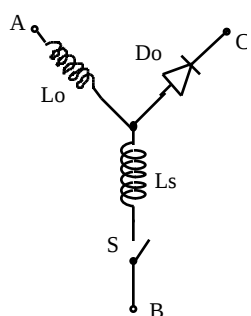1. Controlling $\frac{dI}{dt}$ at 'Turn On' -> Pseudo ZCS




S - type
Turn-On snubber

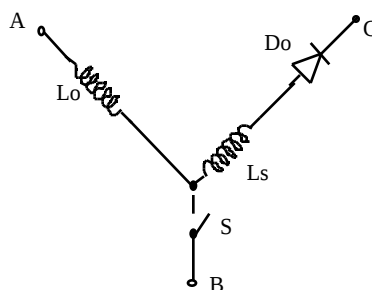

D - type
Turn-On snubber


Fundamental Principles

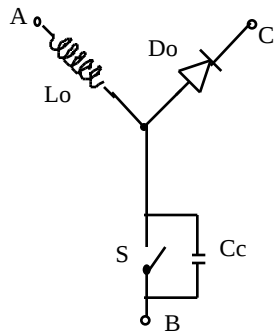2. Controlling $\frac{dV}{dt}$ at 'Turn Off' -> Pseudo ZVS




S - type

Turn-Off snubber

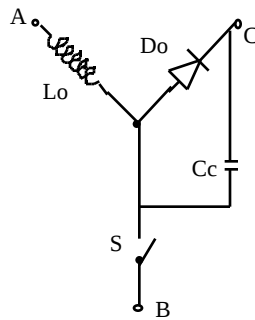

D - type

Turn-Off snubber

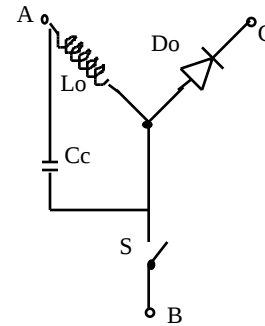

L - type

Turn-Off snubber



The major objective: to circulate the trapped energy

- In a lossless manner
- Without increasing the switch and diode stresses
- As quickly as possible (D_{on} & D_{off} limitations)
- Without generating new parasitic effects (of extra components)
- Inexpensive to implement




Use the followings as check points for comparison

$I_{pk}(\text{switch})$

$V_{max}(\text{switch})$

$V_{max}(\text{diode})$


General Observation

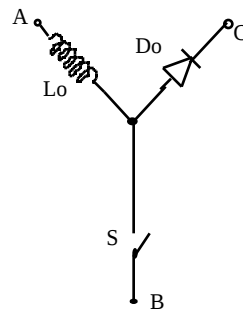


Snubber solution is independent of (PWM) topology if confined to the 'A-B-C' domain

Practical Aspects (1)

Snubber inductor rms current:

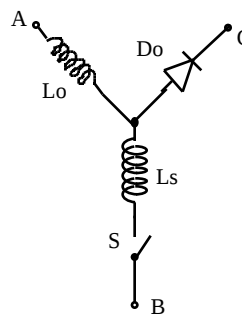

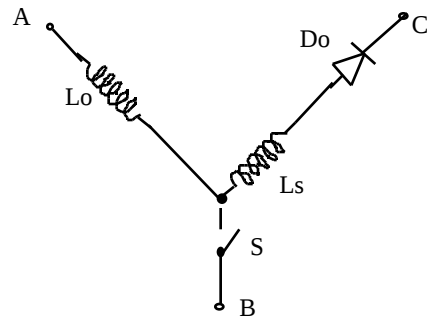
- **Snubber inductor carries switch plus reverse recovery currents**



- Snubber inductor carries diode plus reverse recovery currents

Practical Aspects (2)

Stirring capacitor's ripple current

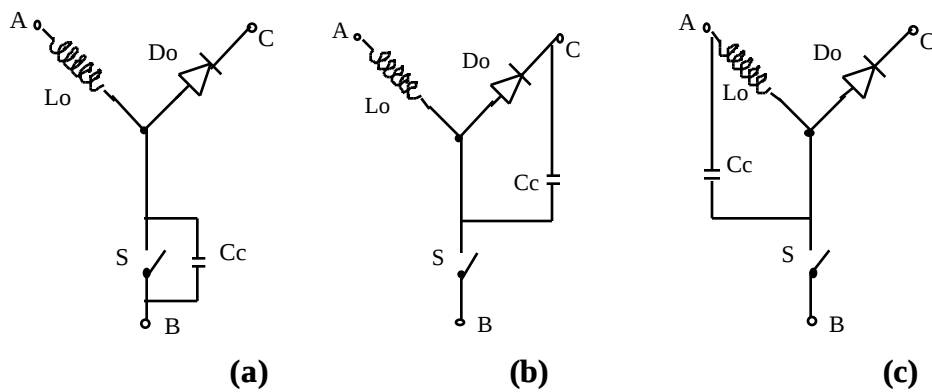

- (a) Ripple stirred to 'ground' - in Boost topology
- (b) Ripple stirred to output - in Boost topology

(c) Ripple stirred to input - in Boost topology

Chapter 3

BASICS OF RESONANT NETWORKS

Reset of Resonant Elements

At steady-state:

- **Volt-Sec of resonant inductor over switching cycle must be zero**

$$\int_{T_s} V_{L_r} dt = 0$$

- **Ampere- Sec of resonant capacitor over switching cycle must be zero**

$$\int_{T_s} I_{C_r} dt = 0$$


- **Sufficient time must be available for reset**
 - **This will cause restriction on duty cycle min & max**

Resonant Networks

-the vehicle of Snubbing and Energy Circulation


- **Energy circulation in passive lossless snubbers is made possible by lossless energy exchange of reactive elements (i.e. C, L)**
- **When the exchange is between L & C one deals with resonant phenomena**

Basic Resonant Network Parameters

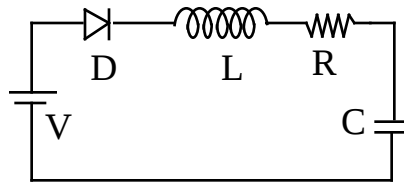

- Typical equivalent circuit of a lossless snubber
- < **Series resonance**
- < **R is normally small (to make the snubber "lossless")**
- < **May or may not include diode**
- < **Peak current equal or higher than main currents**
- < **Resonant frequency need to be shorter than switching frequency**


Basic Resonant Network Parameters

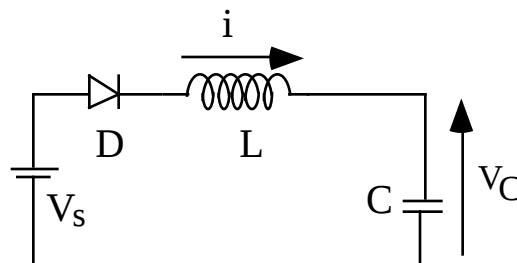

- < **Resonant frequency:** $f_r = \frac{1}{2\pi\sqrt{LC}}$; $\omega_r = \frac{1}{\sqrt{LC}}$; $T_r = \frac{2\pi}{\omega_r}$
- < **Characteristic impedance:** $Z_r = \sqrt{\frac{L}{C}}$

Ideal LC-network with ideal diode fed by a voltage source V_s

$$i(0) = I_0 \quad v_C(0) = V_{C0}$$

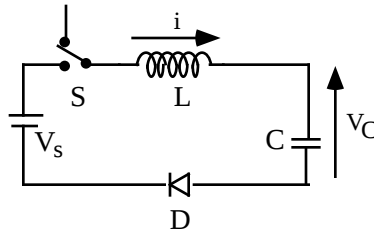

$$i = \frac{V_s - V_{C0}}{Z_r} \sin(\omega_r t) + I_0 \cos(\omega_r t)$$


$$v_C = (V_s - V_{C0})[1 - \cos(\omega_r t)] + I_0 Z_r \sin(\omega_r t) + V_{C0}$$

$$V_{Cp} = (V_s - V_{C0})[1 - \cos y] + I_0 Z_r \sin y + V_{C0}$$

$$y = \tan^{-1}\left(-\frac{I_0 Z_r}{V_s - V_{C0}}\right) + p \quad y < p$$


If $V_{C0} = 0$ and $I_0 = 0$ $y = p$ and $V_{Cp} = 2 V_s$

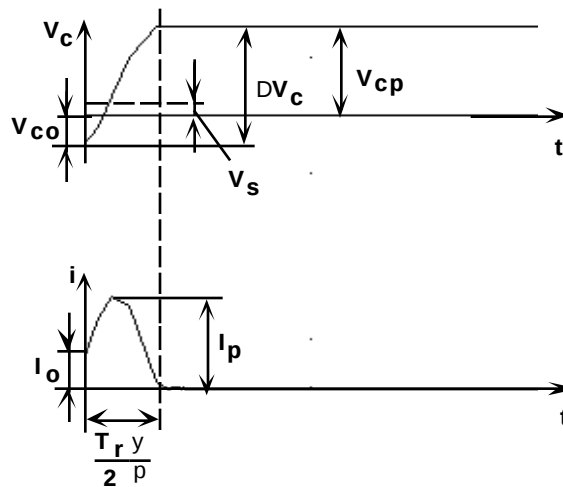If $V_{C0} < 0$ and $I_0 = 0$ $y = p$ and $V_{Cp} > 2 V_s$



SOME TRIVIAL CASES


- **Linear inductor discharge**

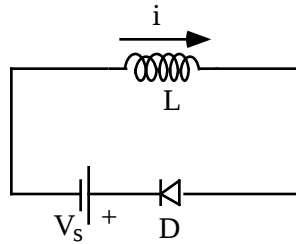

$$\frac{dI_L}{dt} = \frac{V_S}{L}; \quad i_L = I_L(0) - \frac{V_S}{L} t$$

, Large capacitor acts as V_S


- **Linear capacitor discharge**

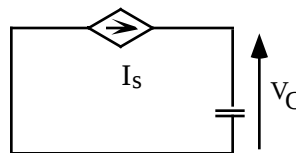


$$\frac{dV_C}{dt} = \frac{I_S}{C}; \quad v_C = V_C(0) + \frac{I_S}{C} t$$

, Large inductor acts as I_S

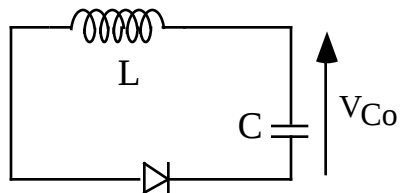- Capacitor voltage reversal $i(0)=0$ $v_C(0)=V_{Co}$



Beginning

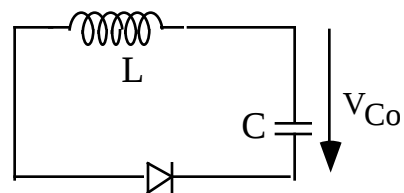


End


Practical Aspects (3)

Practical Snubber Components

- Reverse recovery of snubber diodes

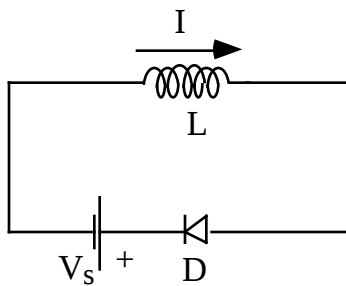

Before reset

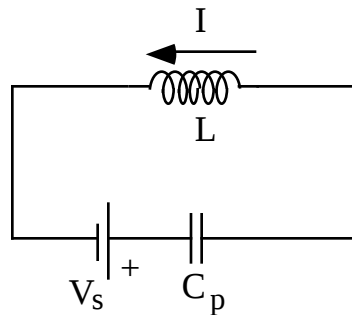

Diode snapped



Parasitic oscillations

4

Remedy -> Saturable Reactor

Practical Aspects (4)


Practical Snubber Components

- ESR of resonant Capacitor

👁 High losses, high temperature

4 Remedy -> Low ESR capacitors:
Polypropylene
Mica (the best !!)

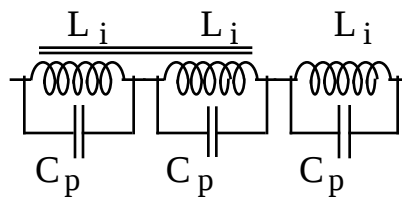- Interwinding capacitance of resonant inductor



👁 Parasitic oscillations , high losses, EMI emission

4 Remedy -> Careful design, toroidal configuration,
good coupling between windings

- Printed circuit layout



Parasitic oscillations , high losses, EMI emission

4 Remedy -> Careful design

Resonant Inductor Design

Typical characteristics

- Low inductance ; Typical range 3mH - 10mH
- High current ; Typical range 1A -30A

Some basic relationships:

$$B_{\max} = \frac{L I_{pk}}{n A_e}; \quad L = \frac{n^2 \mu_o \mu_r A_e}{l_e};$$

$$DB = \frac{\int V_L dt}{n A_e}$$

L - inductance (H)

I_{pk} - peak inductor current (A)

V_L - voltage across inductor (V)

t - time (Sec)

n - number of turns

B_{max} - limit of magnetic flux density (T)

A_e - effective core area (m²)

l_e - effective magnetic length (m)

μ_o - permeability (1.25 10⁻⁶ H/m)

μ_r - relative permeability


From above

$$\frac{I_{pk}}{L} = \frac{1}{L} \frac{B_{max} l_e}{n \mu_o \mu_r}$$

For high $\frac{I_{pk}}{L}$ ratios:

- Long l_e
- Small number of turns n
- Low relative permeability μ_r
- Winding window will no be full

Typical Construction

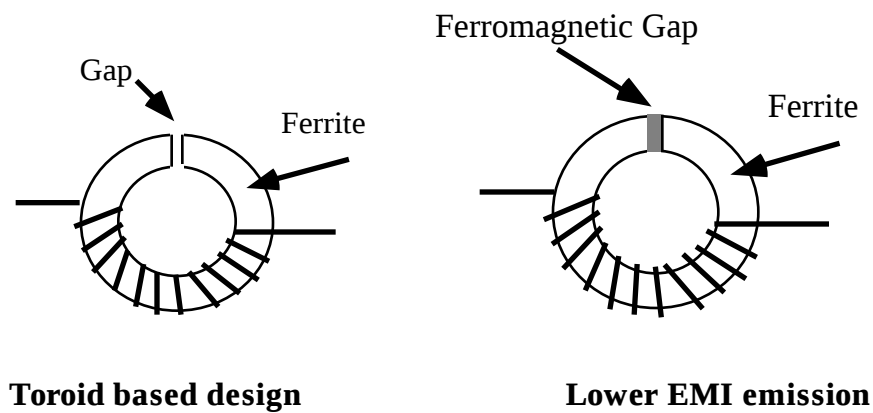

Suggested Design Procedure

1. Choose $DB_{\max}$ based of acceptable losses (mW/gr) from ferrite data (losses as a function of DB and frequency). Use f_r as an indicator but take into account the short period of snubbing by dividing the data sheet losses by (f_r/f_s)
2. Estimate $\{V \text{ Sec}\}$ across resonant inductor $\int V_L dt$ or by an approximation e.g. $V_L * t_{rr}$
3. Calculate nA_e from the relationship:

$$nA_e = \frac{\int V_L dt}{DB_{\max}}$$

4. Select wire cross section according to rms current
5. Based on calculated nA_e and wire size, choose a core for a single layer winding
6. Gap the core for required L value



Chapter 4

SWITCH TURN-OFF LOSSLESS SNUBBERS




SWITCH 'TURN OFF' LOSSLESS SNUBBER (SNB1)

The 'One Way' Capacitor : Version 1 [35]

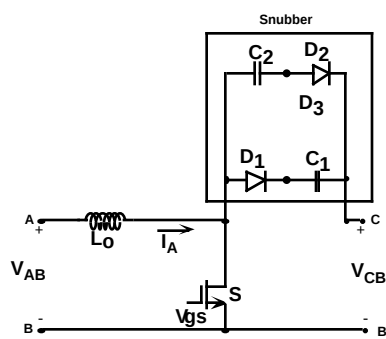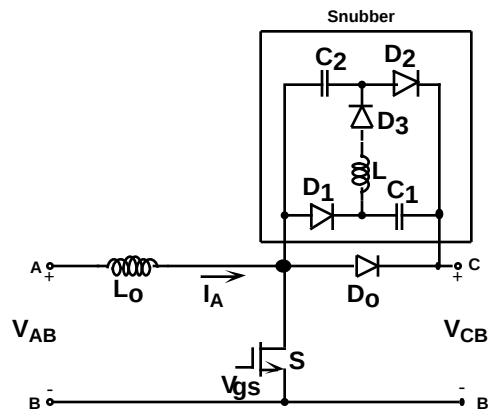

Snubbing

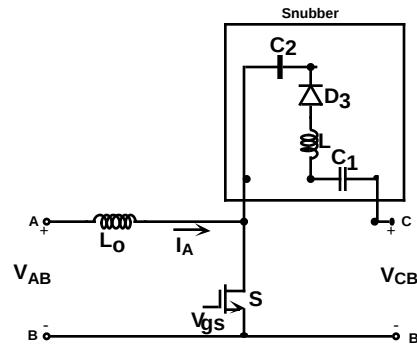


Reset

- Snubber capacitor $C_1 + C_2$
- Resonant reset ($C_1 + C_2, L$)


General Observations (1)

1. Snubbing

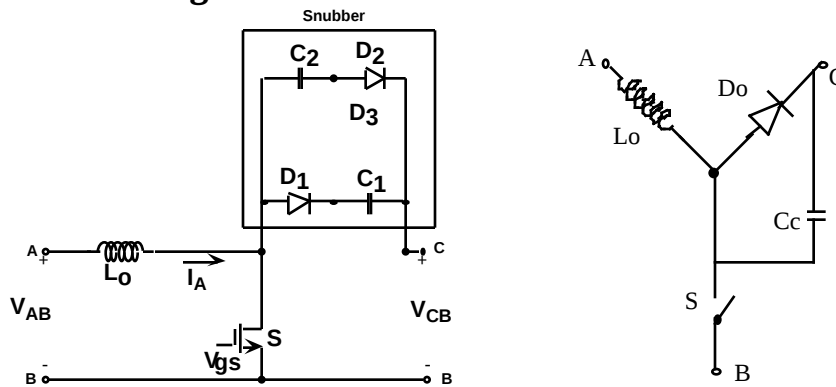

- Prior to 'turn-off', C_1 & C_2 must be charged to V_{CB}


2. Reset

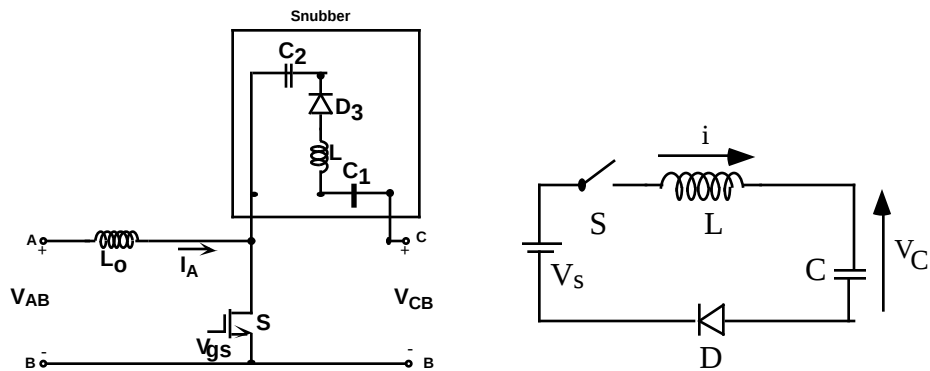


$$V_C = 2 V_{CB}$$

$$\text{if } C_1 = C_2 \rightarrow V_{C1} = V_{C2} = V_{CB}$$

General Observations (2)

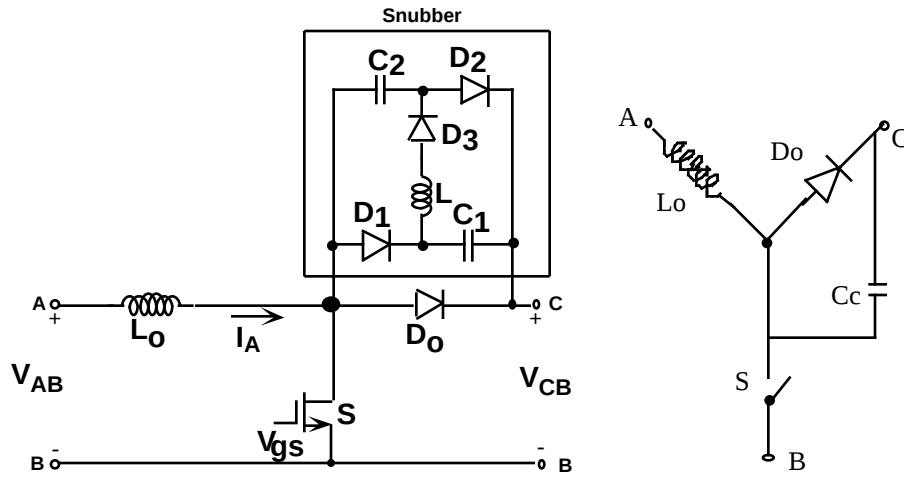

- Topology independent

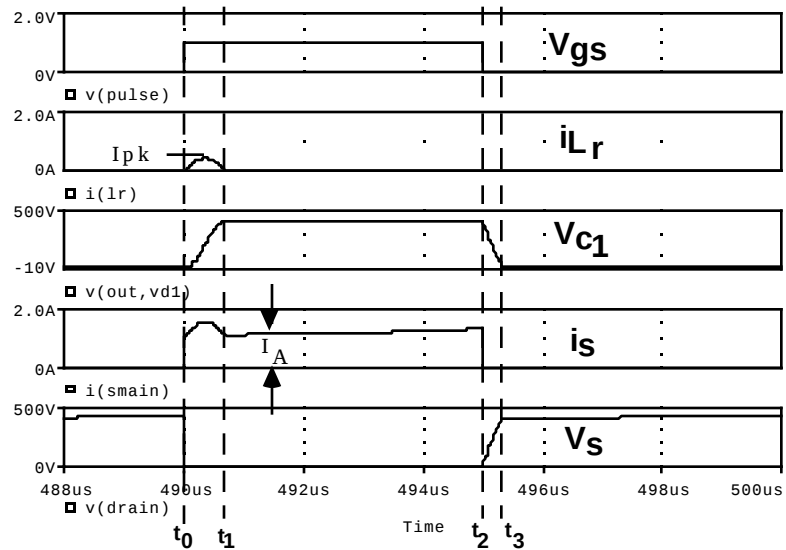

Waveforms of SNB1 (simulation)

Interval t_0-t_1

Assuming: $C_1=C_2=C$

$$t_1-t_0 = \frac{T_r}{2} = \rho \sqrt{\frac{LC}{2}} ;$$

$$i_L = i_{D3} = I_{pk} \sin(2\rho \frac{t}{T_r})$$

$$I_{pk} = \frac{V_{CB}}{\sqrt{\frac{2L}{C}}} ; \quad i_S = I_A + i_L$$

$$v_{C1} = v_{C2} = 0.5 V_{CB} [1 - \cos(2\rho \frac{t}{T_r})]$$

Interval t_1-t_2

$$i_S = I_A ; \quad i_{D0} = i_{D1} = i_{D2} = i_{D3} = 0$$

Interval t_2-t_3

$$v_{C1} = v_{C2} = V_{CB} - \frac{I_A}{2C} (t-t_2) ;$$

$$v_{C1}(t_3) = v_{C2}(t_3) = 0$$

$$\text{from which: } t_3-t_2 = \frac{2CV_{CB}}{I_A} \quad \text{and hence } \left(\frac{dv_S}{dt}\right)_{t_2-t_3} = \frac{I_A}{2C}$$

$$\text{Interval } t_3-(t_0+T_s) \quad i_{D0} = I_A ; i_S = i_{D1} = i_{D2} = i_{D3} = 0$$

Typical Design

Given: V_{CB} , I_A , $\left(\frac{dv_S}{dt}\right)_{t_2-t_3}$, D_{min} , D_{max}

$$1. \quad C \geq \frac{I_A}{2\left(\frac{dv_S}{dt}\right)_{t_2-t_3}} ; \quad 2. \quad t_{2-3} = \frac{2CV_{CB}}{I_A}$$

$$3. \quad f_s \leq \frac{1-D_{max}}{t_{2-3}} \quad 4. \quad L = \frac{2\left(\frac{D_{min}}{f_s}\right)^2}{\rho^2 C}$$

$$5. \quad I_{pk} = \frac{V_{CB}}{\sqrt{\frac{2L}{C}}} \Rightarrow \quad \frac{I_{pk}}{I_A} = \frac{\rho V_{CB}}{t_{on \min} \left(\frac{dv_S}{dt}\right)_{t_2-t_3}}$$

The diodes D_1 & D_2 must be very fast and have a very low storage charge.

Example:

Assuming: $f_s \approx 100\text{KHz}$; $t_{on \min} \approx 1\mu\text{s}$; $(\frac{dv_S}{dt})_{t_2-t_3} \approx 400\text{V}/\mu\text{s}$

$$\frac{I_{pk}}{I_A} = 0.78$$

4 Check points


$$I_{pk}(\text{switch}) = I_A + \frac{I_A \rho V_{CB}}{t_{on \min} (\frac{dv_S}{dt})_{t_2-t_3}}$$

$V_{\max}(\text{switch}) = \text{Same as original}$

$V_{\max}(\text{diode}) = \text{Same as original}$

SWITCH 'TURN OFF' LOSSLESS SNUBBER


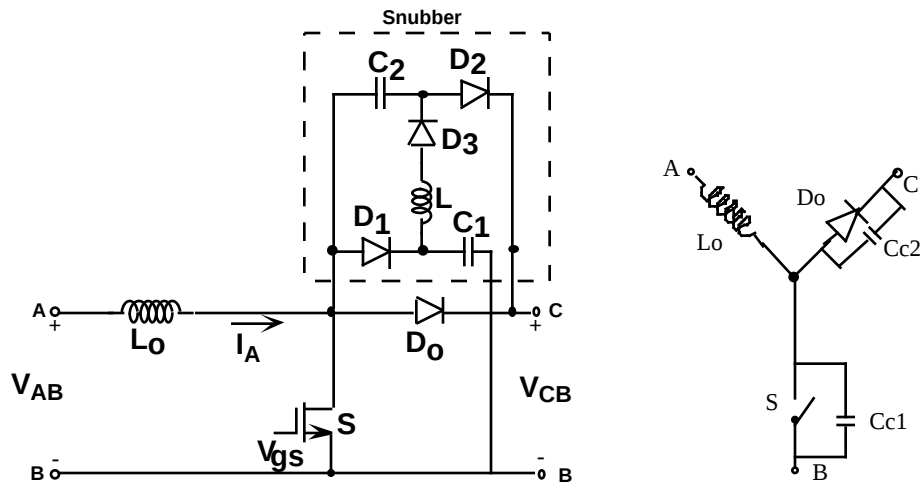
The 'One Way' Capacitor : Version 2 (SNB2) [35]




• Identical to Version 1 (normally drawn differently)

SWITCH 'TURN OFF' LOSSLESS SNUBBER (SNB3) [35]

Reset to Input

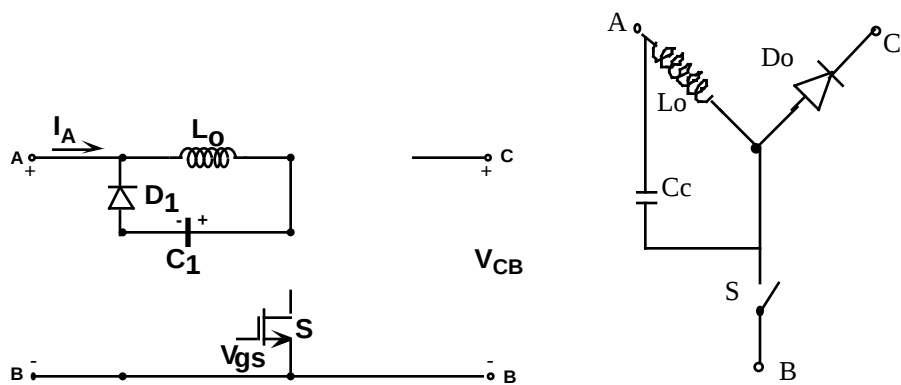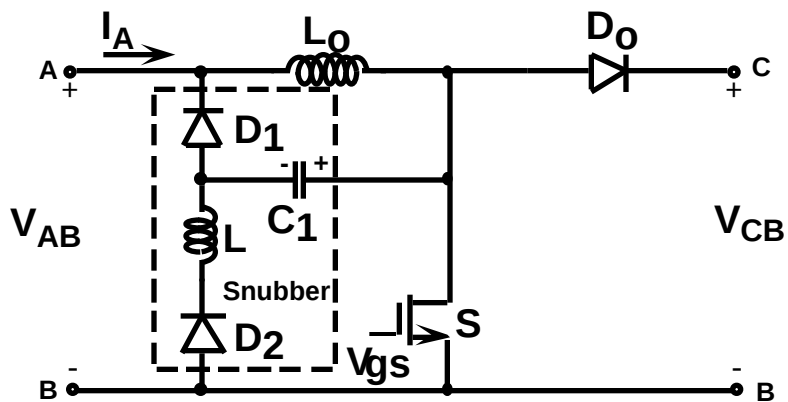


Snubbing

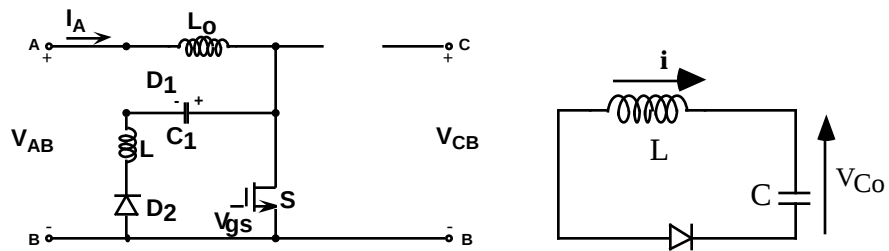


Reset 1

, $V_{CA} > V_{AB} \rightarrow D_{min} = 0.5$

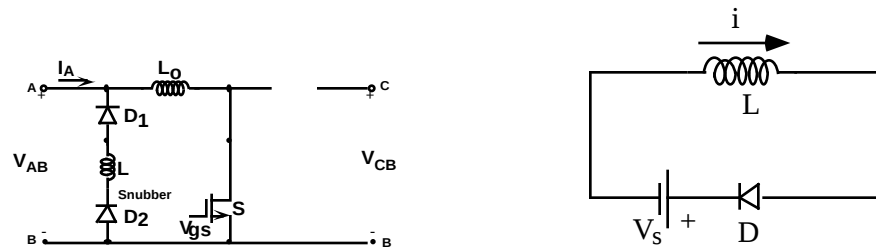

Reset 2

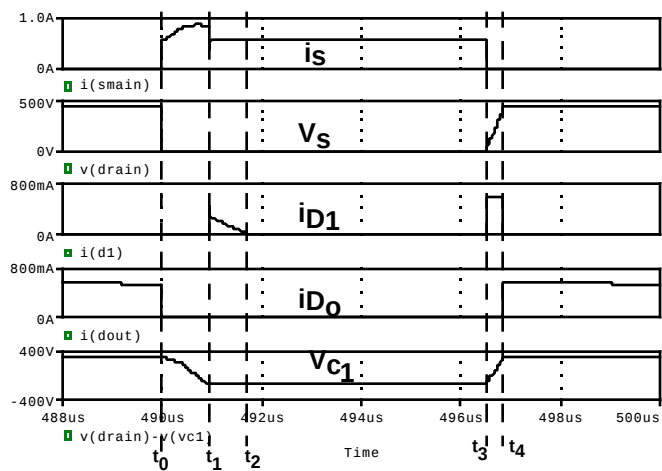

Waveforms of SNB3 (simulation)

Case $V_{CB}-V_{AB} > V_{AB}$, i.e. $V_{CB} > 2V_{AB}$

Interval t_0-t_1 $i_L=i_{D2}=I_{pk}\sin(2\rho\frac{t}{T_r})$

where

$$T_r=2\rho\sqrt{LC_1}$$

$$I_{pk}=\frac{V_{CB}-V_{AB}}{\sqrt{\frac{L}{C_1}}}$$

$$i_S=I_A+i_L$$

$$v_{C1}=(V_{CB}-V_{AB})\cos(2\rho\frac{t}{T_r})$$

t_1 is found from the condition:

$$(v_{C1})_{t_1}=-V_{AB}$$

$$t_1=\frac{T_r}{2\rho}\cos^{-1}\left(\frac{V_{AB}}{V_{CB}-V_{AB}}\right)$$

Interval t_1-t_2 $i_L=i_{D1}=i_{D2}=I_{pk}\sin(2\rho\frac{t_1}{T_r})-\frac{V_{AB}}{L}(t-t_1)$

t_2-t_1 is found

from the condition: $(i_L)_{t_2}=0$

t_2-

$$t_1=\frac{I_{pk}L\sin(2\rho\frac{t_1}{T_r})}{V_{AB}}$$

$$i_A=I_{A0}-i_L$$

Interval t_2-t_3 $i_S=I_A$; $i_{D0}=i_{D1}=i_{D2}=0$

Interval t_3-t_4 $i_S=i_{D0}=i_{D2}=0$

$$v_{C1}=-V_{AB}+\frac{I_{A0}}{C_1}(t-t_3)$$

t_4-t_3 is found from the

condition:

$$(v_{C1})_{t_4} = V_{CB} - V_{AB}$$

$$t_4 - t_3 = \frac{C_1 V_{CB}}{I_{A0}}$$

Interval $t_4 - (t_0 + T_s)$

$$i_{D0} = I_{A0}$$

$$i_S = i_{D1} = i_{D2} = 0 \quad ;$$

Typical Design

Given: V_{CB} , I_{Lo} , $(\frac{dv_S}{dt})_{t_3-t_4}$, $D_{min} \geq 0.5$, D_{max}

$$1. C_1 \leq \frac{1}{f_s} \frac{1}{\sqrt{I_{Lo} (\frac{dv_S}{dt})_{t_3-t_4}}} ; \quad 2. t_{3-4} = \frac{1}{f_s} \frac{1}{\sqrt{C_1 V_{CB} I_{Lo}}} ;$$

$$3. f_s \leq \frac{1}{t_{3-4}} \frac{1}{\sqrt{C_1 V_{CB} I_{Lo}}} ;$$

$$4. L^a \frac{(\frac{D_{min}}{f_s})^2}{p^2 C_1} \quad (\text{assumption: } i_L \text{ has a sine waveform not only during } t_0-t_1 \text{ but also during } t_1-t_2)$$

$$5. I_{pk} = \frac{V_{CB} D_{max}}{\sqrt{\frac{L}{C_1}}}$$

4 Check points

$$I_{pk}(\text{switch}) = I_{Lo} + \frac{p D_{max} V_{CB} I_{Lo}}{t_{on} \min(\frac{dv_S}{dt})_{t_3-t_4}} \quad (\text{no free lunch})$$


$V_{pk}(\text{switch}) = \text{Same as original}$

$V_{pk}(\text{diode}) = \text{Same as original}$


$$\text{Limitation: } V_{AB} \leq \frac{V_{CB}}{2}$$

In Boost Power Factor, hard switching when $V_{in} \geq \frac{V_o}{2}$

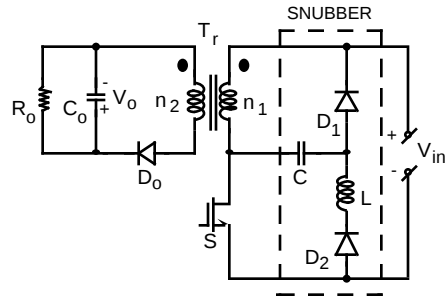Applying snubber SNB3 in a flyback converter [6, 26, 28]




Basic topology

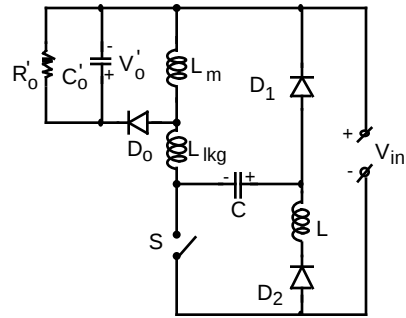


Equivalent circuit

- L_m - output transformer magnetizing inductance
- L_{lkg} - output transformer leakage inductance
- C - snubber capacitance
- L - snubber inductance
- R_0' - reflected load resistance
- C_0' - reflected capacitance of the output filter
- S - switching transistor
- D_0 - output diode
- D_1, D_2 - snubber diodes
- V_{in} - input voltage
- V_0' - reflected output voltage

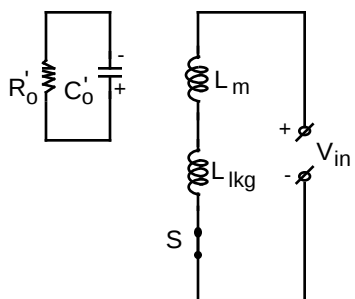
Equivalent circuit at different time intervals




1. ON

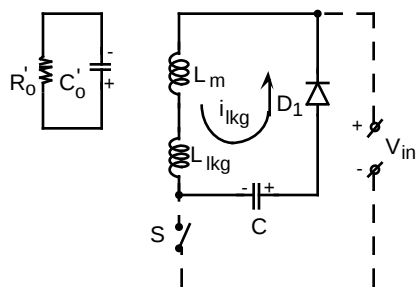


2. Snubbing 1

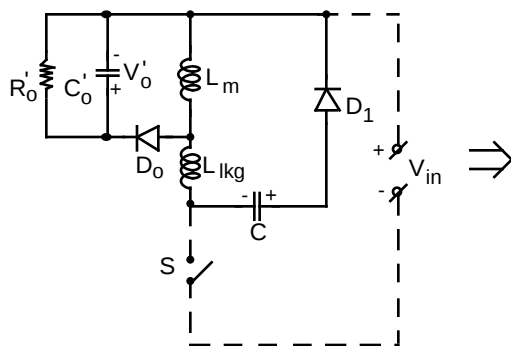


3. Snubbing 2


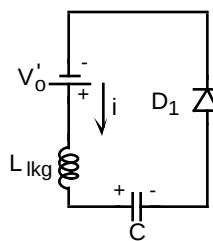


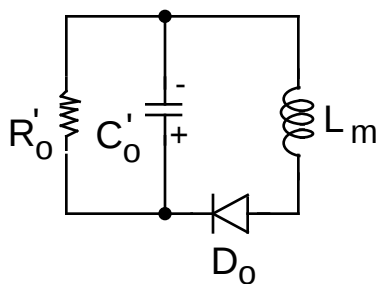

4. OFF

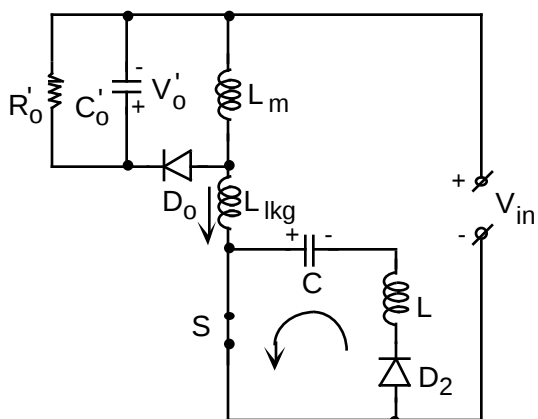

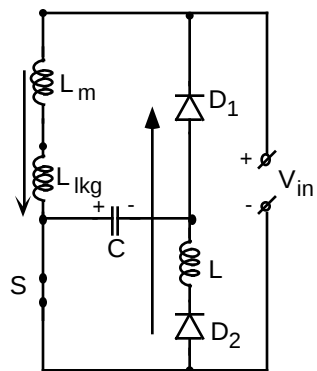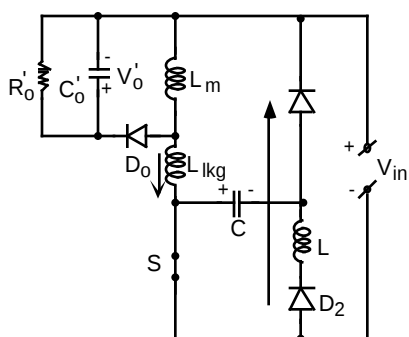
5. Resonant reset - ZCS at 'turn on' by L_{lkg} !!



6 Inductor discharge

General Observation

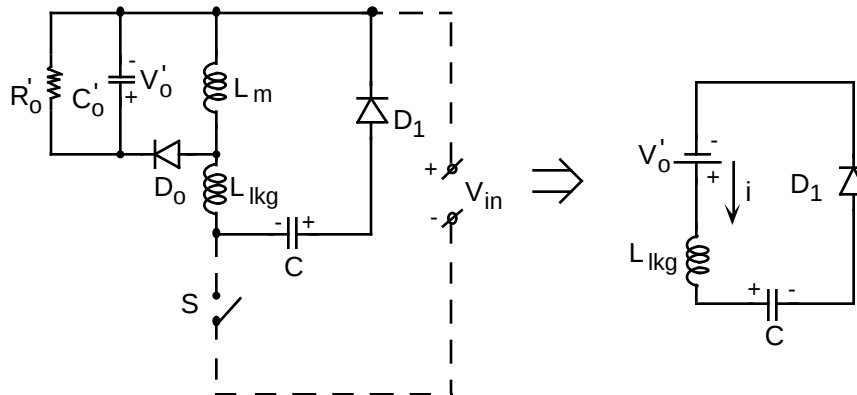1. Switch maximum voltage ($V_{s\text{ pk}}$)



Capacitor's initial voltage $--> V_C(0) = V_{in}$

Capacitor maximum voltage $--> V_{Cpk} > 2 V_o' + V_{in}$

{ additional voltage contributed by energy removed from L_{lkg} }

Switch maximum voltage $--> V_{s\text{ pk}} > 2 (V_{in} + V_o')$


Advantages

- The snubber is simple and inexpensive [28]
- The operational duty cycle range is wider than in the case when this snubber is used in a boost converter


Disadvantage

- High voltage stress on the transistor $V_{s\text{ pk}}$


Reverse recovery of snubber diode

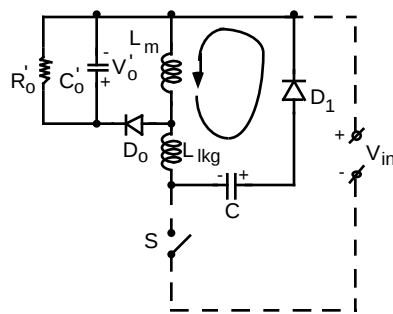

Resonant reset

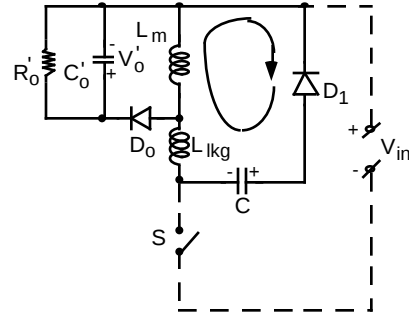


Reverse recovery

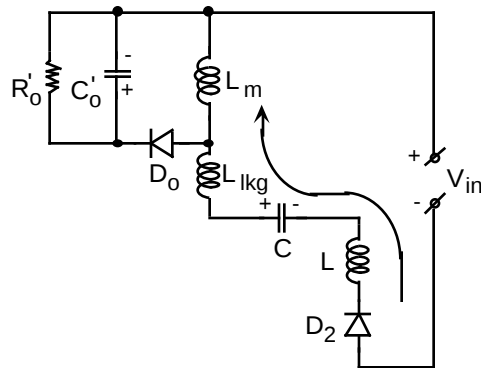

Linear discharge

- **Loss of C charge**
- **C must retain a voltage of at least V_{in} for proper ZVS at 'turn-off'**

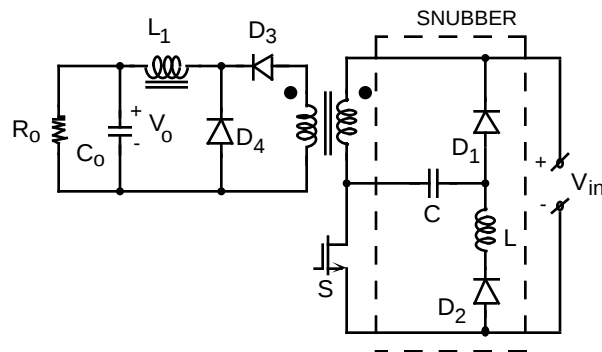Applying snubber SNB3 in a forward converter [40]



Same advantages and disadvantages as for the flyback converter case:

- the snubber is simple and inexpensive
- high voltage stress $V_{s\text{ pk}}$ on transistor.

$$V_{s\text{ pk}} = V_{in} + V_{Cp}$$

where

$$V_{Cp} = \sqrt{\frac{L_m I_m^2 + L_{lkg} I_{Sp}^2}{C}}$$

L_m - magnetizing inductance of the transformer

L_{lkg} - primary leakage inductance

I_m - magnetizing current of the transformer


$I_{s\text{ pk}}$ - switch current in the moment when the switch is turned off

Experimental results [40]

1) $V_{in}=17V$; $P_{out}=17W$; $D=2/3$; $V_{s\text{ pk}}=52V$

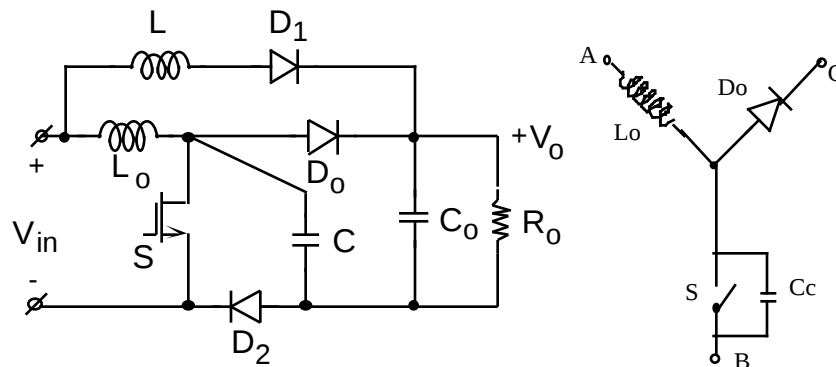2) $V_{in}=34V$; $P_{out}=36W$; $D=1/3$; $V_{s\text{ pk}}=88V$

A switch "turn-off" lossless snubber for a boost converter [30] (SNB4)




Snubber elements:


- L** - the resonant inductor
- C** - the resonant capacitor
- D₁, D₂** - snubber diodes

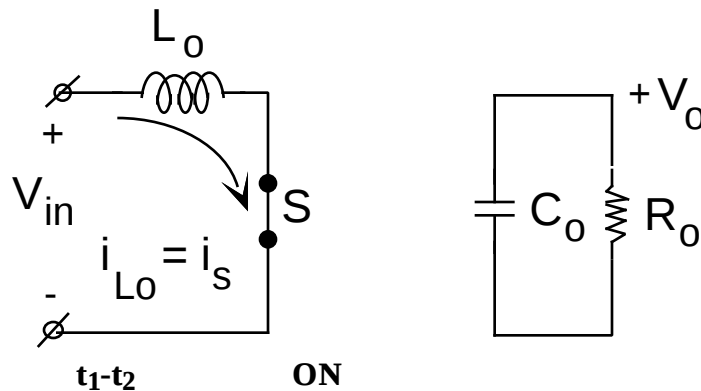 **No common ground !**

Equivalent circuits for different time intervals





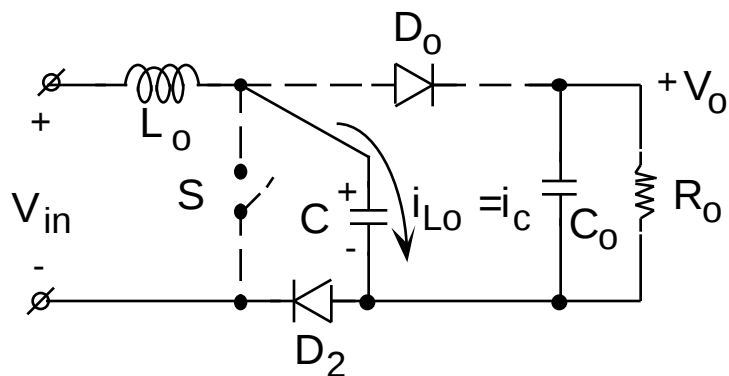


t_2-t_3 , snubbing


$$\frac{dv_S}{dt} = \frac{i_{L0}}{C} \quad \text{ZVS!}$$

$$v_{D0}(t) = v_C(t) - V_0$$

$$v_C(t_3) = V_0 \quad v_{D0}(t_3) = 0$$

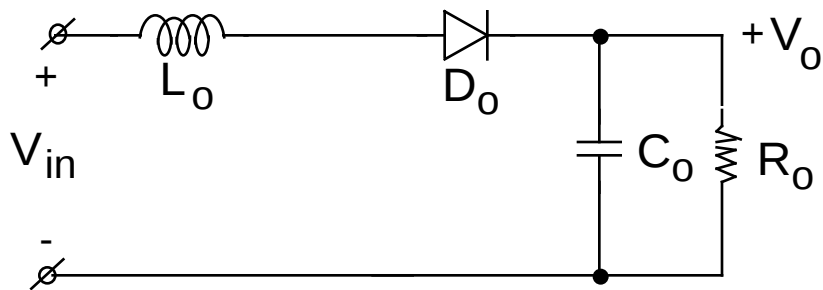

t_3-t_4 OFF

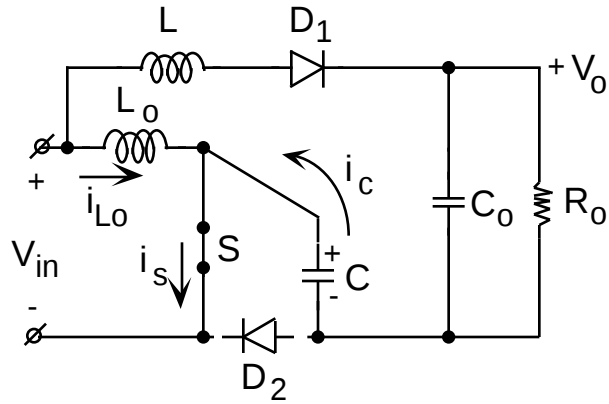


t_4-t_5 , reset

$$v_C(t_4) = V_0 \quad i_L = i_C = \frac{V_{in}}{Z_r} \sin(\omega_r t)$$

$$\omega_r = \frac{1}{\sqrt{LC}} \quad Z_r = \sqrt{\frac{L}{C}}$$

$$i_S = i_{L0} + i_C \quad I_{Sp} = I_{L0} + \frac{V_{in}}{Z_r}$$

$$v_C(t_5) = v_{D2}(t_5) = 0$$

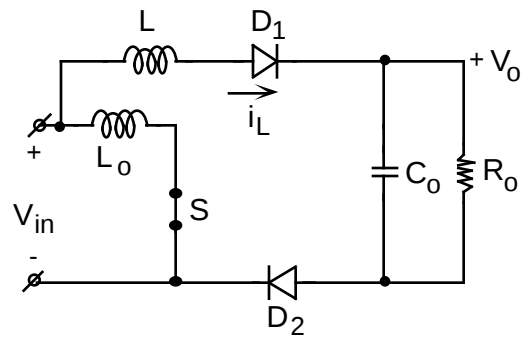

t_5-t_6 , linear discharge

$$i_L(t) = i_{D1}(t) = i_L(t_5) - \frac{V_o - V_{in}}{L} (t - t_5)$$

$$i_L(t_6) = i_{D1}(t_6) = 0$$

**A switch "turn-off" lossless snubber for a boost converter [30]
(SNB4)**

Advantages

- **Soft switching at turn off. Efficiency was reported to increase by 5% to 97% [30] .**

Disadvantage

- **Reverse recovery problems of diodes D_0 , D_1 , and D_2**
- **High current stress of main switch during the interval t_4 - t_5**
- **No common ground between input and output**


Chapter 5

SWITCH TURN-ON AND DIODE TURN-OFF SNUBBERS


SWITCH 'TURN ON' AND DIODE 'TURN OFF' SNUBBER

[35,39]


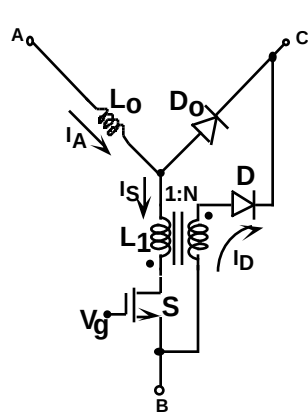
FLYBACK RESET SNUBBER (energy recovery via a catch winding)



Version 1 (SNB5)

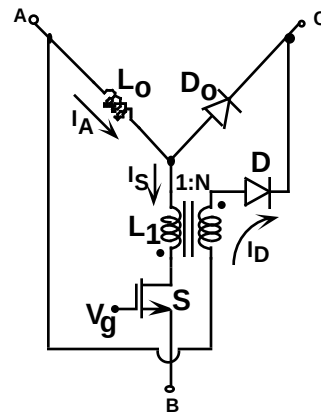


Version 2 (SNB6)

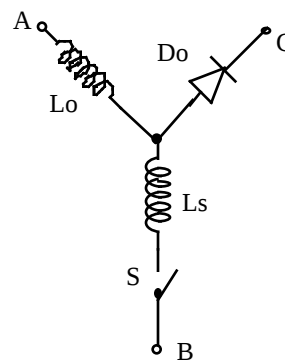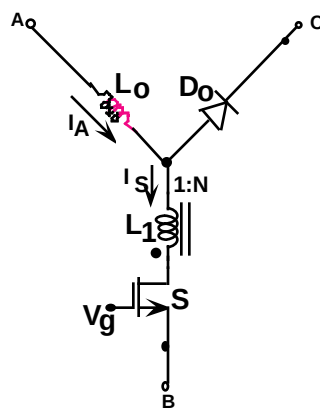

Snubbing



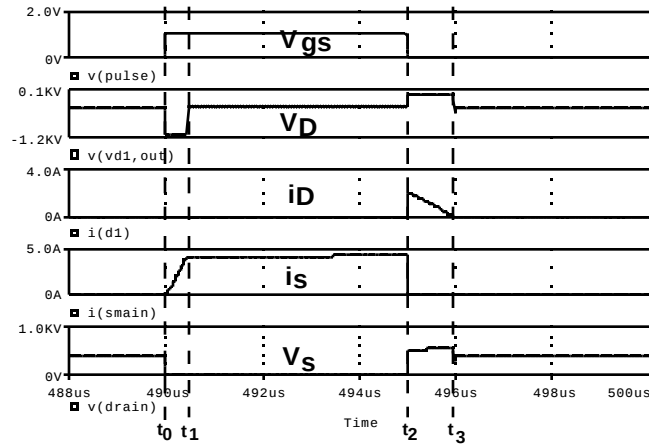

Waveforms of SNB5 (simulation)

Analysis: Version 1 (SNB5)

Interval t_0 - t_1

$$i_s = \frac{V_{CB} t}{L_1}$$

$t_1 - t_0$ is found from the

condition: $i_s(t_1) = I_A$

from where

$$t_1 - t_0 = \frac{L_1 I_A}{V_{CB}}$$

$$V_{D0 \max} = V_{CB}(1+N)$$

Interval t_2 - t_3

$$i_D = \frac{I_A}{N} - \frac{V_{CB}}{N^2 L_1} (t - t_2)$$

$t_3 - t_2$ is found from the

condition: $i_D(t_3) = 0$

$$t_3 - t_2 = \frac{I_A L_1 N}{V_{CB}} ; V_S$$

$$V_{D0 \max} = V_{CB} \left(1 + \frac{1}{N}\right)$$

$$t_3 - t_2 = \sqrt{f(I_A L_1 N, V_{CB})} ; f_s$$

$$f_{s \max} = \frac{1 - D_{\max}}{t_3 - t_2}$$

$$V_{S \max} = V_{CB} \left(1 + \frac{1}{N}\right) ; V_{D_0}$$

$$f_{s \max} = V_{CB}(1 + N)$$

The lower N , the shorter is $t_3 - t_2$ and hence the higher is the upper limit of the switching frequency $f_{s \max}$. The lower N , the higher is $V_{S \max}$. The voltage across the main diode D_0 is high when N is high.

A major disadvantage of the converter is the leakage inductance between the primary and secondary of the coupled inductor : it will cause a large voltage spike across the switch. Beware of reverse recovery problems of the auxiliary diode D .

FLYBACK RESET SNUBBER Version 1 (SNB5)

Typical Design

Given: V_{CB} , I_A , $\left(\frac{di_S}{dt}\right)_{t_0-t_1}$, $D_{\min}$, $D_{\max}$

$$1. L_1 \leq \frac{V_{CB}}{\left(\frac{di_S}{dt}\right)_{t_0-t_1}} ; 2. t_{1-0} = \frac{L_1 I_A}{V_{CB}} ; 3. f_s \leq \frac{D_{\min}}{t_{1-0}}$$

$$4. t_{2-3} \leq \frac{1 - D_{\max}}{f_s} ; 5. N = \frac{V_{CB} t_{2-3}}{L_1 I_A} ; 6. V_{S \max} = V_{CB} \left(1 + \frac{1}{N}\right)$$

$$7. V_{D_0 \max} = V_{CB}(1 + N)$$


4 Check points

$$I_{pk}(\text{switch}) = I_A$$

$$V_{\max}(\text{switch}) = V_{CB} (1 + f(1, N)) = V_{CB} \left(1 + \frac{I_A}{t_{off} \min\left(\frac{di_s}{dt}\right) t_0 - t_1} \right)$$

$$V_{\max}(\text{diode}) = V_{CB} (1 + N) = V_{CB} \left(1 + f\left(t_{off} \min\left(\frac{di_s}{dt}\right) t_0 - t_1, I_A\right) \right)$$

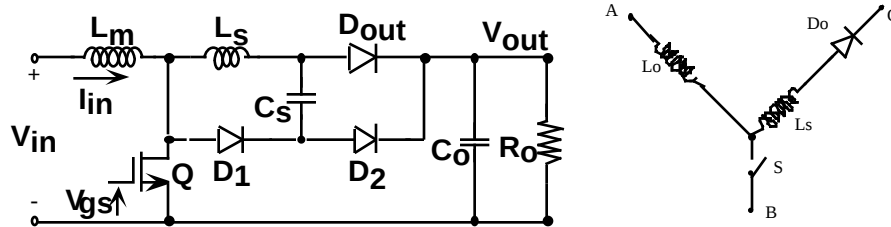LOW STRESS 'TURN ON' SNUBBER (SNB7) [17, 24]



Q - Main switch


Dout - Main diode

D1, D2 - Auxiliary diodes


LS, CS - Resonant network

Basic waveforms of lossless snubber


Interval t_0 - t_1

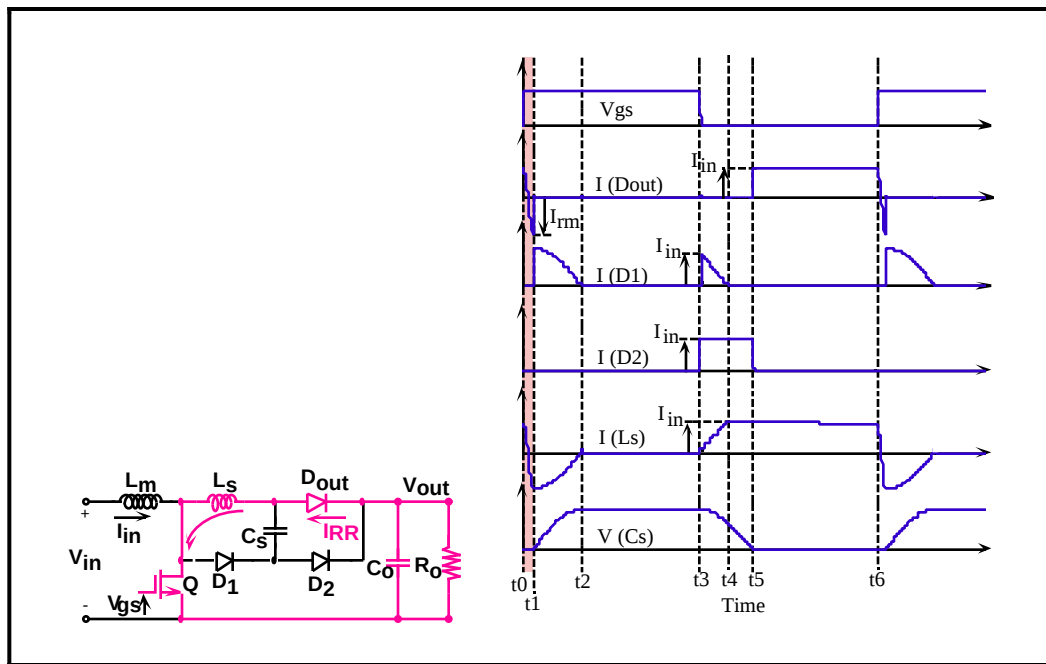



Interval t_1 - t_2

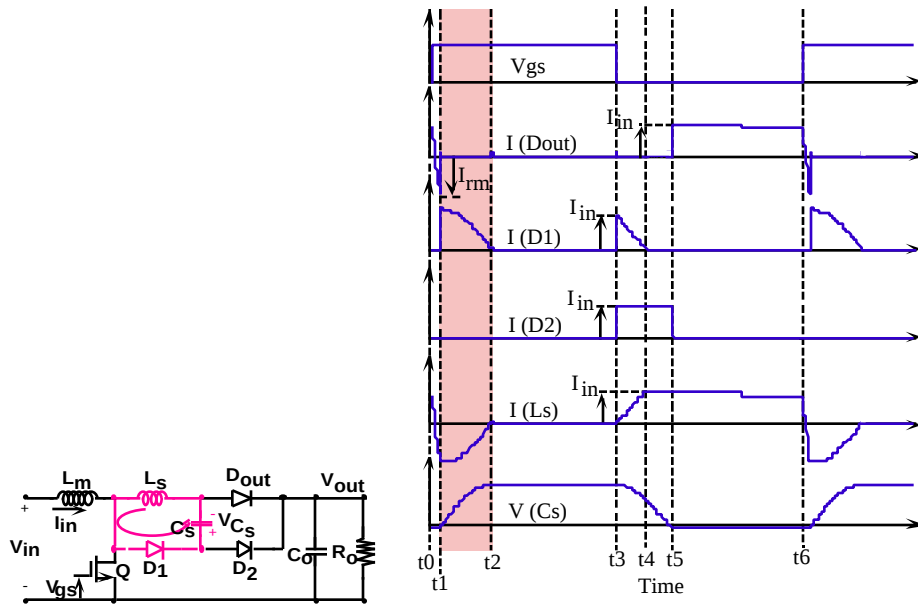



Interval t_2 - t_3

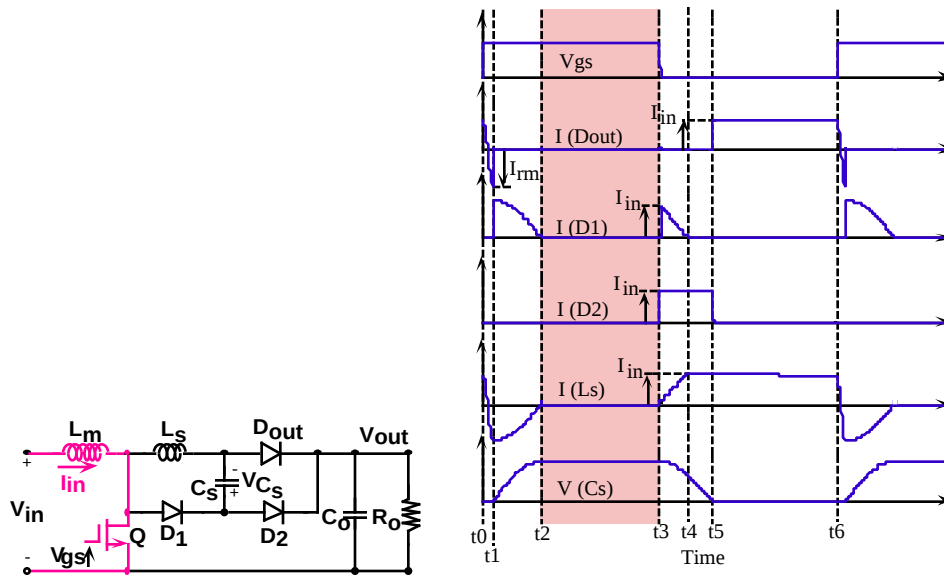


Interval t_3 - t_4

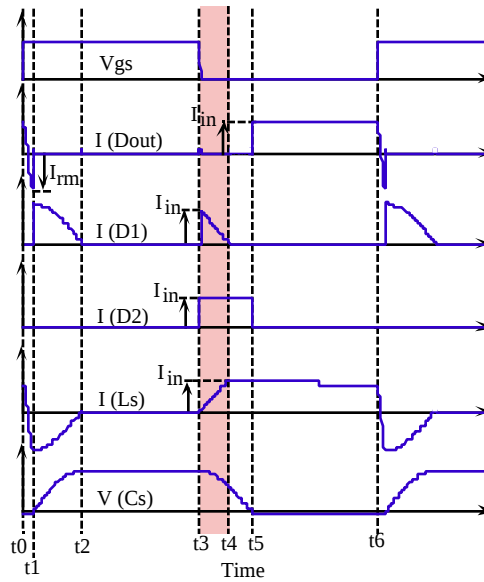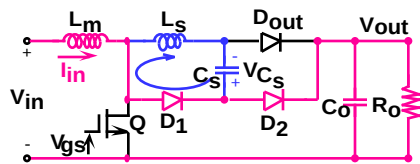


Interval t_4 - t_5

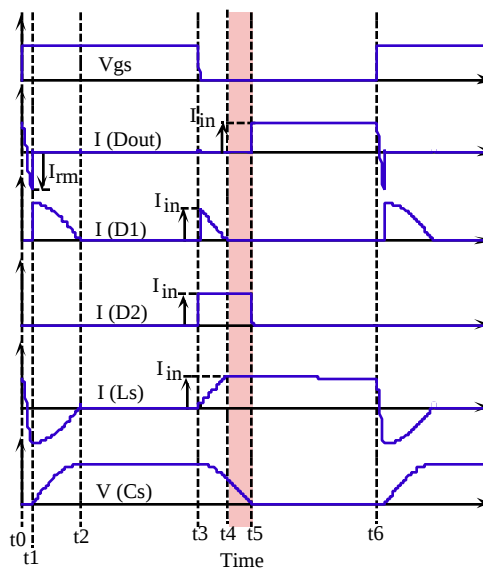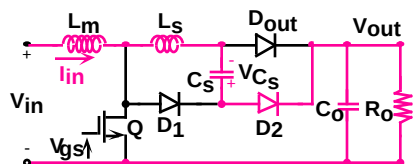

Interval t_5 - t_6

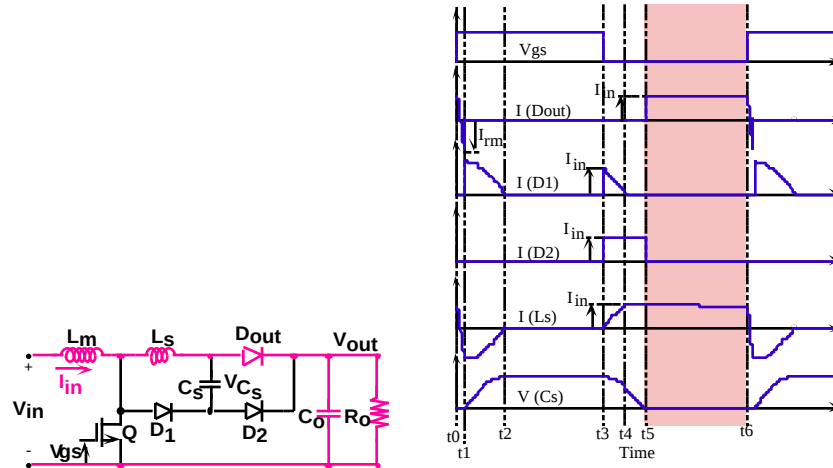

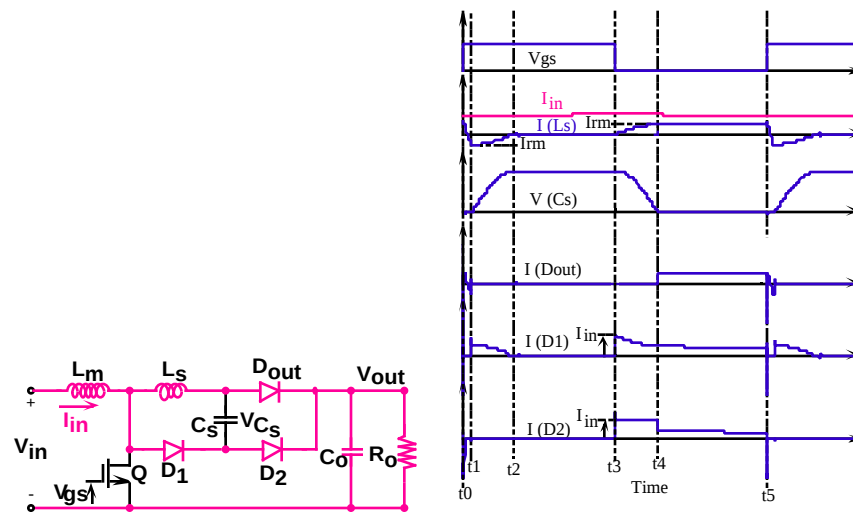
Practical requirement of peak reverse recovery current - I_{rm} If $I_{rm} < I_{in}$



To avoid the above undesired condition

$$I_{rm} > I_{in}$$

The coupled inductor realization

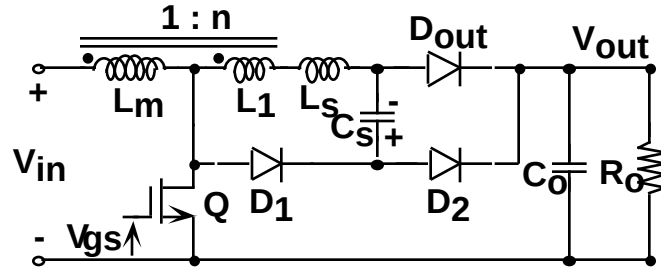

D_{out} - Main diode



D₁, D₂ - Auxiliary diodes

L_s, C_s - Resonant network

L_m, L₁ - Coupled inductors

n - turn ratio

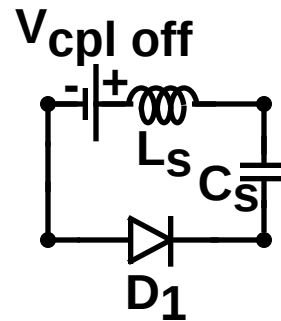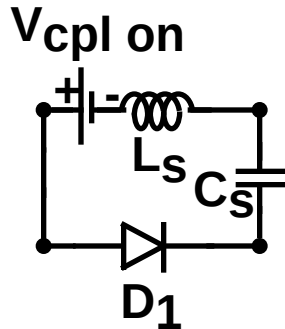
Simplified equivalent circuits of the resonant elements with coupling inductor



$$V_{cpl\ on} = nV_{in}$$

$$V_{cpl\ off} = \frac{n}{1+n} (V_{out} - V_{in})$$

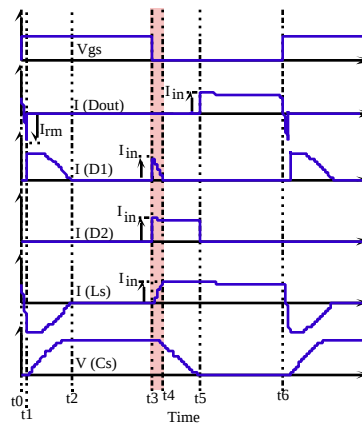Basic waveforms of the lossless snubber with coupling inductor



$V_{Cs}(t_3)$ is larger and therefore t_{3-4} is smaller

Components Stress

Transistor or diode	Current stress	Current stress instance or interval	Voltage stress	Voltage stress instance or interval
Q	$I_{in} + I_{rm}$	t_1	V_{out}	$t_3 - t_4$
D ₀	I_{in} I_{rm}	$t_5 - t_6$ t_1	$V_{out} + V_{Cmax}$	t_2
D ₁	$\sqrt{I_{rm}^2 + \frac{V_{cpl\ on}^2 C_s}{L_s}}$	$t_1 < t_e < t_2$	$V_{out} - V_{cpl\ on}$	$t_0 - t_1$
D ₂	I_{in}	$t_3 - t_5$	V_{out}	$t_1 - t_2$

$$I_{rm} = \frac{(V_{out} + V_{cpl\ on}) t_{rm}}{L_s}$$

formal reverse recovery time

$$t_{rm} \approx t_{rr} \quad t_{rr} =$$

$$V_{cpl\ on} = n V_{in} = n(1-D)V_{out}$$


$$D = \frac{t_{on}}{T_s}$$

$$V_{Cmax} = I_{rm} \sqrt{\frac{L_s}{C_s}} \sin(\omega_r t_{1-2}) + V_{cpl\ on} [1 - \cos(\omega_r t_{1-2})]$$

$$\omega_r t_{1-2} = \tan^{-1} \left(- \frac{I_{rm} \sqrt{\frac{L_s}{C_s}}}{V_{cpl\ on}} \right) + p$$

Smaller reverse recovery current of Do

Power dissipation

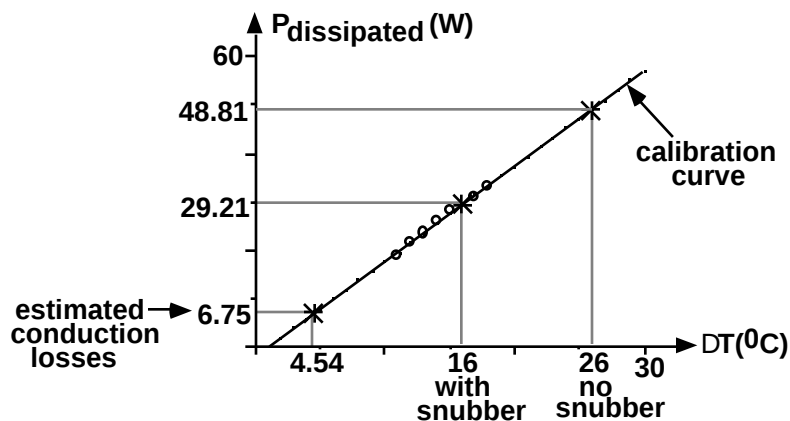

o DC calibration points

Power dissipation dropped by 19.6W


Additional Comments

- 4 The main advantages of the lossless snubber:
 - ZCS in turn-on
 - Smaller reverse recovery current
- 4 The preferred embodiment is coupled inductors
- 7 The main disadvantage of the snubber is limitation of the duty cycle range

4 The overall efficiency of the experimental Boost converter was found to increase by 1%-2%


The snubber can be adopted to other PWM topologies

Implementation in Buck converter

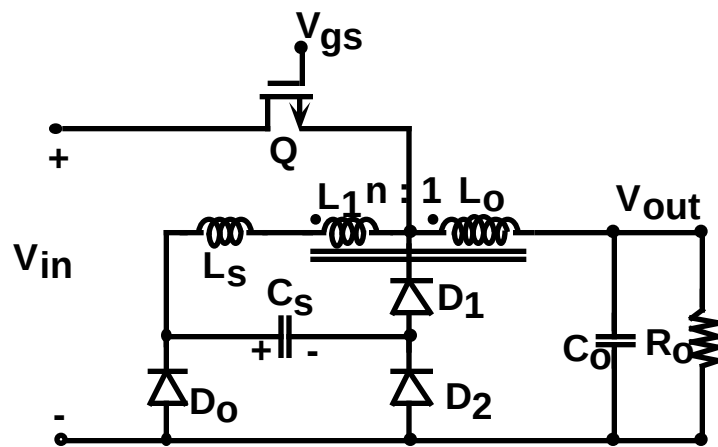


 Proven to increase efficiency by ^a 2%

Implementation in a buck-boost converter

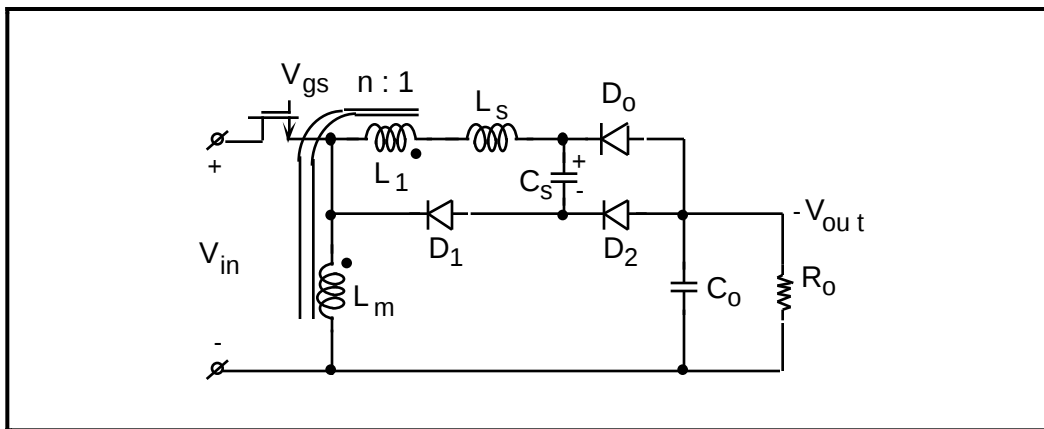


Implementation in APFC

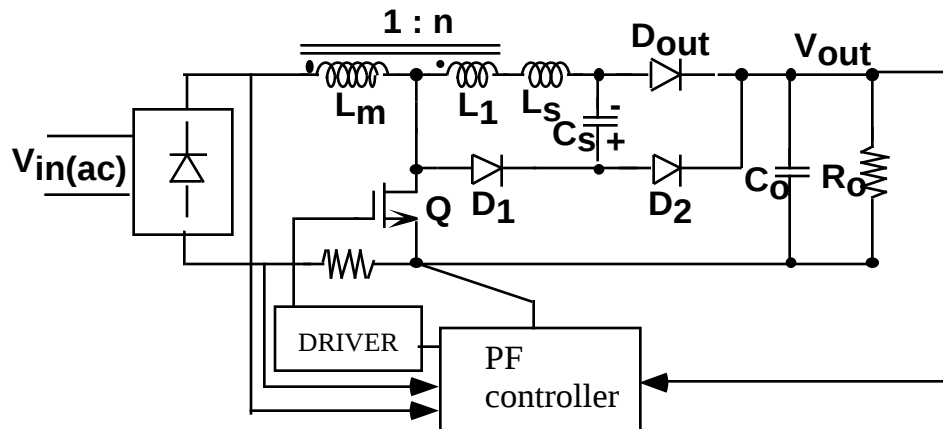

- Simple implementation
- 👁 Watch D_{onmin}
- 📊 Proven to increase efficiency by ^a 2%

RMS current of the snubber inductor in a boost converter implemented in APFC

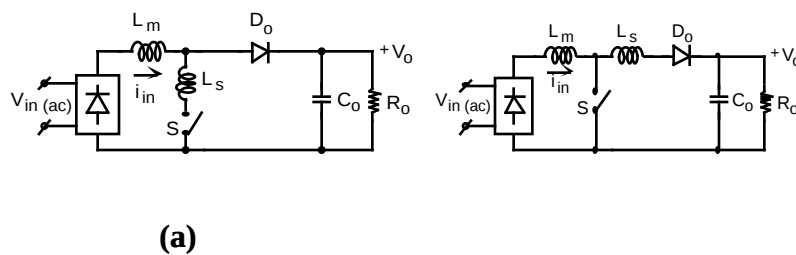Two ways of snubber inductor (L_s) connection:




(snubber elements except L_s are not shown)

RMS current of the snubber inductor in a boost converter implemented in APFC

Main assumptions

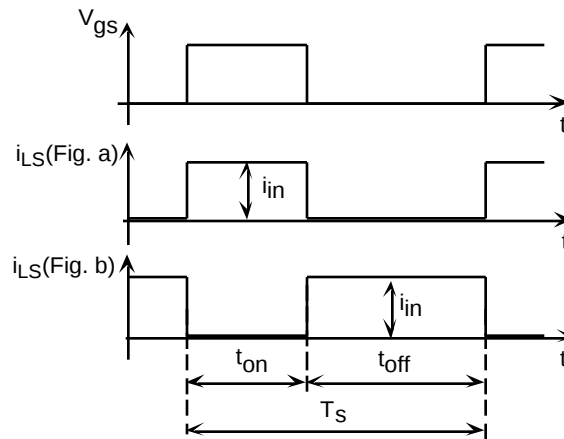1. The duration of transient processes after the switch S is turned on and after S is turned off are neglected.
2. The input inductance L_m is sufficiently large that their current i_{in} is practical constant during one high frequency switching cycle T_s .

Under these conditions the current i_{Ls} of the snubber inductor has a rectangular waveform during one high frequency switching cycle T_s .



For one switching cycle T_s (high frequency period)


$$I_{Ls \text{ rms hf (Fig. a)}} = i_{in} \sqrt{D}$$

$$I_{Ls \text{ rms hf}} (\text{Fig. b}) = i_{in} \sqrt{1-D}$$

$$\text{where } D = \frac{t_{on}}{T_s} \quad (\text{hf - high frequency})$$

RMS current of the snubber inductor in a boost converter implemented in APFC

Ideal APFC

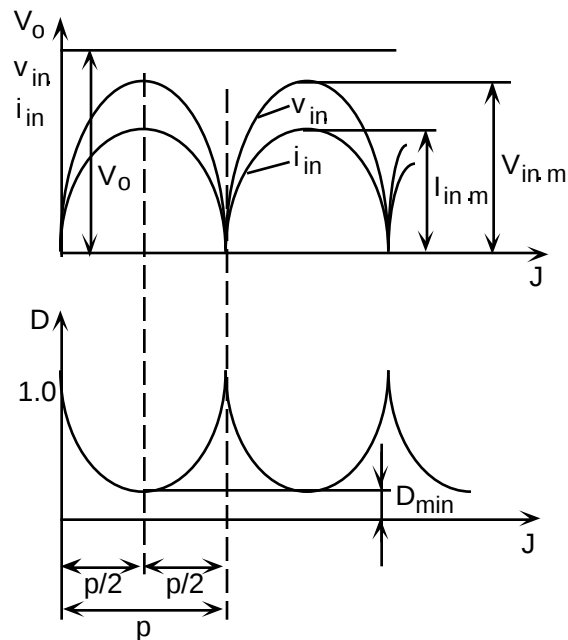

$$v_{in} = V_{in \text{ m}} \sin J$$

$$i_{in} = I_{in \text{ m}} \sin J$$

where

$$J = 2\pi f_{lf} t \quad (f_{lf} = 50 \text{ or } 60 \text{ Hz}) \quad (lf - \text{low frequency})$$

$$V_o = \text{const}$$

In boost converter

$$\frac{V_o}{v_{in}} = \frac{1}{1-D} \quad \rightarrow \quad D = 1 - (1-D_{min})\sin J$$

where

$$D_{min} = 1 - \frac{V_{in\ m}}{V_o}$$

**RMS current of the snubber inductor
in a boost converter implemented in APFC**

Ideal APFC (cont.)


RMS current for low frequency period

$$I_{Ls\ rms\ If\ (Fig.\ a)} = \sqrt{\frac{1}{p} \int_0^p I_{in\ m}^2 [\sin^2 J - (1-D_{min})\sin^3 J] dJ} =$$

$$= I_{in\ m} \sqrt{0.5 - \frac{4}{3p}(1-D_{min})}$$

$$I_{Ls\ rms\ If\ (Fig.\ b)} = \sqrt{\frac{1}{p} \int_0^p I_{in\ m}^2 (1-D_{min})\sin^3 J dJ} =$$
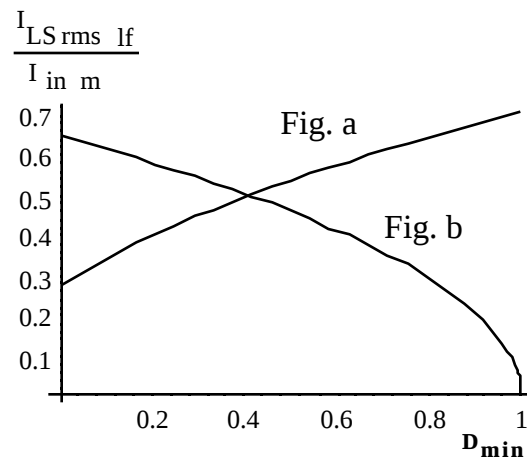
$$= I_{in\ m} \sqrt{\frac{4}{3p}(1-D_{min})}$$



Conclusion: Fig. a is preferable if $D_{min} < 0.4$ and Fig. b is preferable if $D_{min} > 0.4$.

Chapter 6

TURN-ON AND TURN-OFF SINGLE SWITCH SNUBBERS

TURN-ON AND TURN-OFF SINGLE SWITCH SNUBBERS

Possible Realizations:

LCC - one resonant inductor and two resonant capacitors

[10, 16, 22, 31, 32, 34, 39, 46]


LLC - two resonant inductors and one resonant capacitor

[1, 23, 29, 45]

LC - one resonant inductor and one resonant capacitor

[2, 22, 36, 41]

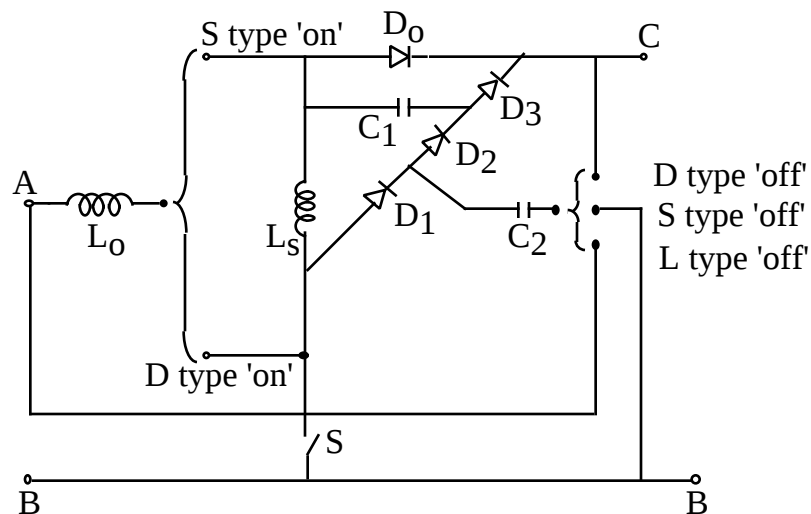Generic LCC 'turn-off' & 'turn-on' snubber topology (see also [32])




- Snubber analysis is identical for all connections

TURN-ON AND TURN-OFF SINGLE SWITCH SNUBBERS

Boost converter with LCC snubber: D type 'on' and S type 'off' (SNB8) [22, 31, 32]


(Modified turn-on snubber SNB7)

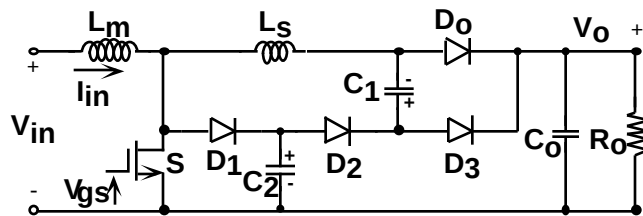


S - main switch


D₀ - main diode

D₁, D₂, D₃ - auxiliary diodes

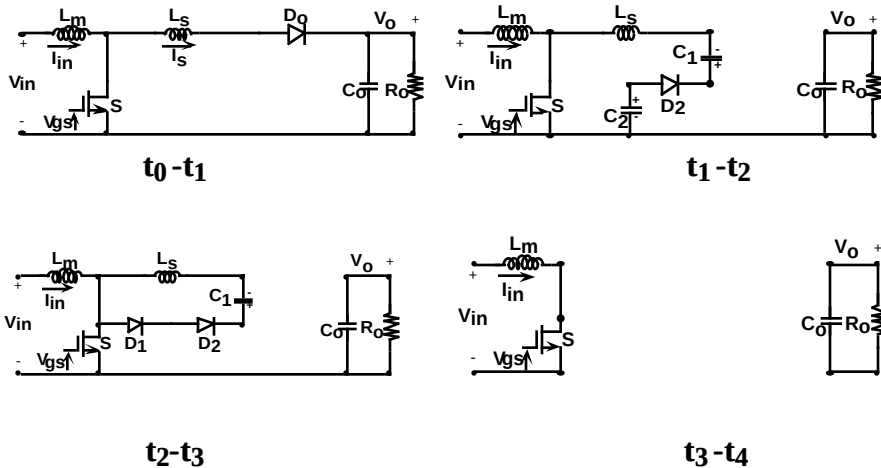

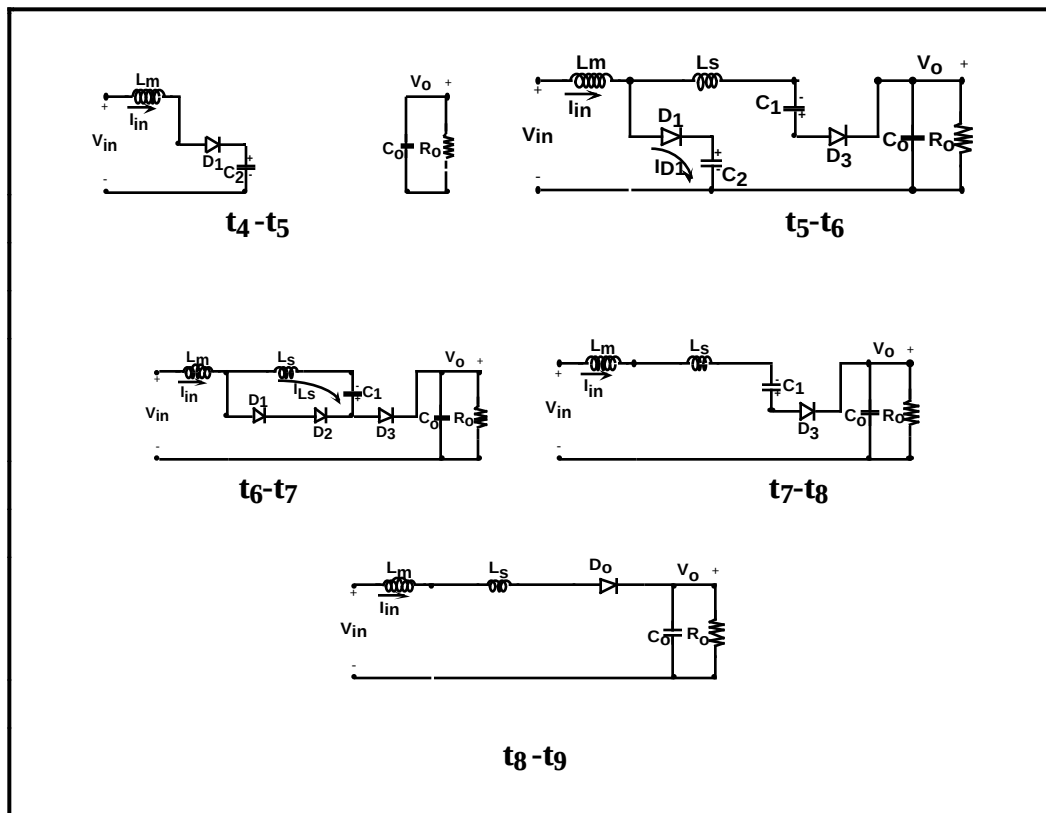

Simulation

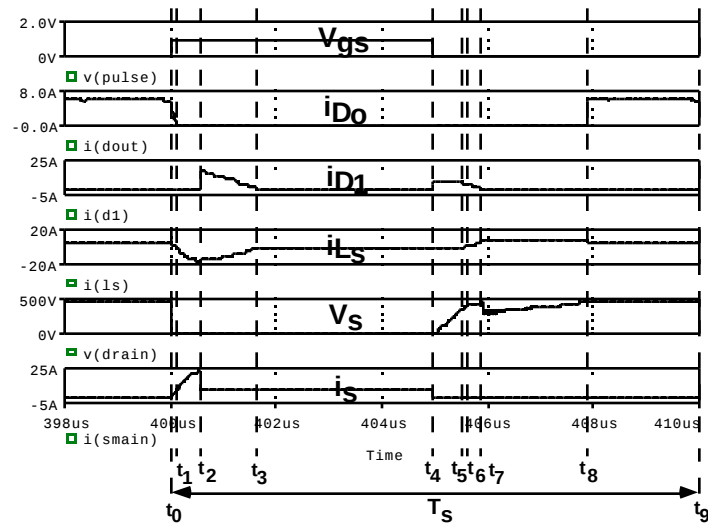

Interval t_0 - t_1

$$i_s = \frac{V_o}{L_s} t \quad \text{ZCS!}$$

$$\frac{di_s}{dt} = \frac{V_o}{L_s}$$

$$i_{D0} = I_{in} - i_s$$

$t_1 - t_0$ is found from the

condition: $i_{D0}(t_1) = 0$

$$t_1 - t_0 = \frac{I_{in} L_s}{V_o}$$

$$v_{C1} = 0 \quad ; \quad v_{C2} = V_o$$

Interval t_1 - t_2	$i_s = I_{in} + i_{Ls}$
$t_1]$	$i_{Ls} = i_{C1} = i_{C2} = i_{D2} = \frac{V_o}{\sqrt{\frac{L_s}{C_{12}}}} \sin[\omega_{r12}(t - t_1)]$
	where $C_{12} = \frac{C_1 C_2}{C_1 + C_2}; \quad \omega_{r12} = \frac{1}{\sqrt{L_s C_{12}}}$ $v_{C1} = V_o \frac{C_2}{C_1 + C_2} \{1 - \cos[\omega_{r12}(t - t_1)]\}$ $v_{C2} = -$ $v_{D1} = V_o \frac{C_2}{C_1 + C_2} \{1 + \frac{C_1}{C_2} \cos[\omega_{r12}(t - t_1)]\}$ $v_{D1}(t_2) = 0$ $\frac{C_2}{C_1}$
	$t_2 - t_1$ is found from the condition: $t_2 - t_1 = \frac{1}{\omega_{r12}} \cos^{-1}(-\frac{C_2}{C_1}) = \sqrt{L_s C_{12}} \cos^{-1}(-\frac{C_2}{C_1})$ $i_{D0} = i_{D1} = i_{D3} = 0$

Interval t_2-t_3 $i_s=I_{in}$

$$i_{Ls}=i_{C1}=i_{D1}=i_{D2}=-\frac{V_{C1}(t_2)}{\sqrt{\frac{L_s}{C_1}}} \sin[w_{r1}(t-t_2)]+i_{Ls}(t_2)\cos[w_{r1}(t-t_2)]$$

where

$$w_{r1}=\frac{1}{\sqrt{L_s C_1}}$$

t_3-t_2 is found from the condition:

$$i_{D1}(t_3)=i_{D2}(t_3)=0$$

$$t_3-t_2=\frac{1}{w_{r1}}\tan^{-1}\left(\frac{i_{Ls}(t_2)\sqrt{\frac{L_s}{C_1}}}{v_{C1}(t_2)}\right)=\frac{1}{w_{r1}}\tan^{-1}\left(\sqrt{\frac{C_1-C_2}{C_2}}\right)$$

$$v_{C1}=v_{C1}(t_2)\cos[w_{r1}(t-t_2)]+i_{Ls}(t_2)\sqrt{\frac{L_s}{C_1}}\sin[w_{r1}(t-t_2)]=$$

$$=V_o\frac{C_2}{C_1}\cos[w_{r1}(t-t_2)]+V_o\sqrt{\frac{C_2(C_1-C_2)}{C_1}}\sin[w_{r1}(t-t_2)]$$

$$v_{C1}(t_3)=V_o\sqrt{\frac{C_2}{C_1}}$$

Interval t_3-t_4

$$i_s=I_{in}$$

$$i_{D0}=i_{D1}=i_{D2}=i_{D3}=0$$

$$v_{D0}=-V_o$$

$$v_{C1}=v_{C1}(t_3)=V_o\sqrt{\frac{C_2}{C_1}}$$

$(C_2 < C_1)$

$$v_{C2}=0$$

Interval t_4-t_5

$$i_s=0$$

$$i_{D1}=I_{in}$$

$$v_s=v_{C2}=\frac{I_{in}(t-t_4)}{C_2}$$

$$\frac{dv_s}{dt}=\frac{I_{in}}{C_2}$$

ZVS!

$$C_1 = v_{C1}(t_3) = V_o \sqrt{\frac{C_2}{C_1}} \quad v_{D3} = v_{C2} + v_{C1} - V_o$$

$t_5 - t_4$ is found from the condition:

$$v_{D3}(t_5) = 0$$

$$t_5 - t_4 = \frac{V_o C_2 (1 - \sqrt{\frac{C_2}{C_1}})}{I_{in}}$$

Interval $t_5 - t_6$

$$i_s = 0; \quad i_{D0} = i_{D2} = 0$$

$$i_{D1} = I_{in} \frac{C_1}{C_1 + C_2} \left\{ \frac{C_2}{C_1} + \cos[\omega_{r12}(t - t_5)] \right\}$$

$$v_{C2} = V_o (1 - \sqrt{\frac{C_2}{C_1}}) + \frac{I_{in}}{\omega_{r12}(C_1 + C_2)} \left\{ \omega_{r12}(t - t_5) + \frac{C_1}{C_2} \sin[\omega_{r12}(t - t_5)] \right\}$$

Two operating modes are possible. They depend on the condition at t_6 of the interval $t_5 - t_6$:

$$\text{Mode 1 will prevail if :} \quad (v_{C2})_{t_6} = V_o$$


$$(i_{D1})_{t_6} > 0$$

$$\text{Mode 2 will prevail if :} \quad (i_{D1})_{t_6} = 0$$

$$(v_{C2})_{t_6} < V_o$$

$$\text{Necessary condition for Mode 1:} \quad \frac{V_o}{I_{in}} \sqrt{\frac{C_2}{L_s}} < k_C$$
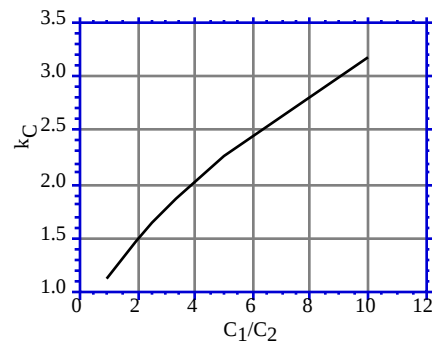
$$\text{where :} \quad k_C = \frac{1}{(1 + \frac{C_2}{C_1}) \sqrt{\frac{C_1}{C_2} + 1}} \left[\cos^{-1} \left(-\frac{C_2}{C_1} \right) + \sqrt{\left(\frac{C_1}{C_2} \right)^2 - 1} \right]$$



The dependence of k_C on $\frac{C_1}{C_2}$

- For Mode 1: $\frac{V_o}{I_{in}} \sqrt{\frac{C_2}{L_s}} < k_C$

t_6-t_5 is found from the condition: $v_{D2}(t_6)=0$; $v_{C2}(t_6)=V_o$

Interval t_6-t_7 , Mode 1, $i_s=0$; $v_s=V_o$

$$i_{D3}=I_{in}$$

$$i_{D1}=i_{D2}=I_{in}-i_{Ls}$$

$$i_{Ls} = \frac{V_{C1}(t_3)}{\sqrt{\frac{L_s}{C_1}}} \sin[\omega_{r1}(t-t_6)]$$

t_7-t_6 is found from the condition:

$$i_{D1}(t_7)=i_{D2}(t_7)=0$$

$$t_7-t_6 = \frac{1}{\omega_{r1}} \sin^{-1} \left(\frac{I_{in} \sqrt{\frac{L_s}{C_1}}}{V_o} \right)$$

$$\frac{1}{\omega_{r1}} \sin^{-1} \left(\frac{I_{in} \sqrt{\frac{L_s}{C_1}}}{V_o} \right) = \frac{1}{\omega_{r1}} \sin^{-1} \left(\frac{I_{in} \sqrt{\frac{L_s}{C_2}}}{V_o} \right)$$

Interval t_7-t_8 , Mode 1, $i_s=i_{D0}=i_{D1}=i_{D2}=0$; $i_{D3}=I_{in}$

$$v_{C1} = v_{C1}(t_7) - \frac{I_{in}(t-t_7)}{C_1}$$

t_8-t_7 is found from the condition:

$$v_{C1}(t_8)=0$$

$$t_8-t_7 = \frac{v_{C1}(t_7)C_1}{I_{in}}$$

$$v_s = V_o - v_{C1}$$

Interval t_8-t_9 , Mode 1,


$$i_s=i_{D1}=i_{D2}=i_{D3}=0;$$

$$i_{D0}=I_{in}$$

$$v_s \approx V_o ; \quad v_{C1}=0 ; \quad v_{C2}=V_o$$

LOSSLESS TURN-ON AND TURN-OFF SNUBBER (SNB8)

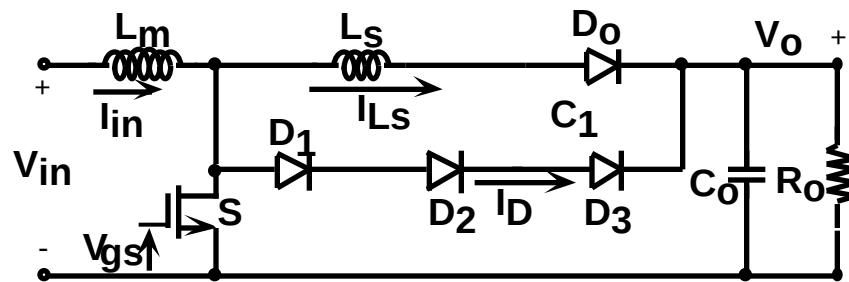Mode 2. Time interval before the switch Q is turned on



- Three auxiliary diodes are conducting
- Hard switching
- Coupling will help to avoid Mode 2.

TURN-ON TURN-OFF SNUBBER (SNB8)

Typical Design

Given: V_o , I_{in} , $(\frac{di_s}{dt})_{t_0-t_1}$, $(\frac{dv_s}{dt})_{t_4-t_5}$, D_{min} , D_{max}

$$1. L_s \geq \frac{V_o}{\left(\frac{di_s}{dt}\right)_{t_0-t_1}}$$

$$2. C_2 \geq \frac{I_{in}}{\left(\frac{dv_s}{dt}\right)_{t_4-t_5}}$$

$$3. k_C > \frac{V_o}{I_{in}} \sqrt{\frac{C_2}{L_s}} > 1$$

4. Select C_1/C_2 using the plot $k_C = j \left(\frac{C_1}{C_2}\right)$.

$$5. t_{on \min} = \frac{I_{in} L_s}{V_o} + \sqrt{L_s C_2} \cos^{-1} \left(-\frac{C_2}{C_1} \right) + \sqrt{L_s C_1} \tan^{-1} \left(\sqrt{\frac{C_1 - C_2}{C_2}} \right)$$

$$6. t_{off \min} = \frac{V_o C_2}{I_{in}} \left[1 + \sqrt{\frac{C_1}{C_2} \left(1 - \frac{I_{in}^2 L_s}{V_o^2 C_2} \right)} \right] + \sqrt{L_s C_1} \sin^{-1} \left(\frac{I_{in} \sqrt{\frac{L_s}{C_2}}}{V_o} \right)$$

$$7. D_{\min} = (t_{on \min}) f_s ; D_{\max} = (1 - t_{off \min}) f_s$$

8. Current stress of the switch S

$$I_{s \text{ pk}} = I_{in} + V_o \sqrt{\frac{C_{12}}{L_s}}$$


9. Voltage stress of the switch S

$$V_{s \text{ pk}} = V_o$$

Apply iteration to approach desired design goals



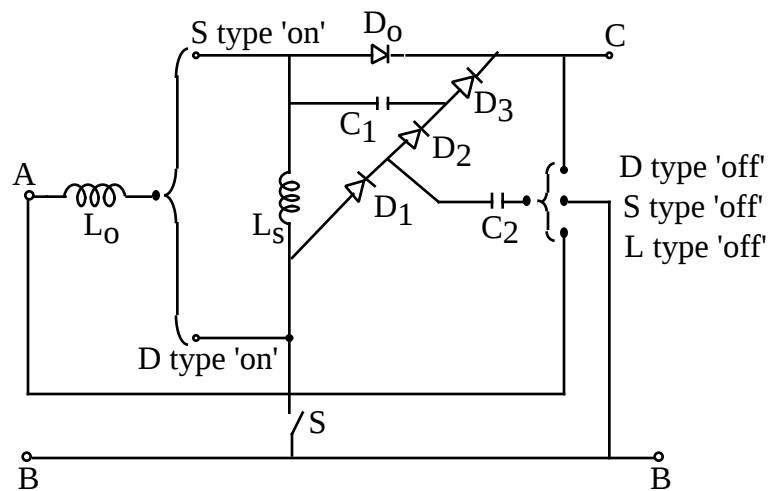
Some Additional Recent Turn-On & Turn-Off Passive Lossless LCC Snubbers



- Generic LCC 'turn-off' & 'turn-on' snubber topology


SNB8 discussed above (drawn differently)

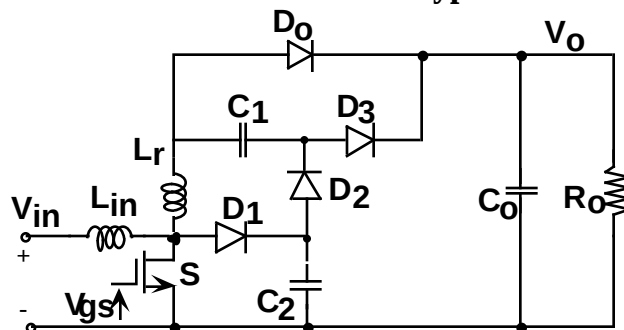Boost converter with LCC snubber: D type 'on' and S type 'off'




Moving the connection point to main inductor

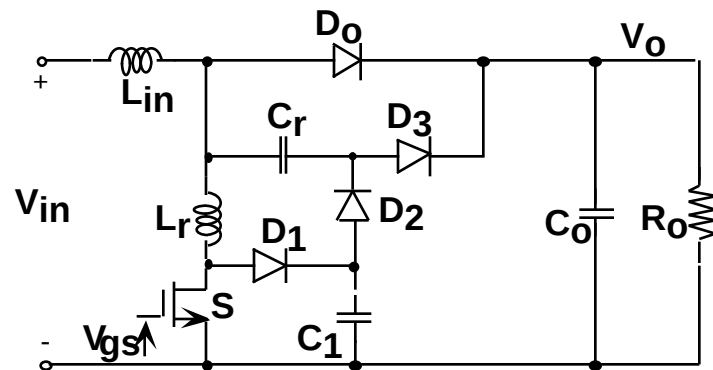Boost converter with LCC snubber: S type 'on'
and S type 'off' (SNB9) [16, 32, 39]




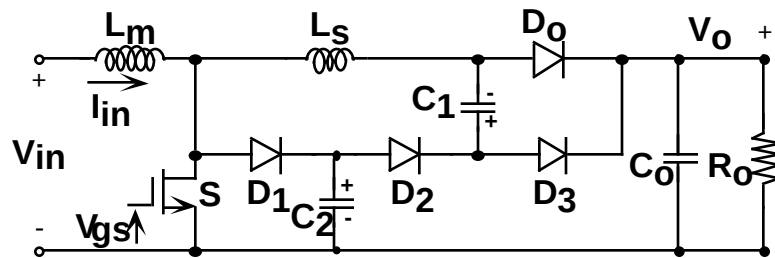Topologies similar to SNB8 and SNB9
with different capacitor C_2 connections [31, 32, 34, 46]



Original

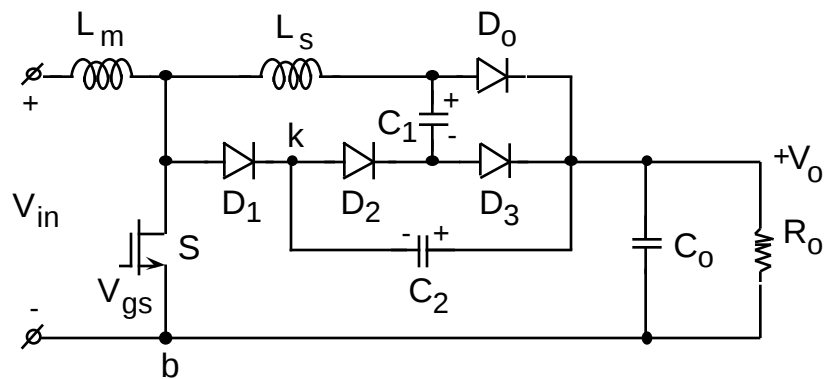SNB10: D type 'on' and D type 'off' [34, 46]




C₂ connected to output



Ripple to output

SNB11: D type 'on' and L type 'off' [32]

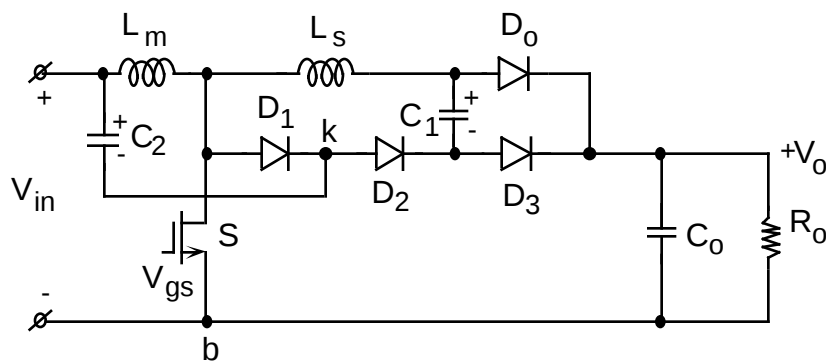


C₂ connected to input



Ripple stired to input

SNB12: D type 'on' and L type 'off' [31]

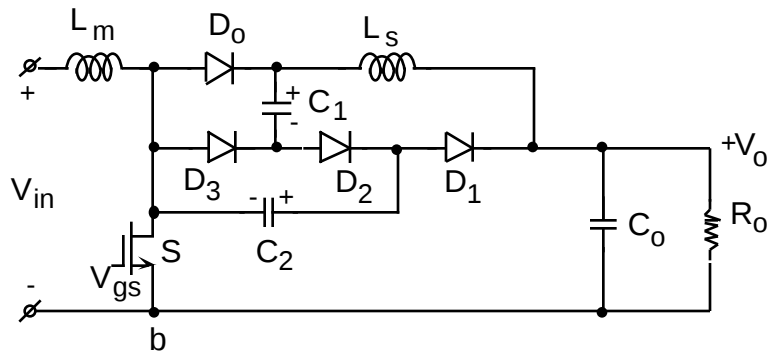


C_2 connected to switch



Stirs ripple to output

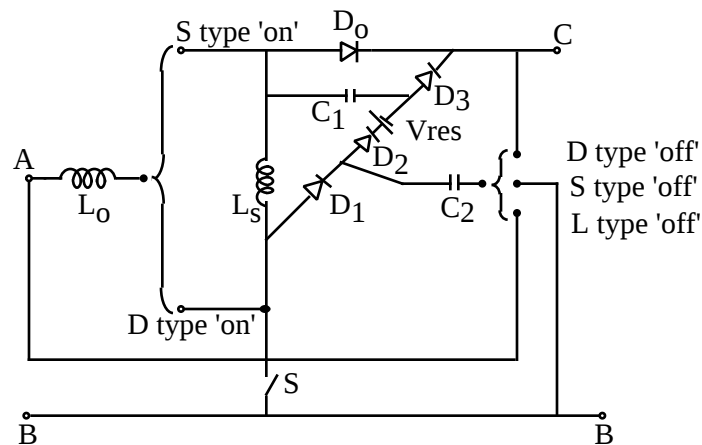
Generic LCC 'turn-off' & 'turn-on' snubber topology with improved reset



- V_{res} accelerates the reset phase

Turn-on and turn-off snubber for single switch converter

Improved Williams snubber SNB13 [10]

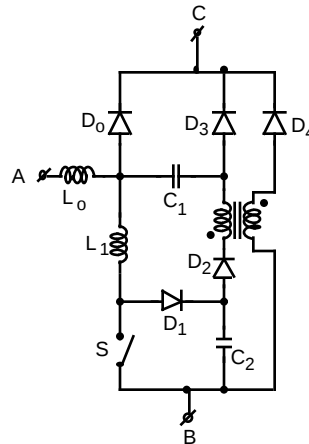

Operating process is based on a dual energy recovery circuit, improvement on SNB9.

- V_{res} replaced by transformer

Claimed to have:

1. Lower peak current in the switch S.
2. Shorter discharge time is needed for the capacitor C_1 at low load . Hence, wider operation range of load current and higher switching frequency.


🔍 Reset through transformer (leakage and reset problems ?)

See also snubbers with recovery transformers


[11-13]

Boost converter with LLC-type snubber (SNB14)

[1, 23, 45]

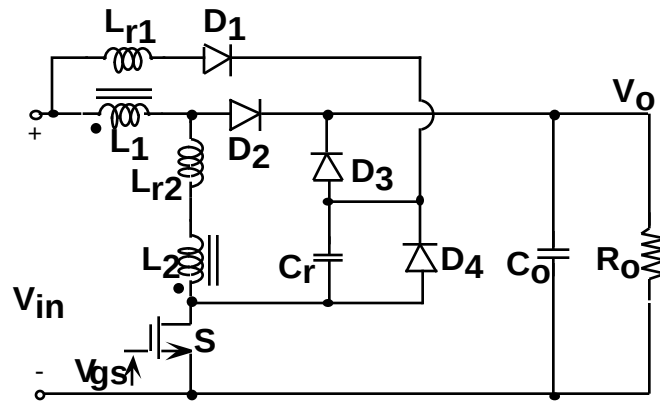

Coupled inductor

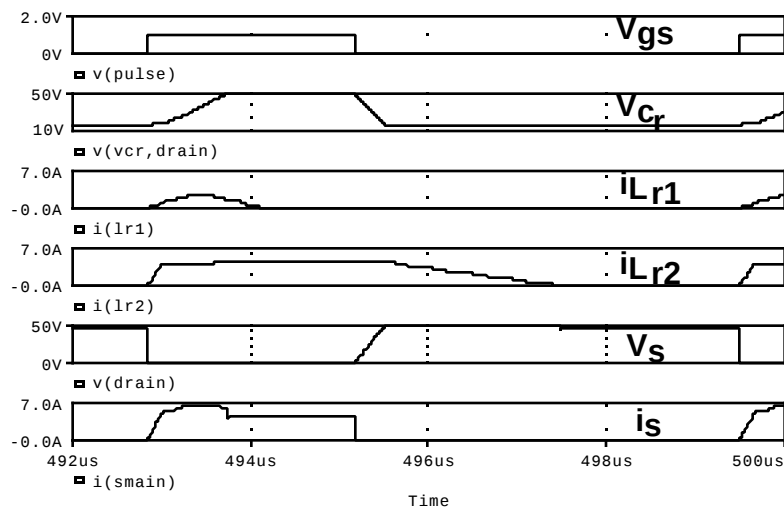

Basic waveforms of SNB14

SNB14 Features


Pro

1. Soft switching at turn-on and turn-off in a wide load range without high current and voltage stresses.
2. Coupling decreases the minimal needed value of turn-off time of the switch.

Con

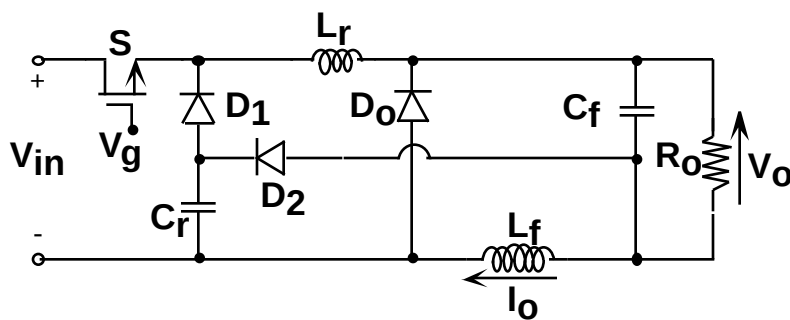
1. The resonant circuit L_1C_r is fed from the input voltage V_{in} . Hence, the peak capacitor's voltage cannot be higher $2V_{in}$. Consequently, when $V_o > 2V_{in} \Rightarrow$ hard switching.

Buck converter with LC type snubber (SNB15) [2, 36] (one inductor and one capacitor)



- No common ground !

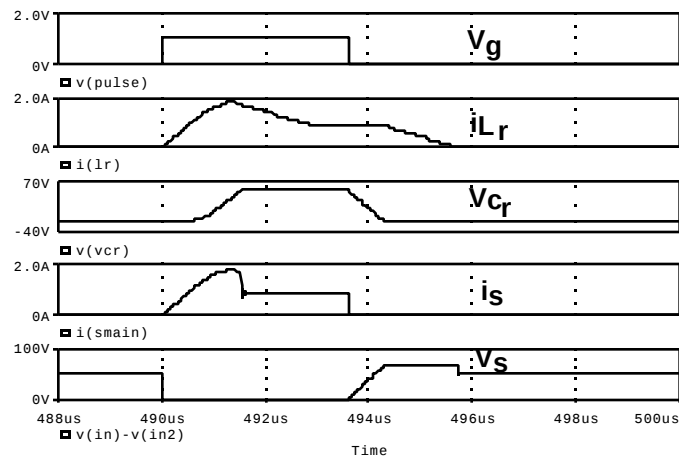See boost converter with LC type snubber in [41]




Waveforms of SNB15

{'Turn-on'}, {'turn-off'} and {'turn-on' - 'turn-off'} snubbers


Can parasitic elements be used ?

1. 'Turn on'

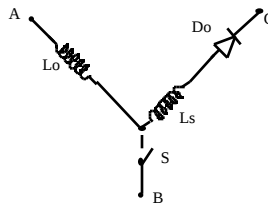

- L_s relatively large inductance to lower $\frac{dI}{dt}$ and hence diode peak reverse current and trapped energy
- Need a mechanism for recovering trapped energy
- 👁 Impractical to obtain by stray inductance such as interconnections
- 👁 Can be part of transformer or flyback coupled inductor

2. 'Turn off'

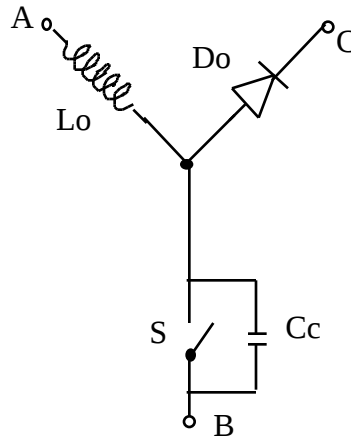

- C_c significant inductance to lower $\frac{dV}{dt}$
- C_c is mainly needed while voltage on switch is low



Switch output capacitance would be helpful and sometime sufficient

2. 'Turn off' - cont.




If internal capacitance is used:

- fast gate 'turn off'
- high sink current
- low source inductance "fast switch"



Look up new MOSFET generations (APT V)

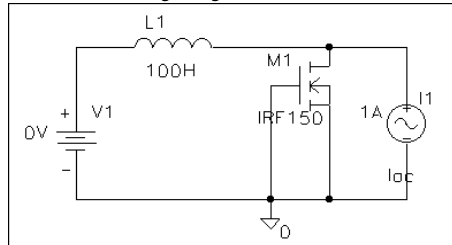
Output Capacitance of MOSFETs A study by Simulation



- Nested AC analysis
- V_1 is swept from 0V to 100V
- I_{ac} is set to 1A (not to worry, used after linearization)
- Capacitance is calculated from:

$$C_{out} = \frac{1}{2 \rho \text{ frequency } v_{ds}}$$

'frequency' -> PSPICE variable

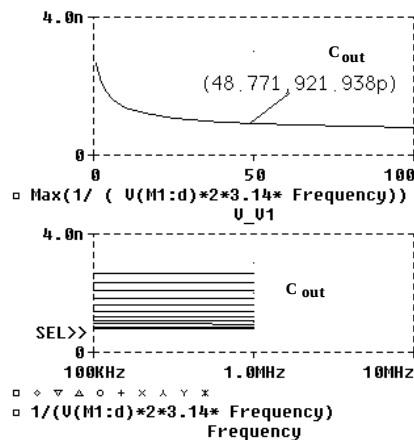


Upper trace: C_{out} as a function of V_{DS}

Lower trace: C_{out} as a function of frequency for various V_{DS} values.


- About 1 nF at 50V
- For significant improvement added snubber capacitance > 1nF

Simulating Snubbing Effects 'turn-off'

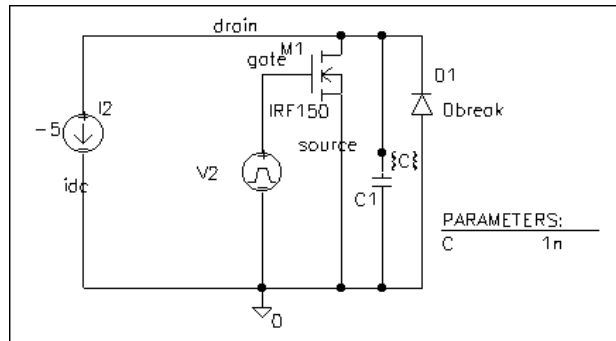

- Transient analysis
- C is swept 0nF - 10nF

C=0

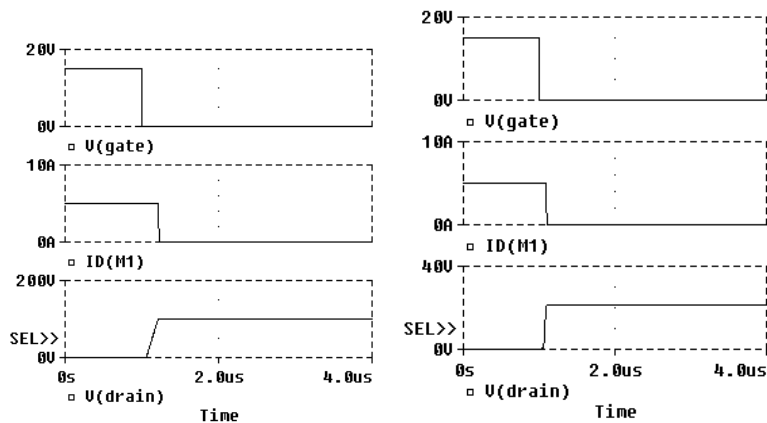


Drain clamped to 100V

Drain clamped to 20V


- Drain current reflects charging of internal capacitor
- Part of energy stored as $\frac{C V^2}{2}$ --> losses at 'turn-on' !
- Not all of $\{I_D \cdot V_{DS}\}$ at 'turn off' duration is lost to heat

C = 0 & 1nF

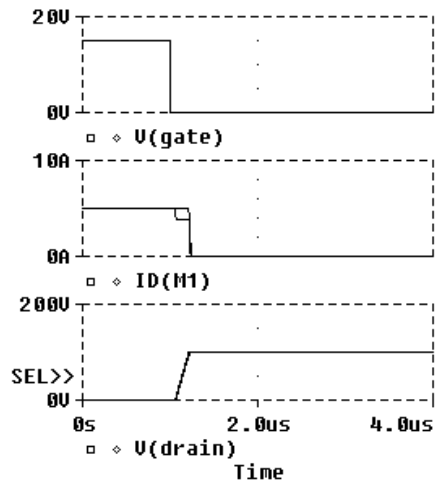

- Small part of current channeled to snubbing capacitor

C = 0 & 10nF

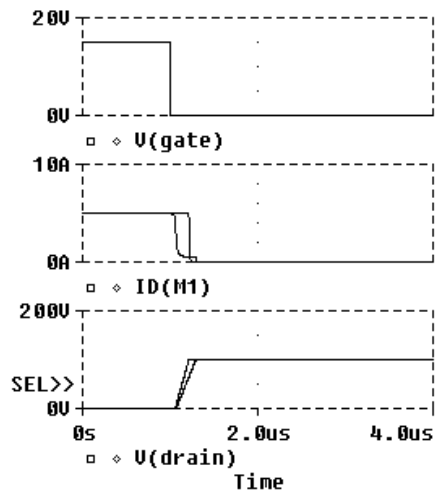


- Current channeled to 10nF capacitor
- Internal capacitor still charges to the same voltage !

Chapter 7

RECTIFIER DIODES LOSSLESS SNUBBERS



PHASE SHIFTED PWM (PSPWM) [18, 19, 27]



ZVS of main switches

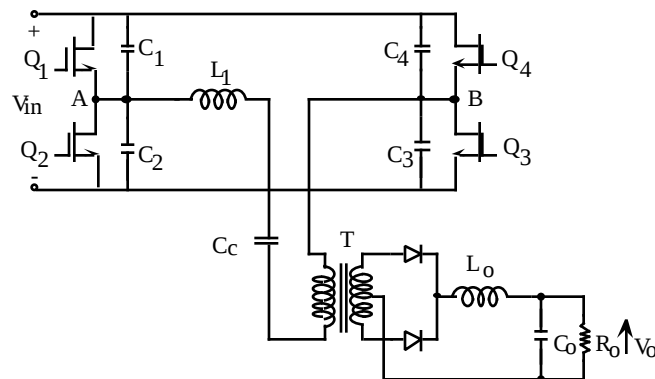


Basic Phase Shifted PWM Stage


- Leading and lagging legs (bridge non-symmetrical)
- Coupling capacitor C_c needed to block current
 - Asymmetry of control (+noise !)
 - Can be eliminated by applying peak current mode control

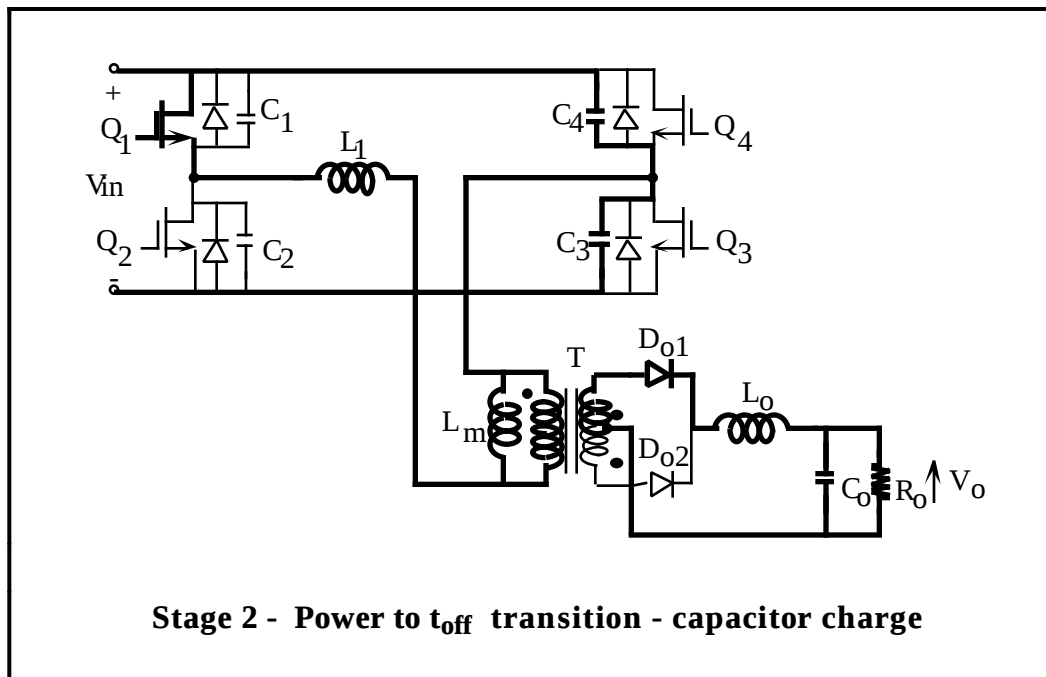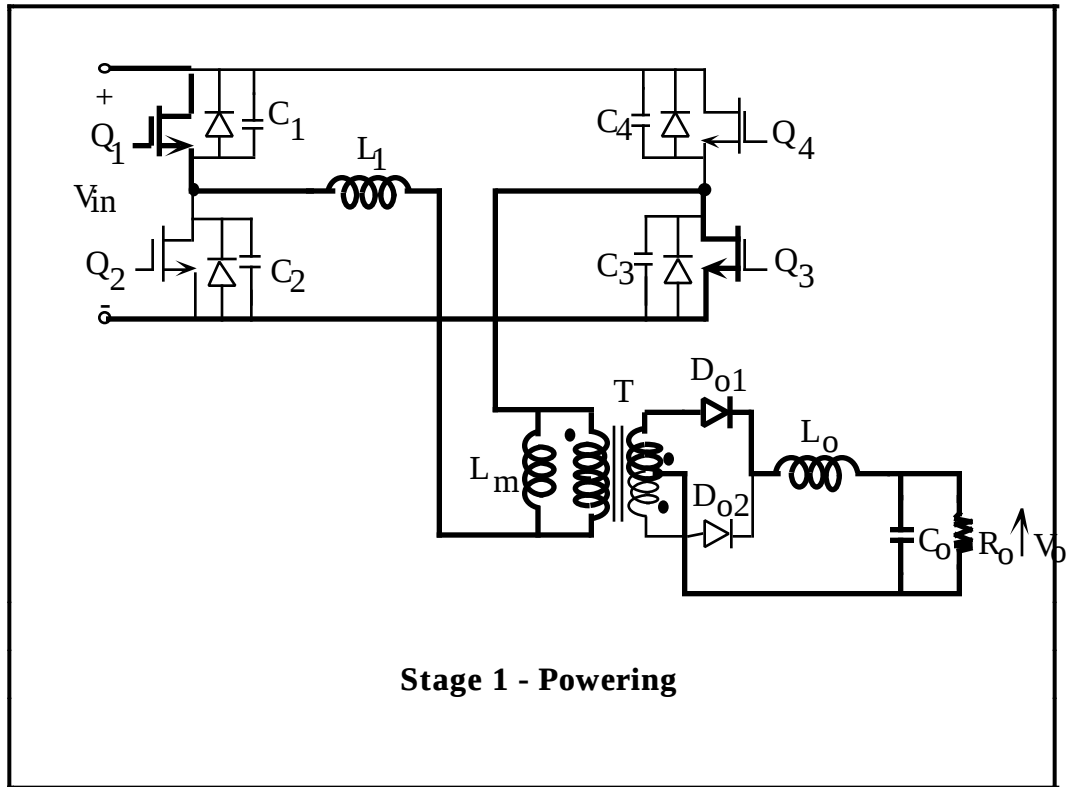

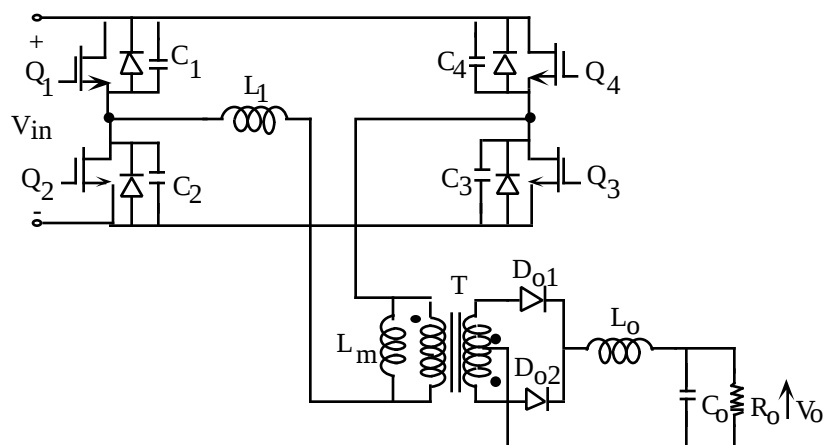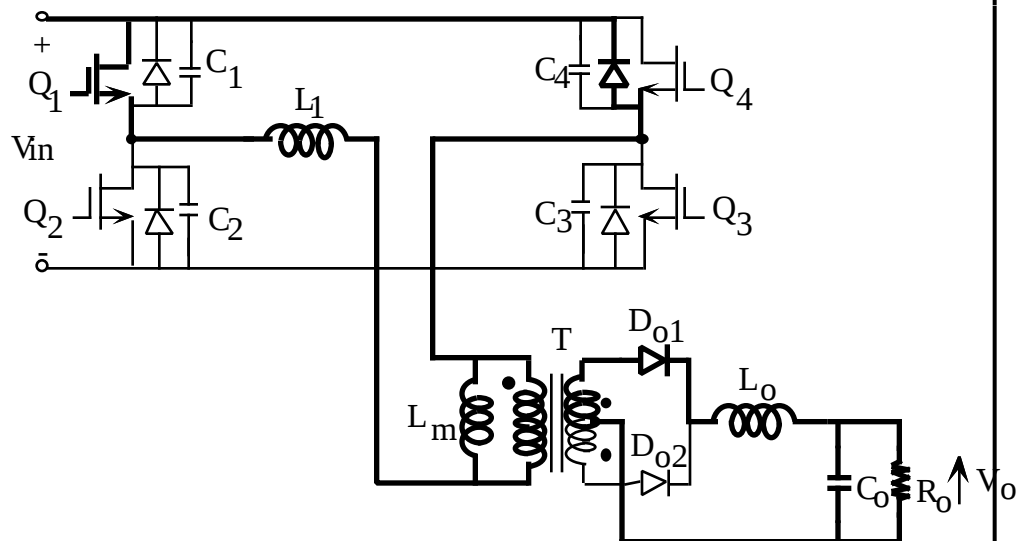


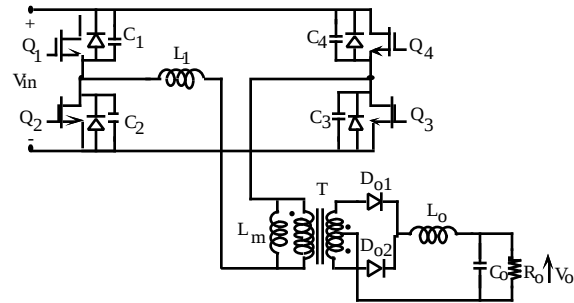

Stage 5 - t_{off} to Power Transition

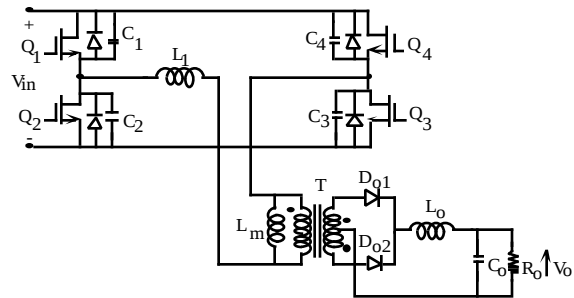

Back to Power Mode

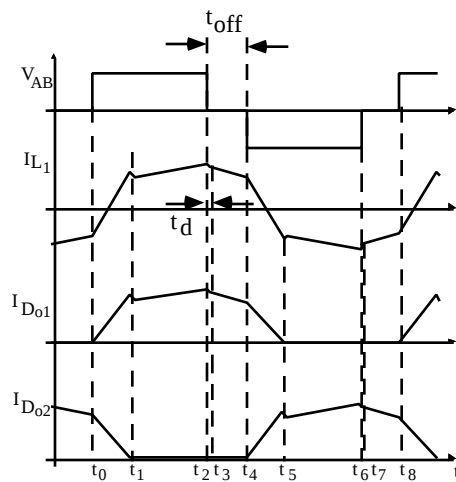

Waveforms

- Two rectifier diodes are conducting during t_{off}

PSPWM DESIGN OVERVIEW

Basic Conventional Phase Shift PWM design equations

$$\frac{I_{off}^2 L_r}{2} \geq \frac{(C_A + C_B) V_{BUS}^2}{2}$$

$C_A + C_B$ = total leg capacitance

or:

$$I_{off} \sqrt{\frac{L_r}{C_A + C_B}} > V_{BUS} \implies I_{off} Z_r > V_{BUS}$$

where the characteristic impedance is defined as usual:

$$Z_r = \sqrt{\frac{L_r}{C_A + C_B}}$$

The transition time (need to be larger than 1/4 of the resonant period)


$$t_d \geq \frac{2\pi \sqrt{L_r(C_A + C_B)}}{4}$$




In the conventional scheme, L_1 need to be relatively large to store sufficient energy at low load current . This can be somewhat improved by making the primary current larger (lower L_m transformers magnetization inductance) .



If the short circuit (two diodes conducting) during t_{off} is avoided (only one diode conducts) L_1 can be small since the energy comes from the secondary

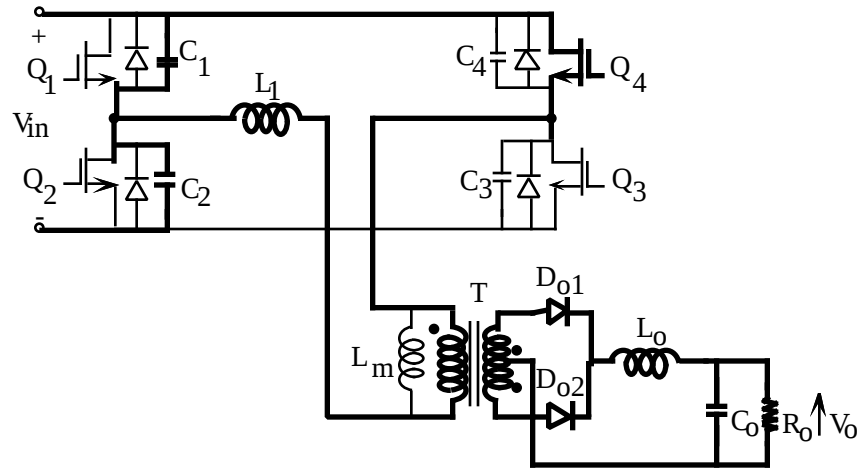

Stage 5 - t_{off} to Power Transition - two diodes conducting

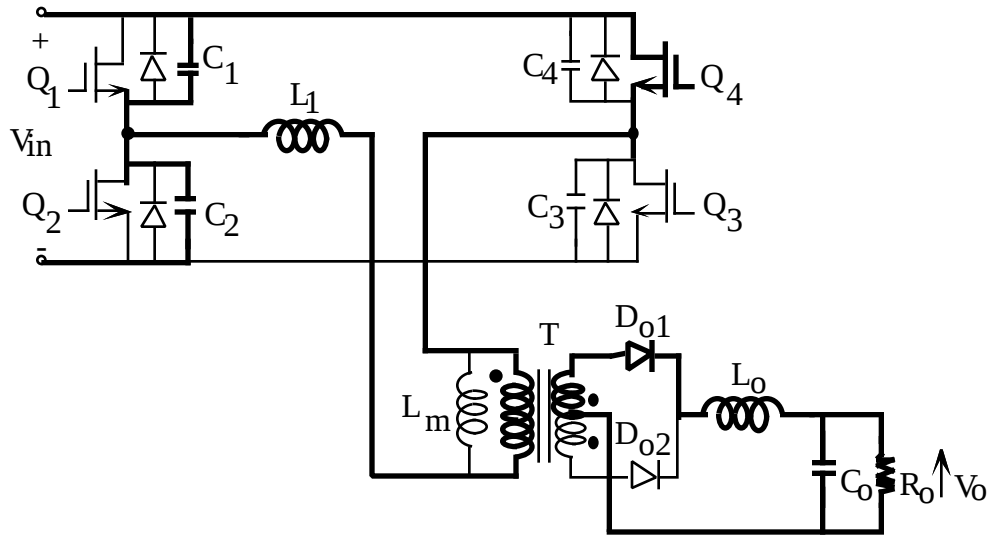


Stage 5 - t_{off} to Power Transition - one diode conducting



If only one diode conducting ==> L_1 id not needed

RESIDUAL ISSUES IN PSPWM


1. Circulating Current

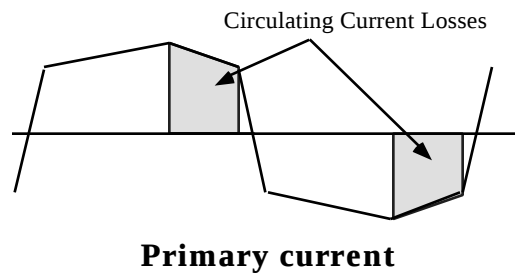

- Thermal design of power stage for duty cycle $D \Rightarrow 1$
 $\Rightarrow$ The circulating current at $D < 1$ not a major problem


• Possible Solution

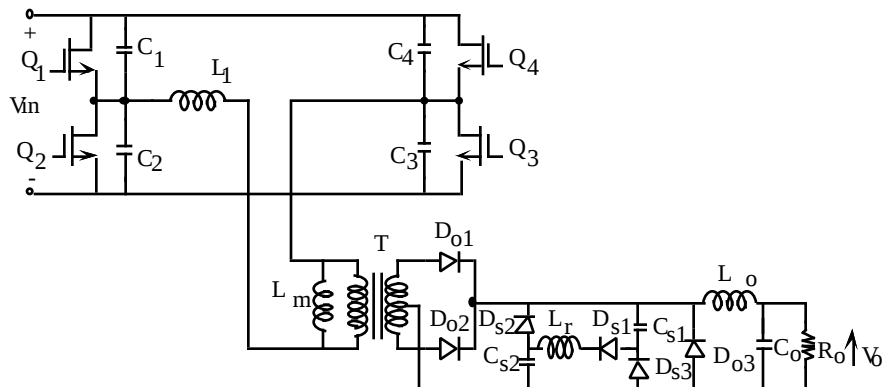Apply the 'One Way' capacitor to block primary current at t_{off}



Lossless output snubber SNB16 [18]


- L_r and C_s form a resonant circuit

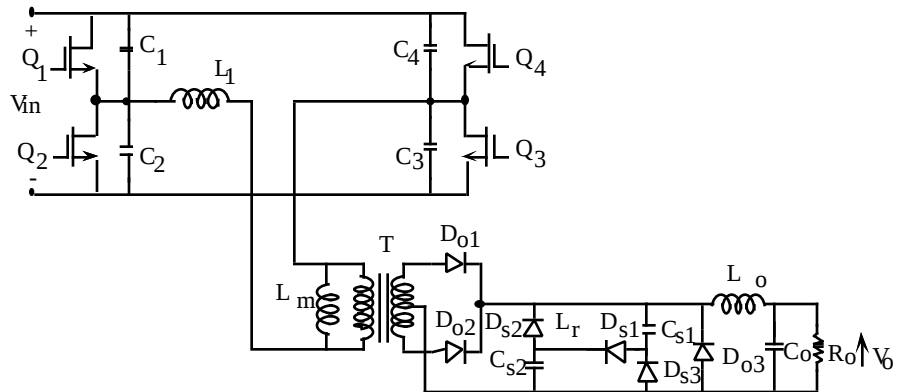

Modified lossless output snubber SNB17 [19]



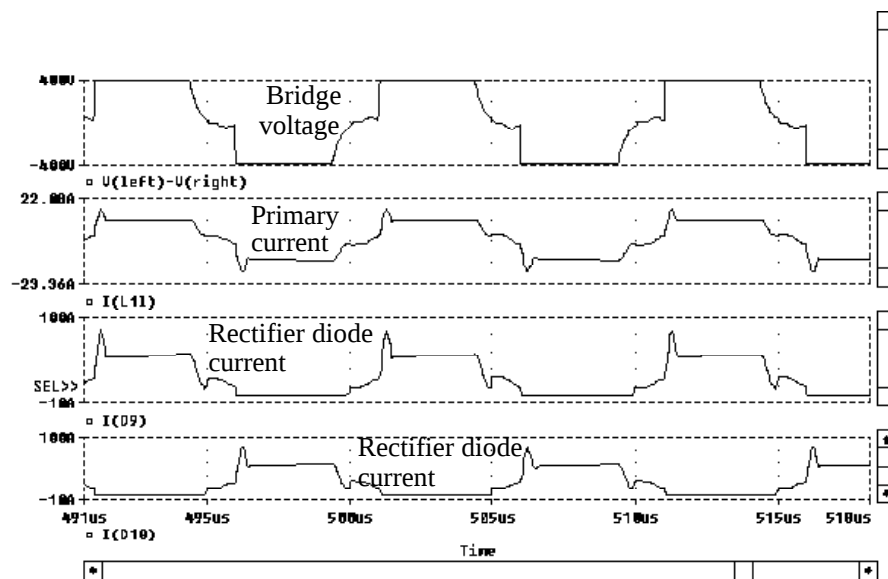Resonant inductor can be moved to primary




Basic waveforms of SNB17 (Simulation)


- Suitable for IGBT (zero current at t_{off} combats current tail)

RESIDUAL ISSUES IN PSPWM

2. Rectifier's diodes reverse recovery

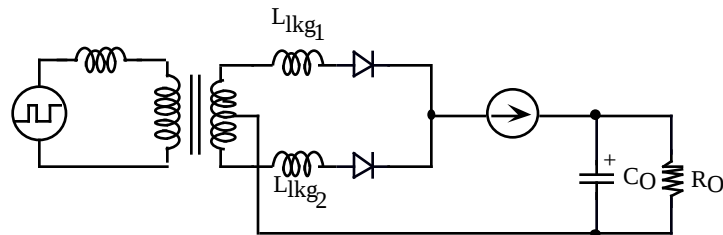

Leakage inductance at secondary

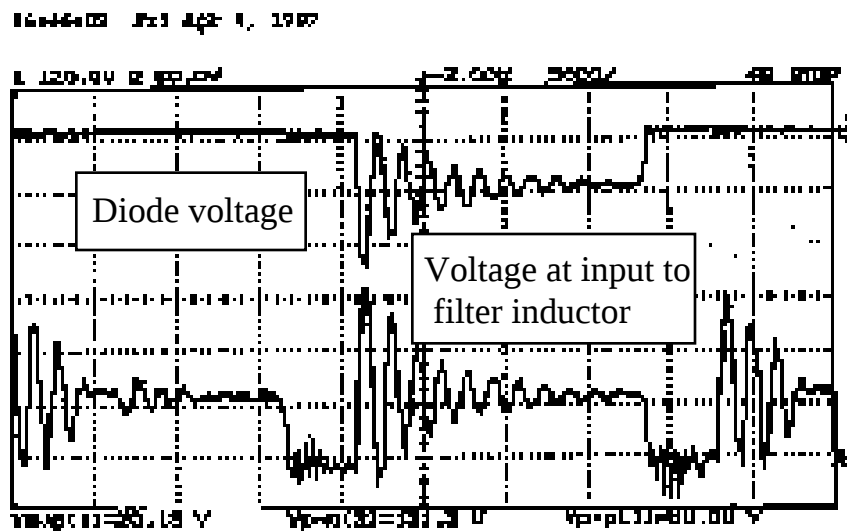



Experimental waveforms

- Greatly influenced by transformer leakage

RESIDUAL ISSUES IN PSPWM

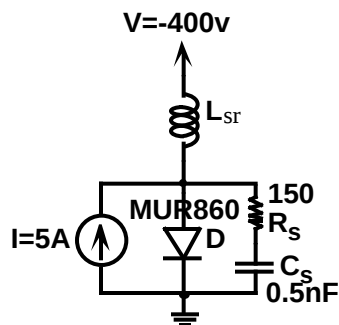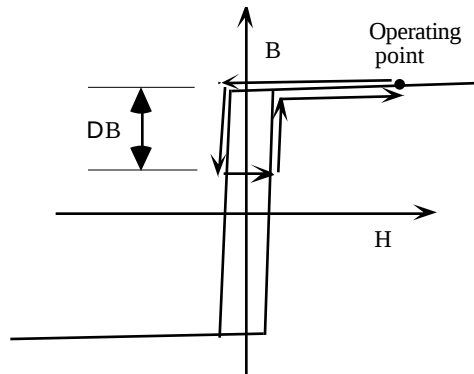
2. Rectifiers' diodes reverse recovery

- Possible Remedy -> Saturable reactor (SR) [7, 8, 9, 14, 43]



Simulation Circuit

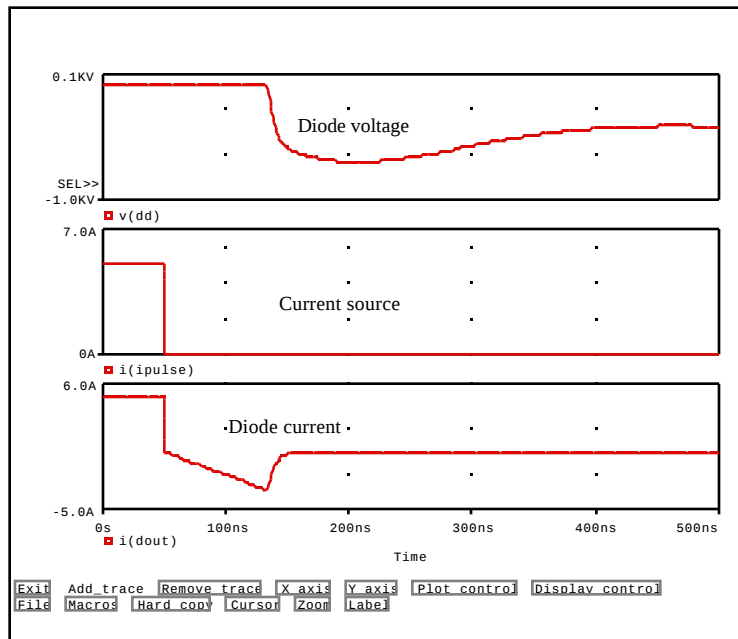- Using fast diode
- Current source establishes the forward current and abrupt change
- L_{sr} emulate "large" back inductance



Simulation waveforms ($L_{sr} = 50\text{nH}$)

RESIDUAL ISSUES IN PSPW

2. Rectifiers' diodes reverse recovery

- Design equations overview

Magnetic flux swing (one sided)

$$DB = \frac{VT}{2 n A_c}$$

VT = volt-second across SR

A_c = core effective cross section area


n = number of turns

For Amorphous Alloy 2714AF (Allied):

Core Losses : P_{core} (W/Kg, mW/gr) = $10^{-6} (f_s)^{1.73} (DB)^{1.88}$

B = Magnetic flux (T) ; f_s = Switching frequency (Hz)
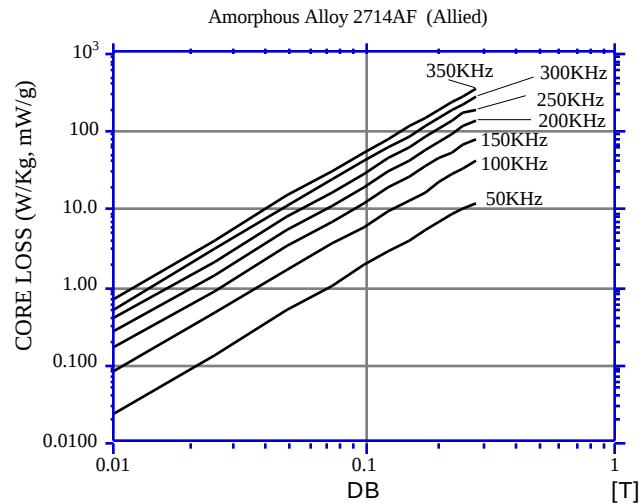
$$DB = (P_{core} / (10^{-6} (f_s)^{1.73}))^{(1/1.88)}$$




Extrapolated from Allied's data (originally given up to 200KHz)

RESIDUAL ISSUES IN PSPWM [42, 43]

2. Rectifiers' diodes reverse recovery

• Implementation in PSPWM

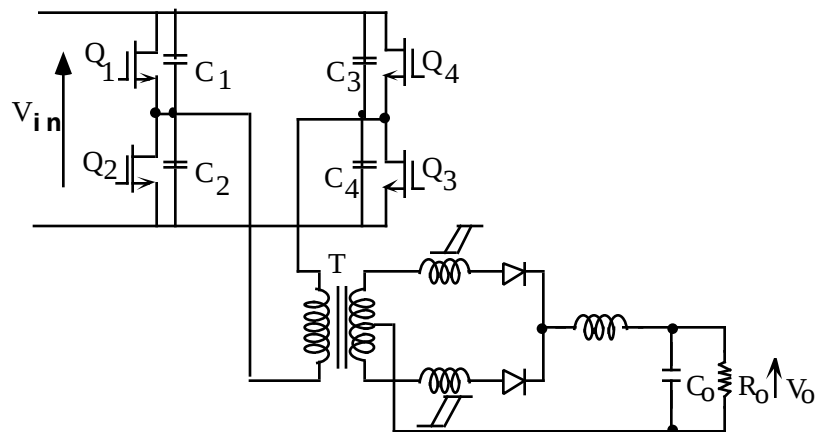


PSPWM with SR at output (SNB18)


RESIDUAL ISSUES IN PSPWM

2. Rectifiers' diodes reverse recovery

• Implementation in PSPWM

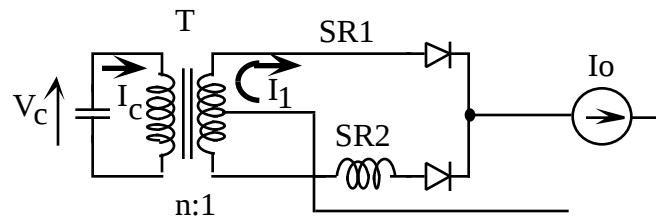


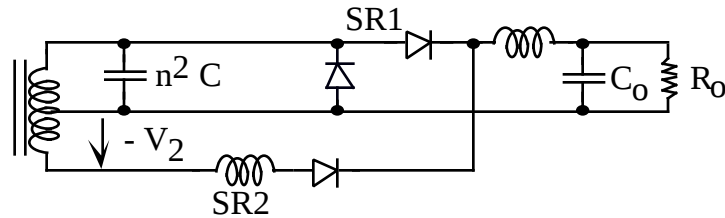
Situation at first commutation instance (power to t_{off})




Equivalent circuit during t_{off}

RESIDUAL ISSUES IN PSPWM


• Theoretical considerations

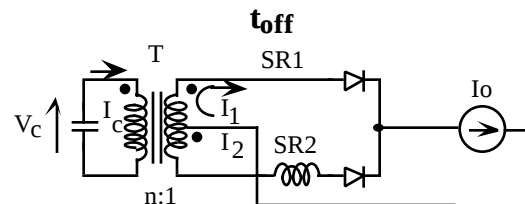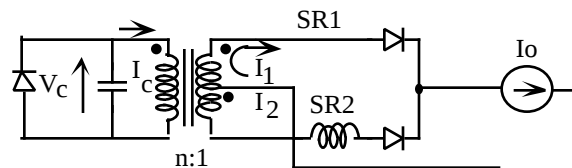


t_{off} release

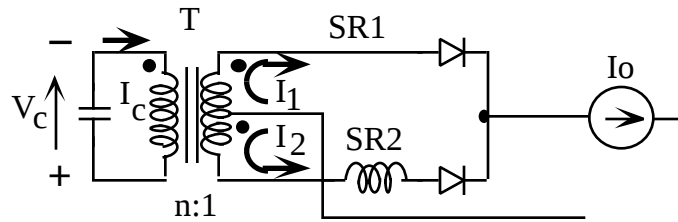


t_{off} to Power transition

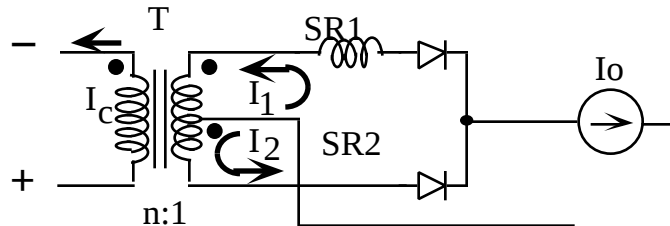

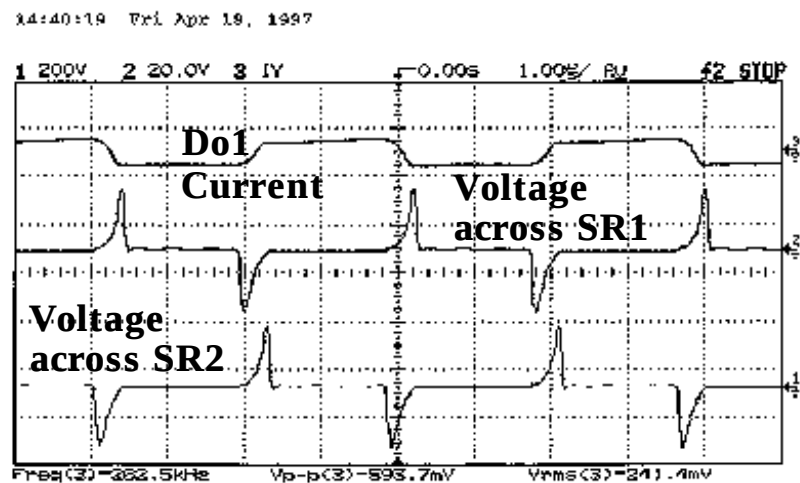Transition end (SR1 blocks reverse recovery current)



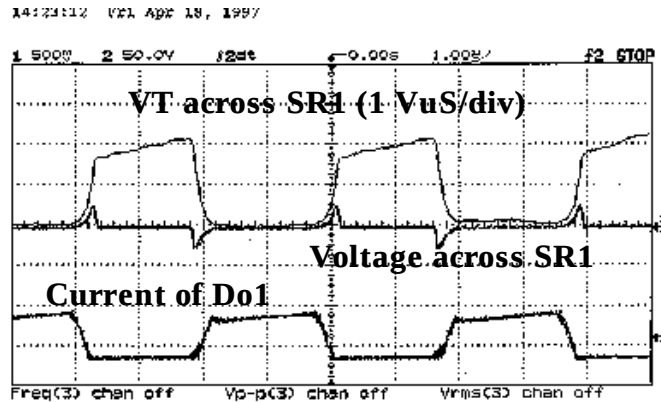Current through rectifier leg and voltage across SR



Volt Second of SR

Design Guidelines

1. Choose SR to keep core losses low say : 50 mW/gr
2. Estimate VT


Example: Diode reverse voltage 100V

$$t_{rr}^a \text{ 100 nSec} \Rightarrow VT^a \text{ 10 Vns}$$

For Amorphous Alloy 2714AF (Allied):

$$P_{core} \text{ (W/Kg, mW/gr)} = 10^{-6} f^{1.73} B^{1.88}$$

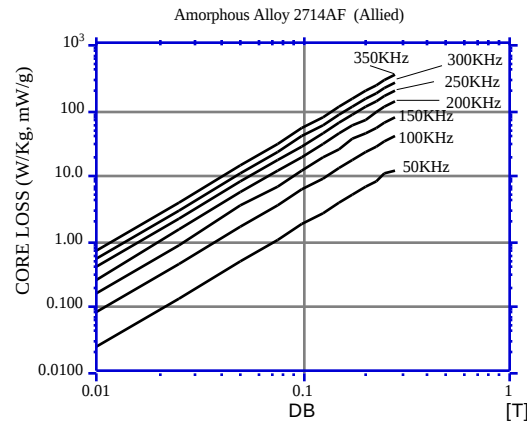Assume $P_{core} = 50 \text{ mW/gr}$; $f = 270 \text{ KHz}$



From loss equation $\Rightarrow DB = 0.125T$

From $DB = \frac{V T}{2 n A_c} \Rightarrow A_c = 0.4 \text{ cm}^2$

Using MP1906P-4AF (Allied):

$OD = 21\text{mm}; ID = 10\text{mm}; A_c = 0.16 \text{ cm}^2; n=1; 6.1 \text{ gr}$



Need at least 3 units per leg



Effective frequency is much higher than switching frequency



Being a small body (small surface area), might get very hot. 4 units per leg were used in experimental converter.

Experimental PSPWM Converter

Transformer: Payton 3000W T250-12-4C

Nominal Operating frequency = 350KHz

Input Voltage = 360 -390 Volt

Max. VT = 864 Vms

Primary to half secondary 6:1

Primary Max rms current: 11 Amp


Dielectric strength (primary to secondary) 2500 Vrms

Dielectric strength (secondary to core) 500 Vdc

Estimated power loss 65W (@ 60⁰C base plate)


Estimated hot spot 110⁰C

Mechanical dimensions 88*65*30(h) mm


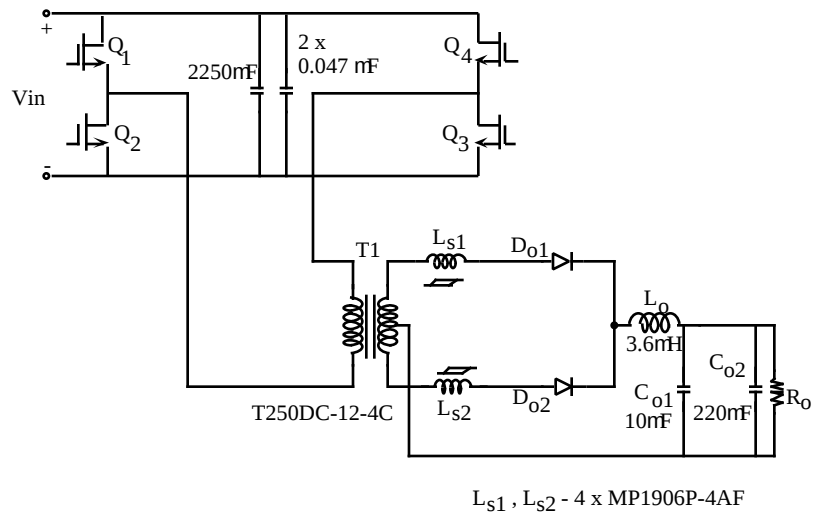


Experimental power stage



Experimental Results

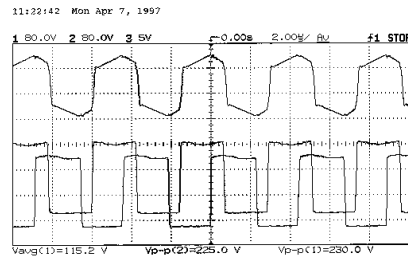

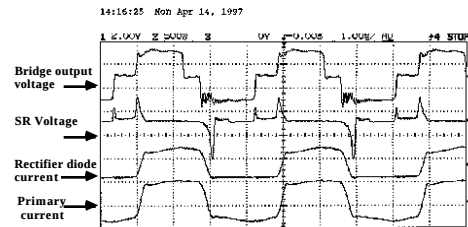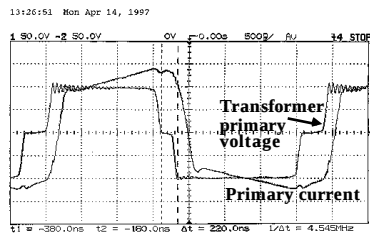
Primary current (upper) and leg voltages (lower)




In circuit SR Performance

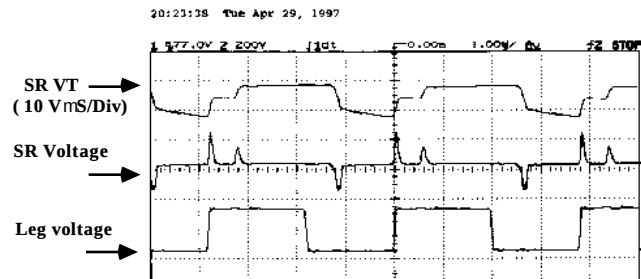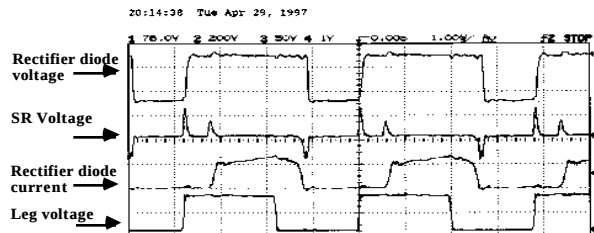

Experimental Results

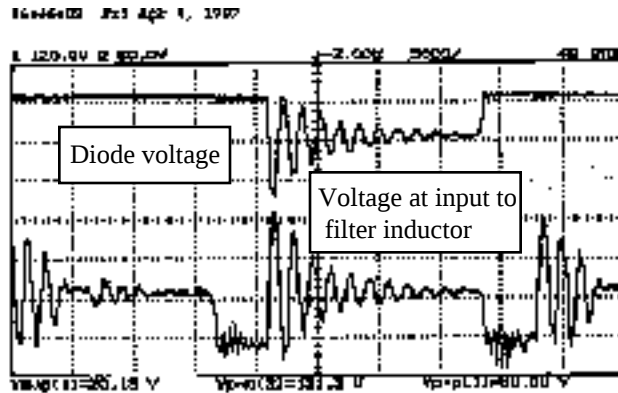


Experimental waveforms (no SR snubber)

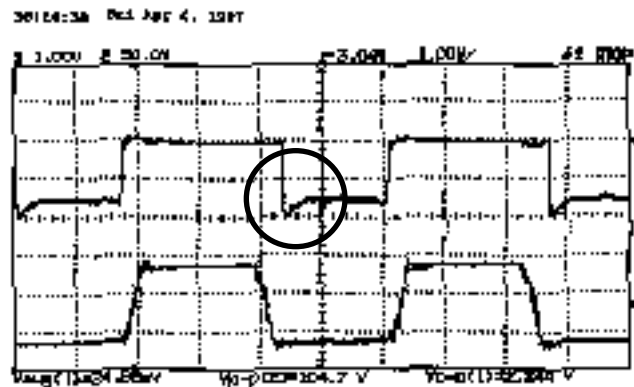

Rectifier diode voltage (upper trace) and current (lower)
with amorphous core


- Some overshoot due to energy stored in SR

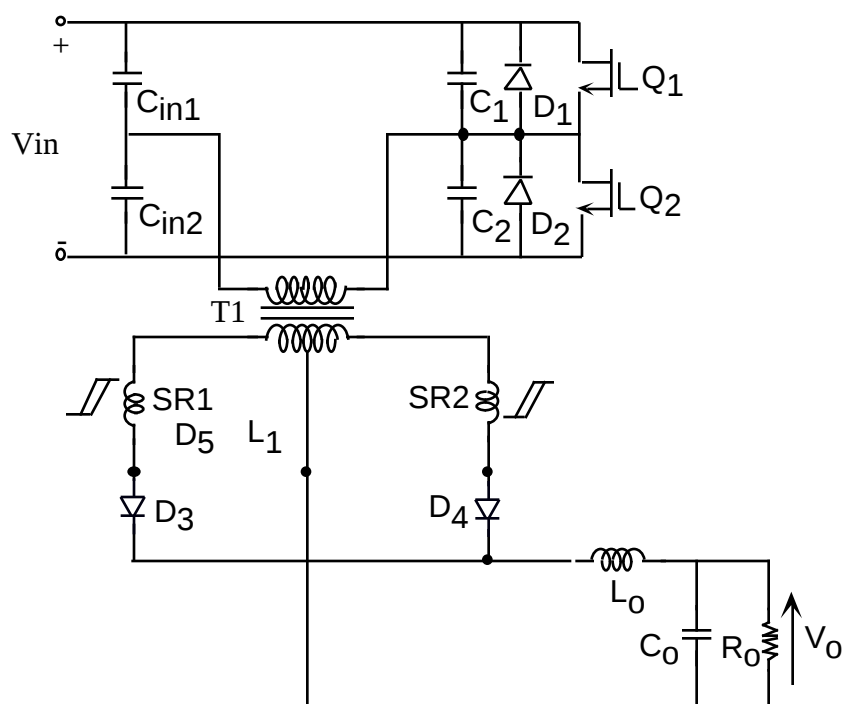Improved magnetic snubber for rectifier diodes in DC/DC converters



- Basic solution [42,43]


Dependence on L - Simulation

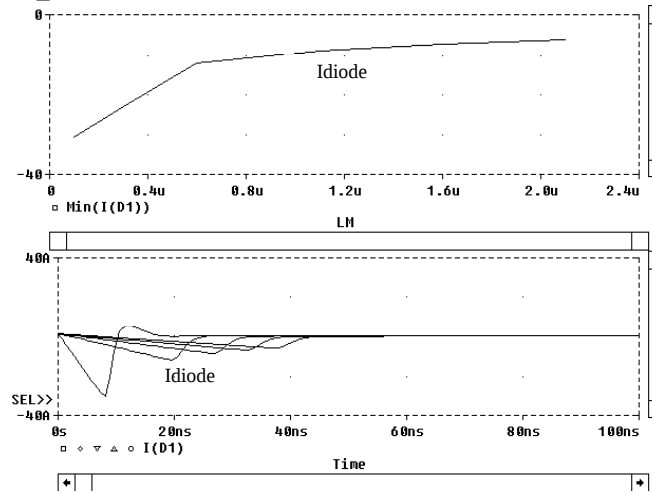

Diode reverse recovery switching waveforms




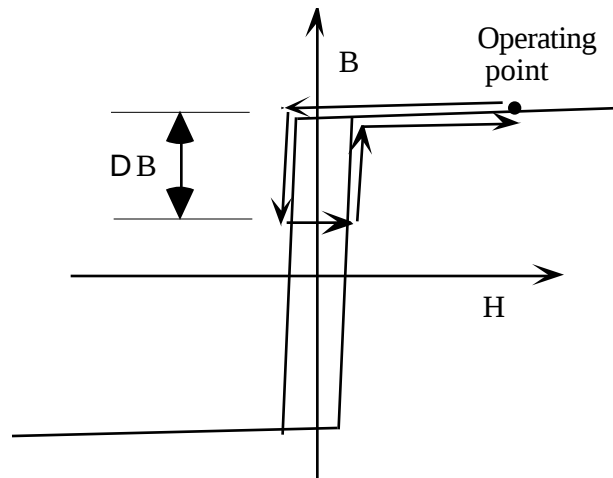Actual reverse recovery time is a function of series inductance




Long reverse recovery time will increase core losses

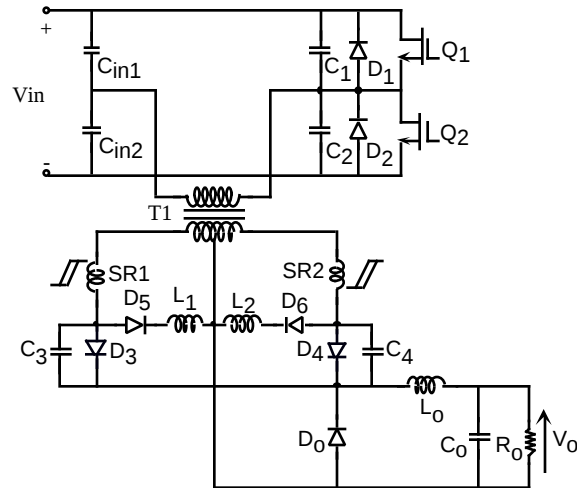Improved magnetic snubber for rectifier diodes in DC/DC converters [44]



Added elements: C_3 , C_4 , D_0 , L_1 D_5 & L_2 D_6

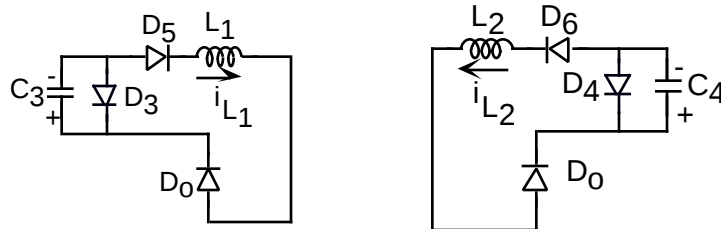-> Extra resonant circuit to sweep out stored charge




The stored charge of the diode D_3 (D_4) is pulled out rapidly ; therefore (t_{rr}) D_3 and (t_{rr}) D_4 decrease and hence core losses in SR1 and SR2 also reduce.

Chapter 8

COMBINING SNUBBER AND POWER SUPPLY FUNCTIONS

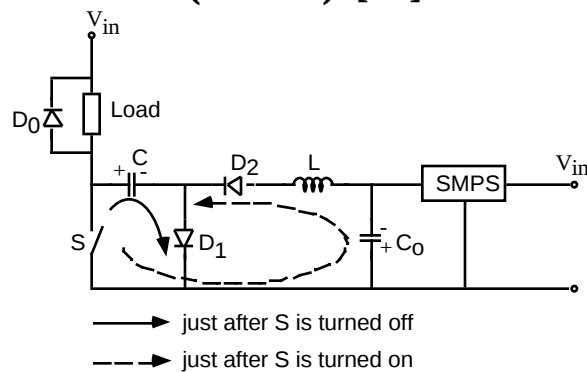Turn-off snubber with energy recovery back to the input bus or into a local power supply (SNB20) [39]



C = Snubber capacitor

C₀ = Filter capacitor


Negative polarity of voltage across C₀ !

- **The main purpose of the device: turn-off snubber**
- **Additional appointment: local power supply**



Watch for power level (in PS applications), might be too high

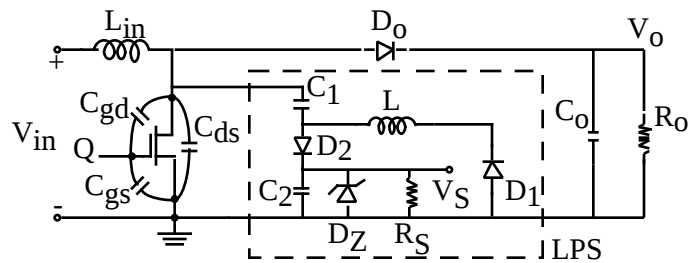A local power supply with turn off snubber features [47]



LPS - local power supply

R_s - load resistance

$C_2 \gg C_1$; D_Z - Zener diode

- **Positive polarity of output voltage V_s**
- **The main purpose of the device: A local power supply.**


Secondary objective: turn-off snubber

A local power supply with turn off snubber features

Main assumptions of analysis


- 1. Ideal diodes and ideal transistor. Parasitic capacitances of MOSFET are taken into account. It is assumed that these capacitances are linear.**
- 2. Lin , C_0 and C_2 are infinitely high**

Equivalent circuits

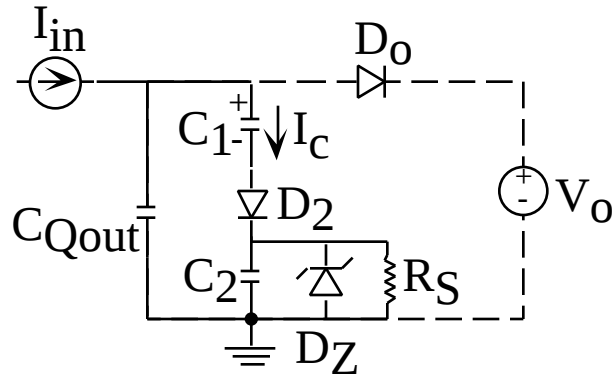


- t_0-t_1 : energy injection into LPS

Equivalent circuits

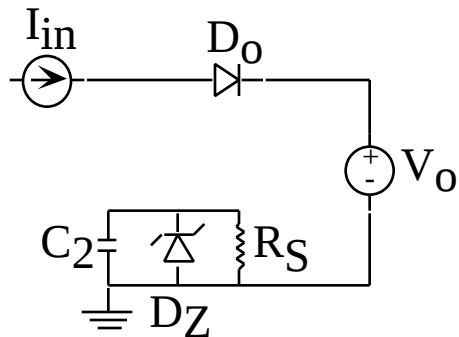


- t_1-t_2 : no interconnection between the processes in the LPS and in the converter

Equivalent circuits

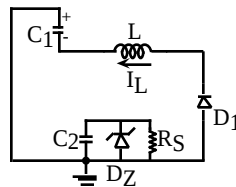


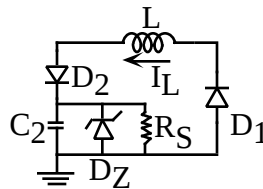t₂-t₃: energy transfer from the capacitor C₁ to the inductor L



- **t₃-t₄: energy transfer from the inductor L to the C₂ - D₂ - R_S circuit**

Current and voltage waveforms

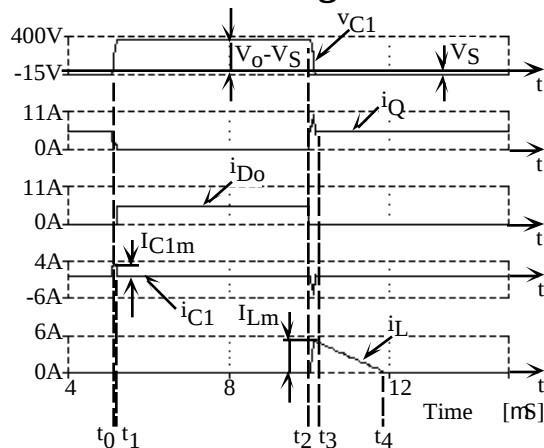

Proposed Local Power Supply (LPS) connected in a boost converter

Main relationships


Energy injected to LPS during one switching period

$$E = \frac{C_1 V_o^2}{2} = V_s (I_s + I_Z) T_s$$

$$I_s + I_Z = f_s C_1 \frac{V_o^2}{2 V_s}$$

$$I_{s \max} = f_s C_1 \frac{V_o^2}{2 V_s} \quad (\text{when } I_Z=0)$$

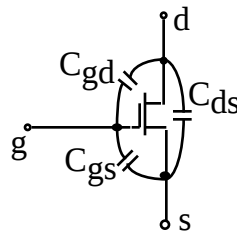LPS loaded by the MOSFET's controller driver



The average input current to the gate of the MOSFET

$$I_{g \text{ av}} = C_{Qin} V_{gs} f_s = k I_{s \max}$$

k = fraction of I_s used to power the gate ($k < 1$)

The required value of C_1

$$C_1 = \frac{2}{k} \frac{V_{gs}}{V_o} \left(C_{gd} \frac{\hat{V}_o}{\hat{V}_s} + \frac{V_{gs}}{V_o} + C_{gs} \frac{V_{gs}}{V_o} \right)$$

If $V_{gs} \ll V_o$

$$C_1 \approx \frac{2}{k} \frac{V_{gs}}{V_o} C_{gd}$$




C_1 is of the same order of magnitude as the parasitic capacitances of the transistor!



If additional power is required (e. g. DC fans) C_1 will be larger.

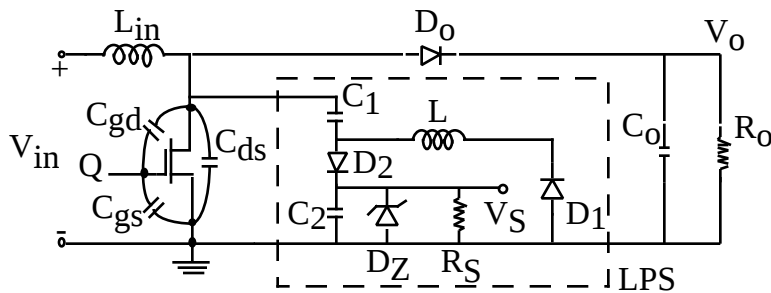Experimental boost converter with proposed LPS



Q=IRFP460; D₀=MUR460; D₁=1N5819; D₂=MUR160


Power stage:

$f_s=100\text{kHz}$; $L_{in}=1\text{mH}$; $L=24.2\text{nH}$; $C_0=1\text{mF}$; $V_o = 260\text{V}$; $P_o=85\text{W}$

Snubber:


$V_s=15\text{V}$; $C_2=100\text{nF}$; $R_s=10\text{-}64\text{W}$; $C_1=1.0\text{-}5.5\text{nF}$

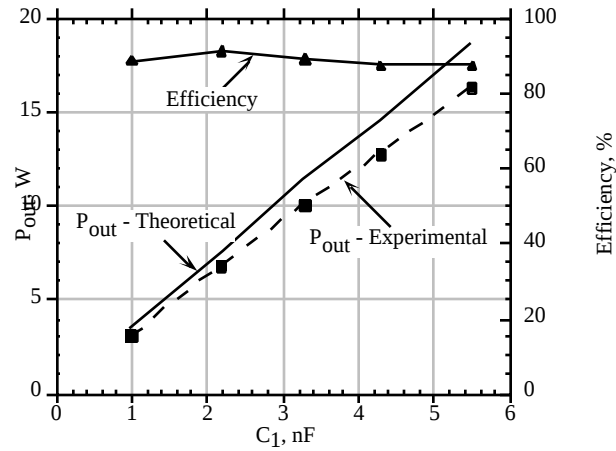Output power and efficiency as functions of the charge pump capacitor C_1




$$P_{out(theor)} = f_s E = \frac{f_s C_1 V_o^2}{2}$$

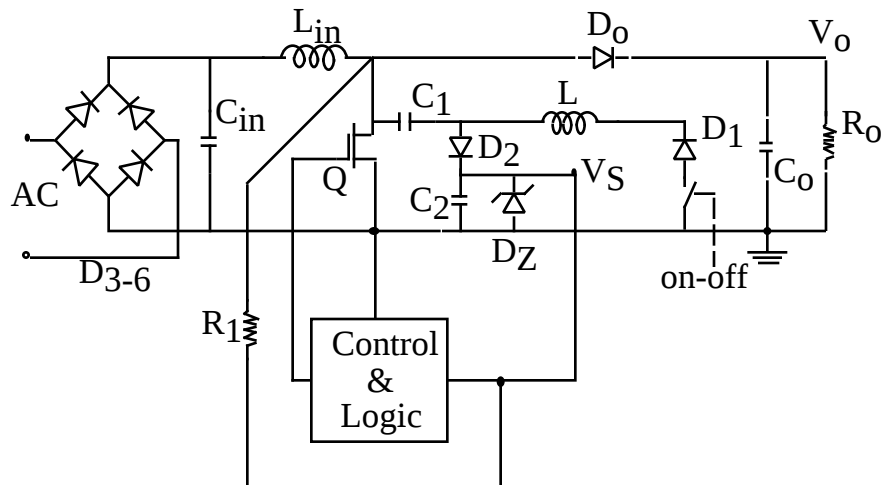Application of proposed local power supply in a boost APFC



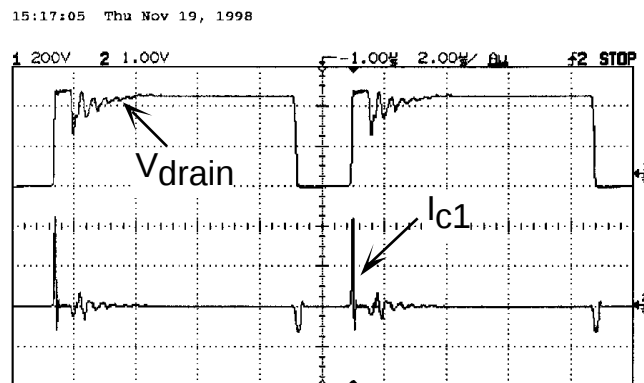Experimental waveforms of the LPS operating in a soft switched APFC circuit



C_1^a 220pF, V_{in} =220V_{rms}, V_o =380V, V_s =12.4V, R_s^a 170W

CONCLUSIONS

- **Passive lossless snubbers can improve performance of switch mode systems:**
 - **Controlled $\frac{di}{dt}$ and $\frac{dv}{dt}$**
 - **Increased efficiency at high switching frequency**
 - **Reduction of voltage and current spikes**
 - **Relatively low cost**
 - **High reliability**
- **The magnitude of the reverse recovery current of the diode may affect performance of the snubber**
- **Check points to watch:**
 - **Extra stresses**
 - **Duty cycle limitation**
 - **Current limitation**



Snubber/LPS combination could be useful in some applications



Methods to increase the snubbing capacitor without increasing LPS power - are now under investigation

REFERENCES

- [1] L. R. Barbosa, J. B. Vieira Jr., L. C. de Freitas, V. J. Farias, "A family of PWM soft-single-switched converters with low voltage and current stresses", *Proceedings PESC'97*, pp. 1192-1197.
- [2] L. R. Barbosa, J. B. Vieira Jr., L. C. de Freitas, M. Vilela, V. J. Farias, "A buck quadratic PWM soft-switching converter using a single active switch", *Proceedings PESC'96*, pp. 69-75.
- [3] S. Ben-Yaakov, "Average simulation of PWM converters by direct implementation of behavioral relationships", *Int. J. Electronics*, vol. 77, no. 5, 1994, pp. 731-746.
- [4] S. Ben-Yaakov, G. Ivensky, O. Levitin, A. Treiner, "Optimization of the auxiliary switch components in ZVS PWM converters", *Int. J. Electronics*, vol. 81, no. 6, 1996, pp. 699-712.
- [5] S. Clemente, A. Dubhashi, B. Pelly, "IGBT characteristics and applications", *IGBT Designer's Manual (IGBT-2, Second Printing)*, International Rectifier, 1991, pp. 93 - 108, AN-983.
- [6] M. Domb, R. Redl, N. O. Sokal, "Nondissipative turn-off snubber alleviates switching power dissipation, second breakdown stress and V_{CE} overshoot: analysis, design procedure and experimental verification", *Proceedings PESC'82*, pp. 445-454.
- [7] S. Hachamov and S. Ben-Yaakov, "Reduction of reverse recovery losses in soft switched PWM converters by saturable reactors", *Proceedings ICPE'95*, pp. 361-365.
- [8] S. Hamada, T. Mii, E. Hiraki, M. Nakaoka, "Saturable reactor & lossless capacitor-assisted soft-switching asymmetrical PWM DC-DC converter with forward-flyback transformer link", *Proceedings PESC'96*, pp. 100-105.
- [9] S. Hamada, J. M. Sun, T. Shimizu, A. Kanbe, E. Hiraki, M. Nakaoka, "A novel zero-voltage soft-switched asymmetrical PWM DC-DC converter with high-frequency transformer link", *Proceedings PCIM'96*, pp. 275-287.
- [10] X. He, S. J. Finney, B. W. Williams, T. C. Green, "An improved passive lossless turn-on turn-off snubber", *Proceedings APEC'93*, pp. 385-392.

- [11] X. He, S. J. Finney, B. W. Williams, Z. M. Qian, "Novel passive lossless soft-clamped snubber for voltage source inverters", *Proceedings APEC'96*, pp. 200-206.
- [12] X. He, S. J. Finney, B. W. Williams, Z. M. Qian, "Novel passive lossless turn-on snubber for voltage source inverters", *IEEE Trans. on Power Electronics*, vol. 12, no. 1, January 1997, pp. 173-179.
- [13] J. Holtz, S. Salama, K. H. Werner, "A nondissipative snubber circuit for high-power GTO inverters", *IEEE Trans. on Industry Applications*, vol. 25, no.4, July/August 1989, pp. 620-626.
- [14] G. Hua, F. C. Lee, M. M. Jovanovic, "An improved zero-voltage-switched PWM converter using saturable inductor," *Proceedings APEC'91*, pp. 189-194.
- [15] G. Ivensky, D. Sidi, S. Ben-Yaakov, "A soft switcher optimized for IGBTs in PWM topologies", *Int. J. Electronics*, vol. 83, no. 5, 1997, pp. 703-716.
- [16] D. Izvorska, J. Leisten, I. Izvorski, R. Petkov, "Frequency limitation of IGBT devices in energy recovery snubber circuits", *Proceedings PCIM'96*, pp. 585-592.
- [17] I. D. Jitaru, "Soft transitions power factor correction circuit", *Proceedings HFPC*, May 1993, pp. 202-208.
- [18] E. S. Kim, K.Y. Joe, M. H. Kye, Y. H. Kim, B. D. Yoon, "An improved soft switching PWM FB dc/dc converter for reducing conduction losses", *Proceedings PESC'96*, pp. 651-656.
- [19] E. S. Kim, K. Y. Joe, M. H. Kye, Y. H. Kim, B. D. Yoon, "An improved ZVZCS PWM FB DC/DC using energy recovery snubber", *Proceedings APEC'97*, pp. 1014-1019.
- [20] A. Kurnia, H. Cherradi, D. M. Divan, "Impact of IGBT behavior on design optimization of soft switching inverter topologies", *IEEE Trans. on Industry Applications*, vol. 31, no. 2, March/April 1995, pp. 280-286.
- [21] A. Kurnia, O. H. Stielau, G. Venkataramanan, D. M. Divan, "Loss mechanisms in IGBT's under zero voltage switching", *Proceedings PESC'92*, pp.1011-1017.
- [22] N. H. Kutkut and K. W. Klontz, "Design considerations for power converters supplying the SAE J-1773 electric vehicle inductive coupler", *Proceedings APEC'97*, pp. 841-847.

- [23] J. A. Lambert, J. B. Vieira Jr., L. C. de Freitas, M. S. Vilela, V. J. Farias, "A boost PWM soft-single-switched converter without high stresses of voltage and current", *Proceedings APEC'96*, pp. 469-474.
- [24] H. Levy, I. Zafrany, G. Ivensky, S. Ben-Yaakov, "Analysis and evaluation of lossless turn-on snubber", *Proceedings APEC'97*, pp. 757-763.
- [25] N. Mohan, T. M. Undeland, W. P. Robbins, "Power electronics", Second edition, *John Wiley & Sons, Inc.*, 1995, 802 p.
- [26] T. Ninomiya, T. Tanaka, K. Harada, "Analysis and optimization of a nondissipative LC turn-off snubber", *IEEE Trans. on Power Electronics*, vol. 3, no.2, April 1988, pp. 147-156.
- [27] H. Ould-Amrouche, D. Sadarnac, W. Abida, "New soft switching phase shifted PWM technique in DC-AC power supply", *Proceedings PCIM'96*, pp. 707-717.
- [28] R. Petkov, L. Hobson, "Optimum design of a nondissipative snubber", *Proceedings PESC'94*, pp. 1188-1195.
- [29] J. Pinto, A. Pereira, V. Farias, L. Freitas, J. Vieira Jr., "A new boost converter using a non-dissipative snubber", *Proceedings PESC'96*, pp. 397-401.
- [30] L. D. Salazar, P. D. Ziogas, G. Joos, "On the minimization of switching losses in dc-dc boost converters", *Proceedings APEC'92*, pp. 703-708.
- [31] K. M. Smith Jr. and K. M. Smedley, "Engineering design of lossless passive soft switching methods for PWM converters. I. With minimum voltage stress circuit cells", *Proceedings APEC'98*, pp. 1055-1062.
- [32] K. M. Smith Jr. and K. M. Smedley, "Properties and synthesis of passive, lossless soft-switching PWM converters", *Proceedings of the 1st International Congress in Israel on Energy Power & Motion Control*, May 1997, pp. 112-119.
- [33] R. Streit and D. Tollik. "High efficiency telecom rectifier using a novel soft-switched boost-based input current shaper", *Proceedings of Intelec'91*, November 1991, pp. 720-726.
- [34] Ching-Junk Tseng and Chern-Lin Chen, "Passive lossless snubbers for DC/DC converters", *Proceedings APEC'98*, pp. 1049-1054.
- [35] Ph. C. Todd, "Snubber circuits: theory, design and application", *Unitrode Corporation*, May 1993, pp. 2-1 - 2-17.

- [36] M. S. Vilela, E. A. A. Coelho, J. B. Vieira Jr., L. C. de Freitas, V. J. Farias, "PWM soft-switched converters using a single active switch", *Proceedings APEC'96*, pp. 305-310.
- [37] K. Wang, G. Hua, F. C. Lee, "Analysis, design and experiment results of ZCS-PWM boost converters", *VPEC Seminar Proceedings*, Blacksburg, Virginia, USA, 1994, pp. 251-256.
- [38] K. Wang, F. C. Lee, G. Hua, D. Borojevic, "A comparative study of switching losses of IGBT's under hard-switching, zero-voltage-switching and zero-current-switching", *Proceedings PESC'94*, pp. 1196-1204.
- [39] B. W. Williams, "Power electronics. Devices, drivers, applications, and passive components", Second edition, *McGraw-Hill, Inc.*, 1992.
- [40] E. H. Wittenbreder, V. D. Baggerly, H. C. Martin, "A duty cycle extension technique for single ended forward converters", *Proceedings APEC'92*, pp. 51-57.
- [41] L. R. Barbosa, J. B. Vieira Jr., L. C. de Freitas, V. J. Farias, "A boost PWM soft-single-switched converter", *Proceedings PESC'98*, pp. 401-406.
- [42] R. Farrington, M. M. Jovanovic, F. C. Lee, "A new family of isolated zero-voltage-switched converters", *Proceedings PESC'91*, pp. 209-215.
- [43] S. Hamada and M. Nakaoka, "Analysis and design of a saturable reactor assisted soft-switching full-bridge DC-DC converter", *Proceedings PESC'91*, pp. 155-162.
- [44] K. Harada, Y. Ishihara, T. Todaka, "An improved magnetic snubber circuit for the diode reverse recovery in DC-to-DC converters", *Proceedings PESC'98*, pp. 701-706.
- [45] J. A. Lambert, J. B. Vieira Jr., L. C. de Freitas, L. R. Barbosa, V. J. Farias, "A boost PWM soft-single-switched converter with low voltage and current stresses", *IEEE Trans. on Power Electronics*, vol. 13, no.1, January 1998, pp. 26-35.
- [46] Ching-Junk Tseng and Chern-Lin Chen, "A passive lossless snubber cell for nonisolated PWM DC/DC converters", *IEEE Trans. on Industry Electronics*, vol. 45, no. 4, August 1998, pp. 593-601.
- [47] S. Ben-Yaakov, I. Zeltser, G. Ivensky, "A resonant local power supply with turn off snubber features", *Proceedings APEC'99*.

