


ÜB: $f_2^A = f_1^B$; $e_2^A = e_1^B$

$$\begin{bmatrix} e_1^A \\ f_1^A \end{bmatrix} = A_A A_B \begin{bmatrix} e_2^B \\ f_2^B \end{bmatrix} \quad \leadsto \quad \underline{\underline{A = A_A \cdot A_B}}$$

$$A_A A_B = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} = \begin{bmatrix} a_{11}b_{11} + a_{12}b_{21} & a_{11}b_{12} + a_{12}b_{22} \\ a_{21}b_{11} + a_{22}b_{21} & a_{21}b_{12} + a_{22}b_{22} \end{bmatrix}$$

Elementarzweige

a.)

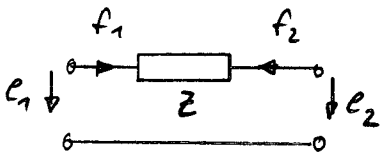

$$Y_{11} = \left. \frac{f_1}{e_1} \right|_{e_2=0} = \frac{1}{Z}$$

$$Y_{12} = \left. \frac{f_1}{e_2} \right|_{e_1=0} = -\frac{1}{Z}$$


(Symmetrie) $Y_{11} = Y_{22}$
 $Y_{12} = Y_{21}$

$$\leadsto \quad \underline{\underline{Y = \begin{bmatrix} \frac{1}{Z} & -\frac{1}{Z} \\ -\frac{1}{Z} & \frac{1}{Z} \end{bmatrix}}}$$

Umrechnungen: Z unbestimmt da $\det Y = 0$!

$$A = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}; \quad H = \begin{bmatrix} Z & 1 \\ -1 & 0 \end{bmatrix}$$

b.)

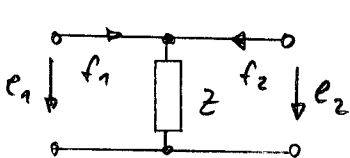

$$Z_{11} = \left. \frac{e_1}{f_1} \right|_{f_2=0} = Z$$

$$Z_{12} = \left. \frac{e_1}{f_2} \right|_{f_1=0} = Z$$




(Symmetrie) $Z_{11} = Z_{22}$
 $Z_{12} = Z_{21}$

$$Z = \begin{bmatrix} Z & Z \\ Z & Z \end{bmatrix}$$

Umrechnungen:

$$A = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z} & 1 \end{bmatrix}; \quad H = \begin{bmatrix} 0 & 1 \\ -1 & \frac{1}{Z} \end{bmatrix}$$

Bsp.:

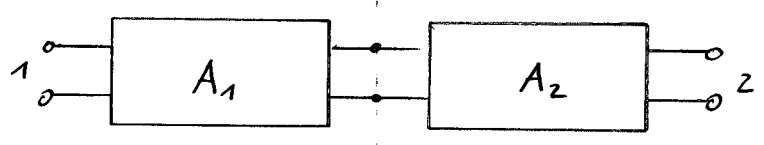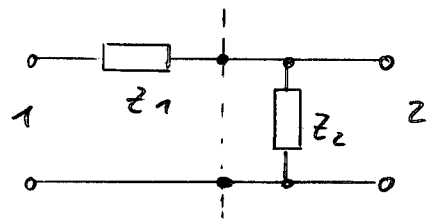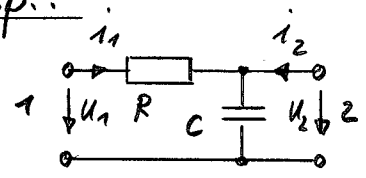

$A = A_1 \cdot A_2$

$A_1 = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix}$

$A_2 = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z_2} & 1 \end{bmatrix}$

$A = \begin{bmatrix} 1 \cdot 1 + Z_1 \cdot \frac{1}{Z_2} & 1 \cdot 0 + Z_1 \cdot 1 \\ 0 \cdot 1 + 1 \cdot \frac{1}{Z_2} & 0 \cdot 0 + 1 \cdot 1 \end{bmatrix}$

$A = \begin{bmatrix} 1 + \frac{Z_1}{Z_2} & Z_1 \\ \frac{1}{Z_2} & 1 \end{bmatrix} \quad \begin{bmatrix} U_1 \\ i_1 \end{bmatrix} = A \cdot \begin{bmatrix} U_2 \\ i_2 \end{bmatrix}$

$U_1 = A_{11} \cdot U_2 + A_{12} \cdot i_2$

Vor: $i_2 = 0$

$U_1 = A_{11} \cdot U_2$


$i_1 = A_{21} \cdot U_2 + A_{22} \cdot i_2$

$A_{11} = 1 + \frac{R j \omega C}{1} = 1 + j \omega RC$

$\frac{U_2}{U_1} = \frac{1}{A_{11}} = \frac{1}{1 + j \omega RC}$

Optimales Wirkungsgrad von modult. Wandlern

Bsp.: Gleichstrommotor

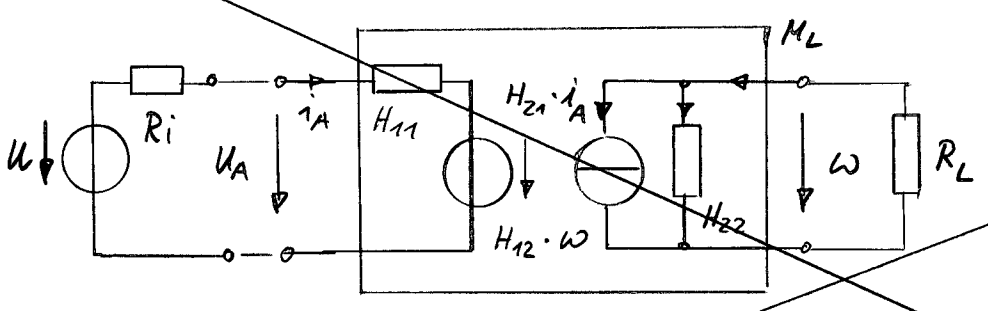

(1) $U_A = H_{11} \cdot i_A + H_{12} \cdot \omega$; $M_L = - \frac{\omega}{R_L} = - \omega G_L \leadsto \omega = - M_L \cdot R_L$

pot. Verstärkung: $V_e = \frac{\omega}{U_A}$

$V_e = \frac{\omega}{H_{11} \cdot i_A + H_{12} \cdot \omega} = \frac{1}{H_{11} \frac{i_A}{\omega} + H_{12}} = \frac{1}{H_{12} - H_{11} \cdot \frac{i_A}{M_L \cdot R_L}}$