



FPGA Design Techniques



Objectives

After completing this module, you will be able to:

- Increase design performance by duplicating flip-flops
- Increase design performance by adding pipeline stages
- Increase board performance by using I/O flip-flops
- Build reliable synchronization circuits


Outline



- **Duplicating Flip-Flops**
- Pipelining
- I/O Flip-Flops
- Synchronization Circuits
- Summary


Duplicating Flip-Flops

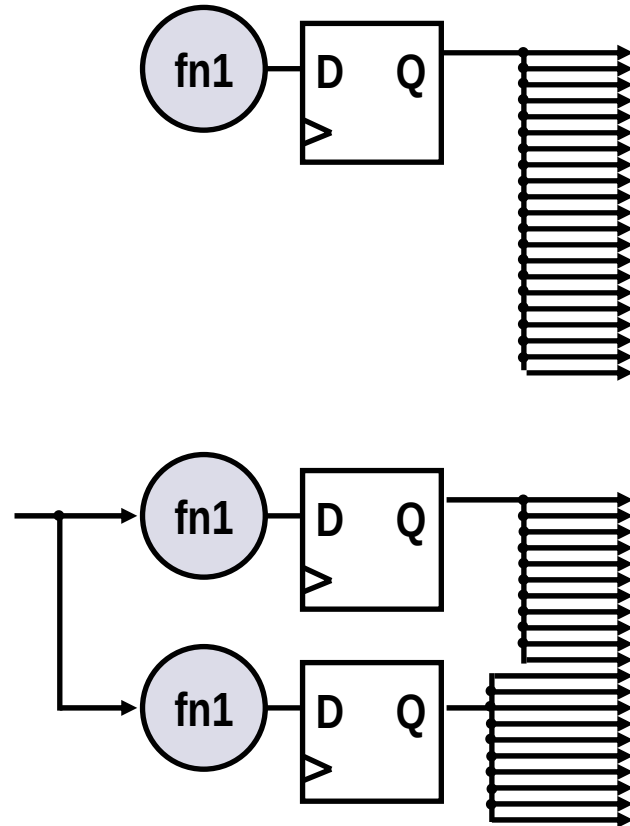- High-fanout nets can be slow and hard to route
- Duplicating flip-flops can fix both problems
 - Reduced fanout shortens net delays
 - Each flip-flop can fanout to a different physical region of the chip to reduce routing congestion
- Design trade-offs
 - Gain routability and performance
 - Increase design area
 - Increase fanout of other nets




Duplicating Flip-Flops Example

 - The source flip-flop drives two register banks that are constrained to different regions of the chip
- The source flip-flop and pad are not constrained
- PERIOD = 5 ns timing constraint
- Implemented with default options
- Longest path = 6.806 ns
 - Fails to meet timing constraint



Duplicating Flip-Flops Example

 - The source flip-flop has been duplicated
- Each flip-flop drives a region of the chip
 - Each flip-flop can be placed closer to the register that it is driving
 - Shorter routing delays
- Longest path = 4.666 ns
 - Meets timing constraint



Tips on Duplicating Flip-Flops

- Name duplicated flip-flops `_a, _b`; *NOT* `_1, _2`
 - Numbered flip-flops are mapped into the same slice by default
 - Duplicated flip-flops should be separated
 - Especially if the loads are spread across the chip
- Explicitly create duplicate flip-flops in your HDL code
 - Most synthesis tools have automatic fanout-control features
 - However, they do not always pick the best division of loads
 - Also, duplicated flip-flops will be named `_1, _2`
 - Many synthesis tools will optimize-out duplicated flip-flops
 - Set your synthesis tool to keep redundant logic
- Do not duplicate flip-flops that are sourced by asynchronous signals
 - Synchronize the signal first
 - Feed the synchronized signal to multiple flip-flops



Outline

- Duplicating Flip-Flops
- **Pipelining**
- I/O Flip-Flops
- Synchronization Circuits
- Summary




Pipelining Concept

$$f_{\text{MAX}} = n \text{ MHz}$$

  
 
$$f_{\text{MAX}} \approx 2n \text{ MHz}$$




Pipelining Considerations

- Are enough flip-flops available?
 - Refer to the MAP Report
 - In general, you will not run out of flip-flops
- Are there multiple logic levels between flip-flops?
 - If there is only one logic level between flip-flops, pipelining will not improve performance
 - Refer to the Post-Map Static Timing Report or Post-Place & Route Static Timing Report
- Can the system tolerate *latency*?


Latency in Pipelines

 - Each pipeline stage adds one clock cycle of delay before the first output will be available
 - Also called “filling the pipeline”
- After the pipeline is filled, a new output is available every clock cycle




Pipelining Example

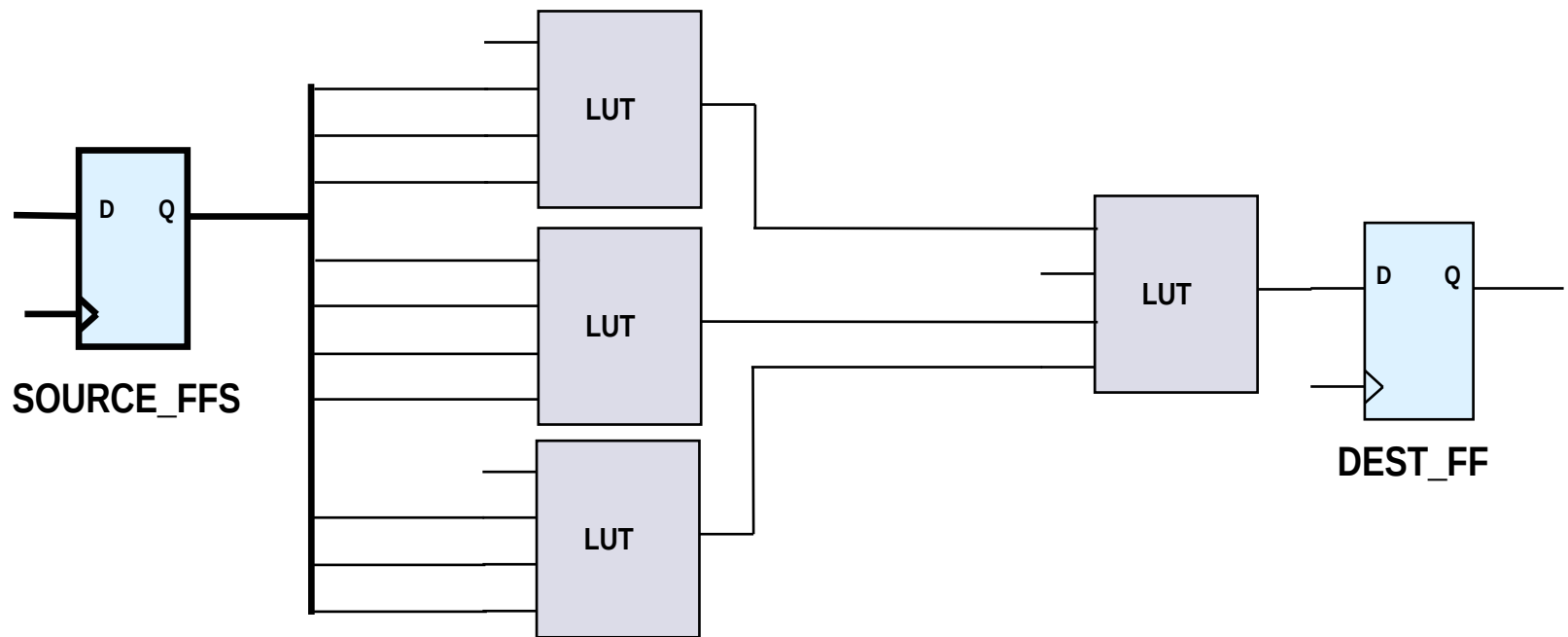- Original circuit
 - Two logic levels between SOURCE_FF and DEST_FF
 - $f_{\text{MAX}} = \sim 233 \text{ MHz}$



Pipelining Example

 
- Pipelined circuit
 - One logic level between each set of flip-flops
 - $f_{\text{MAX}} = \sim 385 \text{ MHz}$




Review Questions

- Given the original circuit, what is wrong with the pipelined circuit?
- How can the problem be corrected?

Original Circuit

 


Pipelined Circuit

 

Answers

 - What is wrong with the pipelined circuit?
 - Latency mismatch
 - Older data is mixed with newer data
 - Circuit output is incorrect
- How can the problem be corrected?
 - Add a flip-flop on *SELECT*
 - All data inputs now experience the same amount of latency



Outline

- Duplicating Flip-Flops
- Pipelining
- **I/O Flip-Flops**
- Synchronization Circuits
- Summary



I/O Flip-Flop Overview

- Each I/O block in the Virtex™-II Pro device contains six flip-flops
 - IN FF on the input, OUT FF on the output, EN FF on the 3-state enable*
 - Single data rate or double data rate support
- I/O flip-flops provide guaranteed setup, hold, and clock-to-out times when the clock signal comes from a BUFG

Accessing I/O Flip-Flops

- During synthesis
 - Timing-driven synthesis can force flip-flops into Input/Output Blocks (IOBs)
 - Some tools support attributes or synthesis directives to mark flip-flops for placement in an IOB
- Xilinx Constraint Editor
 - Select the Misc tab and specify registers that should be placed into IOBs
 - You need to know the instance name for each register
- During the MAP phase of implementation
 - In the Map Properties dialog box, the Pack I/O Registers/Latches into IOBs option is selected by default
 - Timing-driven packing will also move registers into IOBs for critical paths
- Check the MAP Report to confirm that IOB flip-flops have been used
 - IOB Properties section

Outline


- Duplicating Flip-Flops
- Pipelining
- I/O Flip-Flops
- • **Synchronization Circuits**
- Summary

Synchronization Circuits

- What is a synchronization circuit?
 - Captures an asynchronous input signal and outputs it on a clock edge
- Why do you need synchronization circuits?
 - To prevent setup and hold time violations
 - To ensure a more reliable design
- When do you need synchronization circuits?
 - Signals cross between *unrelated* clock domains
 - Between related clock domains, relative PERIOD constraints are sufficient
 - Chip inputs that are asynchronous

Setup and Hold Time Violations

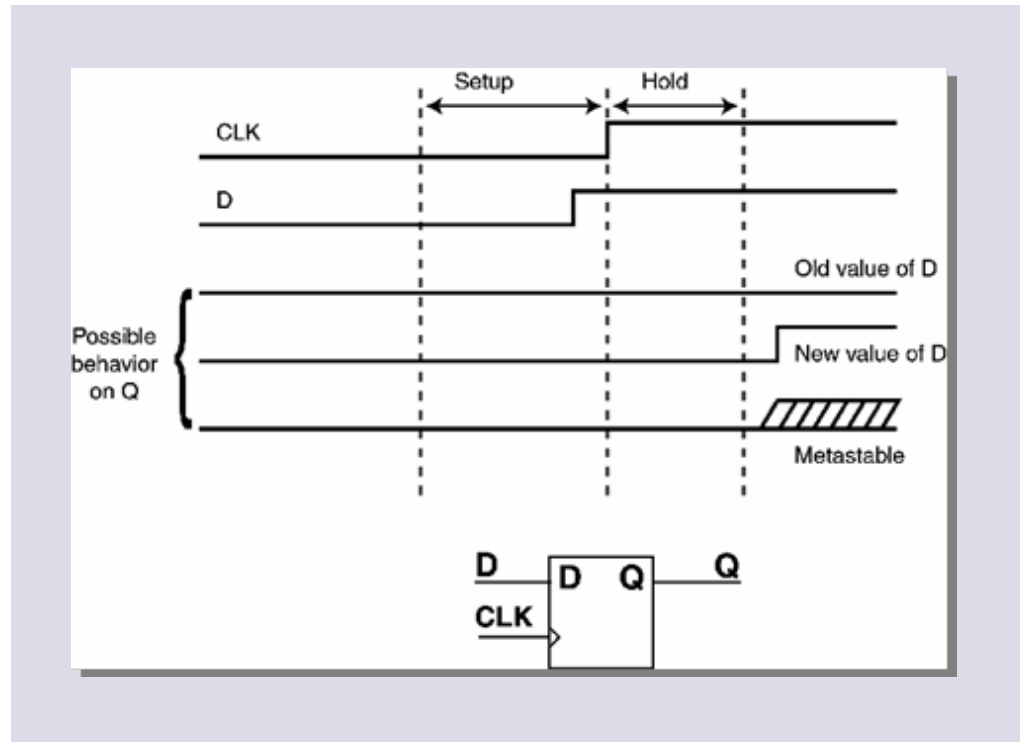- Violations occur when the flip-flop input changes too close to a clock edge
- Three possible results:
 - Flip-flop clocks in an old data value
 - Flip-flop clocks in a new data value
 - Flip-flop output becomes *metastable*




Metastability

- Flip-flop output enters a transitory state
 - Neither a valid 0 nor a valid 1
 - Can be interpreted as 0 by some loads and as 1 by others
 - Remains in this state for an unpredictable length of time before settling to a valid 0 or 1
- Due to a statistical nature, the occurrence of metastable events can only be reduced, not eliminated
- Mean Time Between Failure (MTBF) is exponentially related to the length of time the flip-flop is given to recover
 - A few extra ns of recovery time can dramatically reduce the chances of a metastable event
- The circuits shown in this section allow a full clock cycle for metastable recovery


Synchronization Circuit 1

 - Use when input pulses will always be at least one clock period wide
- The “extra” flip-flops guard against metastability



Synchronization Circuit 2

 
- Use when input pulses may be less than one clock period wide
 - FF1 captures short pulses



Capturing a Bus

- Leading edge detector
 - Input pulses must be at least one CLK period wide


Circuit 1

 

Capturing a Bus


- Leading edge detector
 - Input pulses may be less than one CLK period wide

Circuit 2

 

Synchronization Circuit 3

- Use a FIFO to cross domains

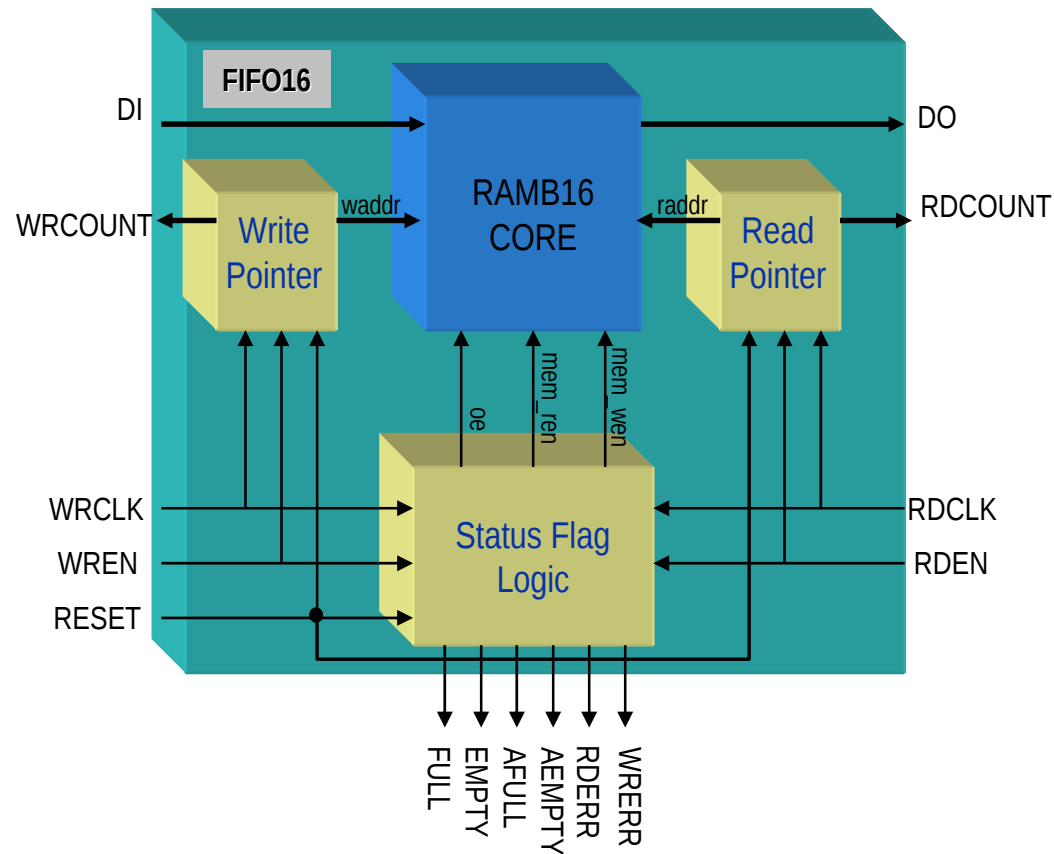

Outline

- Duplicating Flip-Flops
- Pipelining
- I/O Flip-Flops
- Synchronization Circuits
- **Summary**



Review Questions

- High fanout is one reason to duplicate a flip-flop. What is another reason?
- Provide an example of when you do not need to resynchronize a signal that crosses between clock domains
- What is the purpose of the “extra” flip-flop in the synchronization circuits shown in this module?

Answers

- High fanout is one reason to duplicate a flip-flop. What is another reason?
 - Loads are divided among multiple locations on the chip
- Provide an example of when you do not need to resynchronize a signal that crosses between clock domains
 - Well-defined phase relationship between the clocks
 - Example: Clocks are the same frequency, 180 degrees out of phase
 - Use related PERIOD constraints to ensure that datapaths will meet timing
- What is the purpose of the “extra” flip-flop in the synchronization circuits shown in this module?
 - To allow the first flip-flop time to recover from metastability

Summary

- You can increase circuit performance by:
 - Duplicating flip-flops
 - Adding pipeline stages
 - Using I/O flip-flops
- Some trade-offs
 - Duplicating flip-flops increases circuit area
 - Pipelining introduces latency and increases circuit area
- Synchronization circuits increase reliability

Where Can I Learn More?

- User Guides: www.xilinx.com → **Documentation** → **User Guides**
 - Switching Characteristics
 - Detailed Functional Description → Input/Output Blocks (IOBs)
- Application Notes: www.xilinx.com → **Documentation** → **Application Notes**
 - XAPP094: Metastability Recovery
 - XAPP225: Data-to-Clock Phase Alignment