

PCIM 2011 Presentation

by

Dr. Slobodan Ćuk

35 Years Anniversary also of:

1. State-Space Averaging *
2. Ćuk Converter*
3. Coupled Inductors*
4. Integrated Magnetics*
5. Duality in Switching Converters*

*Slobodan Ćuk: “Modelling, Analysis and Design of switching Converters” Ph.D. Thesis, Caltech, November 1976



31 Years Anniversary of Presentation at PCIM 1980:

1. Ćuk Converter*
2. Coupled Inductors*
3. Integrated Magnetics*
4. Duality in Switching Converters*

*Slobodan Ćuk: “Modelling, Analysis and Design of switching Converters” Ph.D. Thesis, Caltech, November 1976

The State-space Averaging Uses Different Criteria

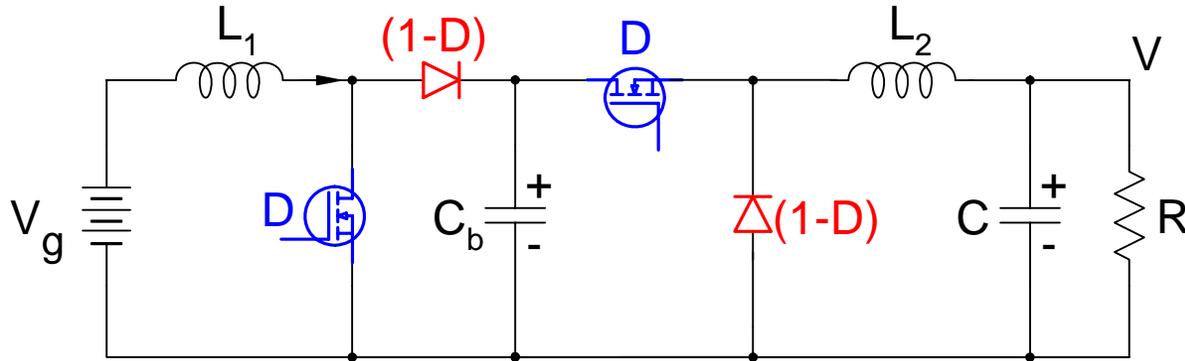
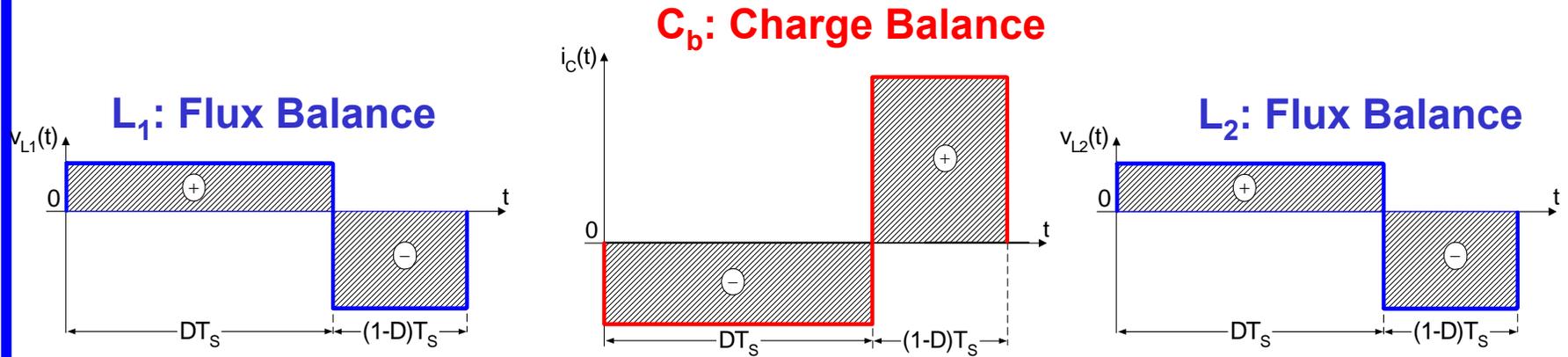
1. Flux Balance on All Inductors
2. Charge Balance on All Capacitors



Boost-Buck Converter

Ćuk Converter


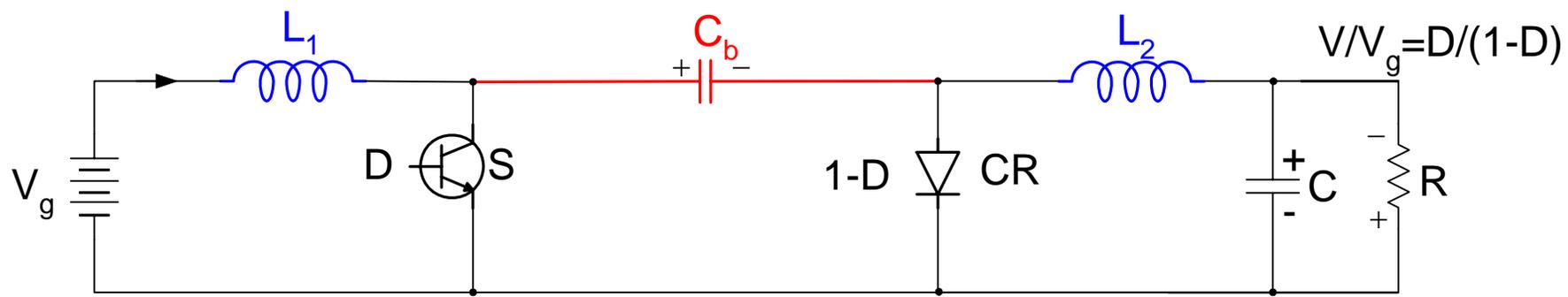
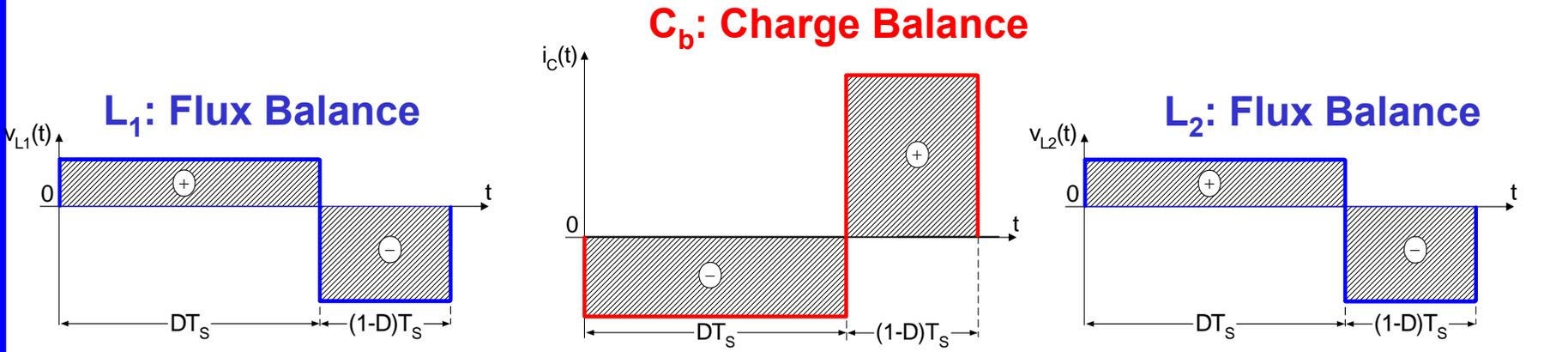
1. Flux Balance on All Inductors
2. Charge Balance on All Capacitors



Ćuk Converter*

*US Patents: 4,184,197; 4,257,087; 4,274,133

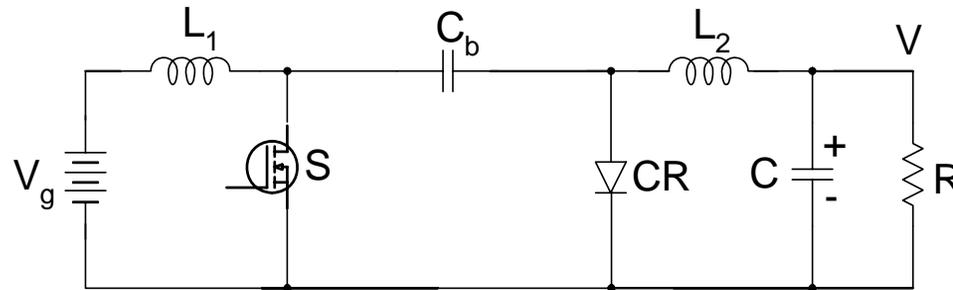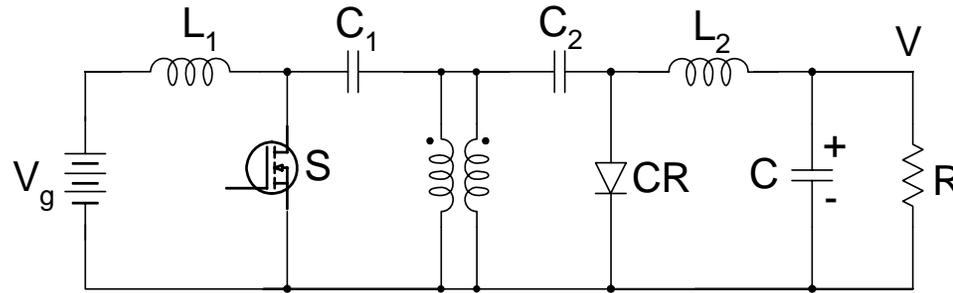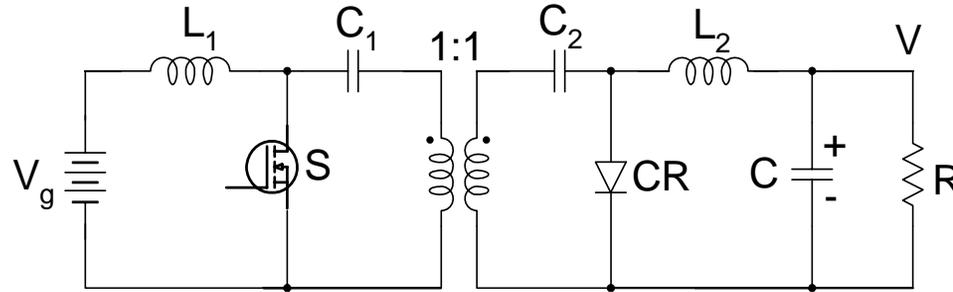From Isolated to Non-isolated Ćuk Converter



Square-wave Switching:

No 3 switches allowed

Eight needed for isolation

No capacitors

Hybrid-Switching Method:


3 switches only

Resonant capacitor


Resonant inductor

What about converters with 3 switches


1. Three Switches

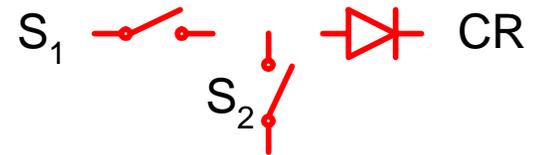

2. A Resonant Capacitor

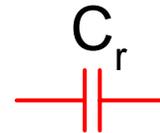

3. A Resonant Inductor

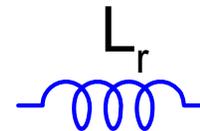



“Birth ” of Hybrid-Switching Method and Related Converter Topologies



DC-DC

Converter Comparison

Buck Converter

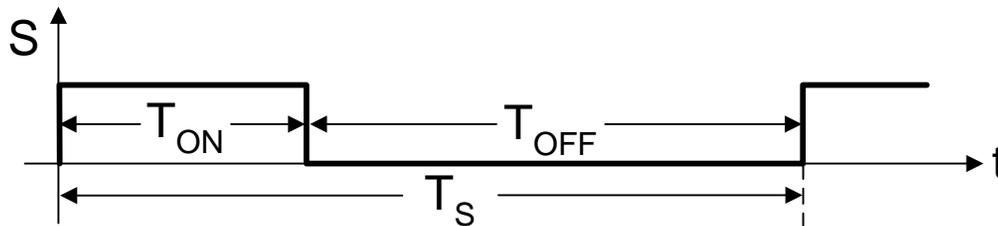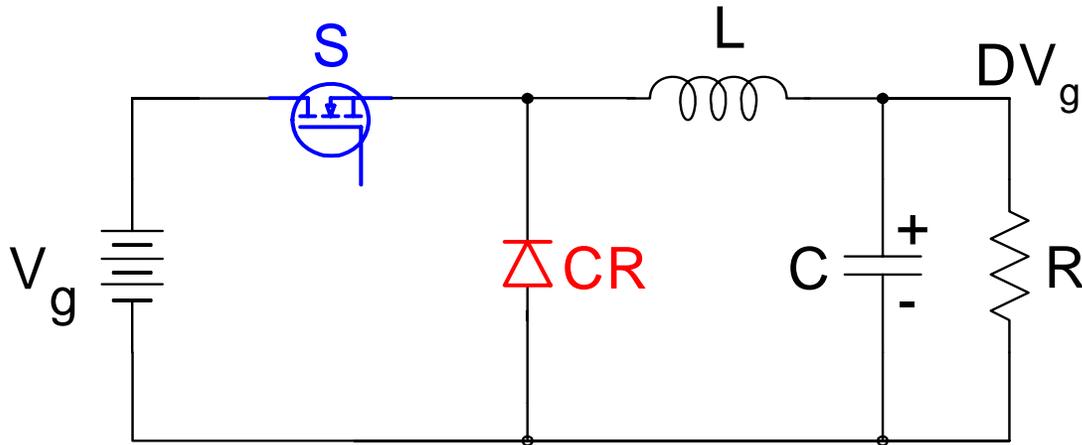


Problem

How to insert AC Isolation Transformer
by using additional switches



Isolated Full-bridge Buck Converter

Two magnetic components


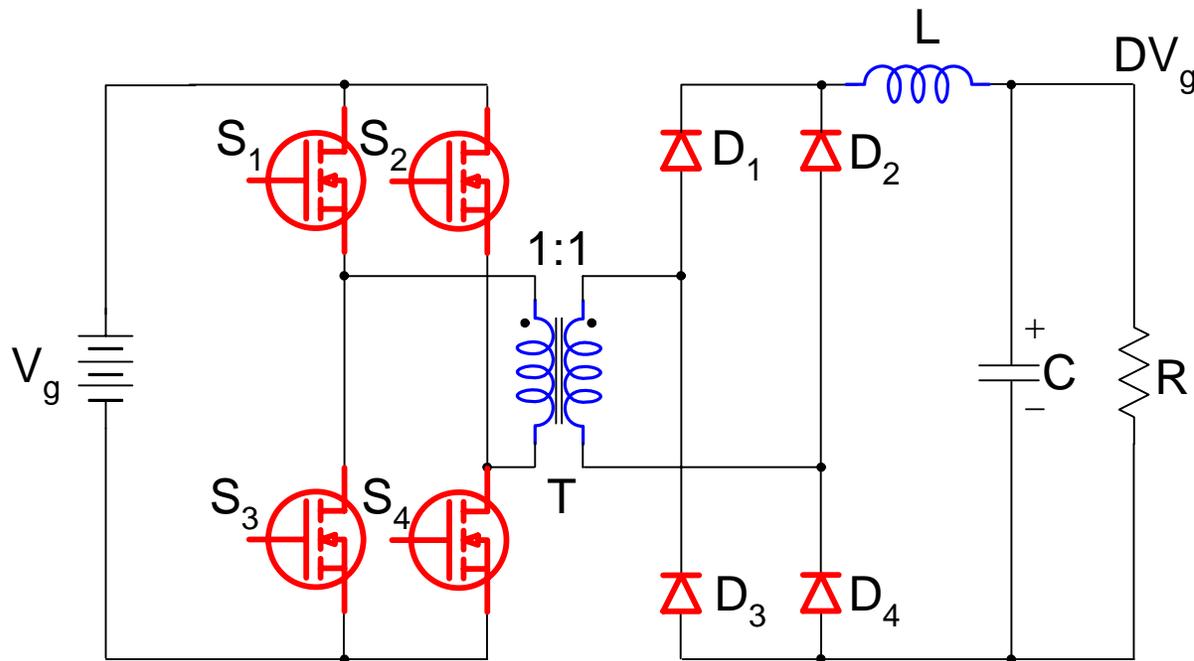


Total of 8 Switches



Step 1 – Insert Resonant Capacitor C_r

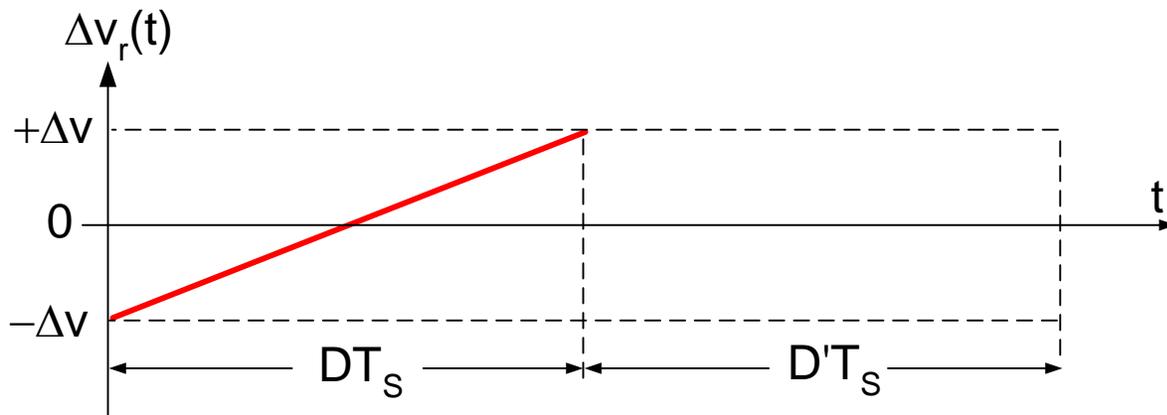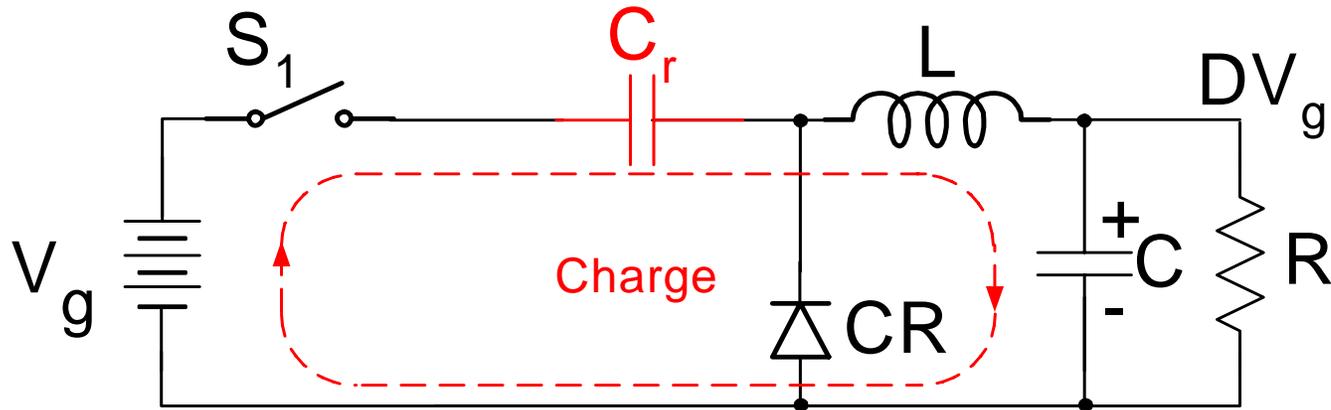

Step 2 – Insert Switch S_2

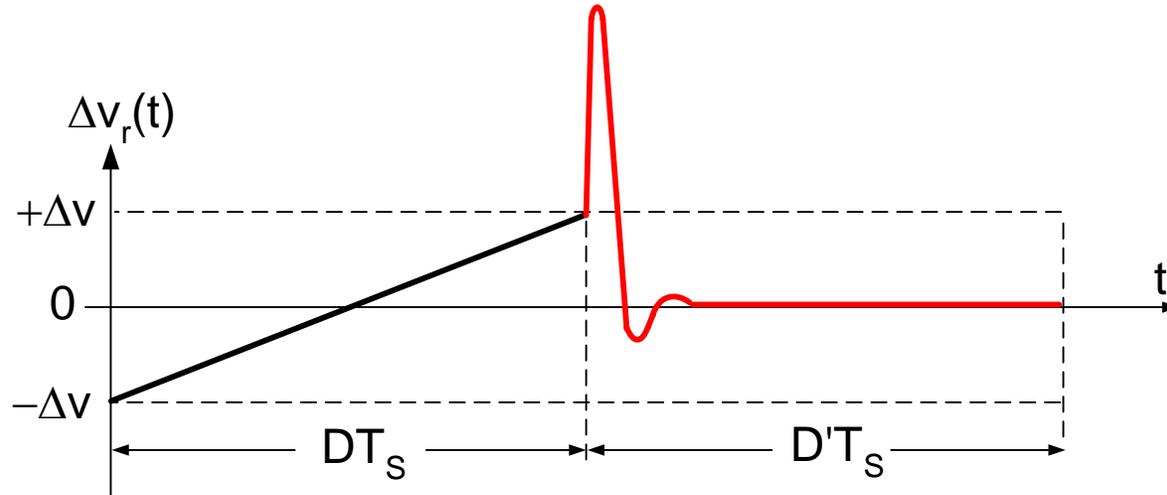
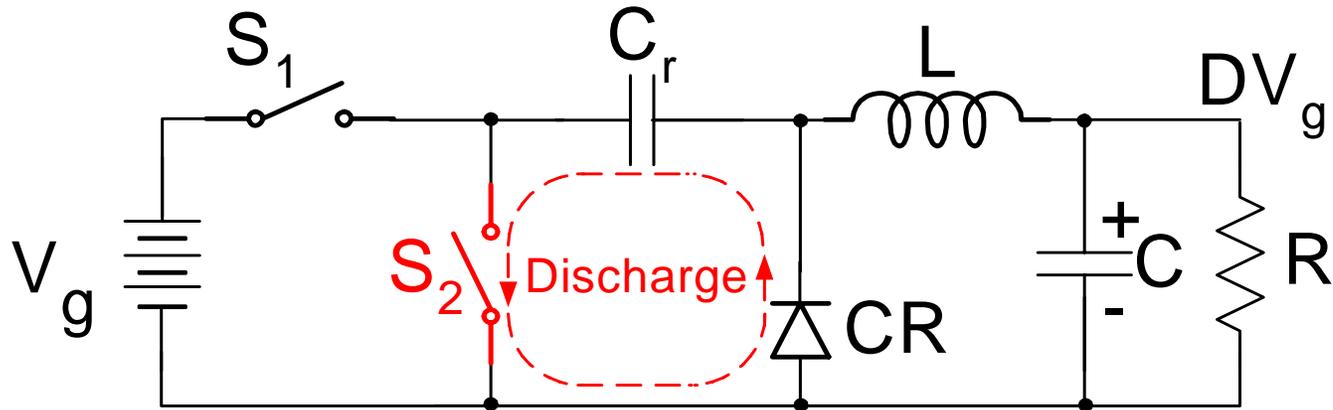


Step 3 – Insert Resonant Inductor L_r

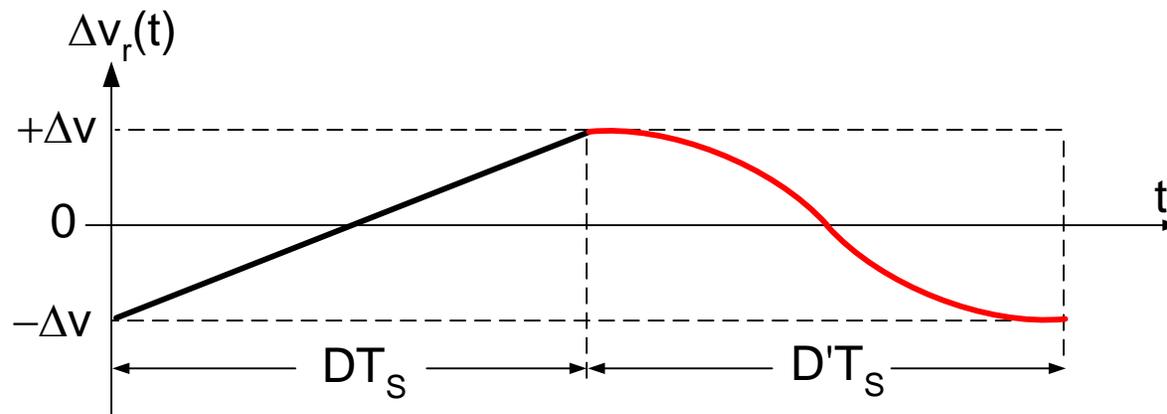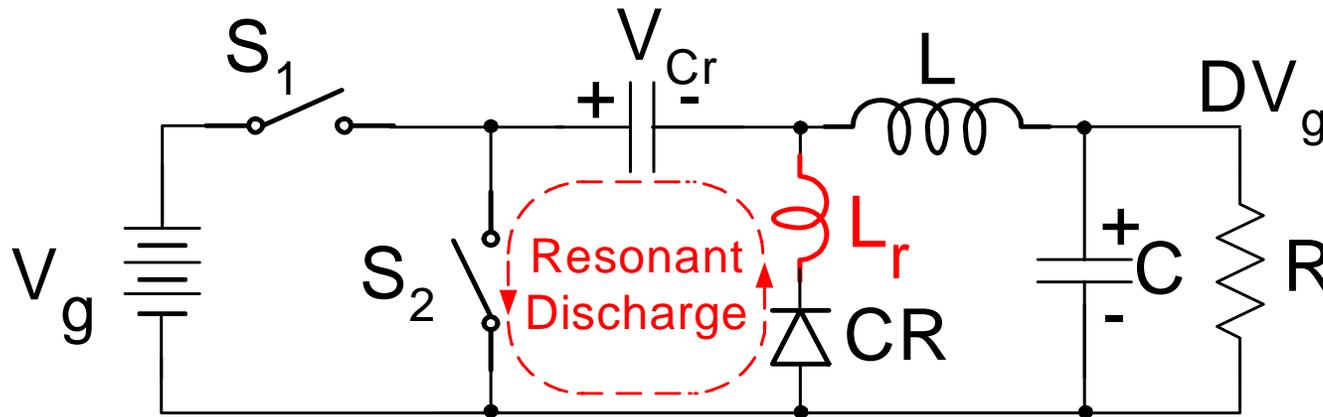


Flux Balance Resonant Inductor $L_r \Rightarrow V_{Cr}=0$

Hybrid-switching

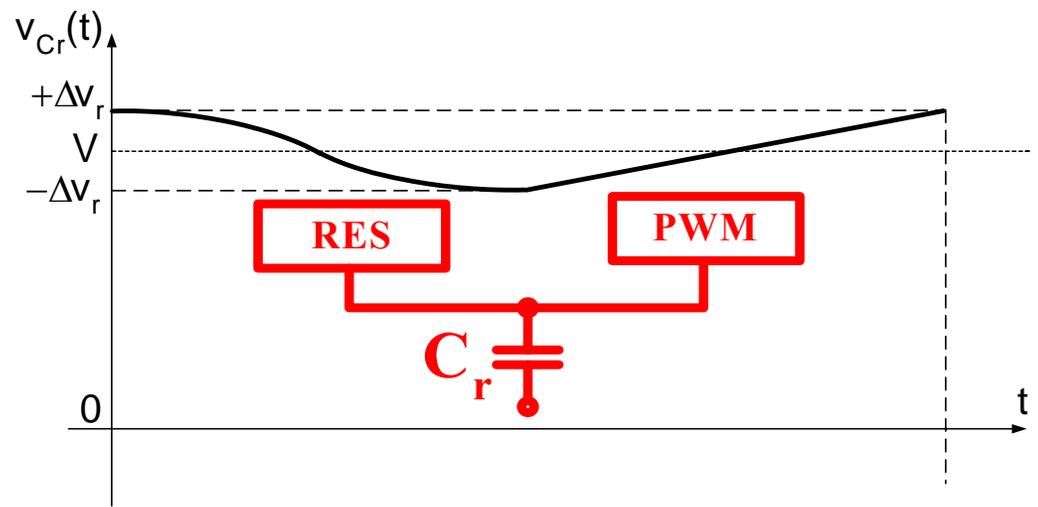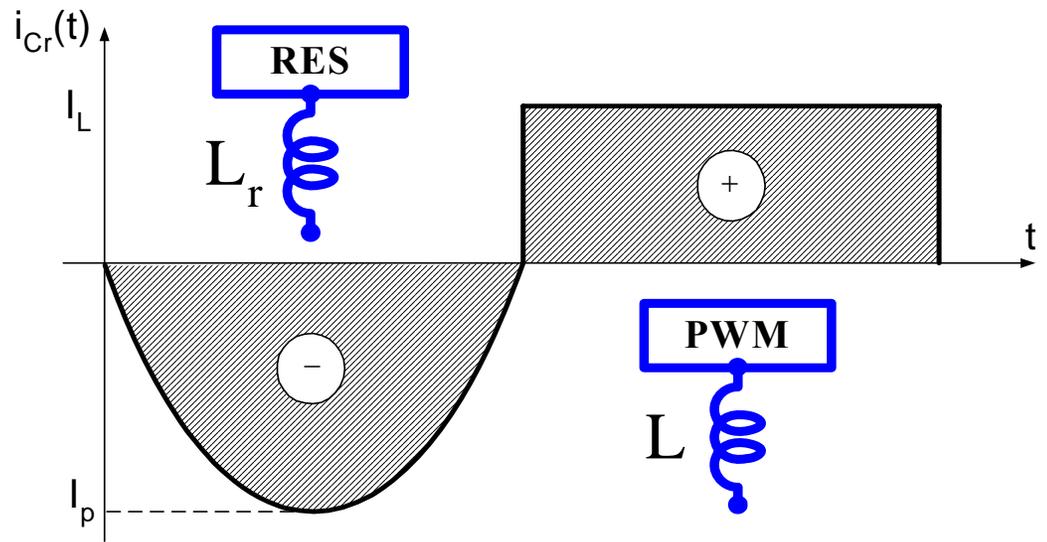

Hybrid-Switching Buck Converter*



One Integrated Magnetics Component

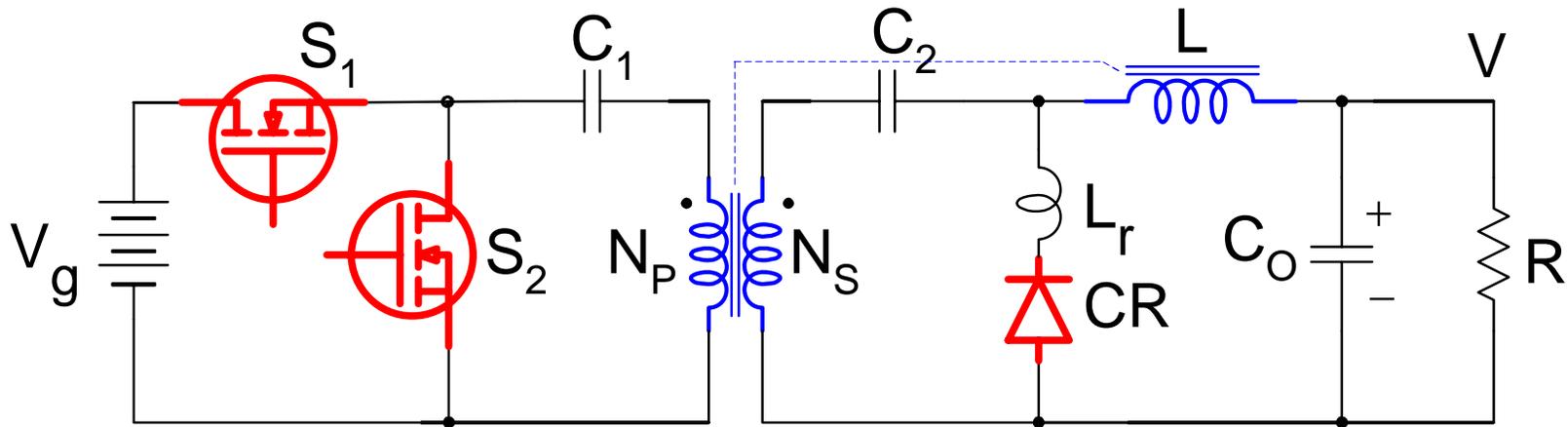

Total of 3 Switches

*US and foreign patents pending

Boost Converter

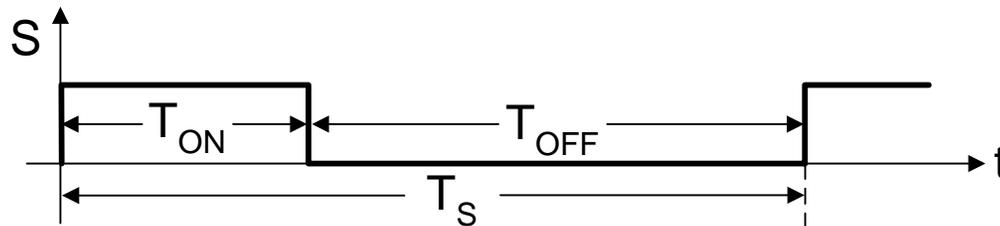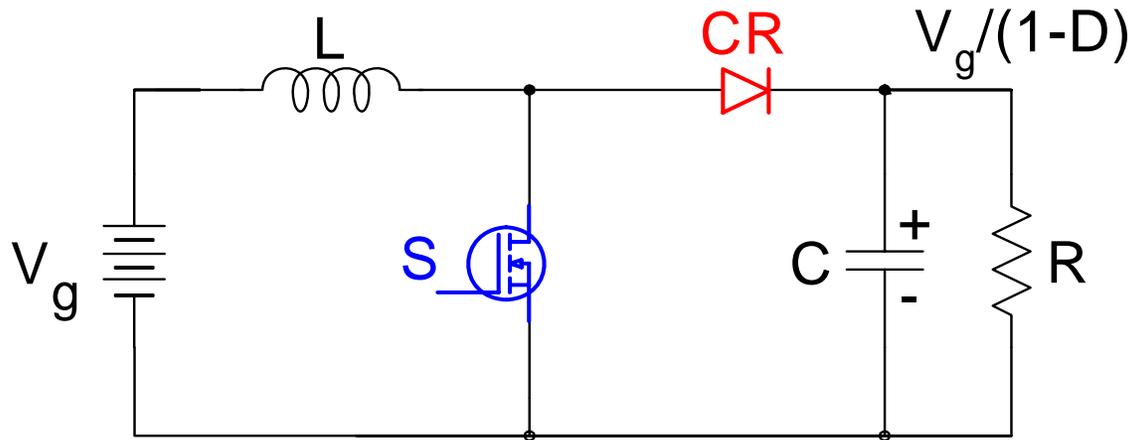


Problem

How to insert AC Isolation Transformer
by using additional switches

Isolated Full-bridge Boost Converter


Two Magnetic Components

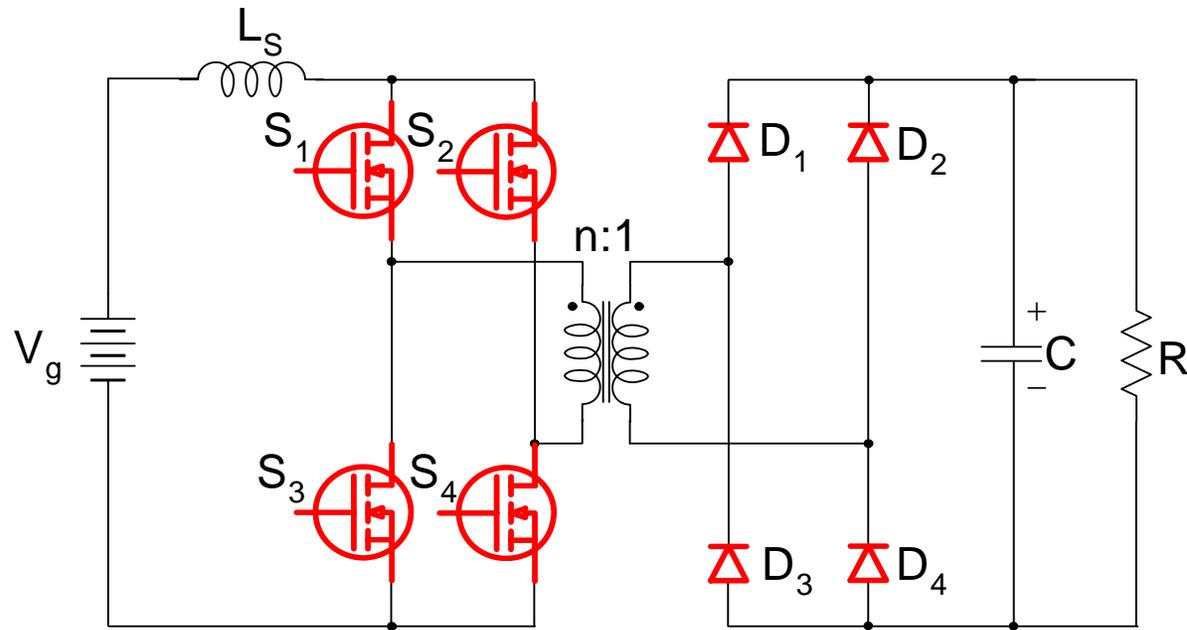

Total of 8 Switches

Hybrid-Switching Boost Converter*

One Integrated magnetic Component

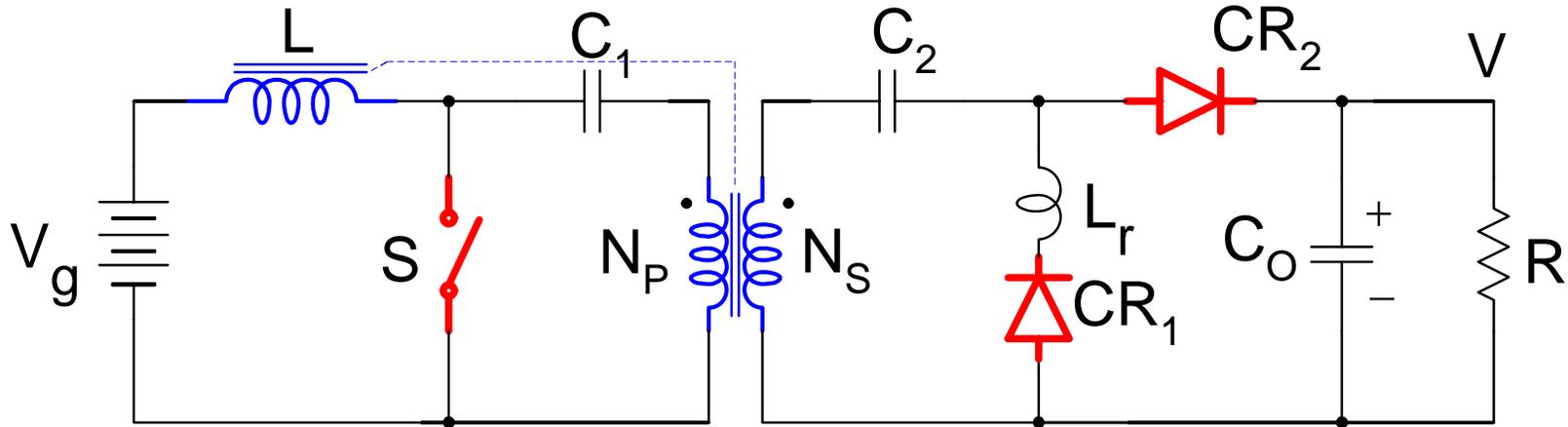


Total of 3 Switches


*US Patent No. 7,778,046

Polarity Inverting DC-DC Converter

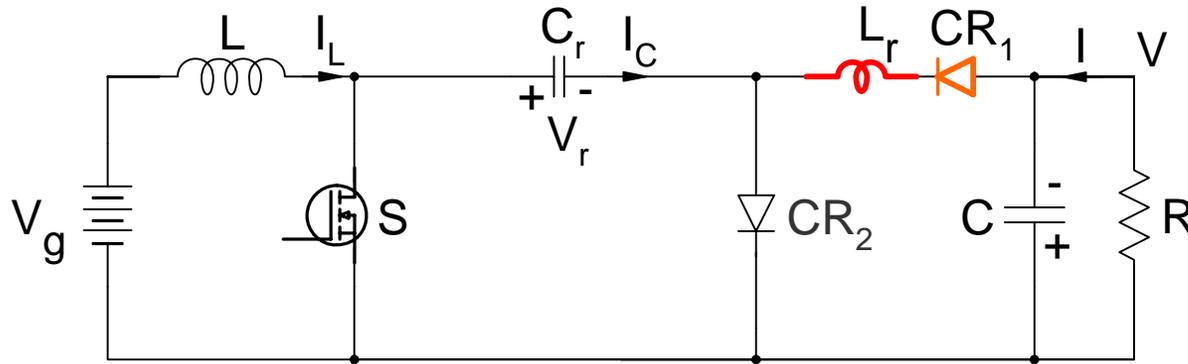Polarity Inverting 3 Switch Boost Converter*




$$V = V_g / (1 - D)$$

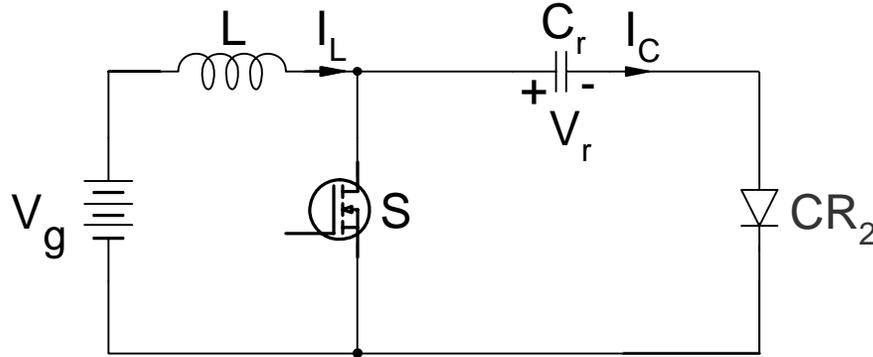

Boost Converter

$$V_r = V_g / (1 - D)$$

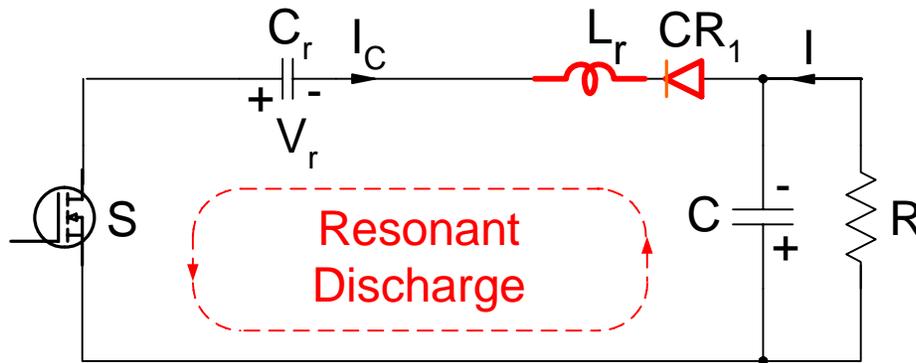

$$V = V_r$$





OFF-time Interval $(1 - D)T_s$

*US Patent No. 7,778,046

State-space Averaging Extension

Flux Balance on Resonant Inductor
During ON-time Interval Only

$$V = V_r = V_g / (1 - D)$$

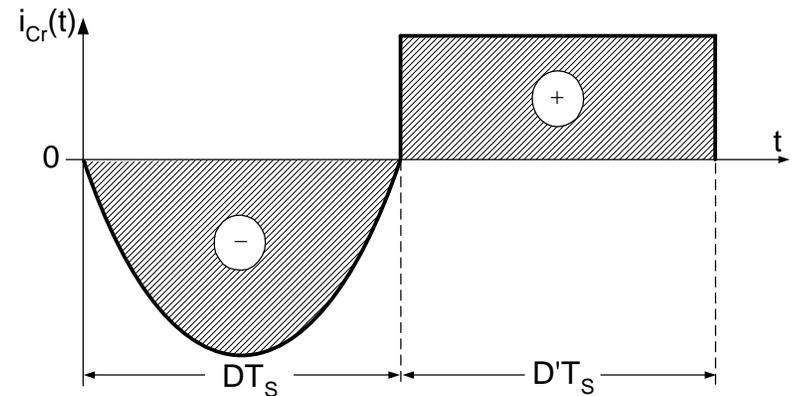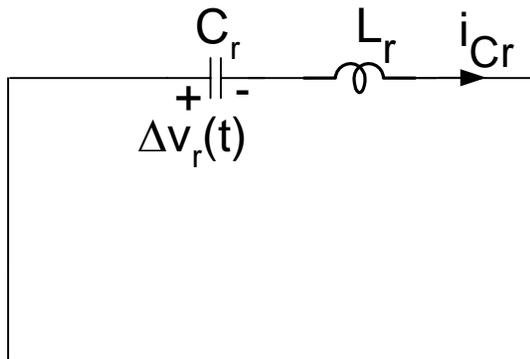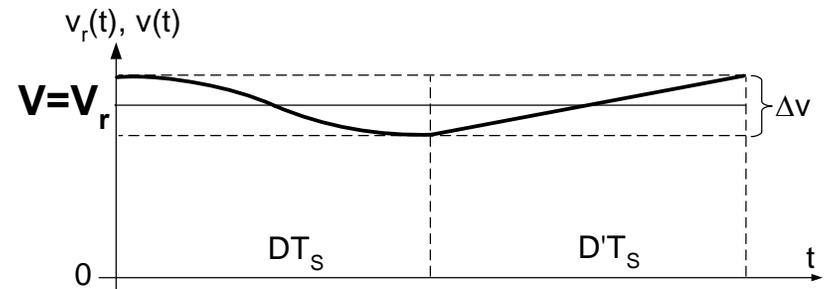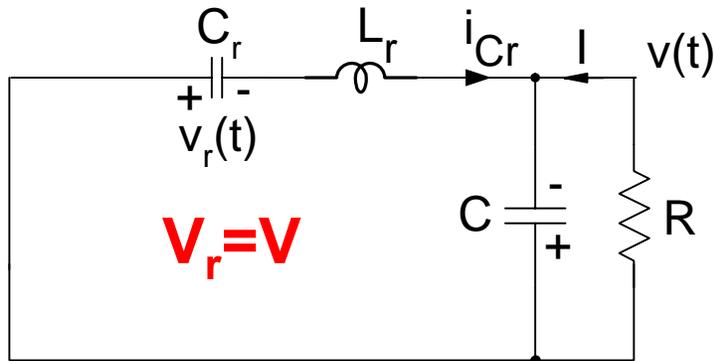



Resonant Inductor Excited by Small Ripple
 Δv_r Voltage Only on Resonant Capacitor

AC-DC

Converter Comparison

True Bridgeless PFC Converter

True Bridgeless PFC Converter*

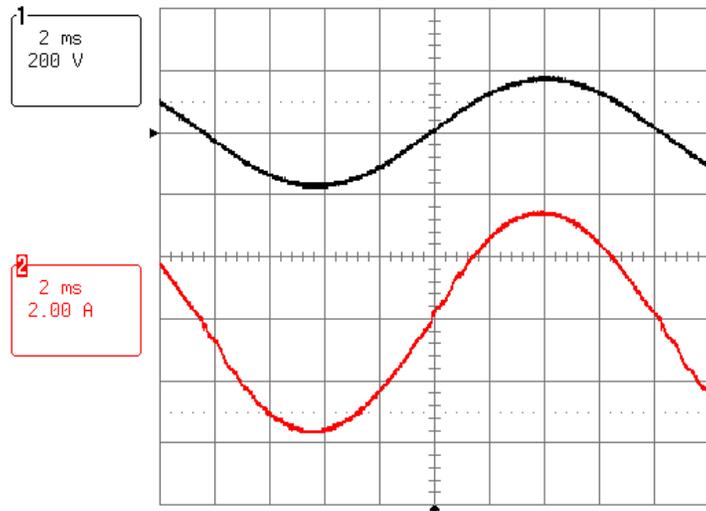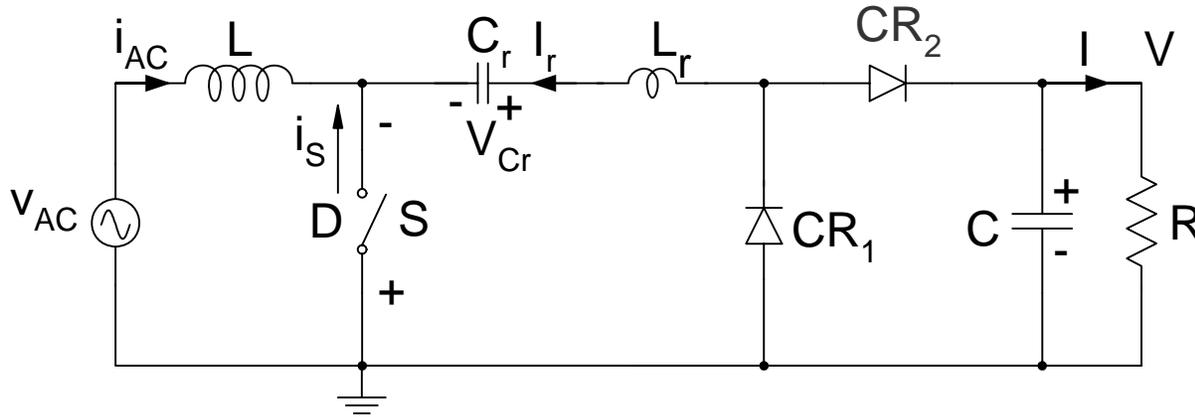


**Input Voltage
110V**

**THD=1.7%
PF=0.999**

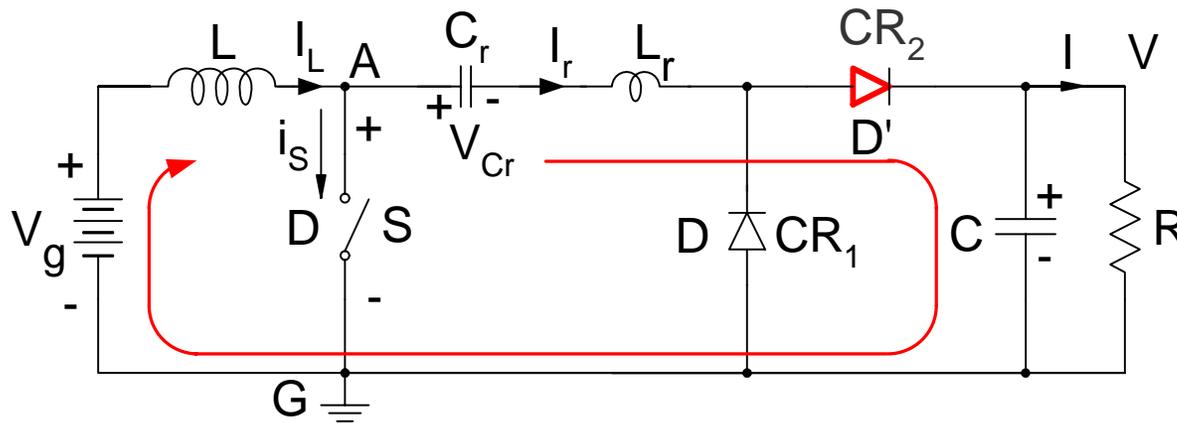
***US and foreign patents pending**

Positive and Negative Half-cycle of Input Voltage



$$V_{Cr} = 0$$

$$V = V_g / (1 - D)$$


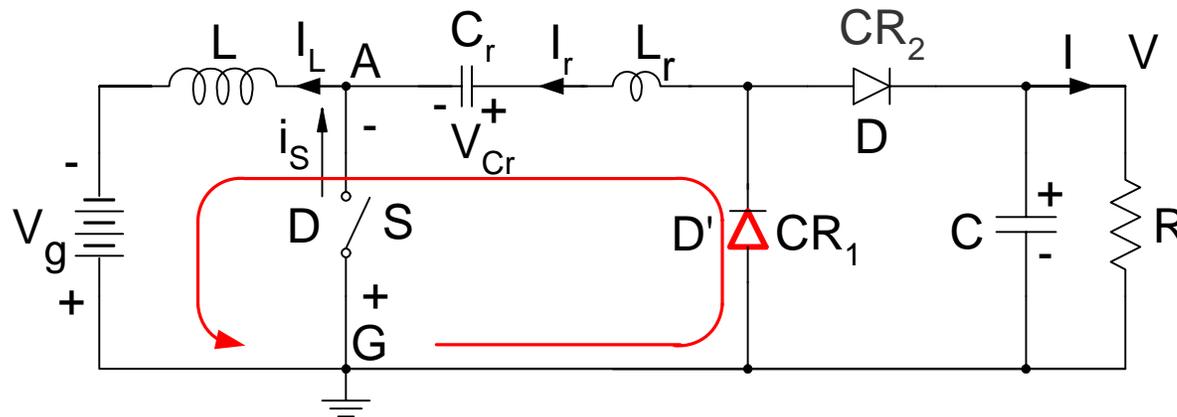


$$V_{Cr} = V$$

Source Polarity Controls Conduction Interval of Two Diodes:


Full-Bridge Eliminated

Flux Balance for Positive Input

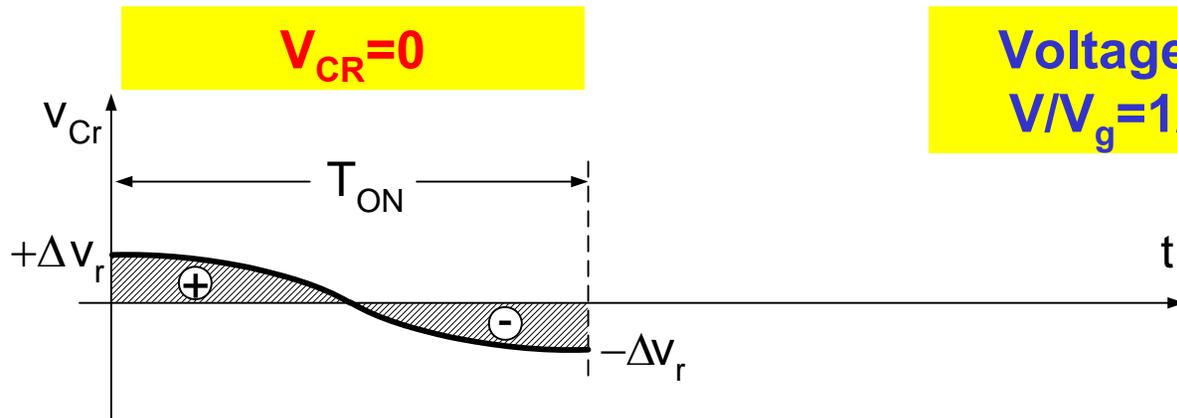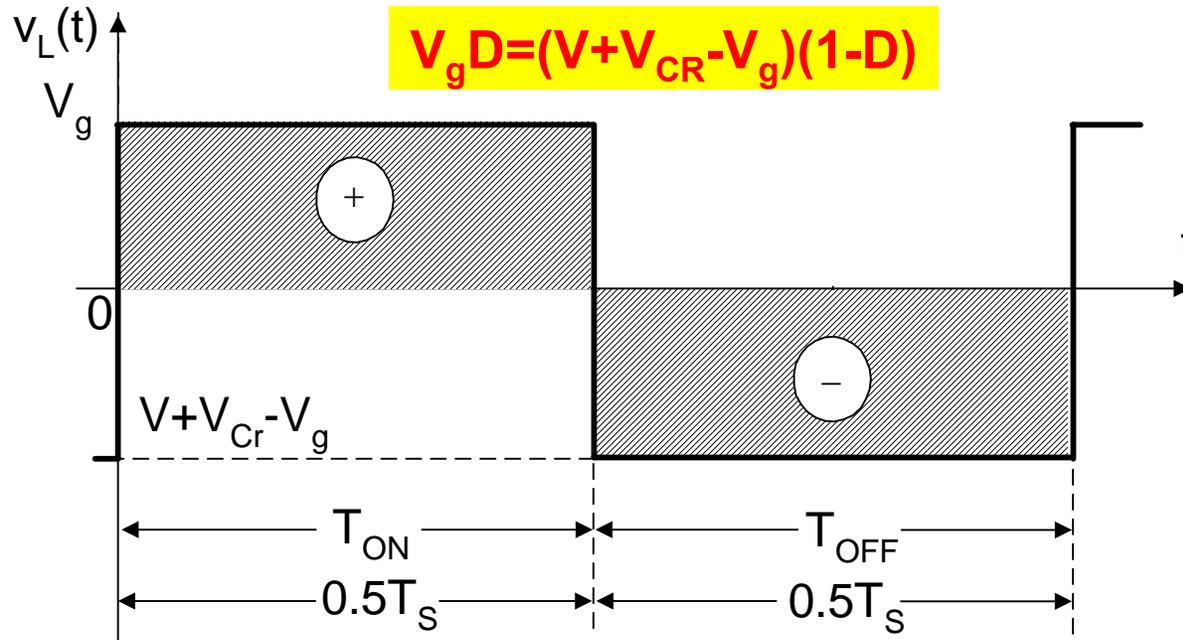

Flux Balance for Negative Input



$$V_g D = (V_{CR} - V_g)(1 - D)$$

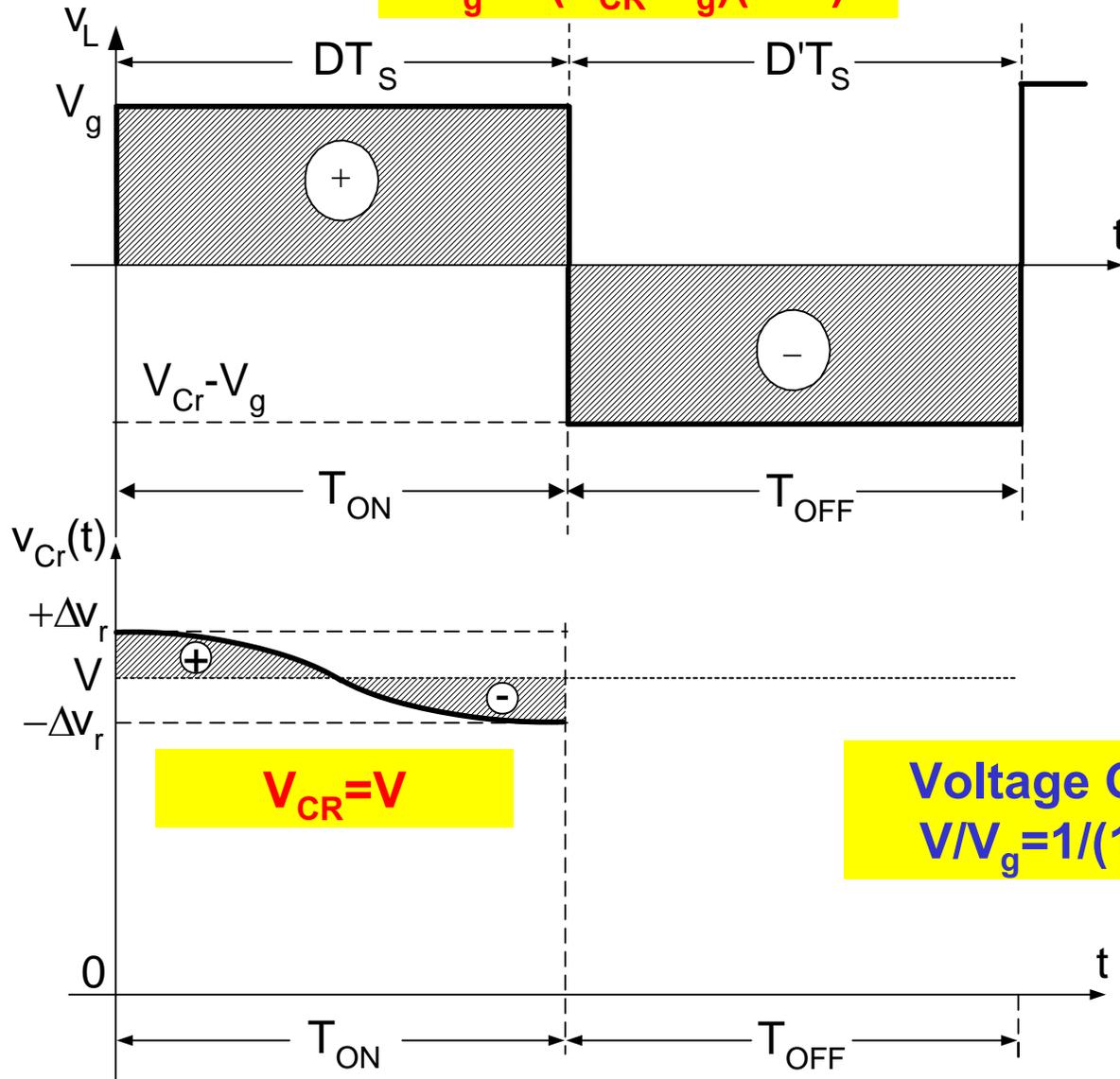




$$V_{CR} = V$$

$$\text{Voltage Gain } V/V_g = 1/(1-D)$$

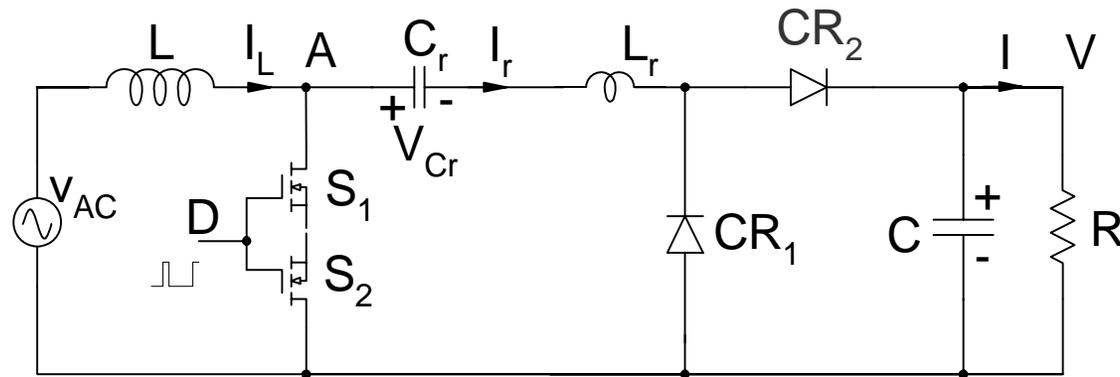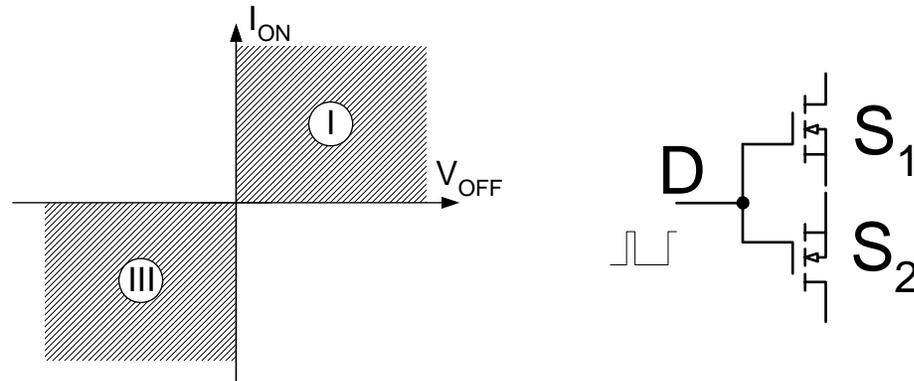One Implementation of the Controlling Switch



Resonant Equivalent Circuit Models

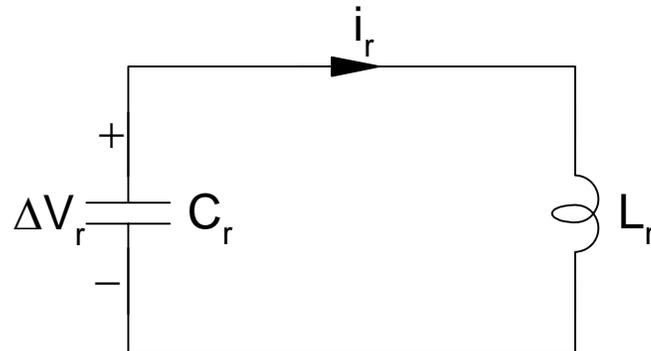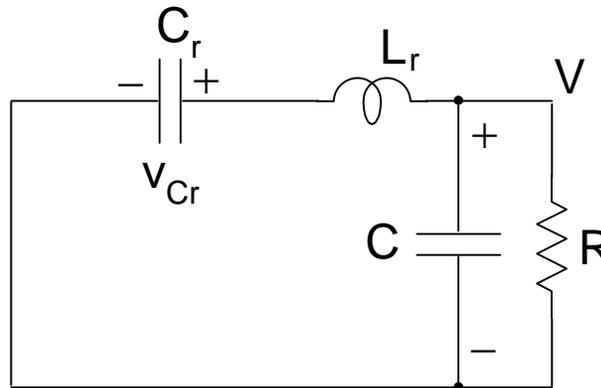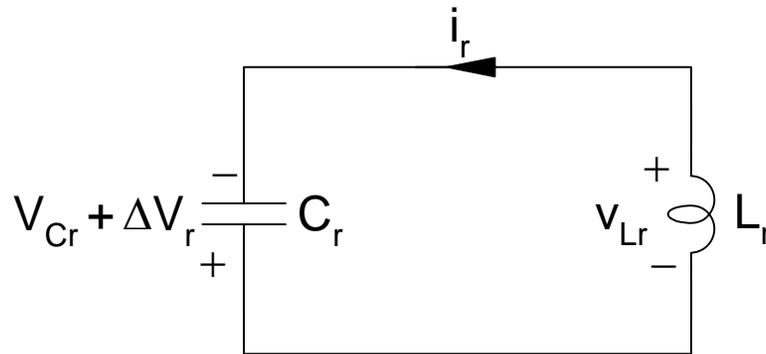

Solutions of Resonant Circuit Equations

$$i_r(t) = I_p \times \sin(\omega_r t)$$

$$v_{C_r}(t) = \Delta v_r \times \cos(\omega_r t)$$


$$\Delta v_r = R_N \times I_p$$

$$R_N = \sqrt{L_r / C_r}$$


$$\omega_r = 1 / \sqrt{L_r C_r}$$

$$f_r = \omega_r / 2\pi$$


Resonant Inductor Current Waveforms

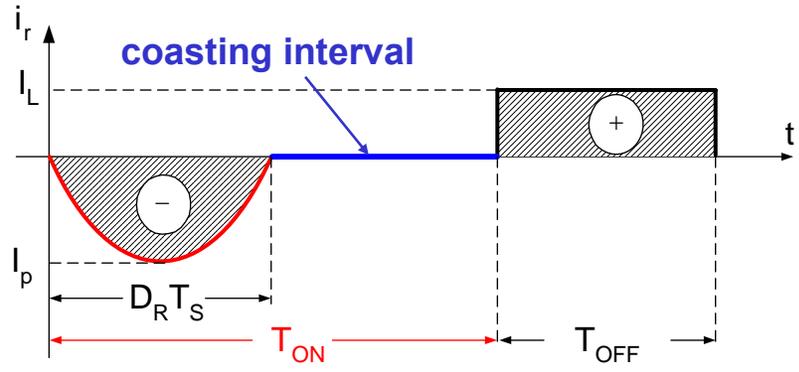

**Variable ON-time
Constant f_s**



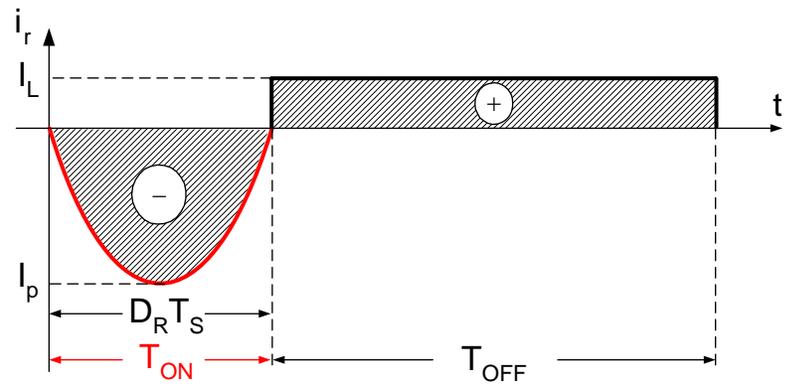


**Constant ON-time
Variable OFF-time**

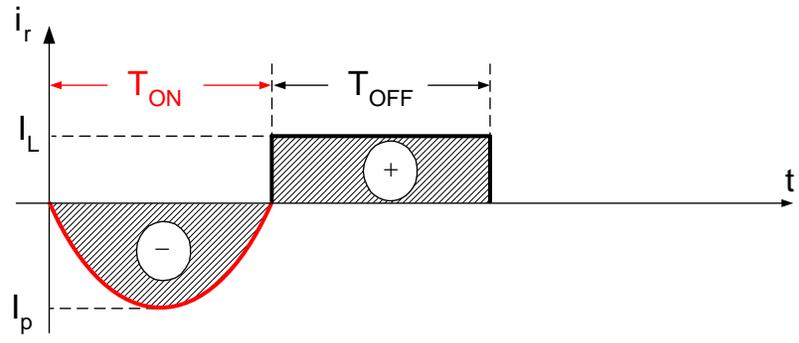


**Constant ON-time
Variable f_s**


Insertion of the Isolation Transformer

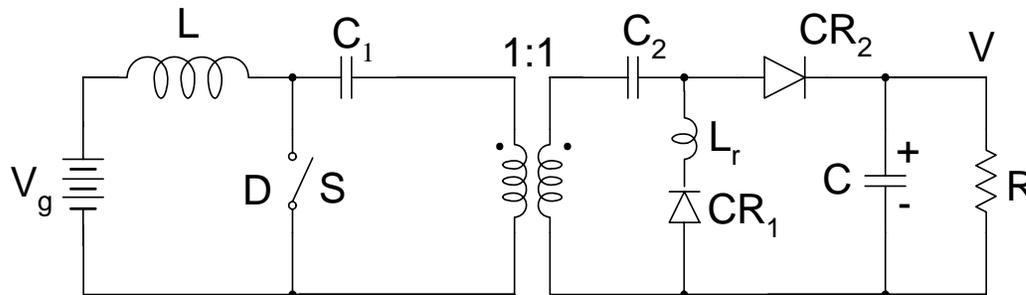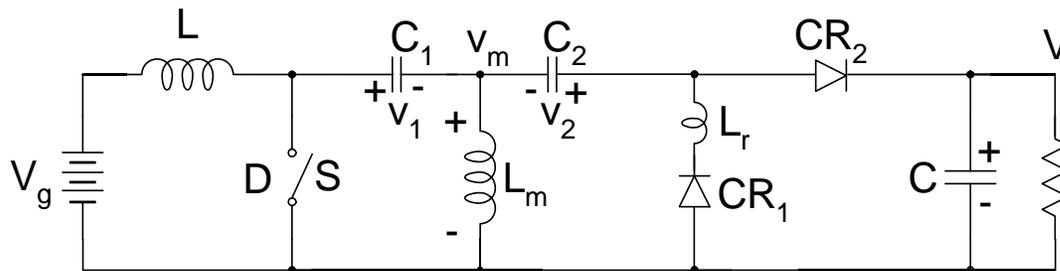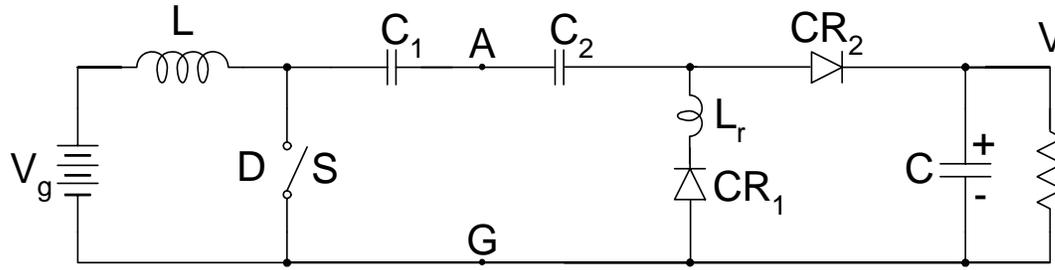

Comparison of Three Transformers Types

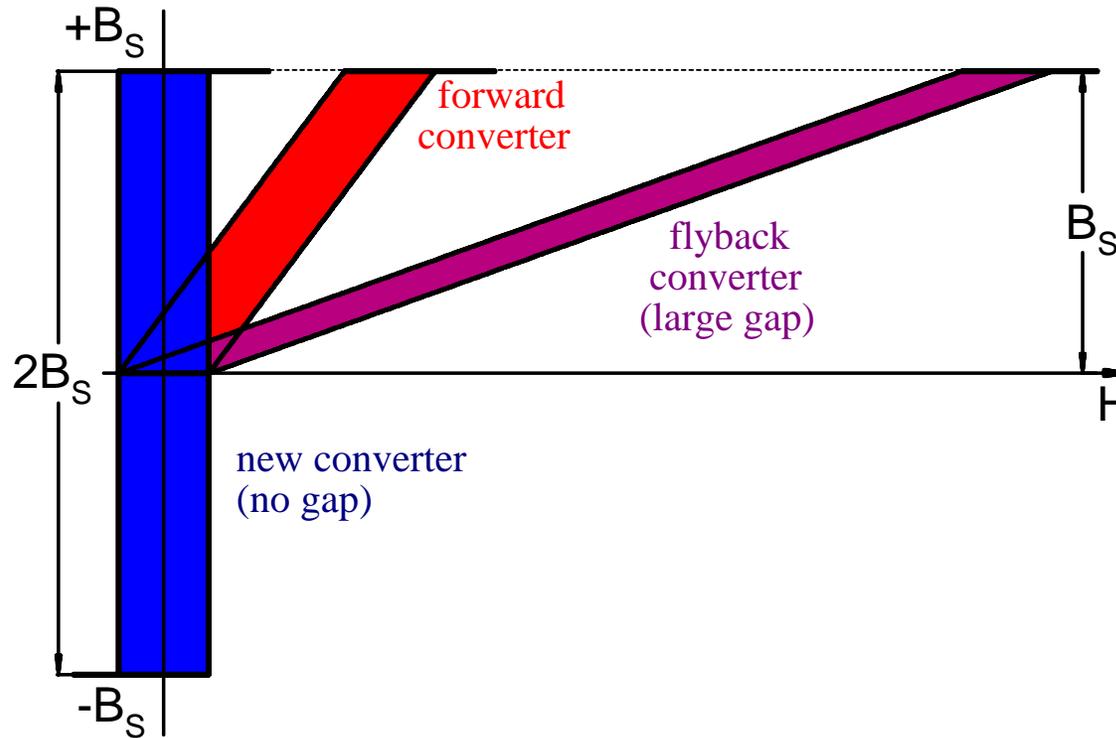




Hybrid-Switching AC-DC Rectifier*

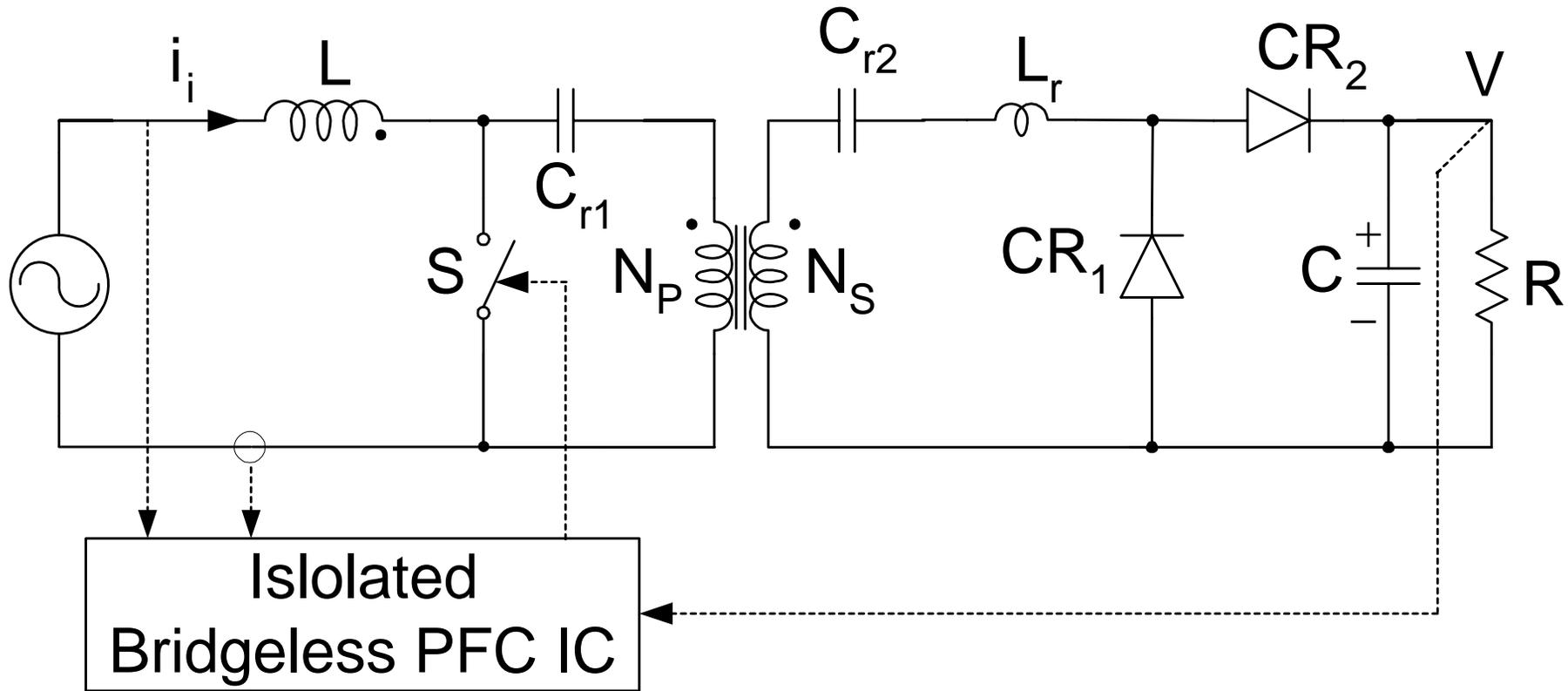

Three Switches Only

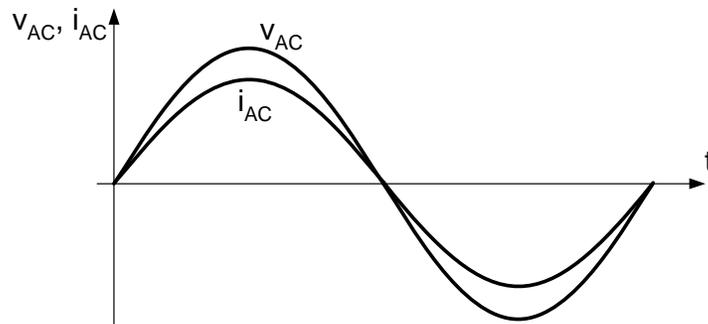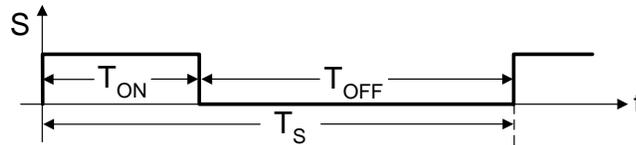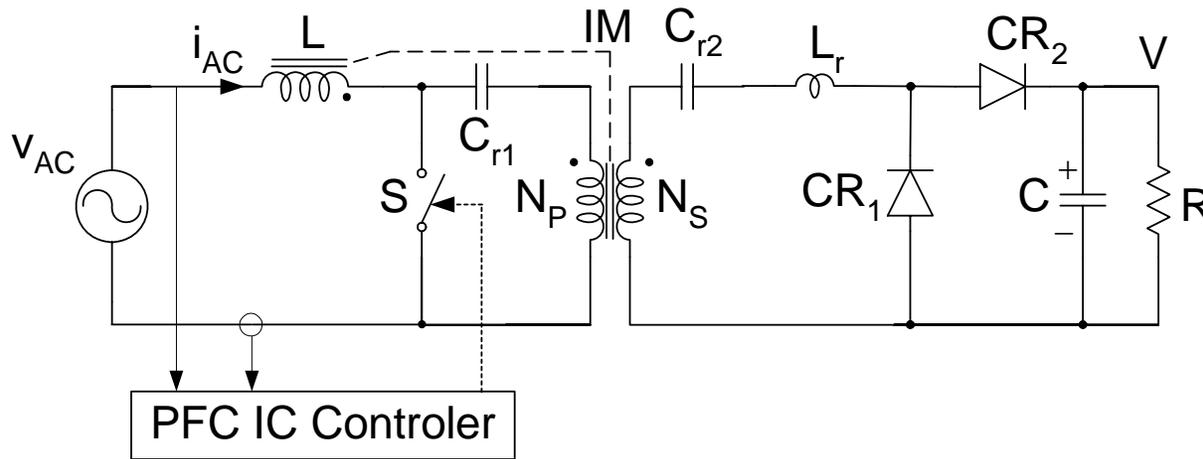
***US and foreign patents pending**

True Bridgeless PFC Converter with Isolation*




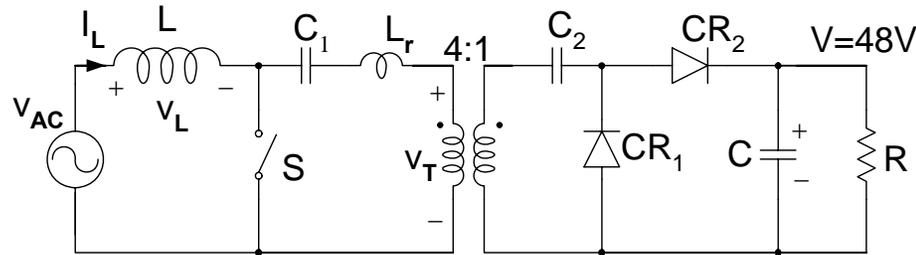***US and foreign patents pending**


Variety of Output Voltages and Applications



Telecom

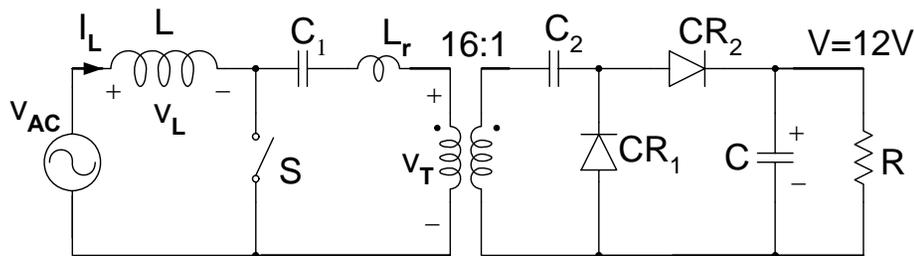

Data Centers

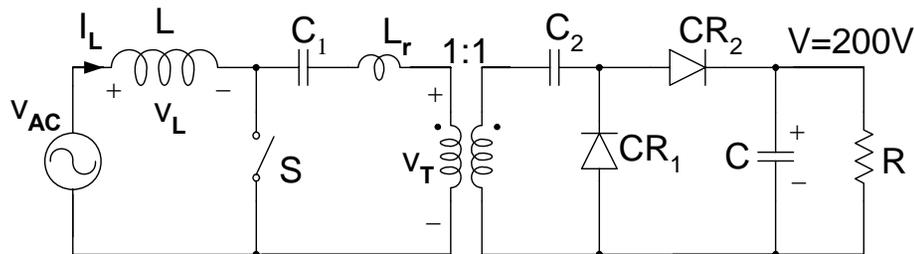


Battery Chargers

AC-DC

Converter Comparison

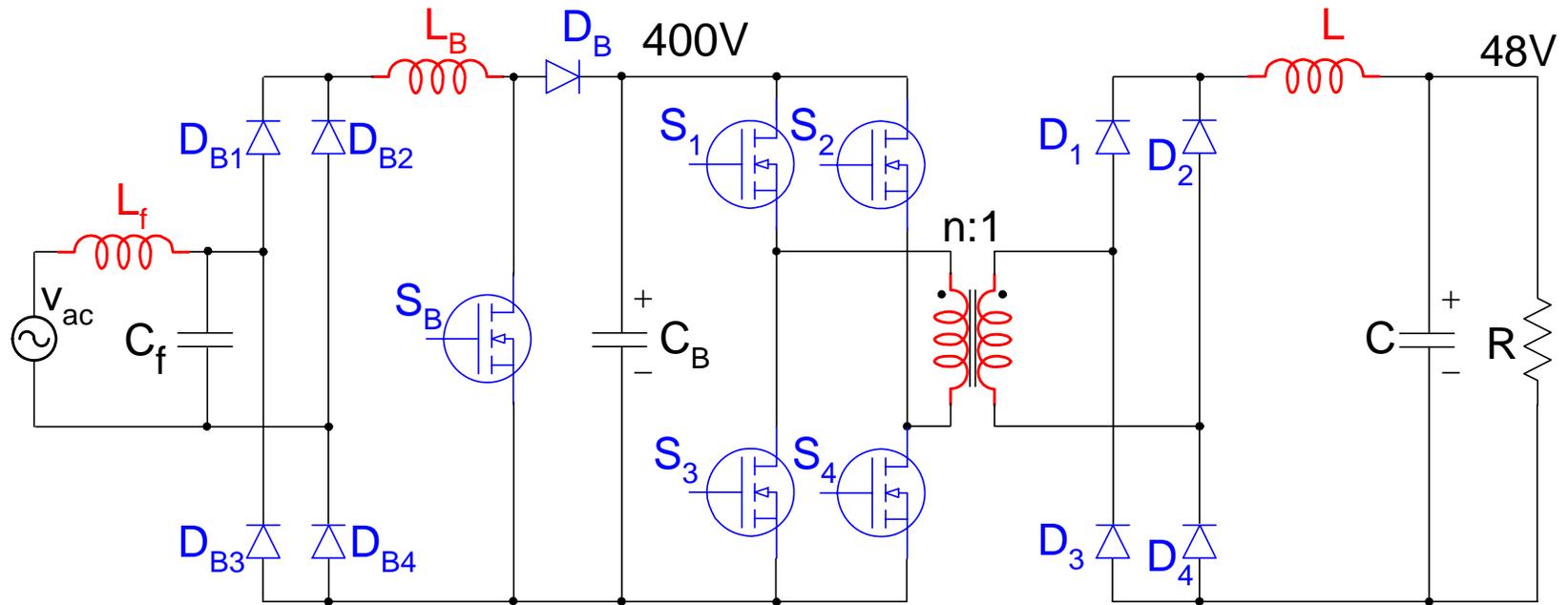Conventional Three Power Processing Stage Approach



Comparison

Power Processing	Single-stage	Three-stage
Type of Converter	Isolated Bridgeless PFC	Bridge-Boost PFC-Full-bridge
Switching Method	HYBRID	Square-wave
Number of switches	3	14
Switch-voltage Stress	Low	High
Lossless-switching	YES	NO
Control	Simple	Complex
Magnetics pieces	1	4
Power Losses	3%	10%
Efficiency	>97%	88% to 90%
Size	Small	Big
Weight	Light	Heavy
Cost	Low	High


AC-DC conversion Summary

- Single stage power processing
- Efficiency greater than 97%
- Power factor greater than 0.99
- Meets IEC 1000-3-2 regulations
- Galvanic isolation
- Low weight and size
- **NO CUSTOM COMPONENTS**
- **LOW COST**

Three-Phase AC-DC


Converter Comparison

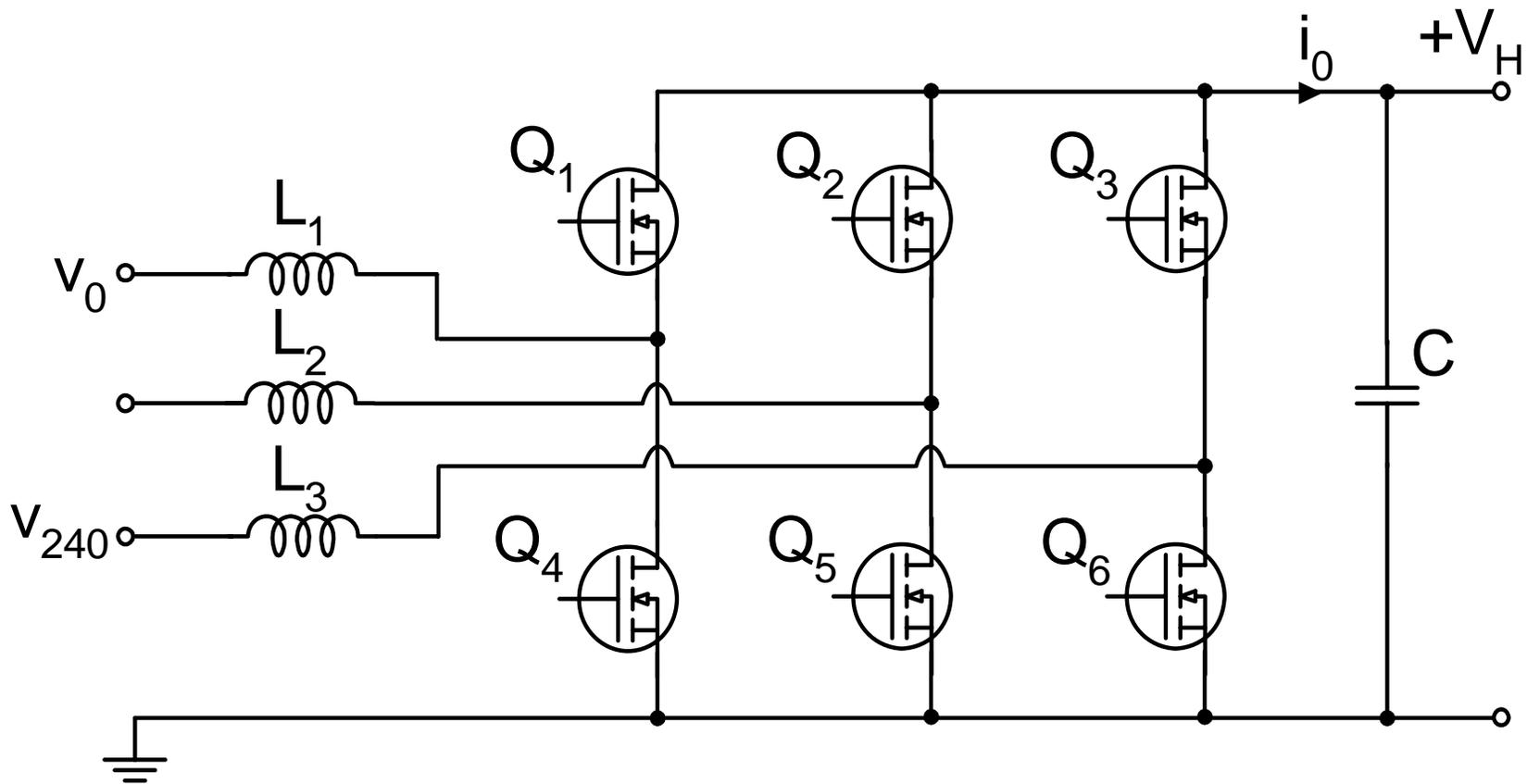Conventional PFC Three-phase to DC Rectification without Isolation Transformer




**Three-phase properties
prematurely lost after rectification**

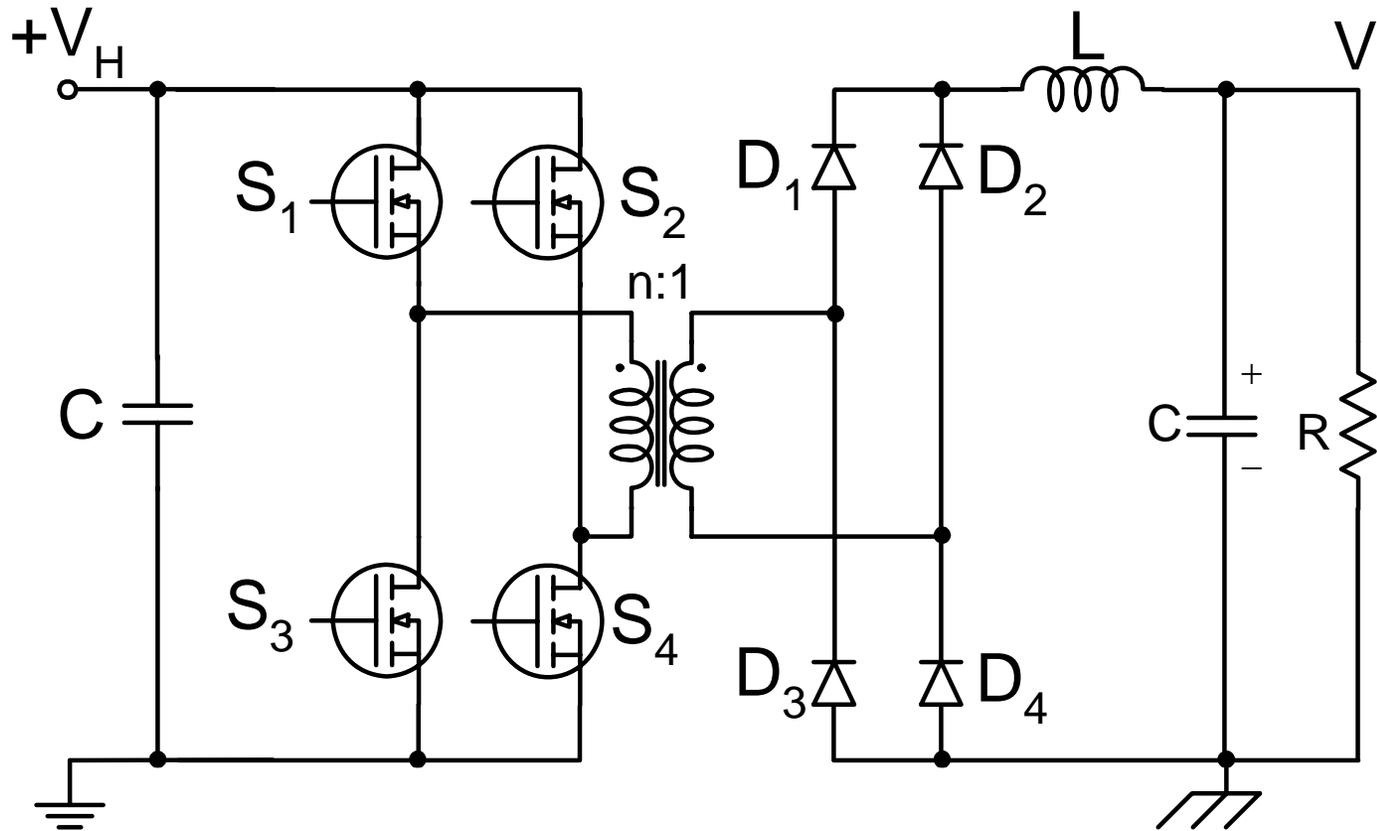Second Stage: Isolated DC-to-DC Converter



DC Storage in output inductor

New Single-stage Three-phase Rectifier

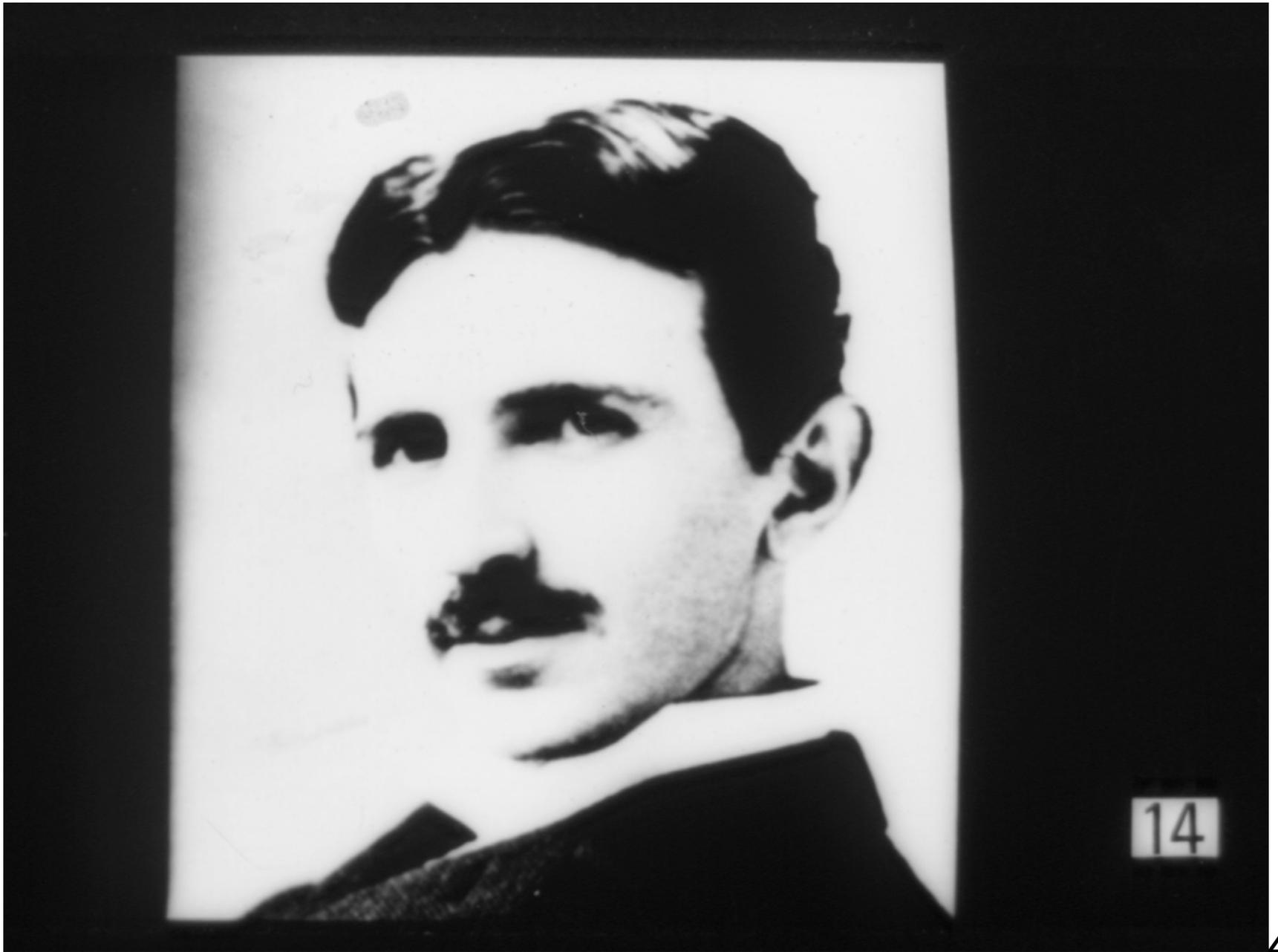

14


$$\Phi = B \cdot S$$

$$\frac{Wb}{m^2} = T$$

(TESLA)

31

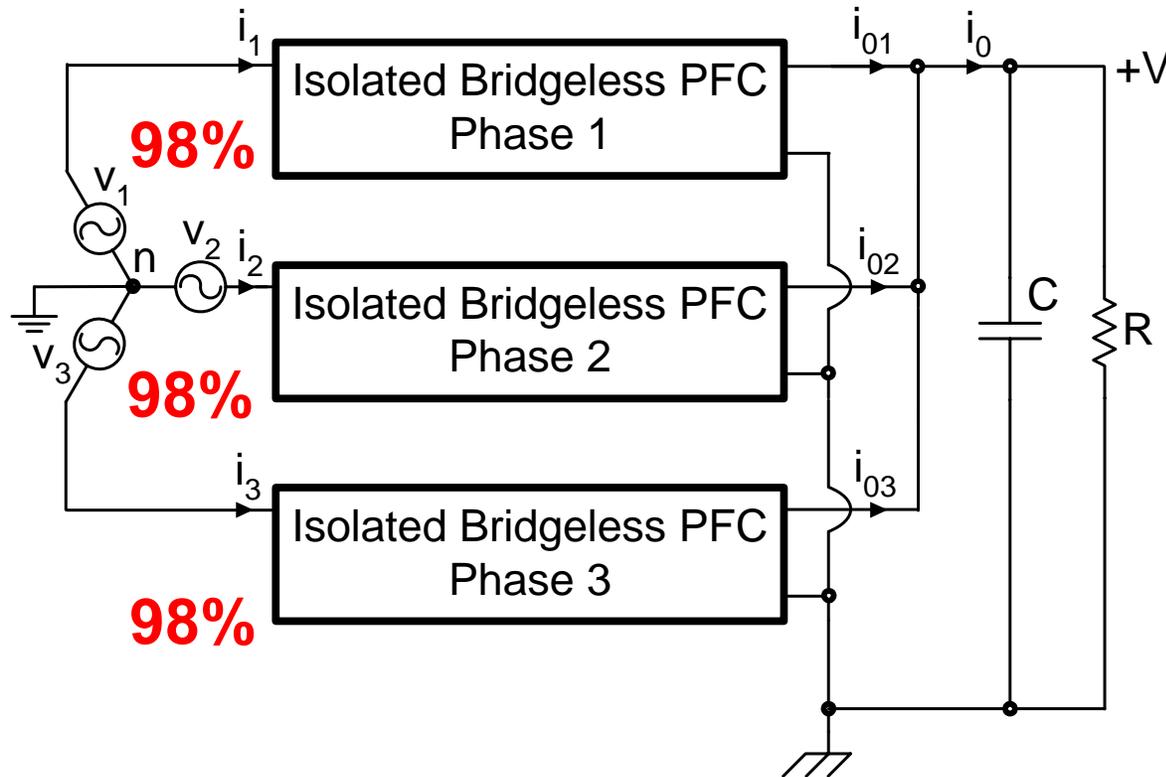New Direct Three-Phase to DC Conversion with PFC and Isolation in a Single Stage




Power processed in parallel and not in series

Each Phase Efficiency 98%; TOTAL Efficiency 98%

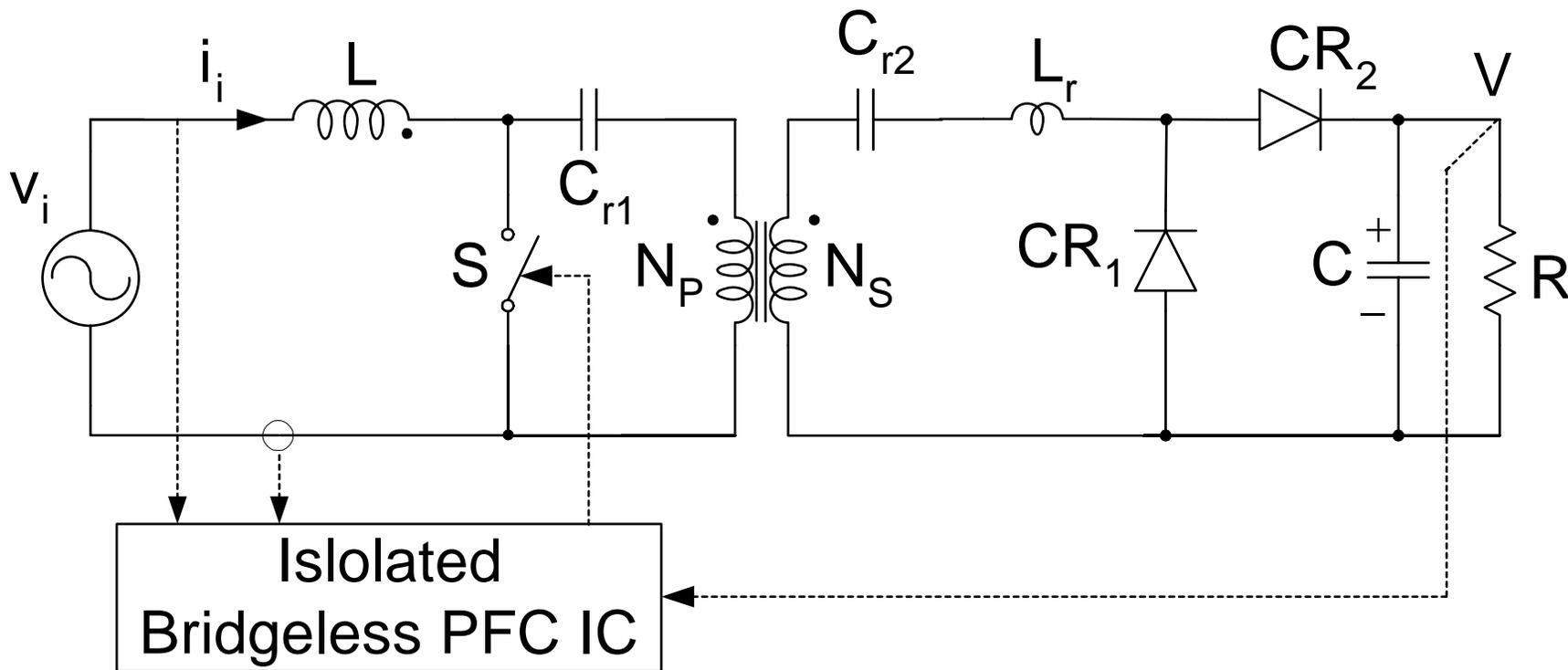***US and foreign patents pending**


AC-DC Converter for Each Phase with PFC and Isolation*



Three Switches Only


***US Patent No. 7,778,046**

Input Currents of Three-phase Input

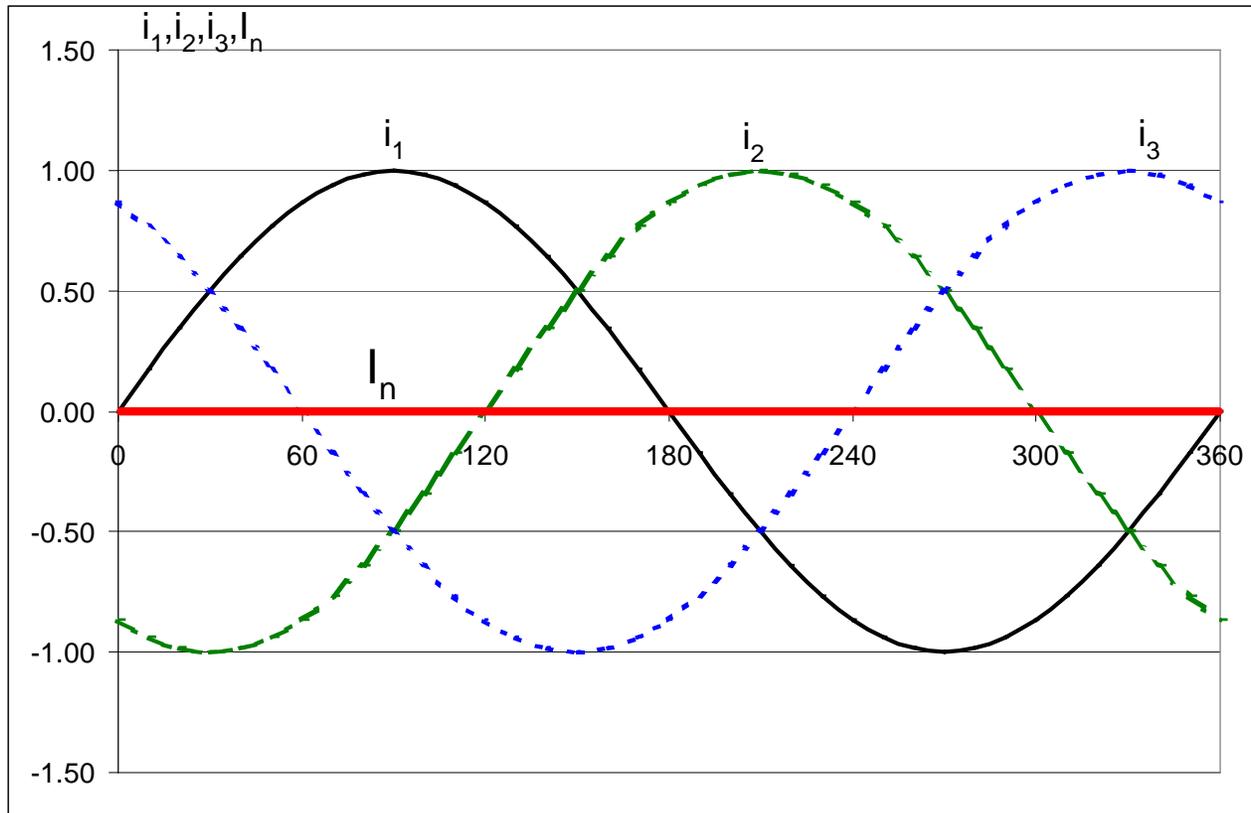


Neutral current is zero

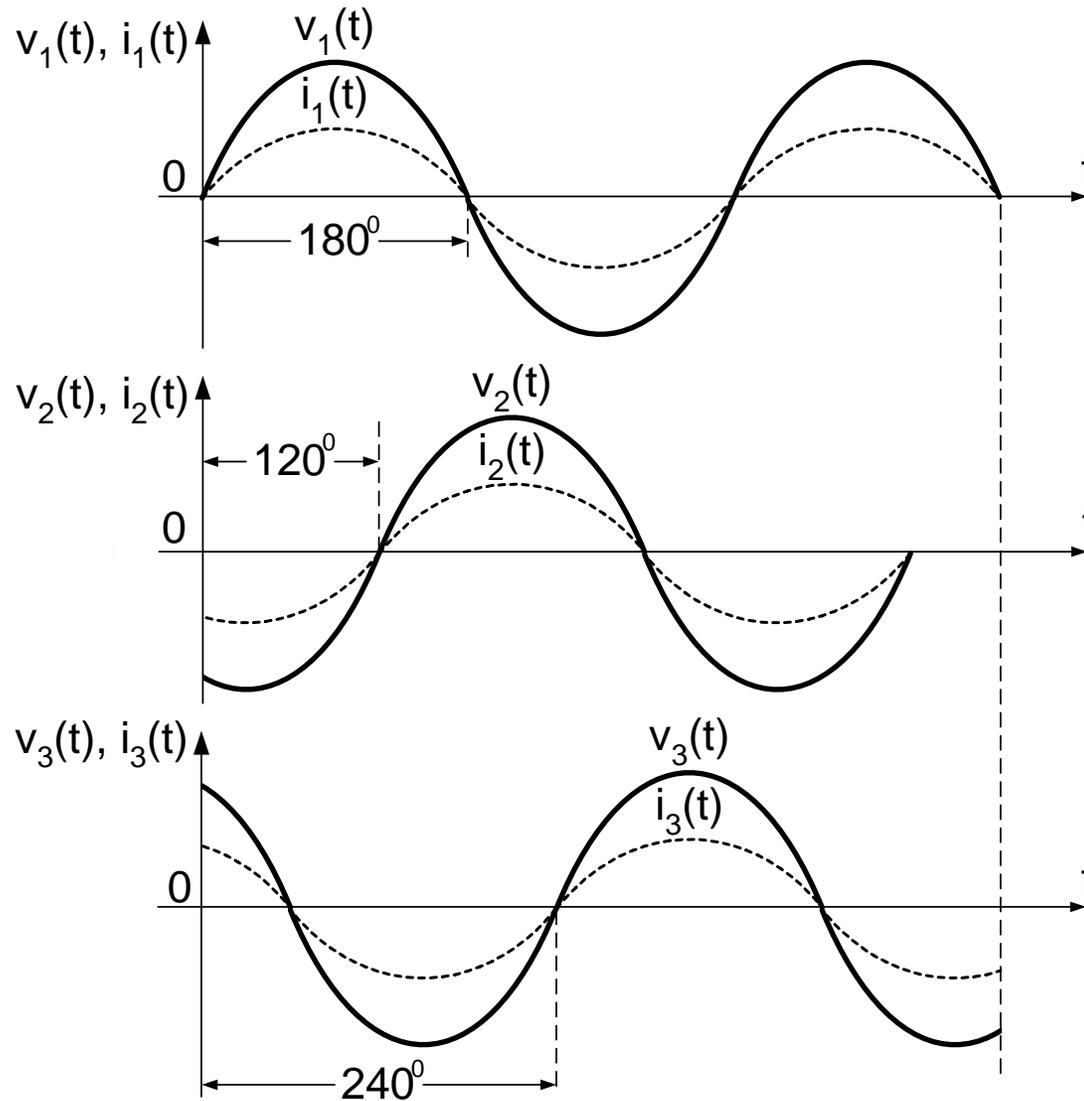
Input Voltages and Input Currents for Unity Power Factor



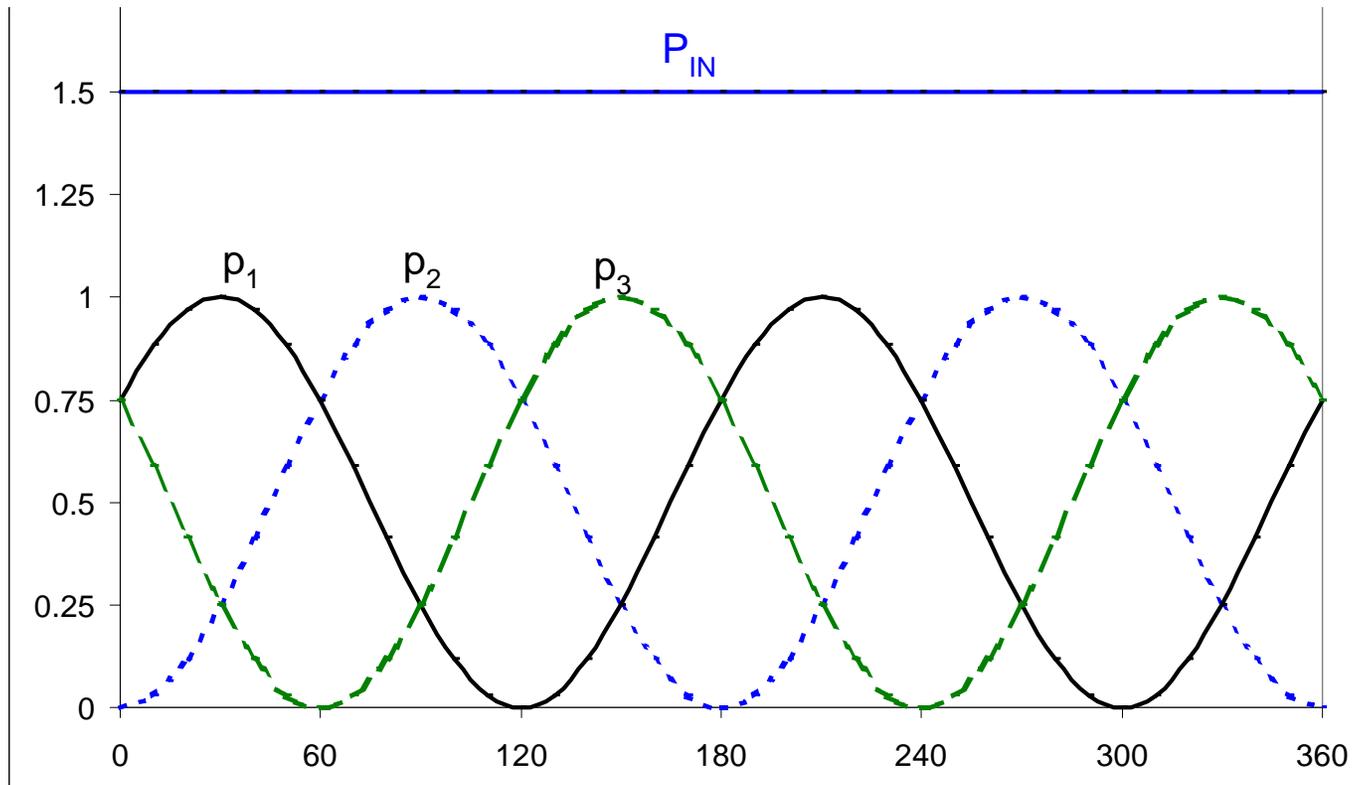Sum of Instantaneous Input Powers of Three Phases is Constant




Instantaneous Input Power is Constant

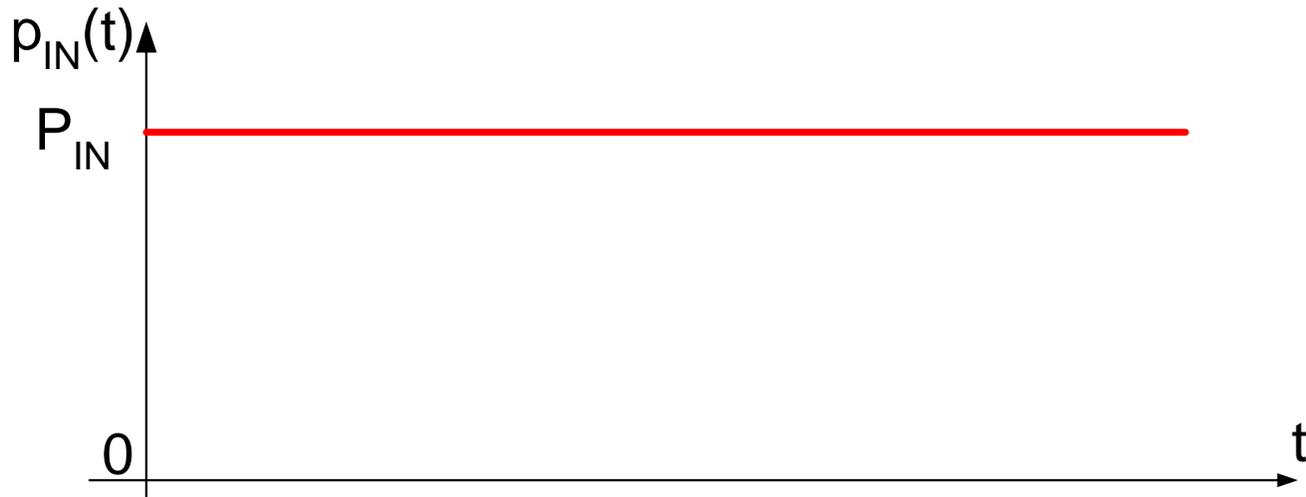



$$P_{IN} = \text{constant}$$

Instantaneous Output Power is Constant

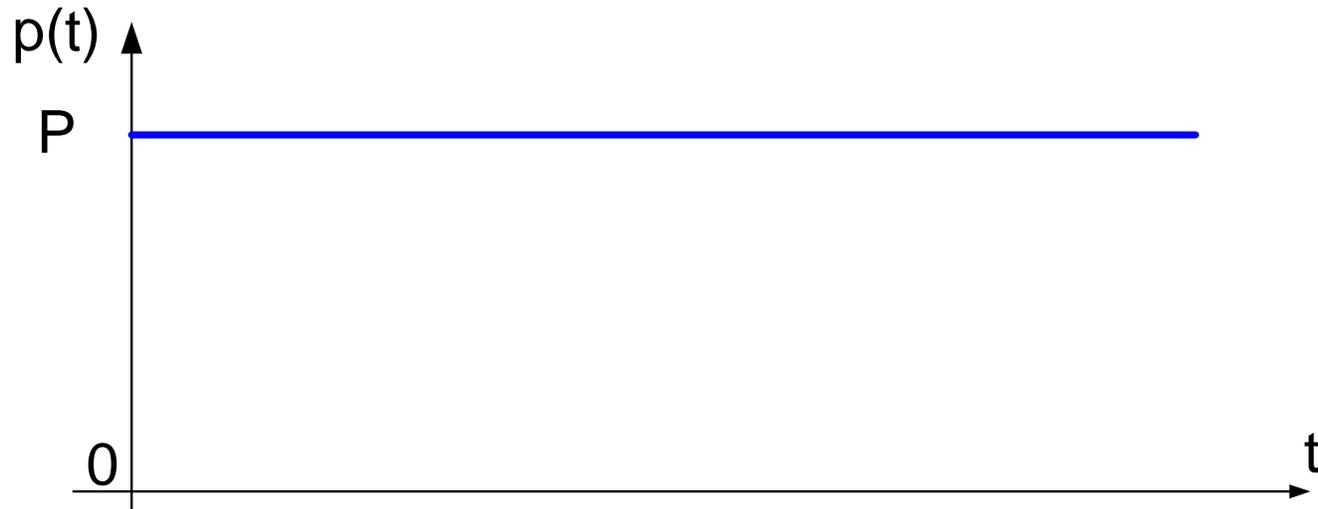


$$P = \text{constant}$$

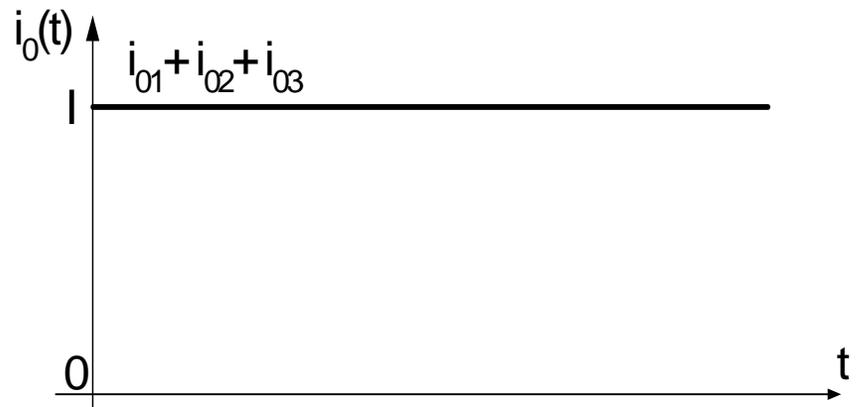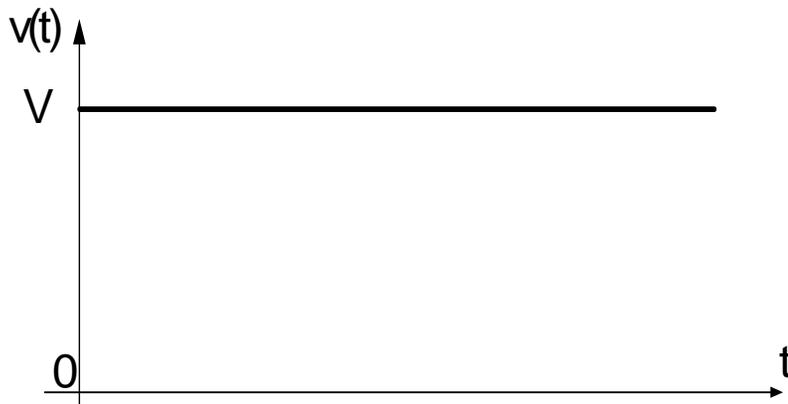Constant Output Power and Constant Output Voltage Lead to Constant Output Current




$P = \text{constant}$
 $V = \text{constant}$ \Rightarrow $I = \text{constant}$

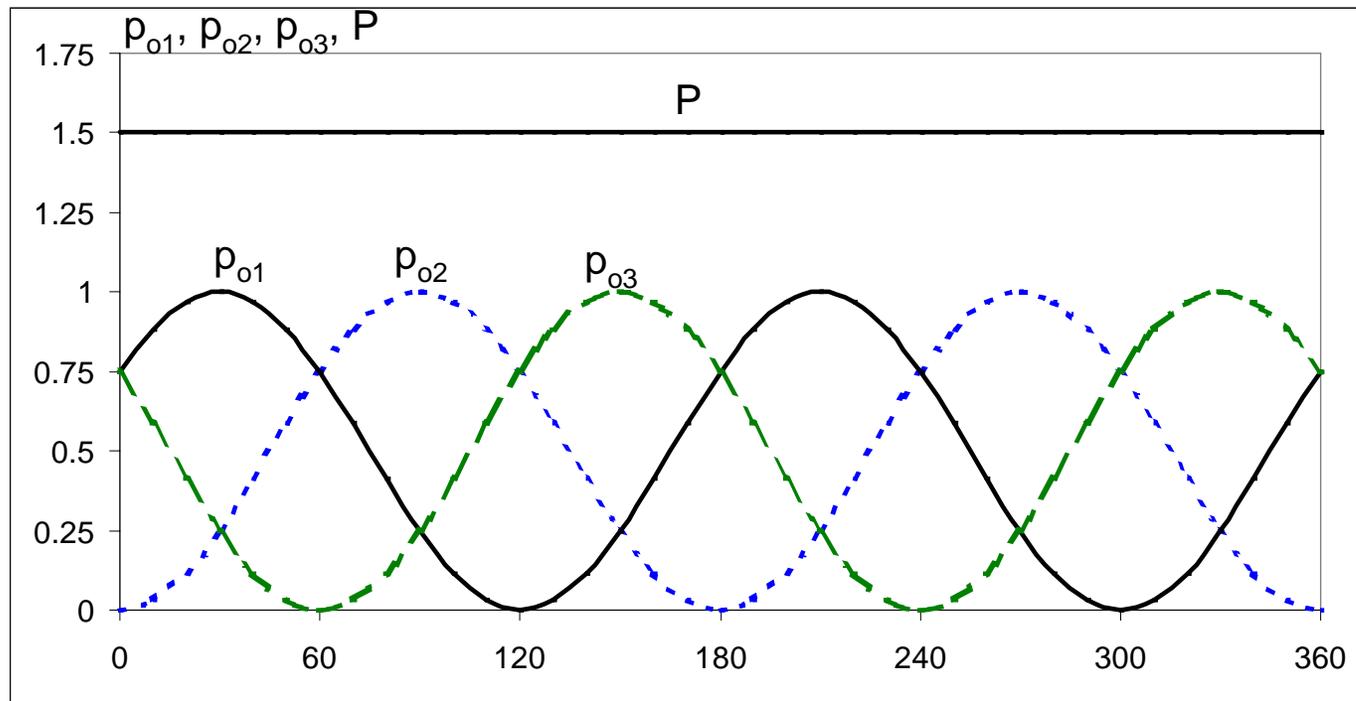Sum of Instantaneous Output Powers of Three Phases is Constant




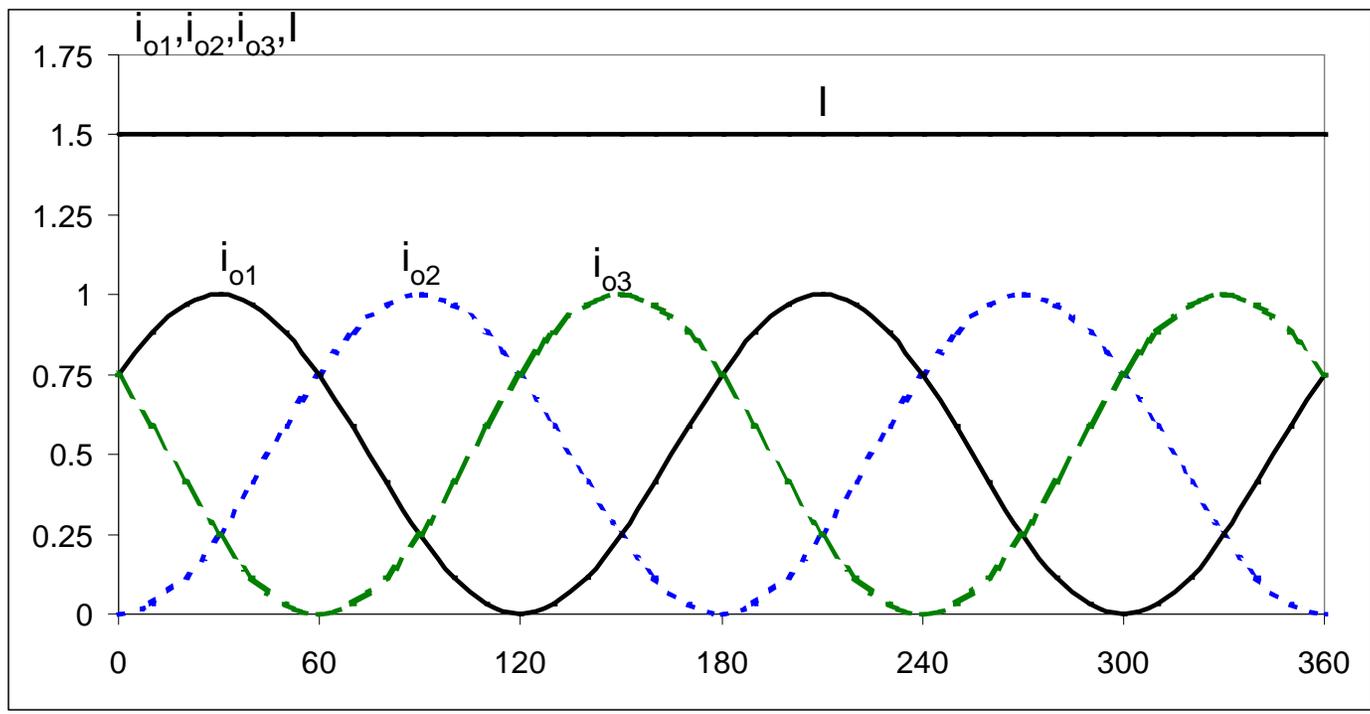
Sum of Instantaneous Output Currents of Each Phase is Constant





DC-AC

Inverter Comparison

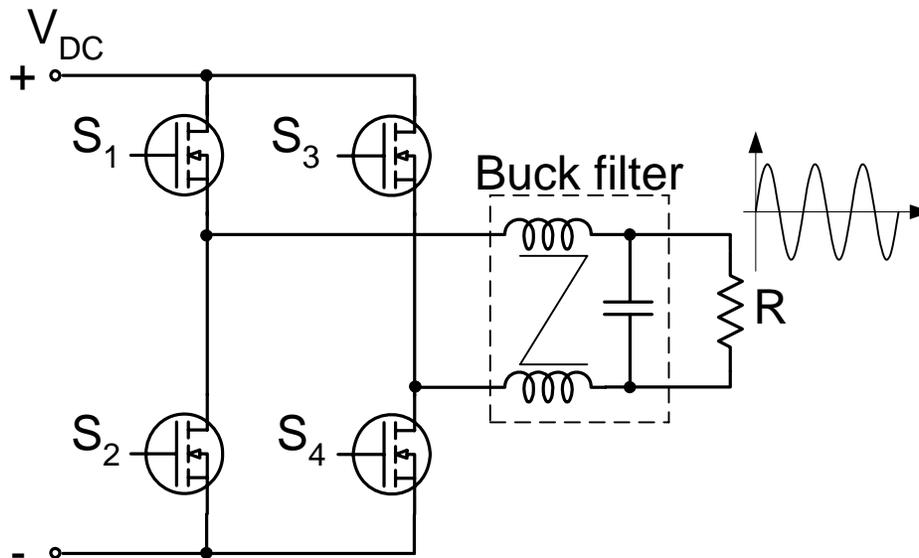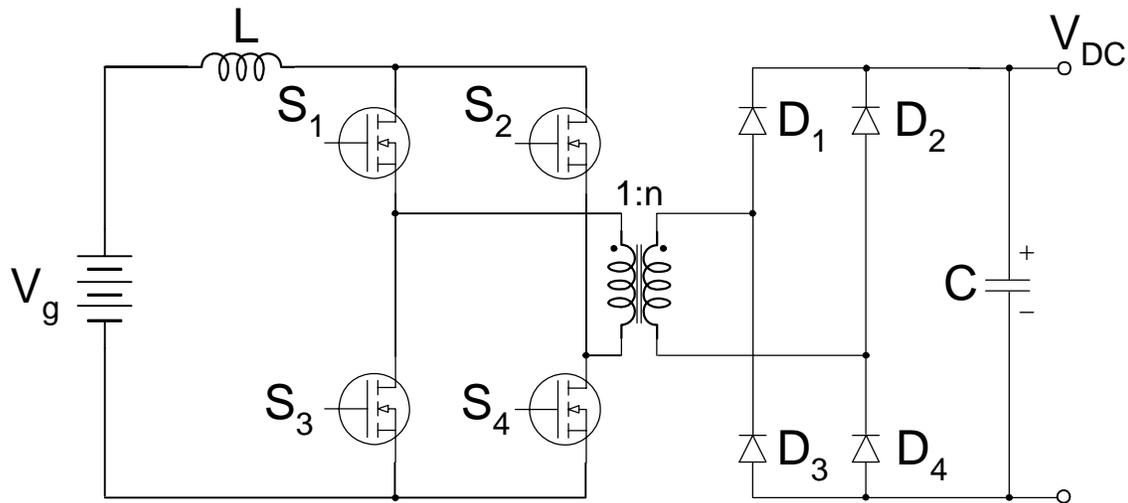DC-AC Inverter with Full-Bridge Boost Converter



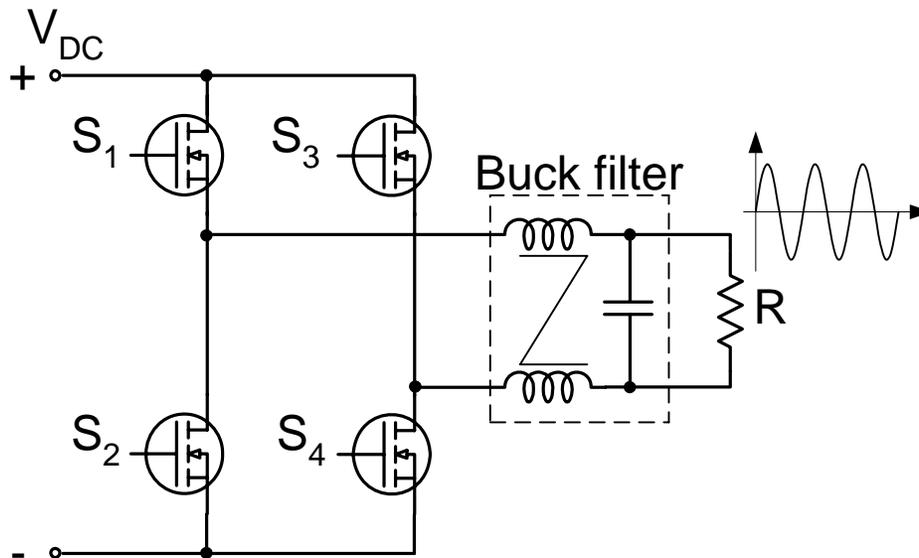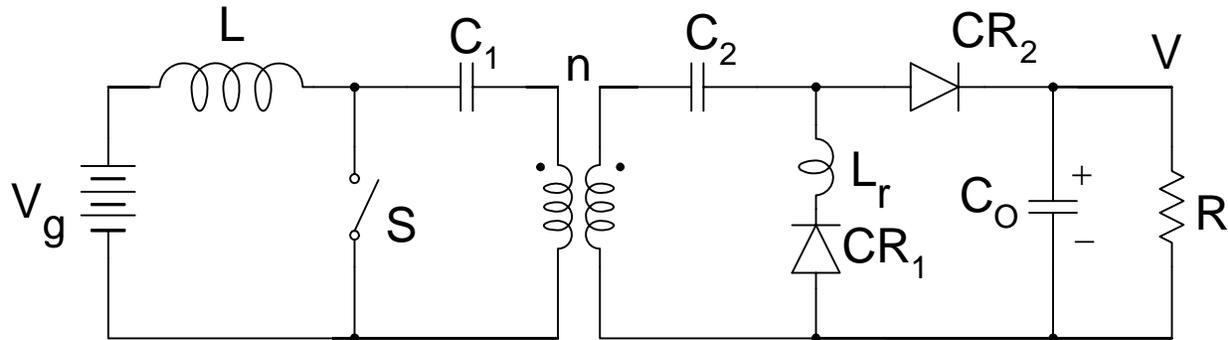DC-AC Inverter with Three switch-boost Converter



Comparison Table

Type of Converter	Cuk-boost Converter	Full-bridge Converter
Switching Method	HYBRID	Square-wave
Number of switches	3	8
Transistors	1	4
Diodes	2	4
Control	Simple	Complex
Magnetics pieces	1	2
Power Losses	2.5%	6.5%
Efficiency	>97.5%	94%

Hybrid-Switching Converters

1. DC-DC converters with high-frequency isolation and 3 switches only
2. Single-stage AC-DC conversion with PFC and high-frequency isolation
3. Single-Stage, Three-Phase AC-DC Rectification with high-frequency isolation
4. Single-stage DC-AC inversion with high-frequency isolation
5. Duty ratio control and high efficiency


New Storageless-Switching Method for DC-DC Converter

Non-isolated and Isolated Converter Topologies

“Birth ” of Storageless Switching Method and Related Converter Topologies



Storageless Switching Method

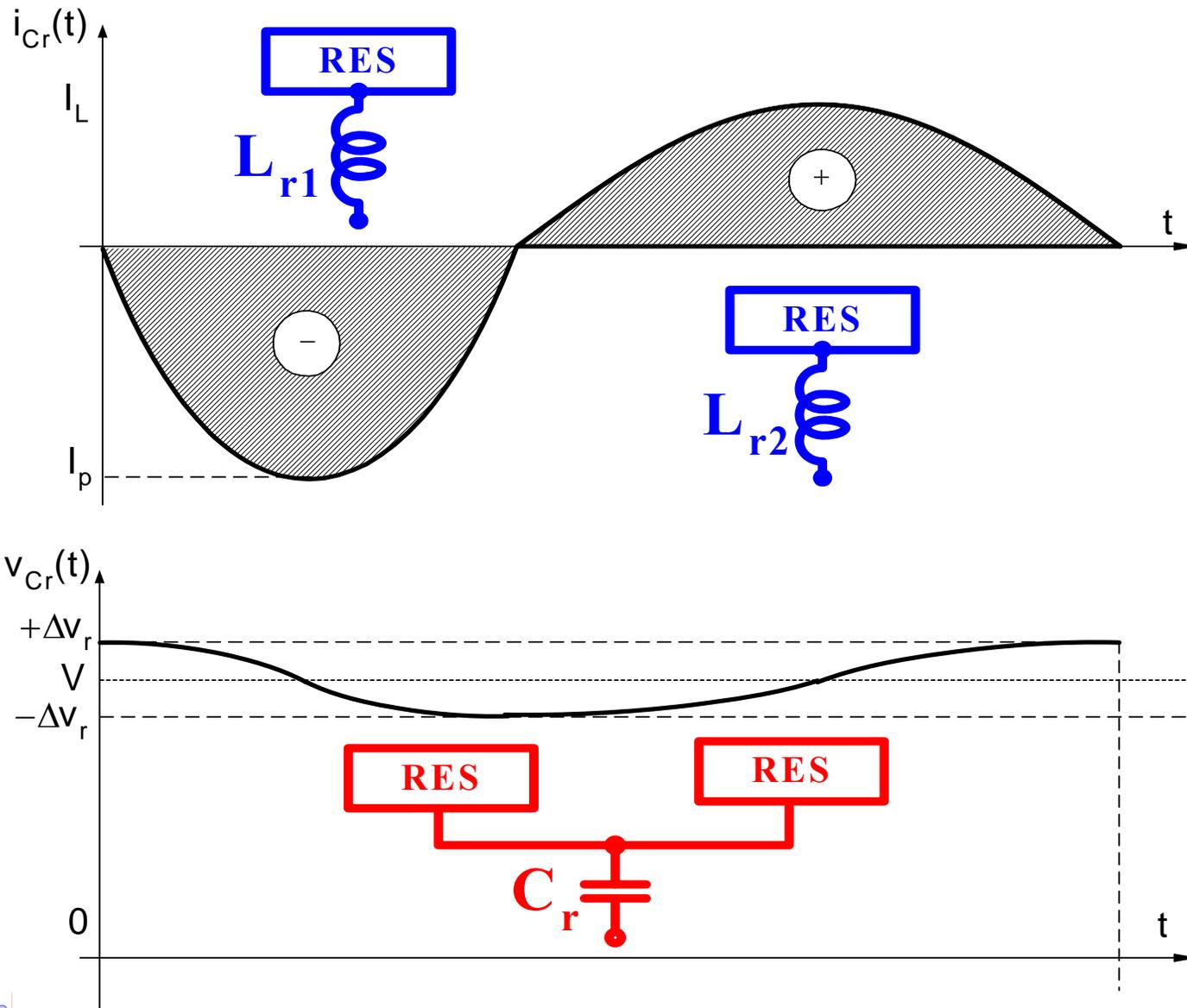

Storageless-Switching Method:

1. Two separate resonant inductors define two independent resonances:
 - a) during ON-time interval
 - b) during OFF-time interval
2. Common resonant capacitor
3. Duty ratio control of output voltage

Power Stage of 750W, 48V Prototype*


Storageless Buck Converter™




Efficiency over 99%

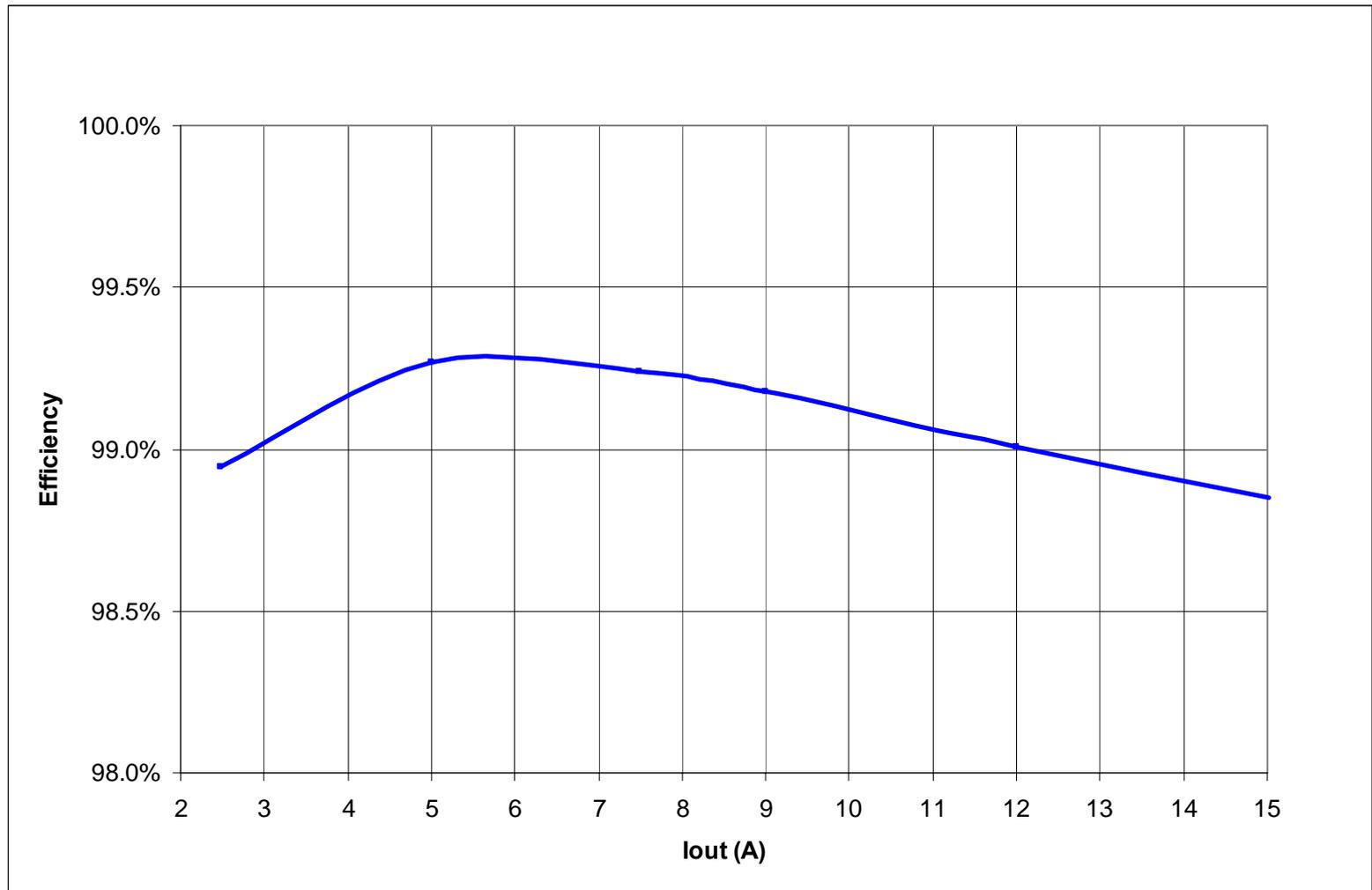***US and foreign patents pending**

Efficiency of 750W, 100V to 48V Converter



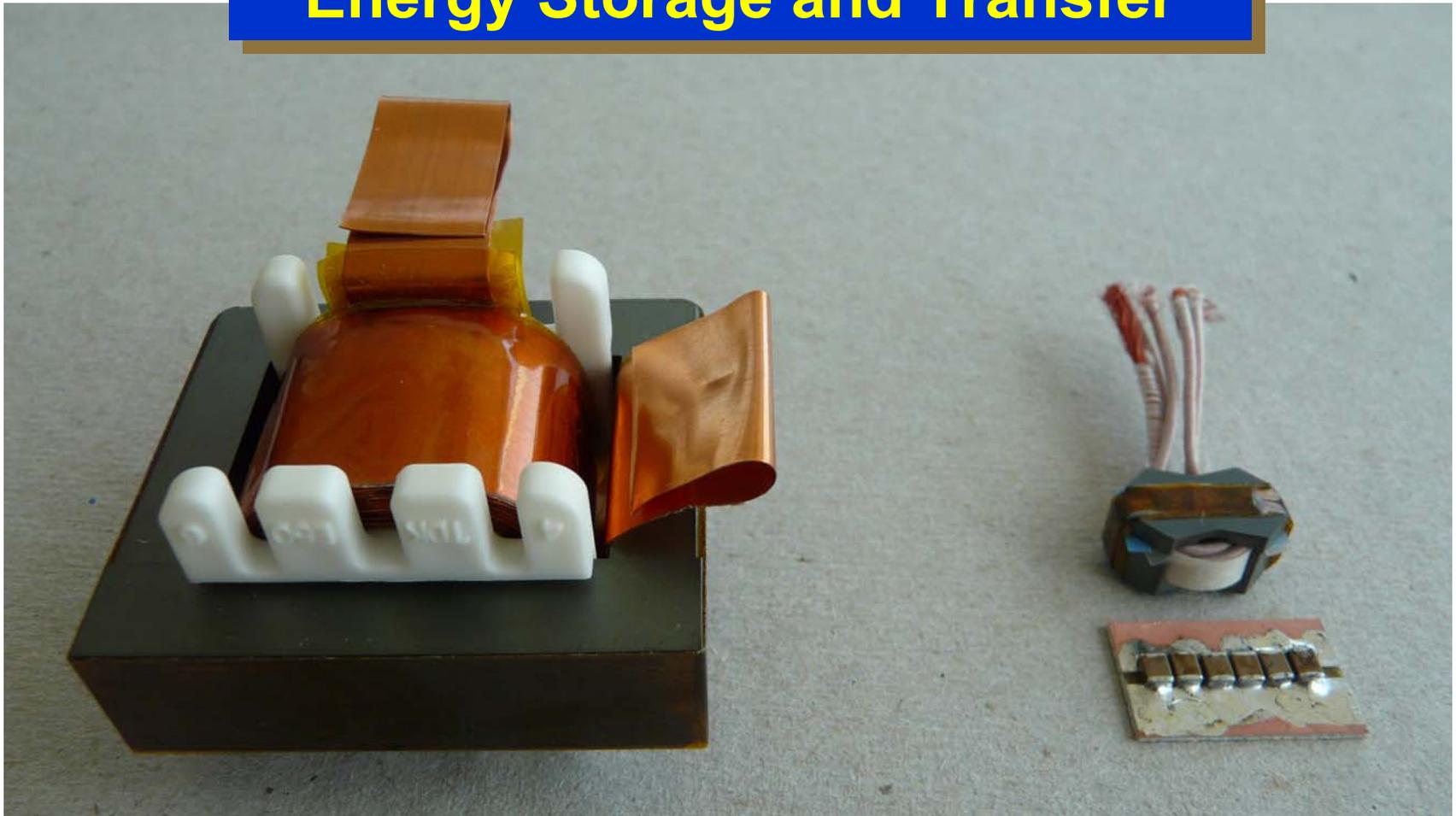
750W, 100V to 48V Converter Energy Storage and Transfer



Inductive Only
Buck

Resonant
Storageless


750W, 48V, 16A Energy Storage

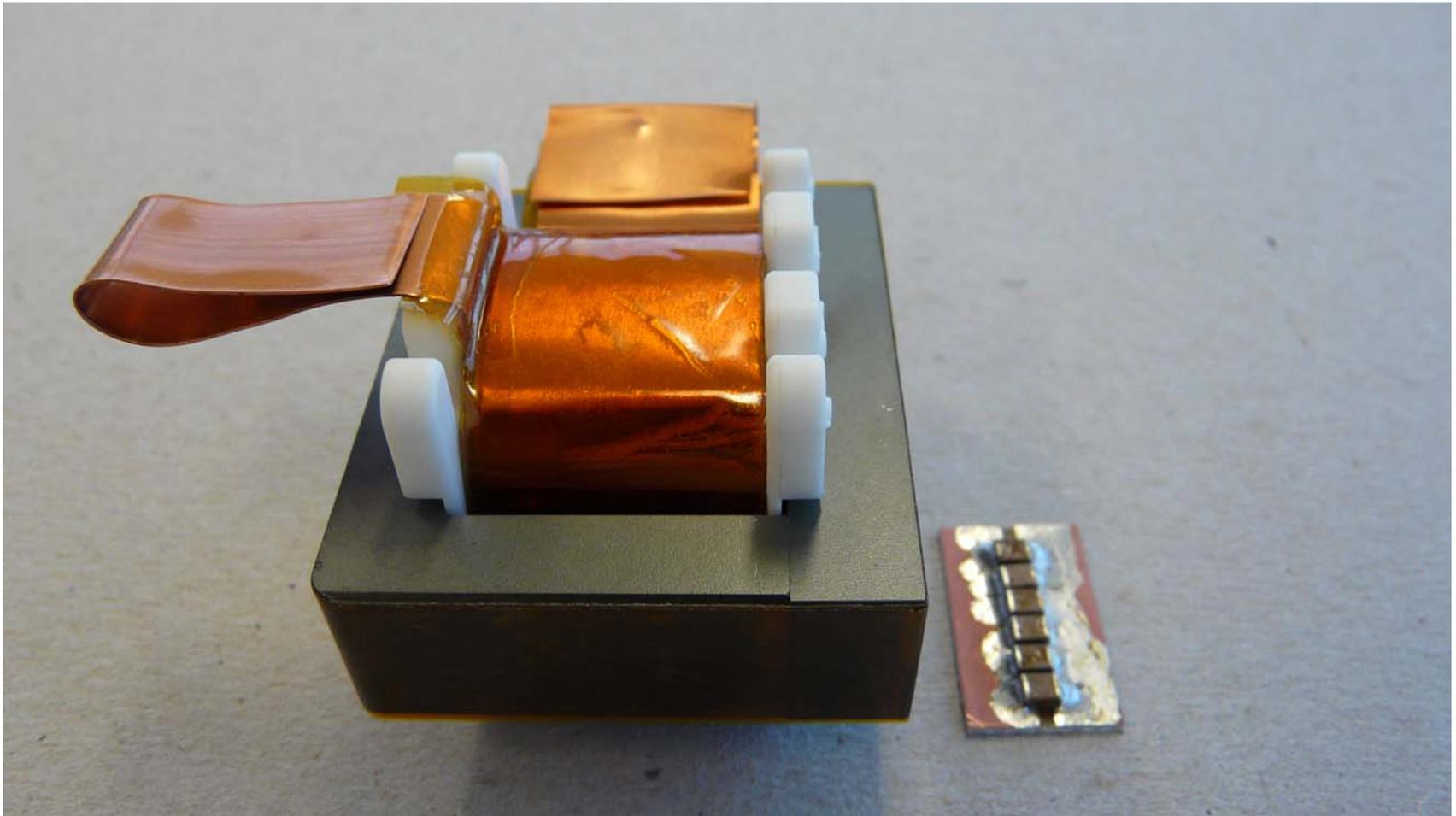

Inductive

Capacitive

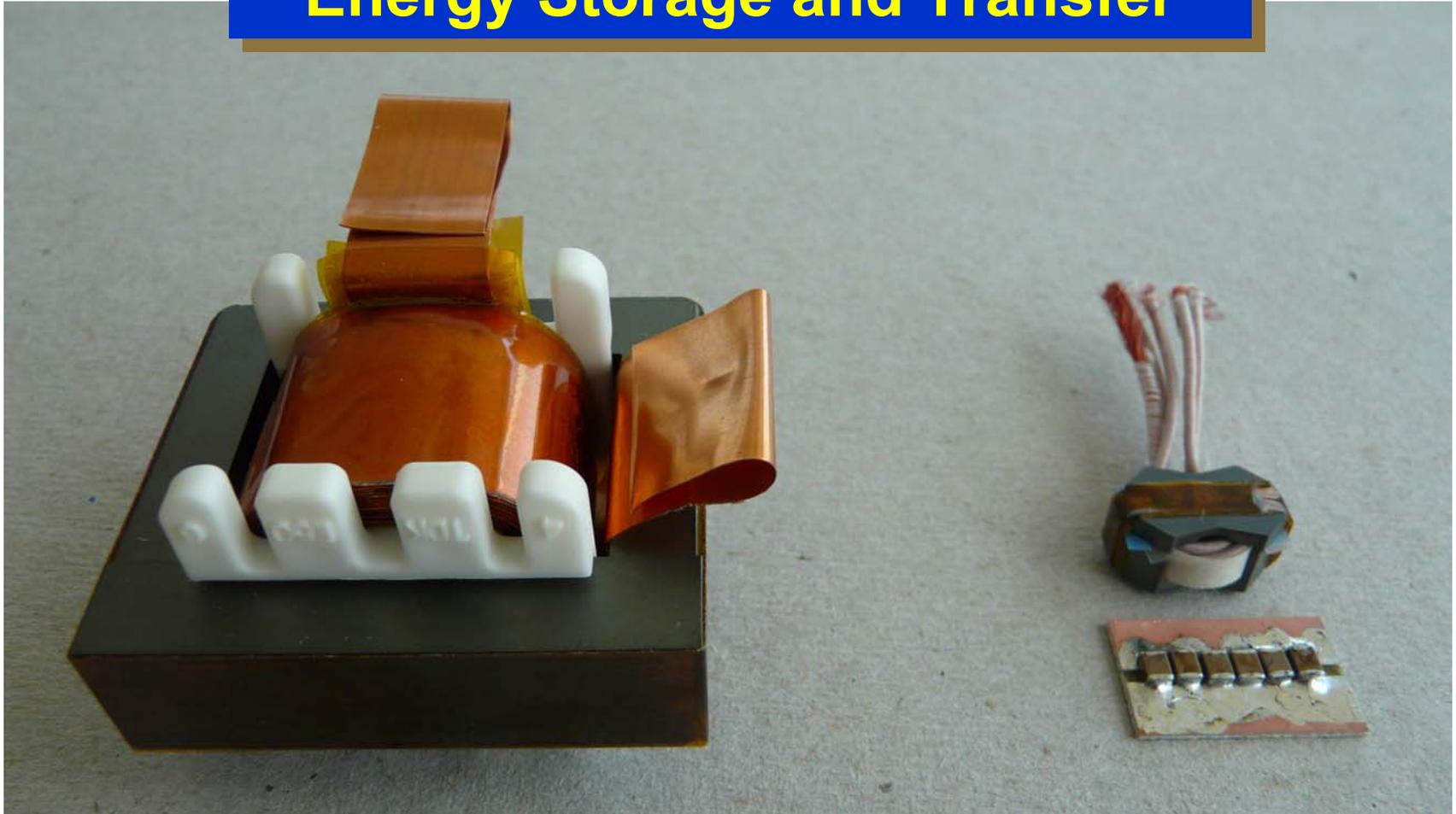
750W, 100V to 48V Converter Energy Storage and Transfer



Inductive Only
Buck



Resonant
Storageless

Isolated Storageless Converter*

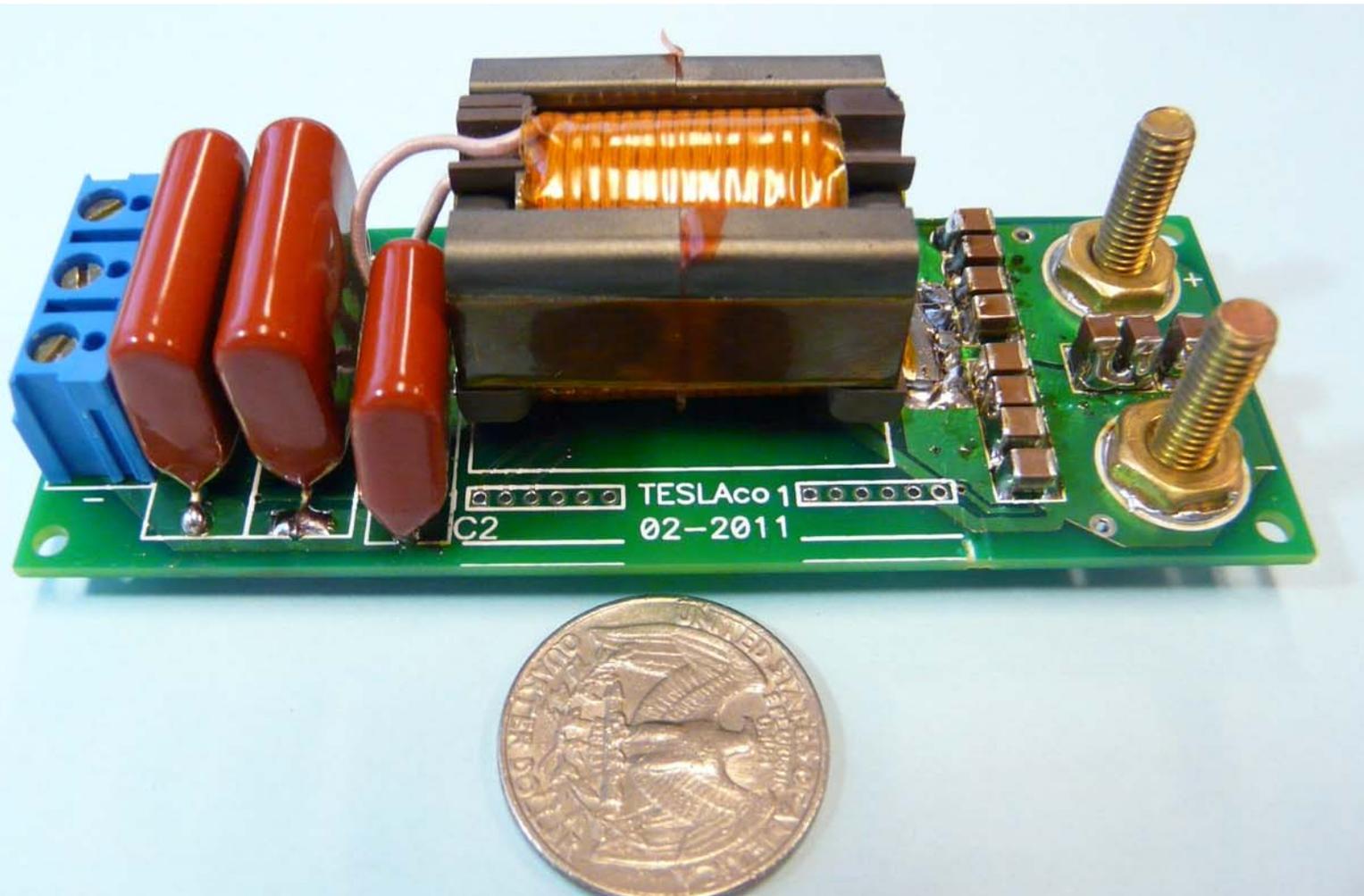


*US and foreign patents pending

Storageless Transformer Flux

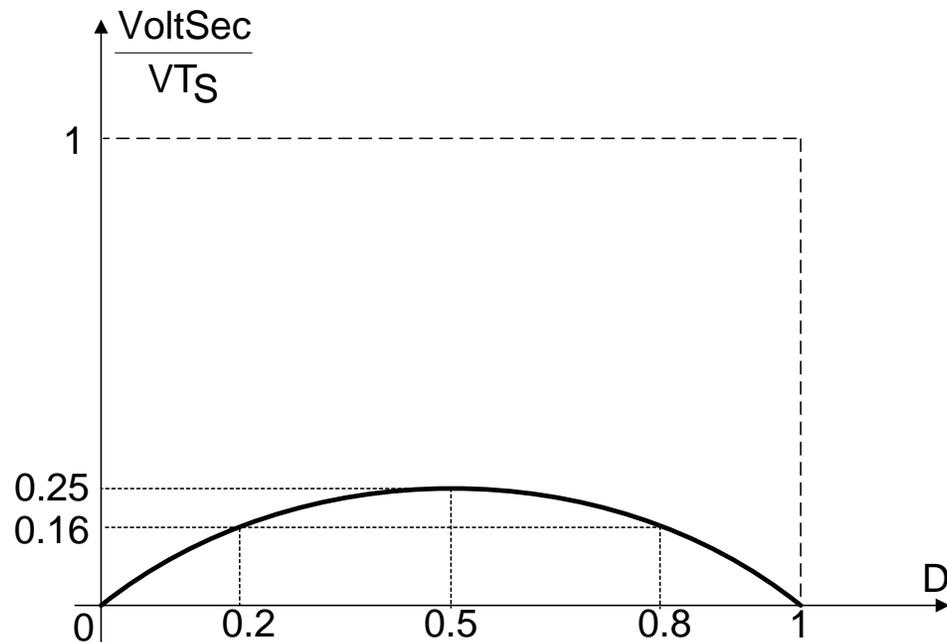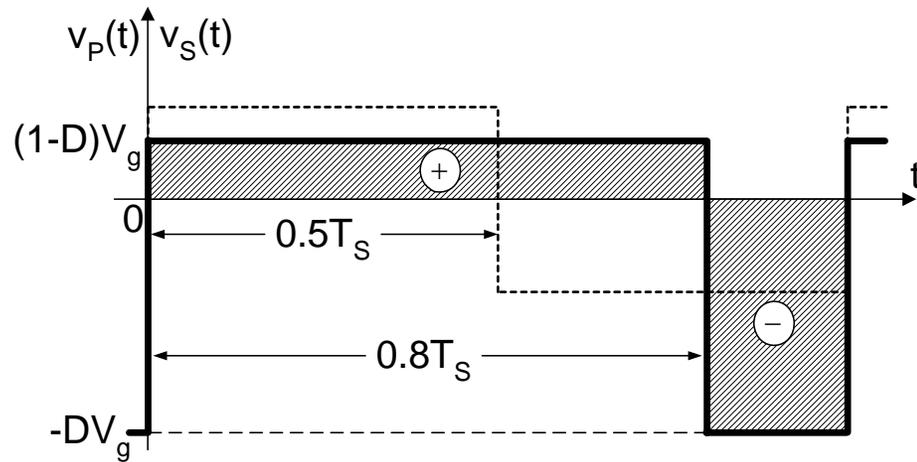


Efficiency of Isolated Storageless Converter

98.2% efficiency

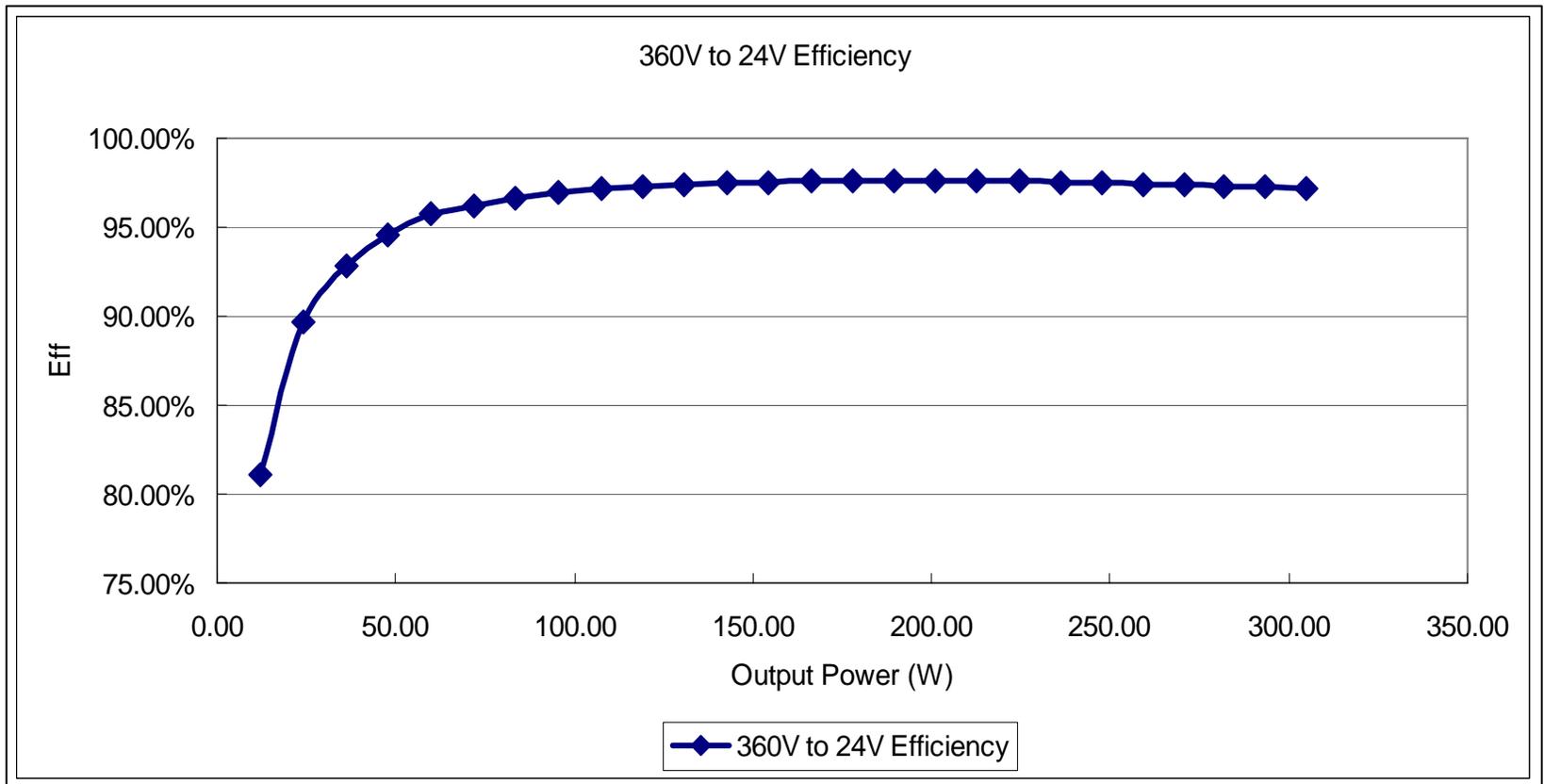

Losses of Isolated Storageless Converter

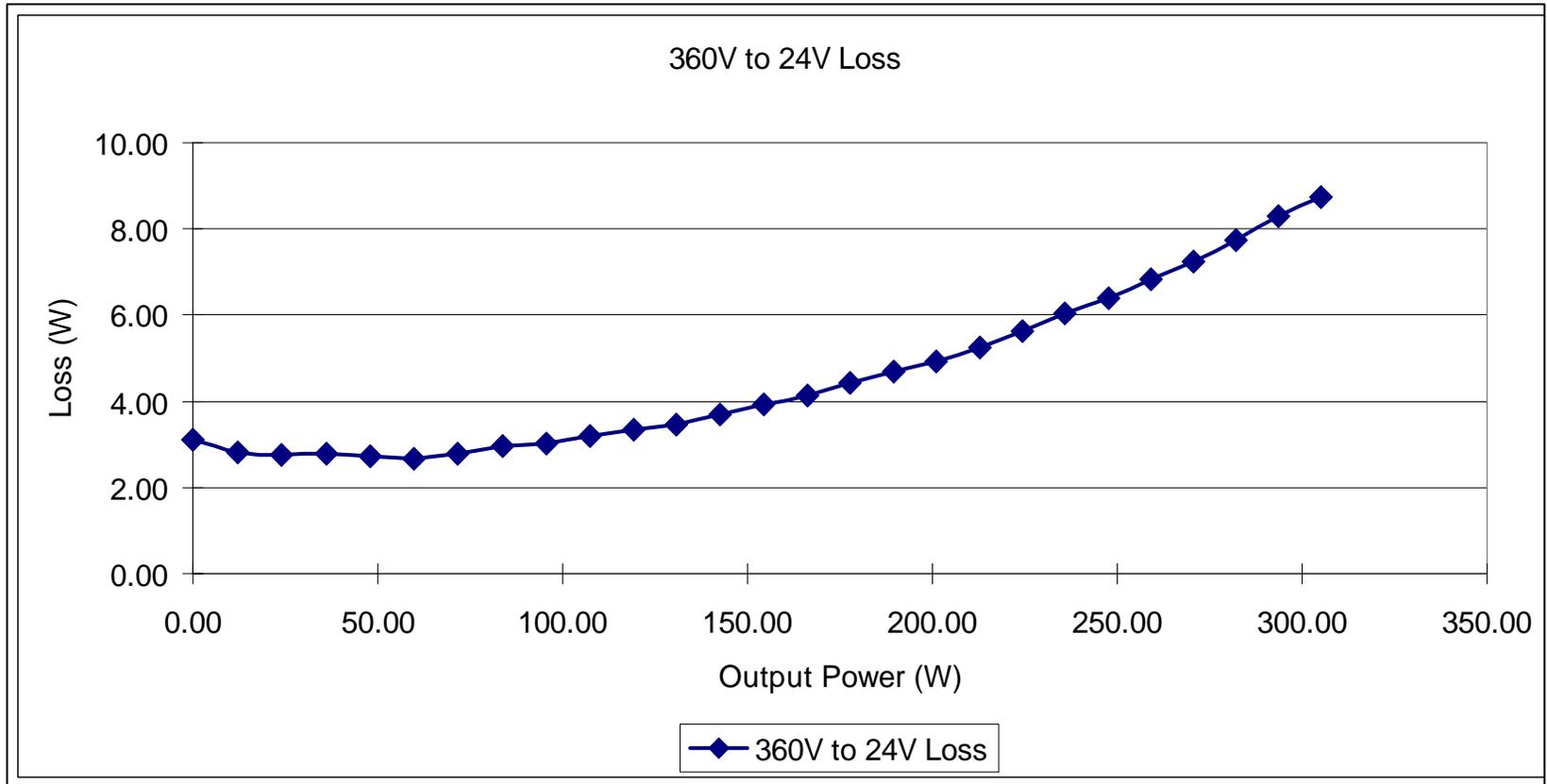

Storageless-switching Converters

1. DC-DC non-isolated converters with efficiency over 99% and 10 times reduction of size
2. DC-DC Isolated converters with efficiency over 98%, 4 times size reduction and minimum voltage stresses of the switches
3. Duty ratio control

Applications Summary

- Wide range of applications:
- Computer servers
- Battery chargers
- Desktop computers
- AC Adapters, projectors, etc.
- Solar photovoltaic conversion


Green Dream Power Technology™

Efficiency

98%

99%

97%

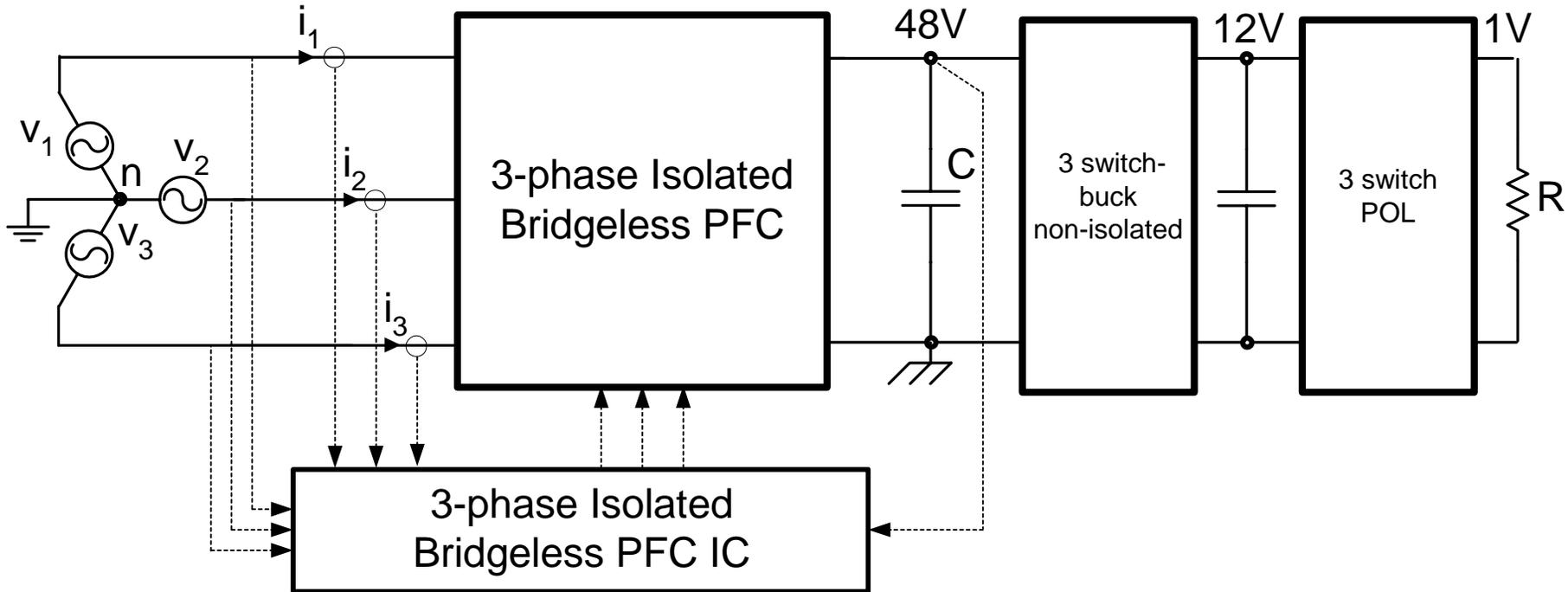

**Switching
method**

Hybrid

Storageless

POL



Appendix

Hybrid-Switching

Step-down Converter

48V to 1V nonisolated

Two-switch Buck Converter

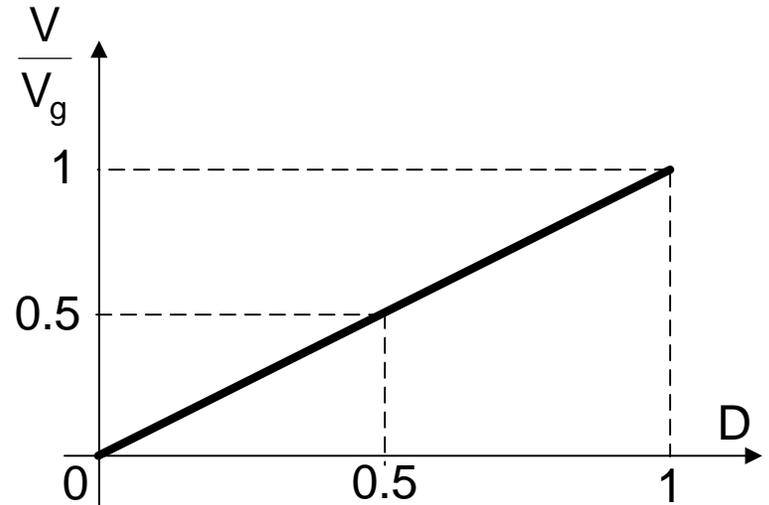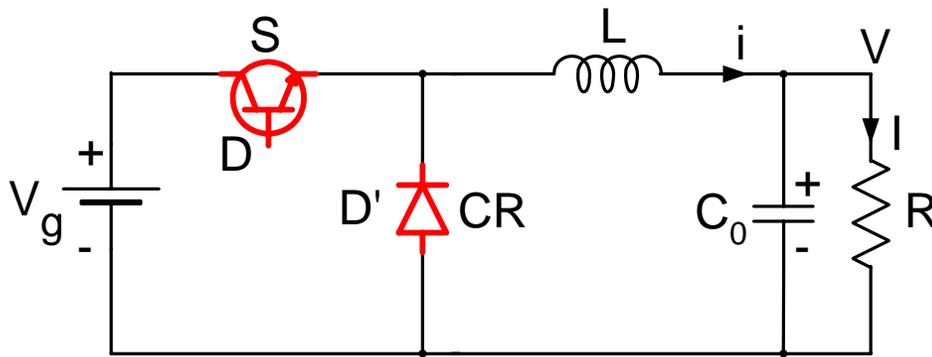

$V_g = 12V$


$V = 6V$ at $D = 0.5$

Switches 25V rating

Could Converter with More Switches be More Efficient and at Lower Cost?

Alternative to 2 Switch Buck Converter


New Converter with 3 Switches*

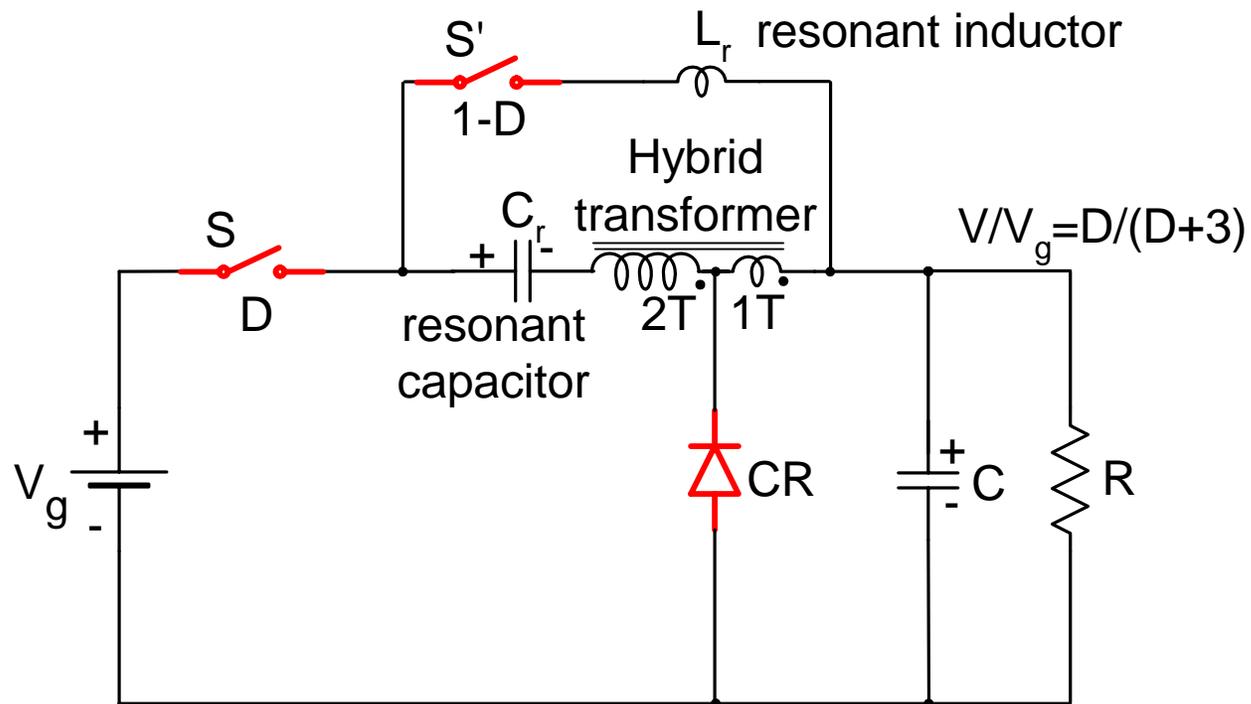

Three Switches: Two Transistors and Diode

*US Patent No. 7,915,874

Voltage Stress on Diode


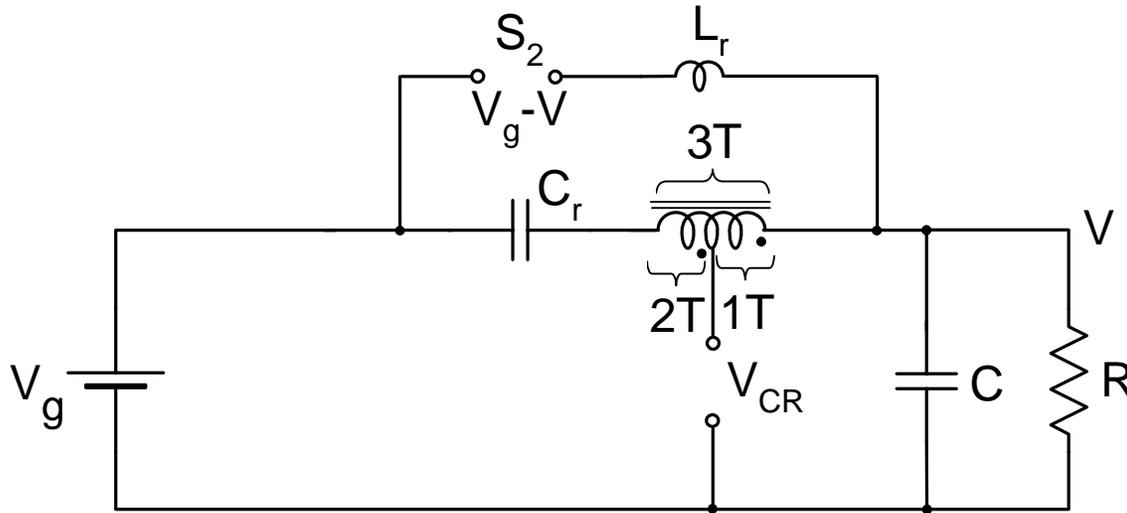


Diode Blocking Voltage $V_{CR} < V_g/3 = 4V$

Diode 5V rating


Silicon needed 20% or less than for Synchronous Buck Converter

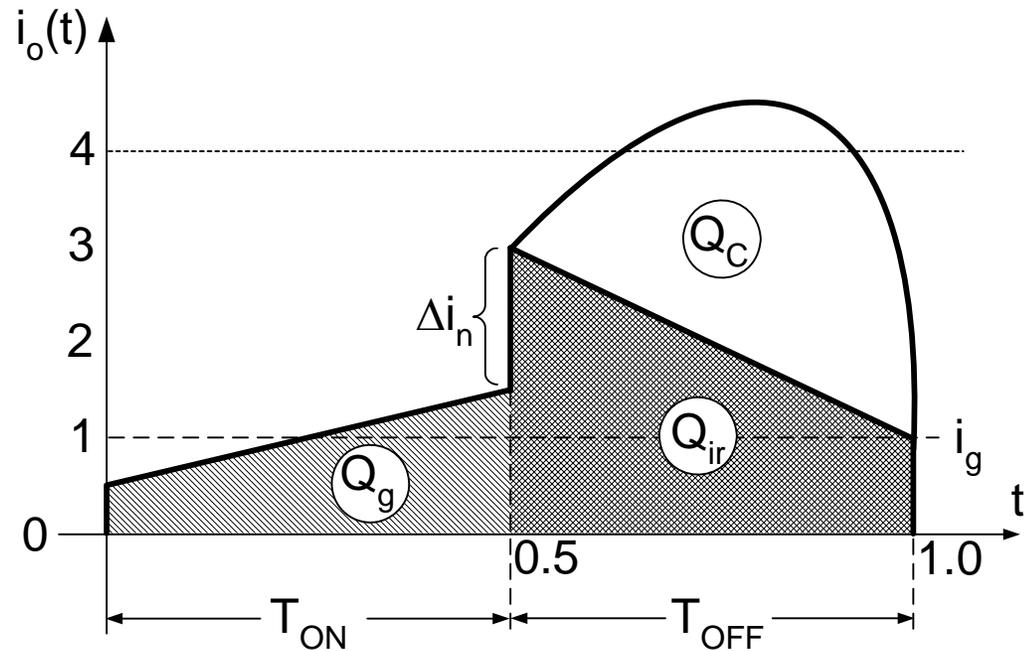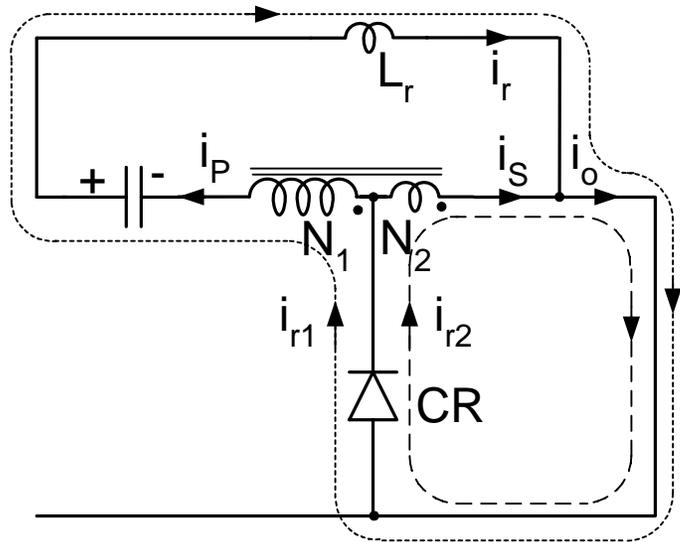Hybrid Transformer and Its Current Multiplication



$I_r = I_L / 5$ $I_L = 30A$ $I_{r(cap)} = 6A$ (2 chip capacitors in parallel)

Large Step-down at D=0.5

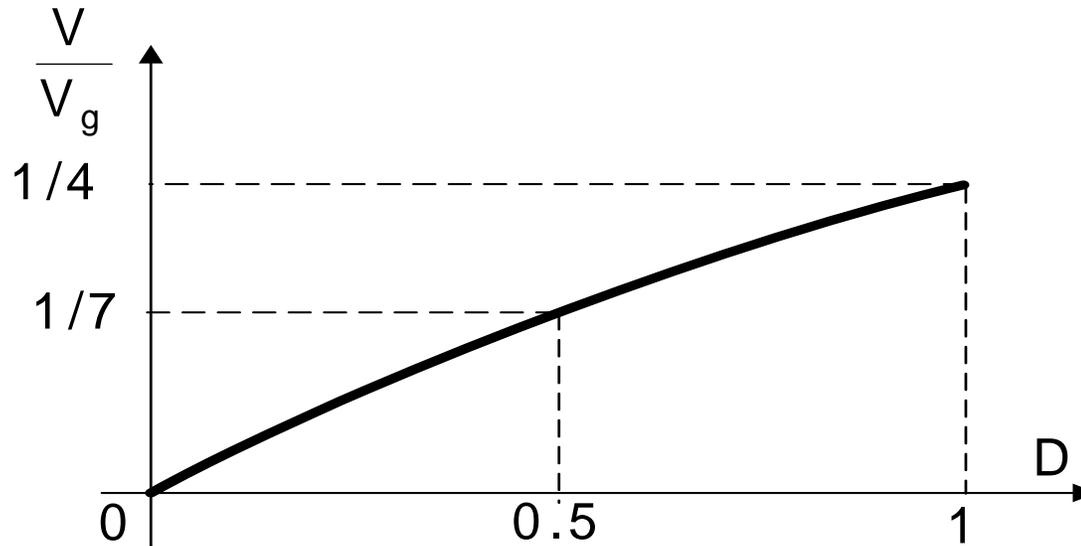

$$V/V_g = D/(D+3) = 1/7$$

$$V_g = 12V$$

$$V = 1.7V \text{ for } D = 0.5$$