



Figure 1

A switching voltage regulator forms a good basis for a constant-current source.