

# DC-DC Step-up Converter for 6 - 9 - 12 V from 4-cell NiMH Battery

Open Hardware Project Design Decisions and Background

## 1. Input Filter for Boost Converter

### Filter Inductor Selection

We basically take the same 4.7 uH/2A shielded model we also use for the DC/DC boost converter (see below):

- <http://www.mouser.de/ProductDetail/EPCOS-TDK/B82472G6472M000/>  
(<http://www.mouser.de/ProductDetail/EPCOS-TDK/B82472G6472M000/>)

We follow the recommendations from <http://www.ti.com/lit/an/snva489c/snva489c.pdf>  
(<http://www.ti.com/lit/an/snva489c/snva489c.pdf>).

So the parameters of this inductor are given.

### Filter Capacitor Selection

1. Make sure resonance frequency is at least one decade below switching frequency

$$C_{fa} = \frac{C_{IN}}{C_{IN}L_f(2\pi f_S/10)^2 - 1}$$

2. Ensure proper attenuation of the EMI filter

$$C_{fb} = \frac{1}{L_f} \left( \frac{10^{Att_{dB}/40}}{2\pi f_S} \right)^2$$

In [11]:

```
import math

C_in = 10 * 10**-6 # 10 uF
L = 4.7 * 10**-6 # 4.7 uH
f_S = 1.3 * 10**6 # 1.3 MHz
Attenuation = 90 # dB

C_fa = C_in / (C_in * L * (2 * math.pi * f_S/10)**2 -1)
C_fb = 1/L * ( 10**(Attenuation/40)/(2 * math.pi * f_S) )**2

C_f = max(C_fa, C_fb )
print 'C_f >= %.3f uF' % (C_f * 10**6)
```

C\_f >= 31.890 uF

## Damping Capacitor Selection

$$C_d \geq 4 \times C_{IN}$$

ESR:

$$ESR_d \approx \sqrt{L_f/C_{IN}}$$

In [36]:

```
C_d = 4 * C_in
ESR_d = math.sqrt(L/C_in)
print '%.3f uF' % (C_d * 10**6)
print '%.3f ESR' % ESR_d
```

40.000 uF

0.686 ESD

## 2. Output Filter for Boost Converter

According to <http://www.aimtec.com/site/Aimtec/files/documents/ApplicationNotes/a016e%20-%20reduction%20of%20output%20ripple%20&%20noise.pdf>

(<http://www.aimtec.com/site/Aimtec/files/documents/ApplicationNotes/a016e%20-%20reduction%20of%20output%20ripple%20&%20noise.pdf>),

Minimum capacitor value:

$$(V_{max-ripple}/V_{converter-ripple}) = \frac{XC}{XC + XL}$$

with

$$XC = \frac{1}{2 * \pi * f * C}$$

$$XL = 2 * \pi * f * L$$

$f$  = Switching frequency of converter

$C$  = Filter capacitance

$L$  = Filter Inductance

In [13]:

```
V_max_ripple = 5 * 10**-3 # 10mV, just an estimate
V_converter_ripple = 800 * 10**-3 # 600mV, just an estimate
f = 1.3 * 10**6
L = 4.7 * 10**-6

XL = 2 * math.pi * f * L

# XC/(XC + XL) = V_max_ripple / V_converter_ripple
# XC = (V_max_ripple * (XC + XL)) / V_converter_ripple
# XC * V_converter_ripple = V_max_ripple * XC + V_max_ripple * XL
# XC(V_converter_ripple - V_max_ripple) = V_max_ripple * XL
XC = V_max_ripple * XL / (V_converter_ripple - V_max_ripple)

# XC = 1 / (2 * math.pi * f * C)
# C * XC = 1 / (2 * math.pi * f)
C = 1 / (2 * math.pi * f * XC)

print 'XC = %.3f Ohm' % XC
print 'XL = %.3f Ohm' % XL
print 'C_min = %.3f uF' % (C * 10**6)
```

```
XC = 0.241 Ohm
XL = 38.390 Ohm
C_min = 0.507 uF
```

### 3. Boost Converter Components

#### Voltage Divider for Output Voltage Setting

See <http://www.mouser.com/ds/2/761/down-766913.pdf> (<http://www.mouser.com/ds/2/761/down-766913.pdf>)

$$R_1 = R_2 \left( \frac{V_{OUT}}{1.25V} - 1 \right)$$

In [20]:

```
V_out = 12
R2 = 50 * 10**3 # 50k

for v in [12, 9, 6]:
    R1 = R2*(v/1.25 -1)
    print 'R1 for %i V_out: %.2f kOhm' % (v, R1/10**3)
```

```
R1 for 12 V_out: 430.00 kOhm
R1 for 9 V_out: 310.00 kOhm
R1 for 6 V_out: 190.00 kOhm
```

However, we want to achieve the resistance for the lower output voltage by adding additional resistors parallel to R1.

So

$$R_1 = \frac{R_{1a} * R_{1b}}{R_{1a} + R_{1b}}$$

where

$$R_{1a} = \text{Resistor for } V_{out} = 12V \Rightarrow 430k$$

So rearranged to compute R1b:

$$R_{1b} = \frac{R_1 * R_{1a}}{R_{1a} - R_1}$$

In [21]:

```
R1a = 430 * 10**3
for R1 in [310*10**3, 190*10**3]:
    R1b = (R1 * R1a)/(R1a - R1)
    print 'For R1 = %.2f kOhm: R1a = %.2f kOhm, R1b = %.2f kOhm' % (R1/10**3, R1a/10**3, R1b/10**3)
```

For R1 = 310.00 kOhm: R1a = 430.00 kOhm, R1b = 1110.00 kOhm

For R1 = 190.00 kOhm: R1a = 430.00 kOhm, R1b = 340.00 kOhm

So we choose

- R1b = 1 MOhm for 9 V

and

- R1b = 330 kOhm for 6 V.

## Inductor Selection

See p. 10 of the SC4503 datasheet, <http://www.mouser.com/ds/2/761/down-766913.pdf>  
(<http://www.mouser.com/ds/2/761/down-766913.pdf>)

The inductor should be chosen such that the ripple current  $\Delta I$  will be between 0.35A and 0.6A.

$$L = \frac{V_{IN}}{f \Delta I_L} \left( 1 - \frac{V_{IN}}{V_{OUT} + V_D} \right)$$
$$\Delta I_L = \frac{V_{IN}}{fL} \left( 1 - \frac{V_{IN}}{V_{OUT} + V_D} \right)$$

We want to use the same 4.7 uH/2A shielded model we also use for the filters:

- <http://www.mouser.de/ProductDetail/EPCOS-TDK/B82472G6472M000/>  
(<http://www.mouser.de/ProductDetail/EPCOS-TDK/B82472G6472M000/>)

In the following, we compute whether this is a good choice.

In [10]:

```
delta_I_L_min = 0.35 # A
delta_I_L_max = 0.6 # A
f = 1.3 * 10**6 # 1.3 MHz
V_in_min = 4.0
V_in_nominal = 4.8
V_in_max = 6
V_out = 12
# Diode: http://cdn-reichelt.de/documents/datenblatt/A400/SS12L\_SS13L\_SS14L-TSC.pdf
V_D = 0.55 # V
L = 4.7 * 10**-6 # 4.7 uH

def delta_I_L(V_in, f, L, V_out, V_D):
    i = (V_in / (f * L)) * (1 - (V_in/(V_out + V_D)))
    return i

for v_out in [12, 9, 6]:
    print 'V_out = %i V' %v_out
    for v in [V_in_max, V_in_nominal, V_in_min]:
        print '\tV_in = %.1f V, delta_I = %.3f A' % (v, delta_I_L(v, f, L,
v_out, V_D))
```

```
V_out = 12 V
    V_in = 6.0 V, delta_I = 0.513 A
    V_in = 4.8 V, delta_I = 0.485 A
    V_in = 4.0 V, delta_I = 0.446 A
V_out = 9 V
    V_in = 6.0 V, delta_I = 0.365 A
    V_in = 4.8 V, delta_I = 0.391 A
    V_in = 4.0 V, delta_I = 0.380 A
V_out = 6 V
    V_in = 6.0 V, delta_I = 0.082 A
    V_in = 4.8 V, delta_I = 0.210 A
    V_in = 4.0 V, delta_I = 0.255 A
```

In [ ]: