

$$\underline{Z}_1 = R_1 + j \cdot \omega \cdot L$$

$$\varphi_1 = \arg(\underline{Z}_1) = \tan^{-1}\left(\frac{\omega \cdot L}{R_1}\right)$$

$$\underbrace{\tan(\varphi_1)}_{q_1} = \underbrace{\tan(2 \cdot \varphi_2)}_{\frac{2 \cdot \tan(\varphi_2)}{1 - \underbrace{\tan^2(\varphi_2)}_{q_2^2}}}$$

$$\rightarrow q_2 = \sqrt{\frac{1}{q_1^2} + 1 - \frac{1}{q_1}}$$

$$\underline{Z}_2 = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{j \cdot \omega \cdot L}}$$

$$\varphi_2 = \arg(Z_2) = \tan^{-1}\left(\frac{1}{\underbrace{\frac{\omega \cdot L}{R_2} + \frac{R_1}{R_2} \cdot \left(\frac{R_2}{\omega \cdot L} + \frac{\omega \cdot L}{R_2}\right)}_{q_2}}\right)$$

$$\rightarrow R_2 = \frac{\frac{1}{2} \cdot \omega \cdot L + \sqrt{\left(\frac{1}{2} \cdot \omega \cdot L\right)^2 + R_1 \cdot \left(\frac{\omega \cdot L}{q_2} - R_1\right)}}{\frac{1}{q_2} - \frac{R_1}{\omega \cdot L}}$$