

$$U = 12V$$

$$I = 600mA = 0,6A$$

$R_{12345} = \text{alle gleich groß}$

R_1
ges: Einzelwiderstände

R_{ges}

U_1, U_3, U_5

