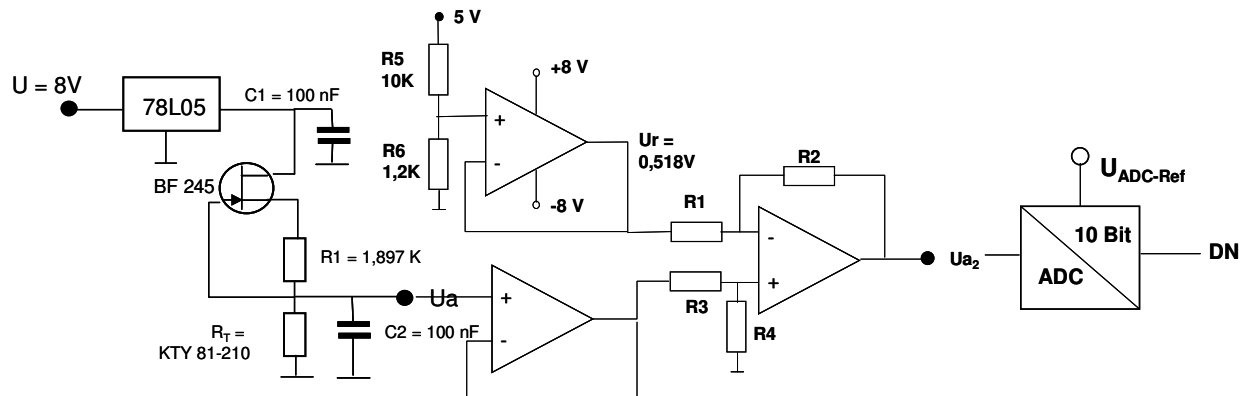


Temperaturmess-Schaltung



Gemessene Werte		Approximation	
Ua (V)	T (C)	X ²	Fehler (C)
1,579	-0,7	-0,7	-0,01
1,744	11,0	10,9	0,08
1,800	14,9	15,0	-0,05
1,860	19,2	19,3	-0,13
1,904	22,7	22,6	0,12
2,129	39,6	39,6	-0,04
2,154	41,6	41,6	0,02
2,172	43,0	43,0	0,01

Kalibrierung

$$T [C] = T [C] = 7,7285 * ((U_{a2}-b)/a)^2 + 44,667 * (U_{a2}-b)/a - 90,488$$

$$U_{a2} = U_{ADC-Ref} * DN / 1024$$

$$T [C] = 7,7285 * ((U_{ADC-Ref} * DN / 1024-b)/a)^2 + 44,667 * (U_{ADC-Ref} * DN / 1024-b)/a - 90,488$$

U _{ADC-Ref} =	5,0	Volt
DN =	600	0 - 1023
a =	3,542	
b =	-3,587	
U _{a2} =	2,930	Volt
U _a =	1,840	Volt
Temp. =	17,9	C

mit $U_{a2} = a * U_a + b$


Gleichung Differenzverstärker:

$$U_a = -U_r \cdot R_2/R_1 + U_e \cdot R_4/(R_3+R_4) \cdot (1+R_2/R_1)$$

$$U_a = U_r \cdot x + U_e \cdot y$$

Eingabewerte:

$U_{e1} = 1,100$
 $U_{e2} = 2,300$
 $U_{a1} = 0,500$
 $U_{a2} = 4,500$
 $U_r = 0,518$
 $R_1 = 10.050$
 $R_3 = 10.050$

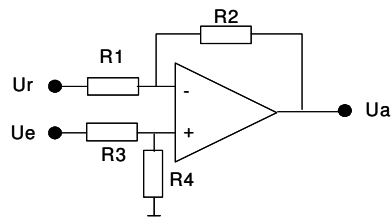**Zwischenwerte:**

$x = -6,113$
 $y = 3,333$

$$x = (U_{a2} - U_{e2} \cdot y) / U_r$$

$$y = (U_{a1} - U_{a2}) / (U_{e1} - U_{e2})$$

Soll-Widerstände:

$R_2 = 61.438$
 $R_4 = 8.863$

$$k = y / (1 + R_2/R_1)$$

$$R_2 = -x \cdot R_1$$

$$R_4 = R_3 \cdot k / (1-k)$$

Einsetzen der R Normwerte:

$R_2 = 69.600$
 $R_4 = 8.120$

Mit den Normwerten gilt:

$U_{a1} = f(U_{e1}) = 0,309$
 $U_{a2} = f(U_{e2}) = 4,559$

Kalibrationsgleichung:

$$U_a = a \cdot U_e + b$$

$$U_e = (U_a - b) / a$$


$a = 3,542$
 $b = -3,587$

$$a = (U_{a1} - U_{a2}) / (U_{e1} - U_{e2})$$

$$b = U_{a2} - a \cdot U_{e2}$$

Gemessene Werte

U_e	U_a
1,236	0,812
1,328	1,128
1,452	1,555
1,581	2,000
1,631	2,171
1,716	2,464
1,873	3,003
1,965	3,321
2,087	3,740
2,151	3,970

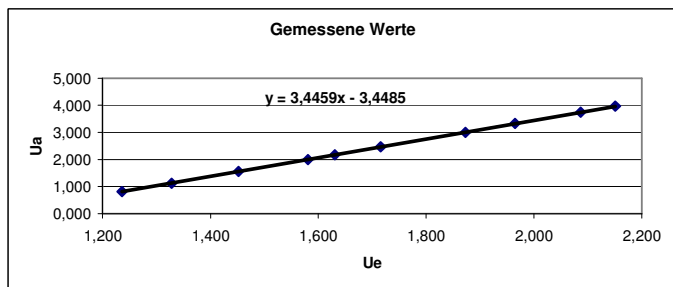**Kalibration mit $U_e = 0,2902 \cdot U_a + 1,0008$**

U_a	U_e	Fehler
0,812	1,236	0,000
1,128	1,328	0,000
1,555	1,452	0,000
2,000	1,581	0,000
2,171	1,631	0,000
2,464	1,716	0,000
3,003	1,873	-0,001
3,321	1,965	0,000
3,740	2,087	-0,001
3,970	2,151	0,002

