

Basic LC VCOs


Behzad Razavi

**Electrical Engineering Department
University of California, Los Angeles**

Outline






- **Operation of Oscillators**
- **One-Port View**
- **Cross-Coupled Oscillator**
- **VCO Techniques**
- **Discrete Tuning**

Voltage-Controlled Oscillators

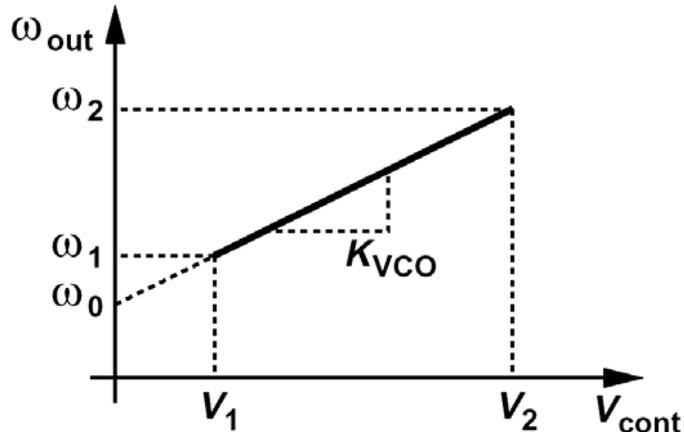


- Center Frequency
- Tuning Range:
 - Band of Interest
 - PVT Variations
- Gain (Sensitivity)
$$K_{VCO} \geq \frac{\omega_2 - \omega_1}{V_2 - V_1}$$
- Supply Rejection
- Tuning Linearity
- Intrinsic Jitter
- Output Amplitude


Feedback Oscillator

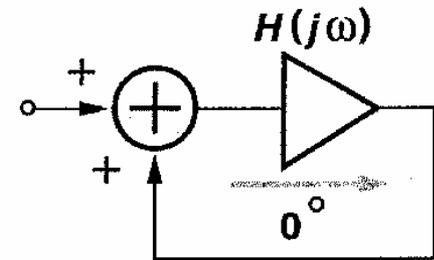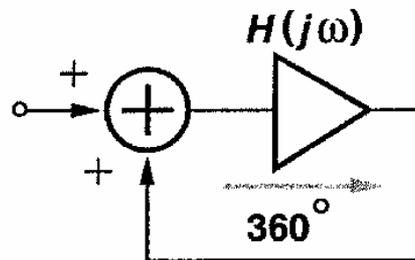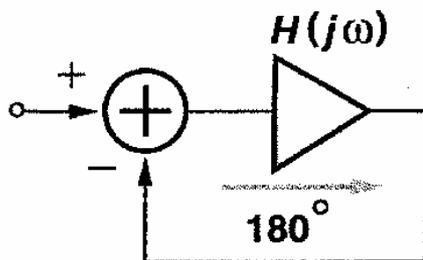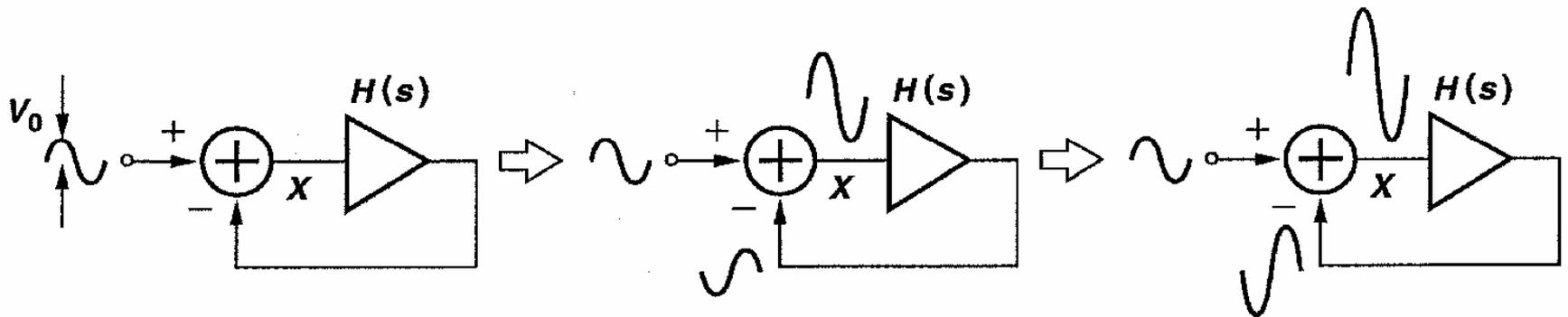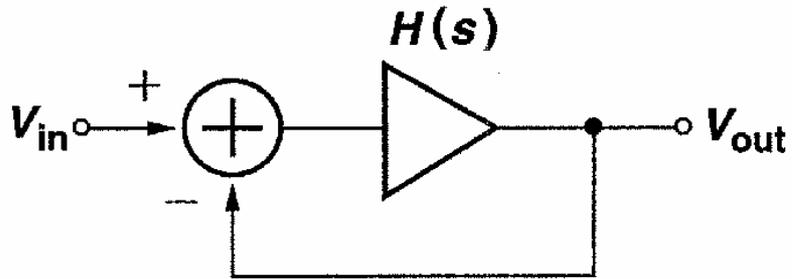

One-Port View

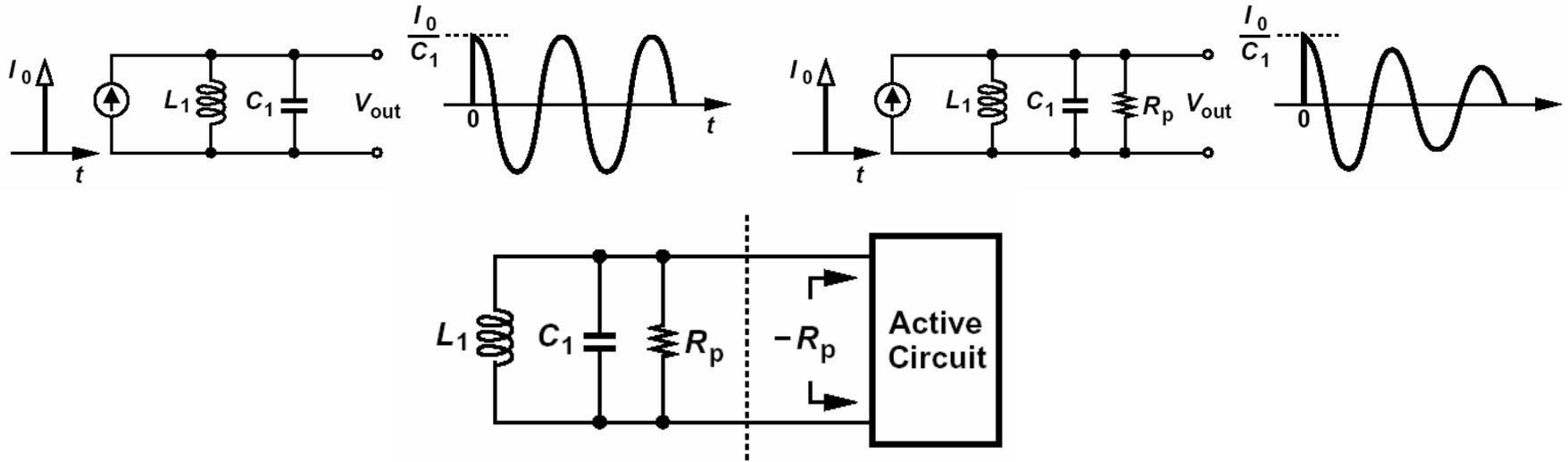


- **Example of negative resistance:**

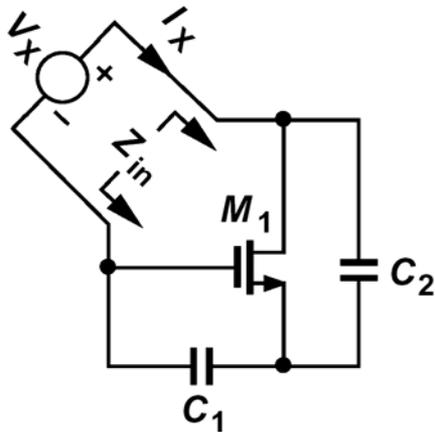


$$\frac{V_X}{I_X}(j\omega) = \frac{1}{jC_1\omega} + \frac{1}{jC_2\omega} - \frac{g_m}{C_1C_2\omega^2}$$

Use of Resonance in Oscillator Design


Series-Parallel Transformation

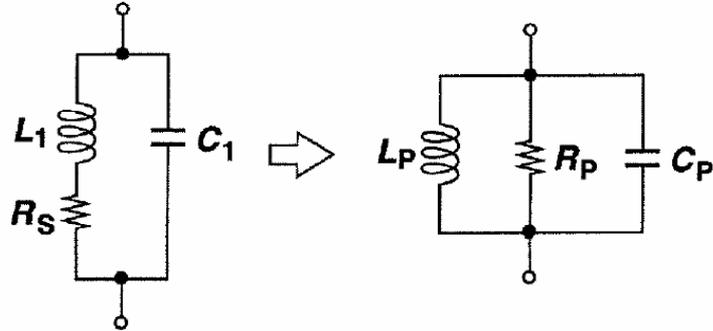


Tuned Amplifier

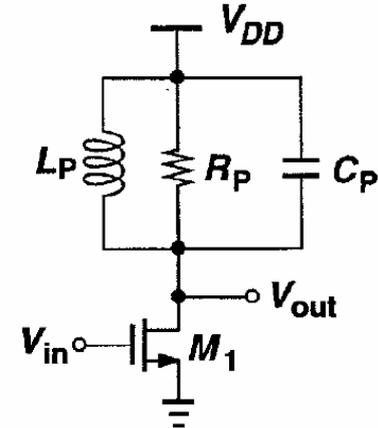





Tank Impedance Characteristics

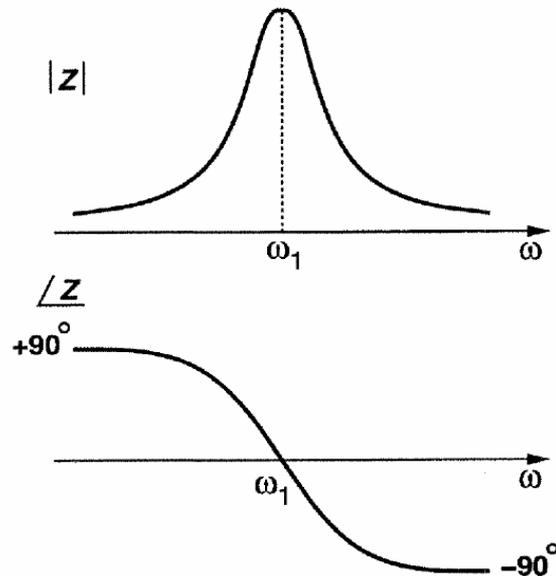

Voltage Swings

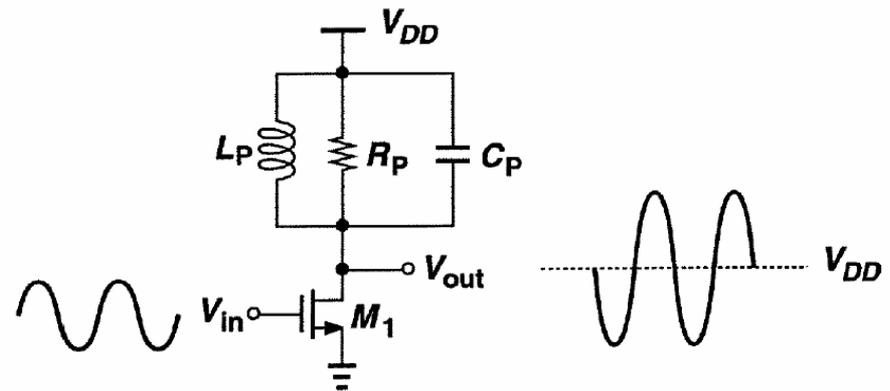


Cross-Coupled Oscillator

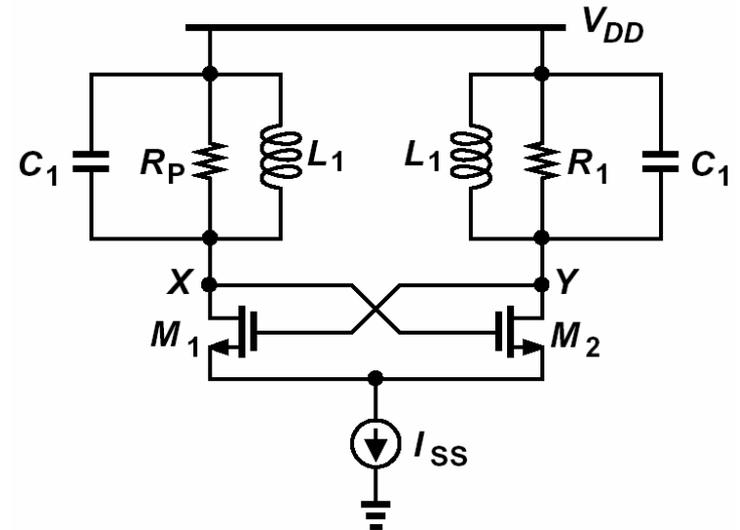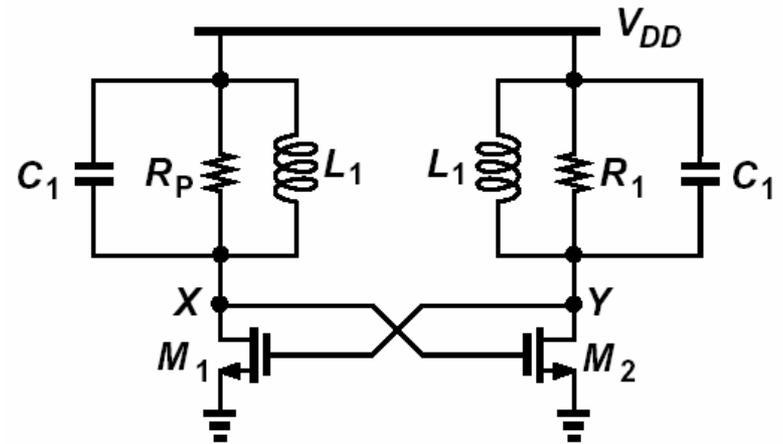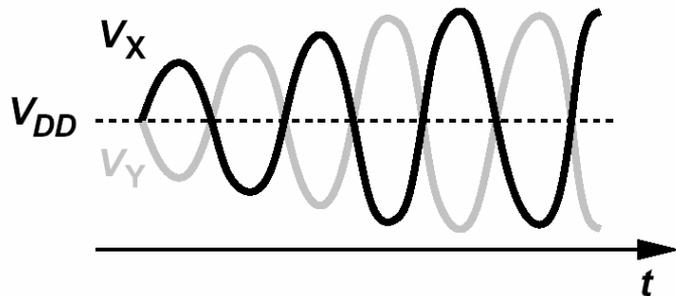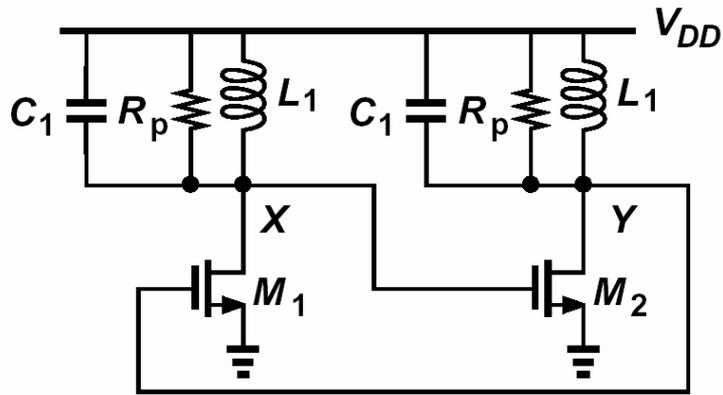



- Looks like a diff pair with positive feedback.
- Oscillation freq is given by:

Use of Symmetric Inductor

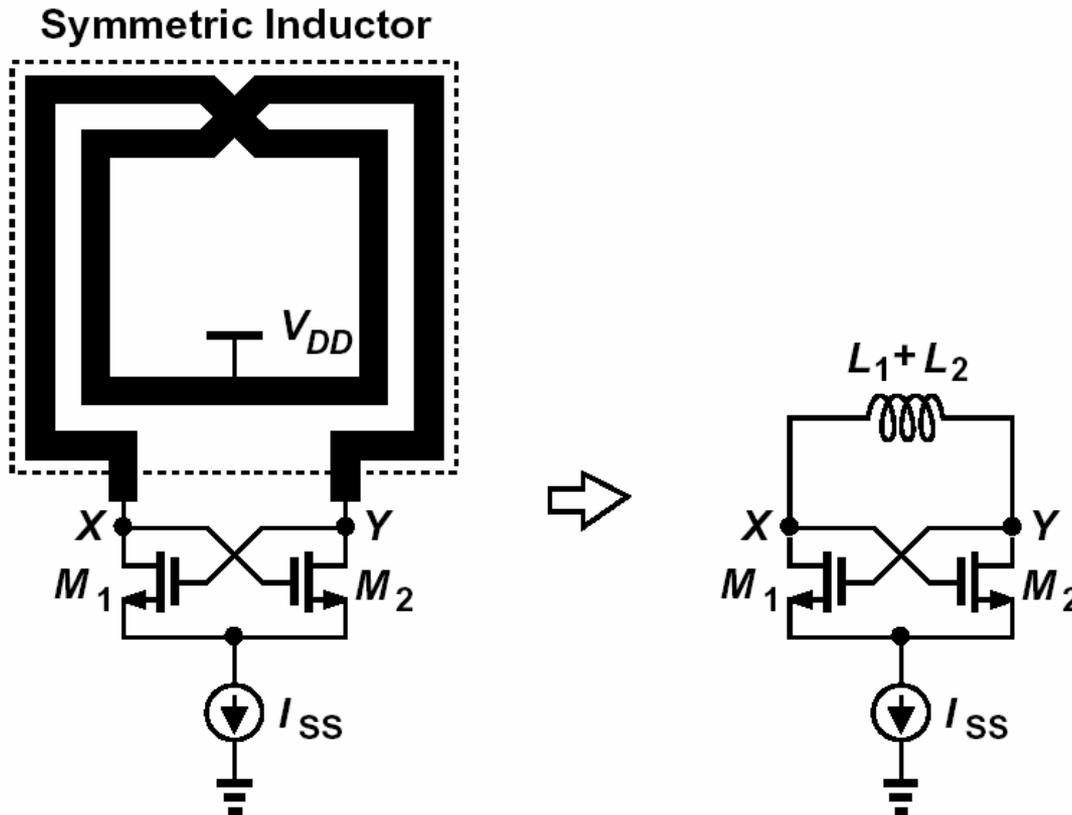

- Requires accurate model of inductor.
→ can't begin design without a useful inductor library.

Output Swing

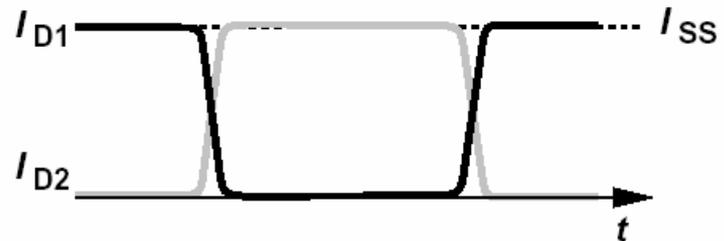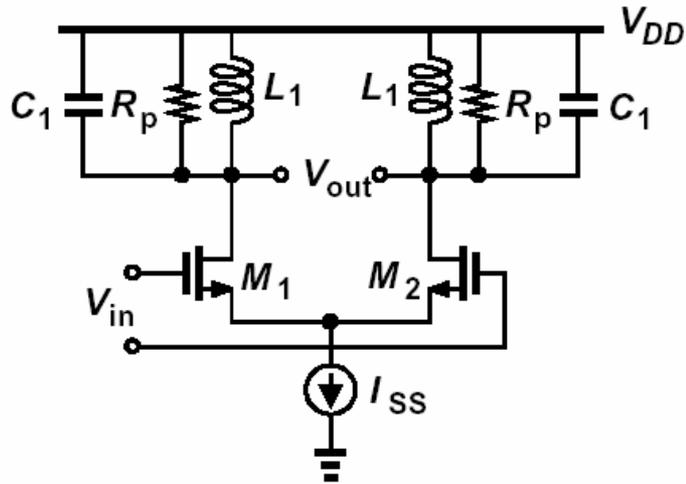


- Peak differential output voltage swing is given by:

$$V_{out,P} = \frac{4}{\pi} I_{SS} R_P$$

- How much is the output CM level?

Supply Sensitivity

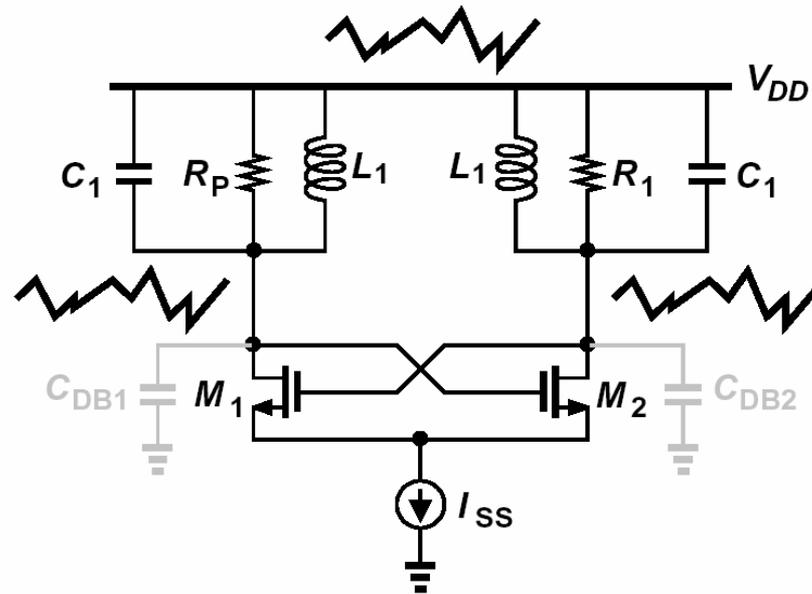




- **Voltage-dependent C_{DB} results in a finite K_{VCO} from V_{DD} to output frequency:**

$$\omega_{osc} = \frac{1}{\sqrt{L_1(C_1 + C_{DB})}} \quad C_{DB} = \frac{C_{DB0}}{\left(1 + \frac{V_{DD}}{\phi_B}\right)^m}$$

$$K_{VCO} = \frac{\partial \omega_{out}}{\partial V_{DD}} = \frac{\partial \omega_{osc}}{\partial C_{DB}} \cdot \frac{\partial C_{DB}}{\partial V_{DD}}$$



One-Port View

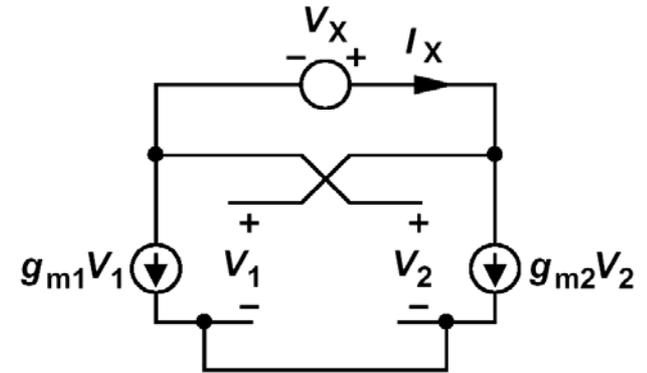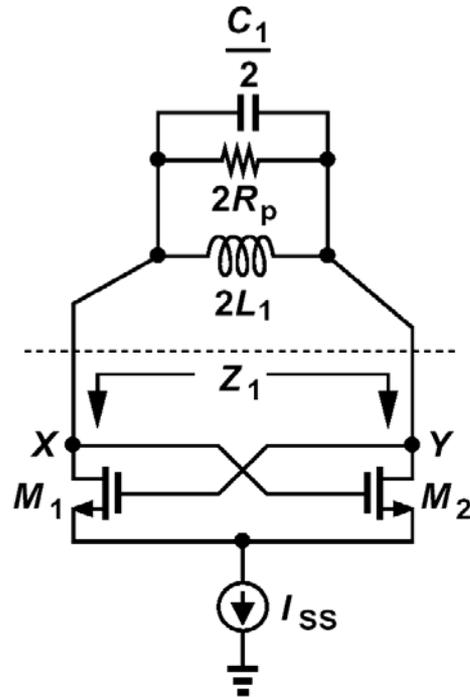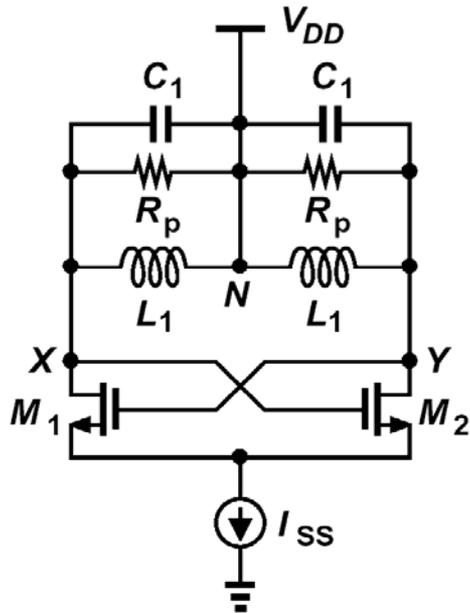


$$\frac{V_X}{I_X} = -\frac{2}{g_m}$$


$$g_m R_P \geq 1$$

How Do We Vary the Frequency?


- Use a MOS varactor.

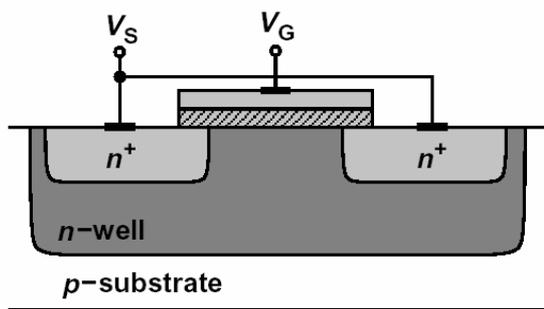


(a)

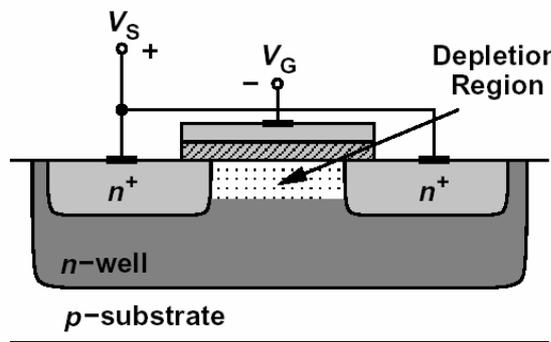


(b)

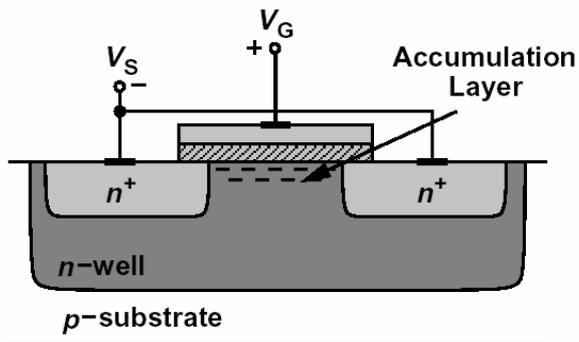



(c)

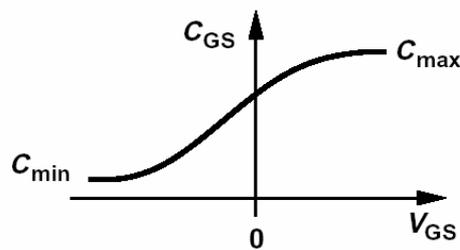

(d)

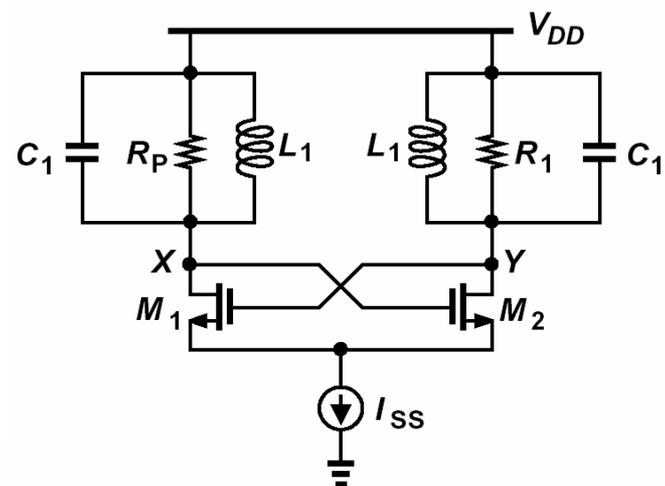




VCO Type I

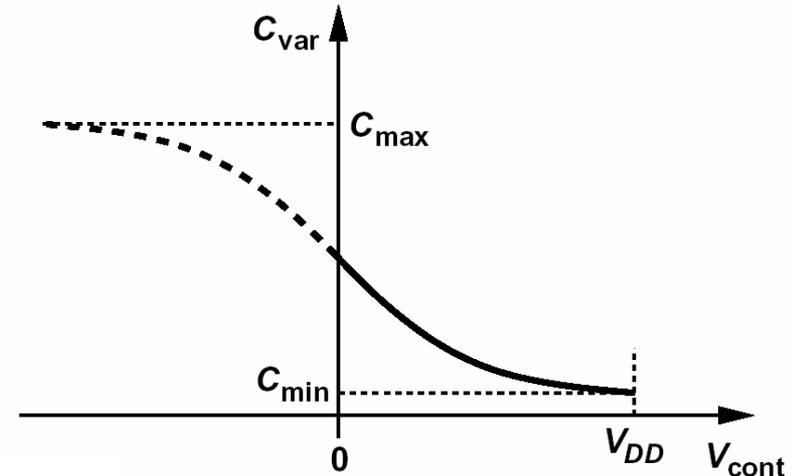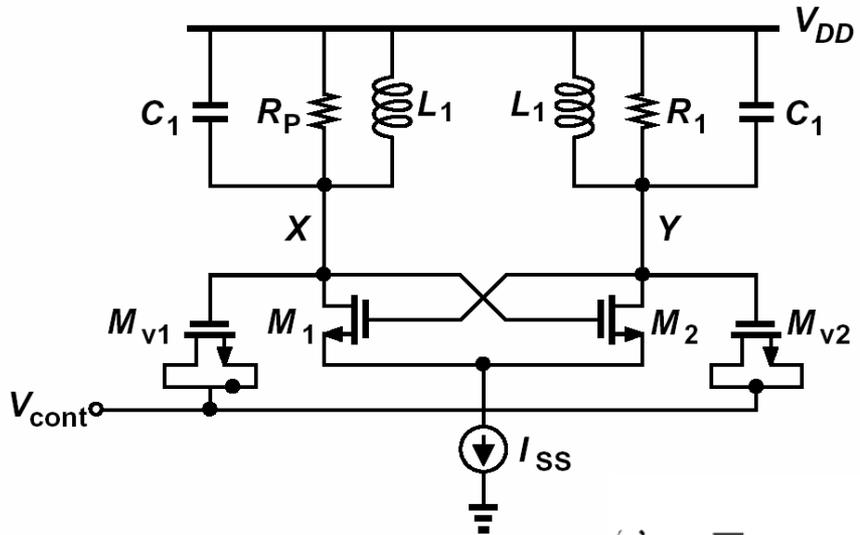

$$\omega_{osc} = \frac{1}{\sqrt{L_1(C_1 + C_{var})}}$$


- To maximize tuning range, we wish to minimize C1.
- But C1 is given by:
 - Caps of M1 and M2 (including 4Cgd)
 - Cap of L1
 - Input cap of next stage
- Tuning range may be limited.

VCO Type II

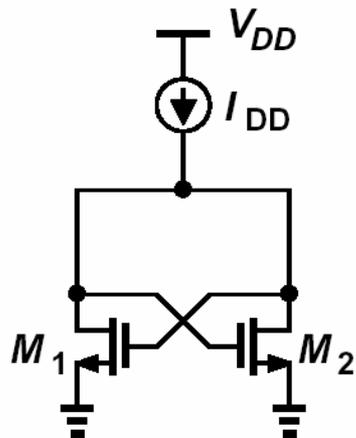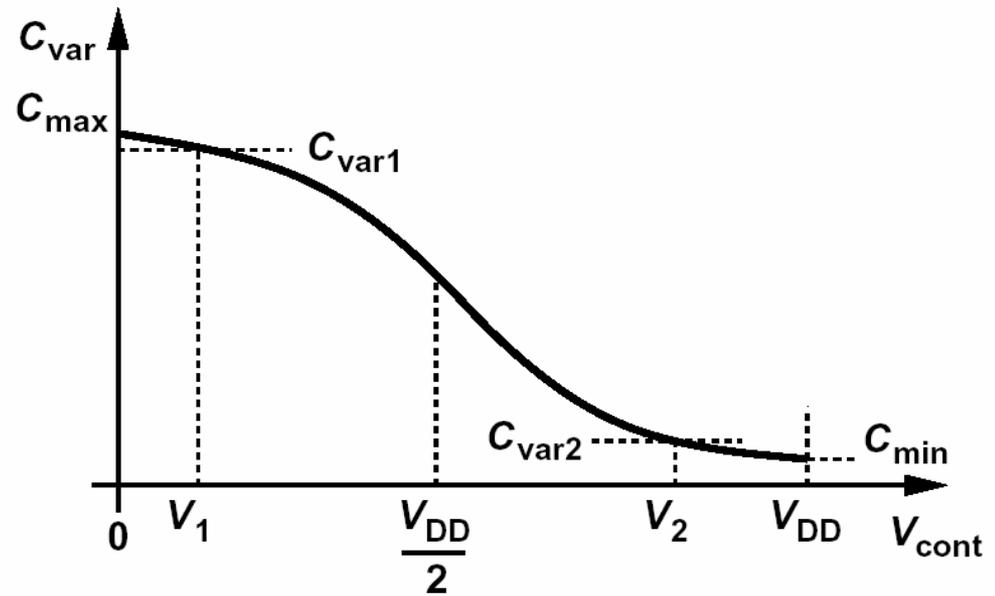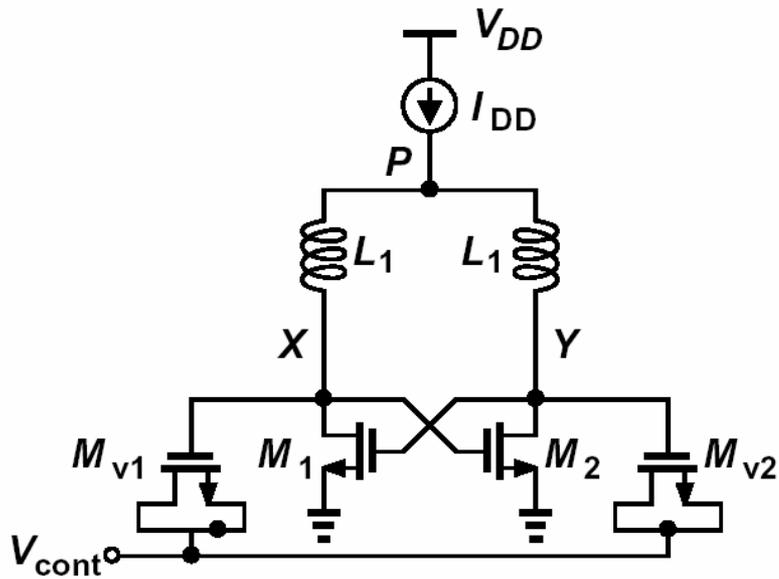

- Select device dimensions to set the output CM level to about $V_{DD}/2$.

Varactor Modulation by I_{DD}


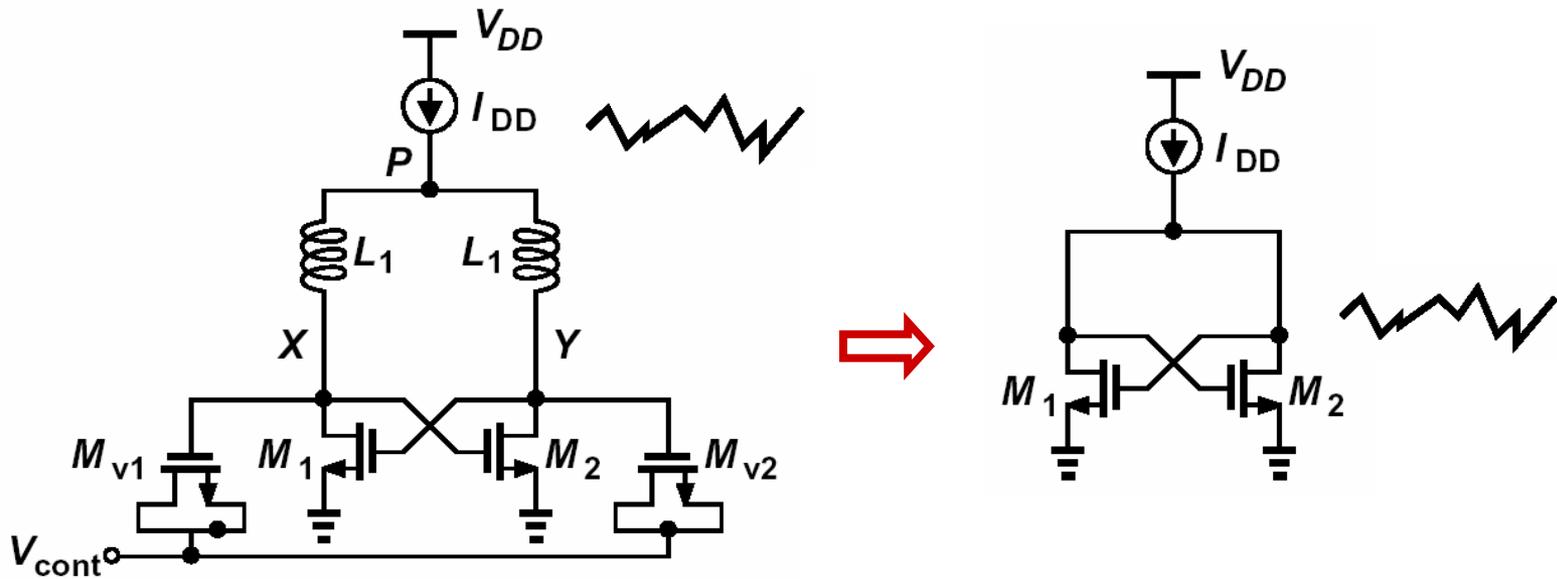


$$\Delta V = \frac{1}{g_m} \frac{i_n(t)}{2} \Rightarrow V_{out}(t) = V_0 \cos \left[\omega_0 t + \int K_{VCO} \frac{i_n(t)}{2g_m} dt \right]$$

$$V_{out}(t) \approx V_0 \cos \omega_0 t - V_0 \frac{K_{VCO}}{2g_m} \left[\int i_n(t) dt \right] \sin \omega_0 t \Rightarrow S_{\phi_n}(f) = \left(\frac{K_{VCO}}{2g_m} \frac{1}{2\pi f} \right)^2 \frac{\alpha}{f}$$

- Noise of current mirror becomes the dominant source.
- Does this effect exist in Type I VCO?

VCO Type III

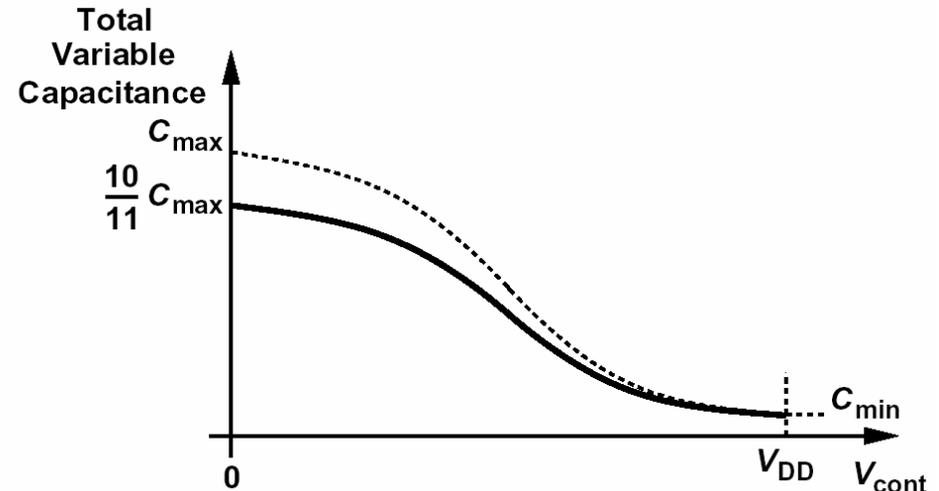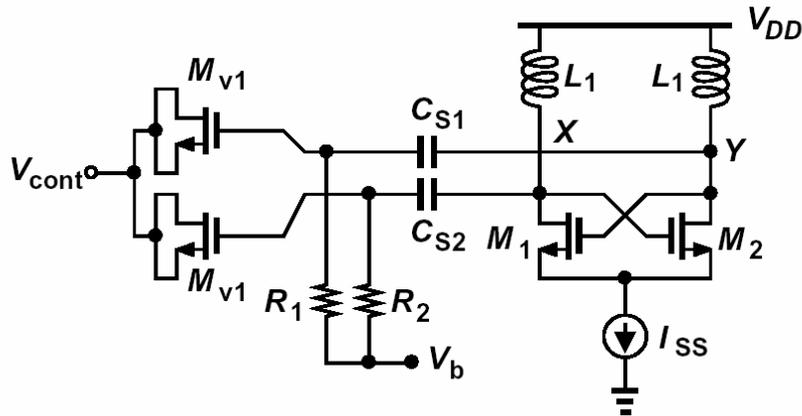


- **Tuning range:**

$$\Delta\omega_{osc} \approx \frac{1}{\sqrt{L_1 C_1}} \cdot \frac{1}{2C_1} \cdot \frac{C_S^2 (C_{var2} - C_{var1})}{(C_S + C_{var2})(C_S + C_{var1})}$$



- **With 5% bottom-plate parasitic cap:**

$$\Delta\omega_{osc} \approx \frac{1}{\sqrt{L_1 (C_1 + 0.5C_{max})}} \times \frac{0.43C_{max}}{2(C_1 + 0.5C_{max})}$$



VCO Type IV

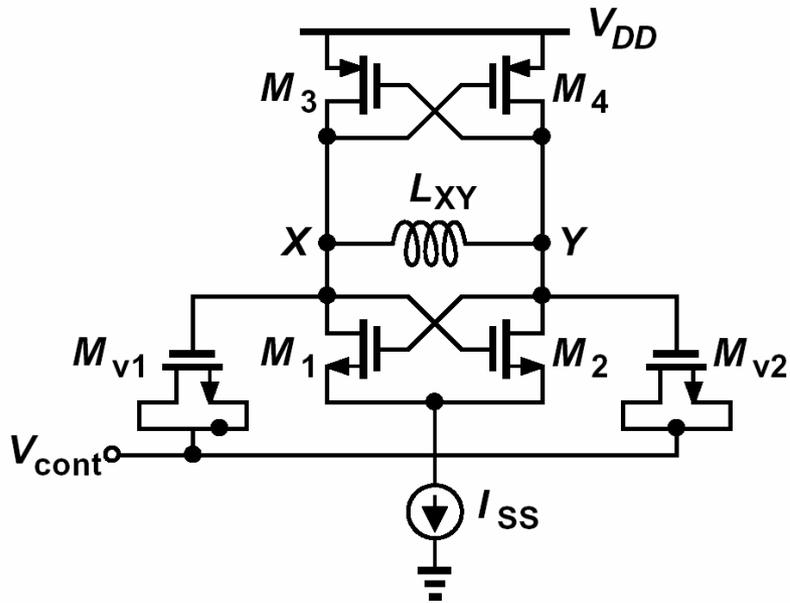

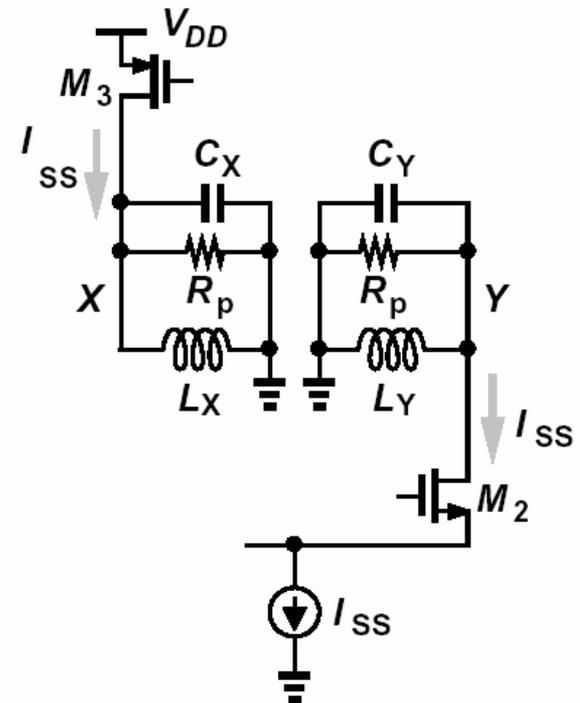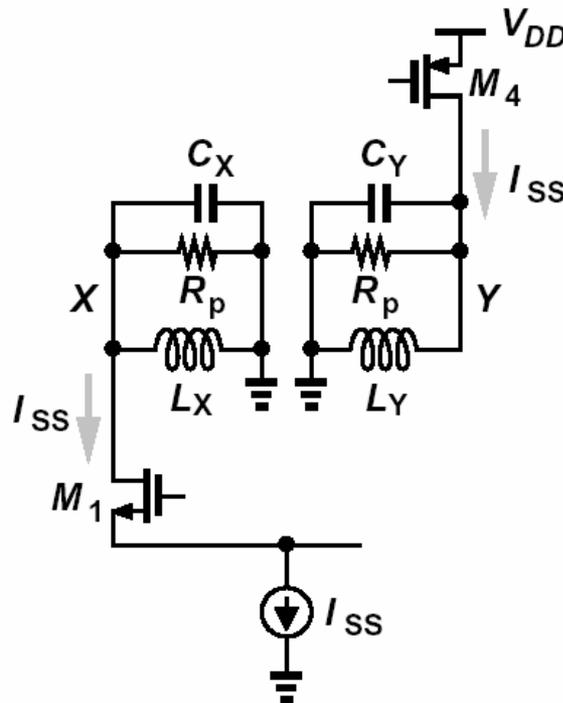
- Select device dimensions to set the output CM level to about $V_{DD}/2$.
- Output swing twice that of previous topologies.
- But tail noise modulates varactors.



Discrete Tuning

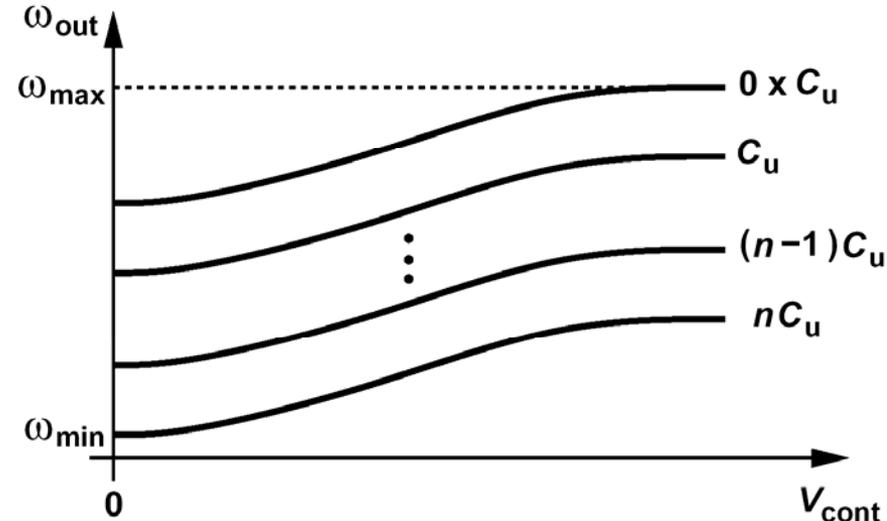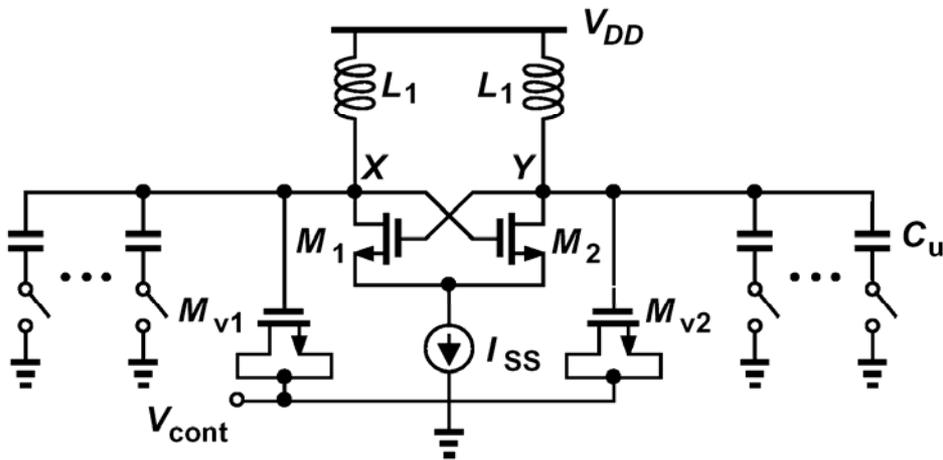

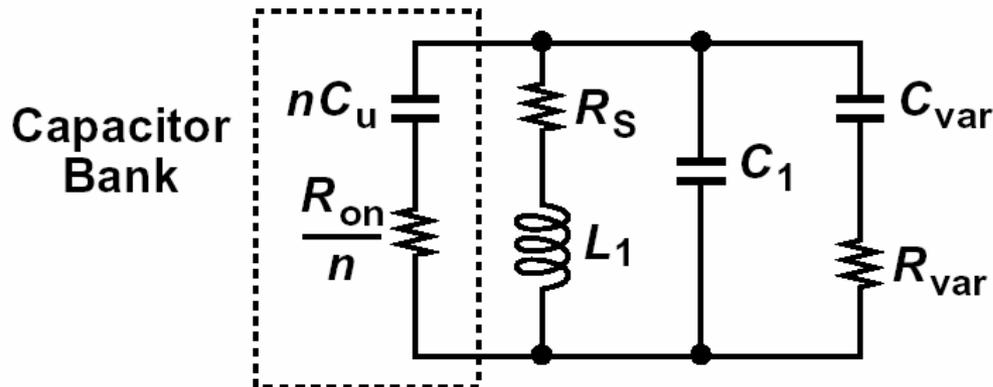- But on-resistance of switches lowers tank Q:



$$\begin{aligned} \frac{1}{Q_{tot}} &= \frac{1}{Q_L} + \frac{1}{Q_{var}} + \frac{1}{Q_{caps}} \\ &= \frac{R_S}{L_1 \omega} + R_{var} C_{var} \omega + R_{on} C_u \omega \end{aligned}$$

Use of "Floating" Switch

