 


# LTspice: Using .MEAS and .STEP Commands to Calculate Efficiency

by **Gabino Alonso**

Predicting the efficiency of an application is vital to evaluating design trade-offs of a switching mode power supply. Two useful tools, the `.step` and `.meas` commands, can be used to calculate and plot efficiency over a range of load currents.

To evaluate efficiency, clearly label your input and output voltage net as *IN* and *OUT*, respectively. Press **F4** to place net names. Replace your resistive load with an independent current source as shown below and define the value using a global variable `{Iload}`. Press **F2** and type `load2` in the search box to select and place the component. Edit the component value by right-clicking on the symbol and enter the variable `{Iload}`. Note the names of the input voltage source (*V1*) and the load current source (*I1*).



The `.step` command is useful for sweeping a variable across a range of values in a single simulation run. The variable can be temperature, a model parameter, a global parameter or in our case an independent source. These steps can be defined as linear, logarithmic or as a list of specific values.

Insert a `.step` command into your schematic as a SPICE directive and step the independent current source from a light load to maximum current load and define the step increments. (You can use the **S** hotkey to add and place a SPICE directive.)

Here, we step the independent current source, *I1*, from 0.2A to 1.2A in 0.1A increments using a global variable defined as `{Iload}`. The `param` directive is used here in the `.step` command to allow for the creation of this user-defined variable. Please see the help file (**F1**) for more details on `.step` command and `param` directive.

```
.step param Iload .2 1.2 .1
```

It is important to calculate efficiency when the circuit is operating in a steady state. To ensure this, simulate your circuit, and note when steady state is achieved for all conditions in the `.step` command, extending simulation stop time if needed. Use this observation to set the "time to start saving data" and "stop time" to encompass a short duration within the observed steady state period. In the `.tran` statement below, we start to save data at 2ms and stop at 2.1ms.

```
.tran 0 2.1m 2m startup
```


The `.meas` command is useful for measuring a range over the abscissa (as well as one point on the abscissa). Add the following expressions as a SPICE directive to calculate the average input power (*Pin*), average output power (*Pout*) and the efficiency (*Eff*). Please note the current direction convention for the input voltage source, *V1*, is into the device, hence the negative sign in the *Pin* calculation. The final expression calculates the efficiency using the `param` directive for clarity. Run your simulation. Please see the help file (**F1**) for more details on `.meas` command.

```
.meas Pin AVG -V(IN)*I(V1)
.meas Pout AVG V(OUT)*I(I1)
.meas Eff param Pout/Pin
```

Once the simulation completes, right-click one of the windows, select view and select *Spice Error Log* (or use the **Ctrl+L** hotkey). The *Spice Error Log* contains data points for the `.meas` statements to include the efficiency calculations.

step	pout/pin
1	0.92574
2	0.938018
3	0.942728
4	0.941408
5	0.939225
6	0.938991
7	0.935248
8	0.932547
9	0.93128
10	0.930117
11	0.927577

 One neat feature of LTspice is the ability to plot the stepped `.meas` data over the abscissa (*Iload*). To plot the data, right-click the error log and select the *Plot stepped .meas data*, right-click on the blank screen to select *Add Trace* (or use **Ctrl+A**) and select *Eff*. This will display the efficiency calculation over stepped load current.



Of course, calculating efficiency is only one example. The `.meas` and `.step` commands can be combined in countless other ways to characterize your analog circuit designs.

## Author



**Gabino Alonso**



## Ahead of What's Possible

15,000

Problem Solvers

4,700+

Patents Worldwide

125,000

Customers

50+

Years

Analog Devices is a global leader in the design and manufacturing of analog, mixed signal, and DSP integrated circuits to help solve the toughest engineering challenges.

See the Innovations

Analog Devices. Dedicated to solving the toughest engineering challenges.

### SOCIAL



### QUICK LINKS

- About ADI
- Analog Dialogue
- Contact us
- News Room
- Sales & Distribution
- Alliances
- Careers
- Investor Relations
- Quality & Reliability

### LANGUAGES

- English
- 简体中文
- 日本語
- Русский

### NEWSLETTERS

Interested in the latest news and articles about ADI products, design tools, training and events? Choose from one of our 12 newsletters that match your product area of interest, delivered monthly or quarterly to your inbox.

Sign Up