



Es gilt

$$P_L = U_L \cdot I = I^2 \cdot R_L = \frac{U_0^2}{(R + R_L)^2} \cdot R_L$$

$R_L \Rightarrow$ Widerstand NCT
von $182,6 \Omega$
bis $10 k\Omega$

$$\frac{dP_L}{dR_L} = U_0^2 \cdot \left(\frac{1}{(R + R_L)^2} - \frac{2R_L}{(R + R_L)^3} \right)$$

$$= U_0^2 \cdot \left(\frac{R_L + R - 2R_L}{(R + R_L)^3} \right)$$

$$= U_0^2 \cdot \left(\frac{R - R_L}{(R + R_L)^3} \right)$$

$$\Rightarrow \frac{dP_L}{dR_L} = 0 \quad \text{wenn} \quad R = R_L$$

... also

$$P_{Lmax} = \frac{U_0^2}{(2R)^2} \cdot R = \frac{U_0^2}{4R}$$

$$\Rightarrow R = \frac{U_0^2}{4 \cdot P_{Lmax}}$$

$$P_{Lmax} \leq 15 mW$$

$$R \geq \frac{U_0^2}{4 \cdot P_{Lmax}} \geq \frac{(3,3V)^2}{4 \cdot 15 \cdot 10^{-3} W} = 181,5 \Omega$$