X2Y® Component Connection and PCB Layout Guidelines

Best practices for EMI filtering and IC bypass/ decoupling applications





Common X2Y® Circuit Uses

EMI FILTERING


Conducted and Radiated Emission Filtering RFI Susceptibility Filtering



Systems with separate ground

External + Line + External - Line Bulkhead or Device Pins

Systems without separate ground

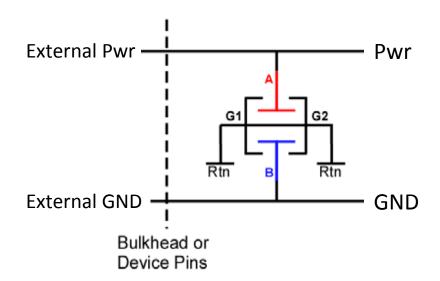


A/B terminations attach to pairs of signal or power conductors G1/G2 terminations attach to GND (0V reference)

For circuits having just power and GND (two conductors only), the A/B terminations attach to the power & GND return wires and the G1/G2 terminations attach to the board GND (0V reference)

Trace - Via Layouts, EMI Filtering

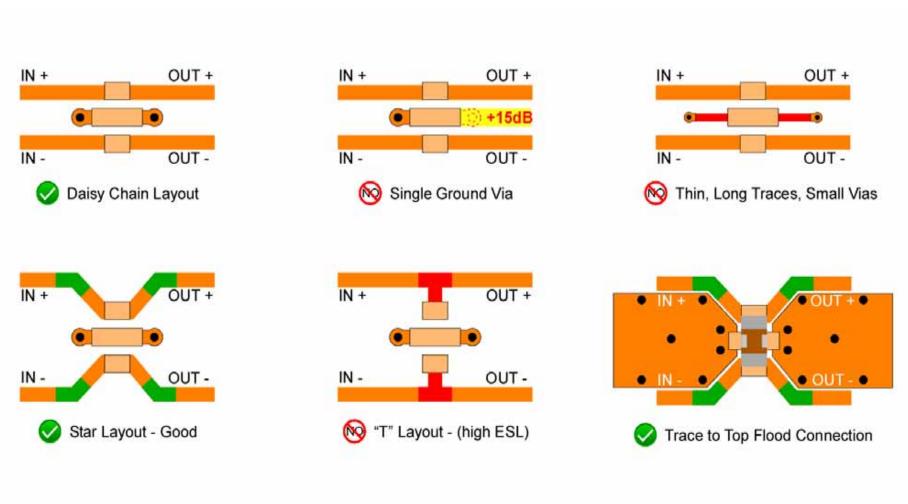The following are key elements of Good Mounting Practice when applying X2Y components with traces and vias on the PCB.



Source: NEW - X2Y EMI Filter Evaluation & Design Guide for comprehensive information






Common X2Y® Circuit Uses

BYPASS / DECOUPLING

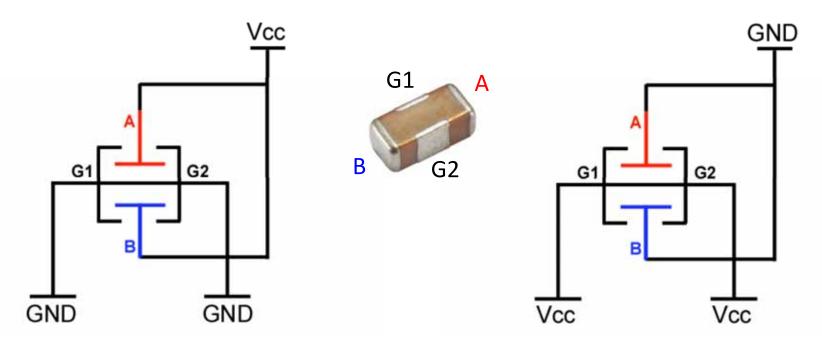There are two basic connection options for power bypass, either is equally effective.




Often used for inner-plane bypassing

More convenient when bypassing a surface power trace

Trace - Via Layouts, Bypass / Decoupling

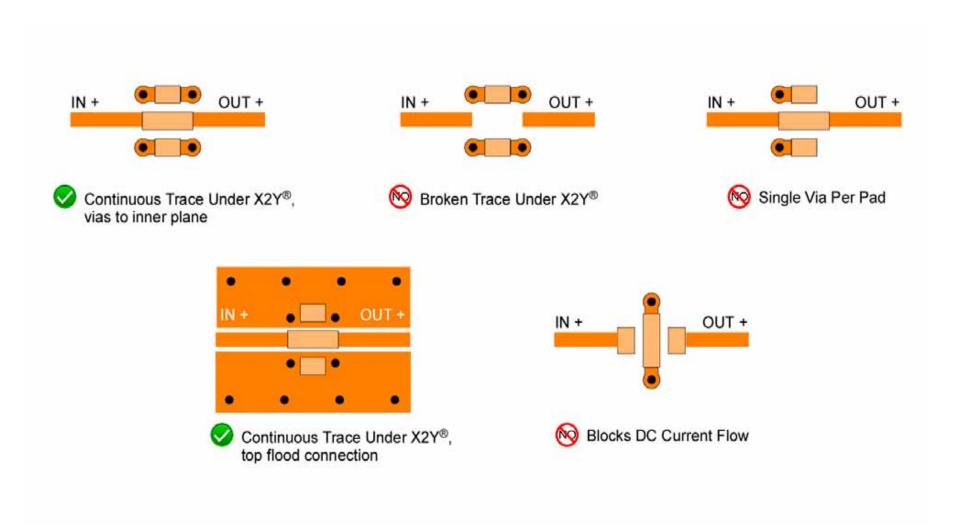The following are key elements of Good Mounting Practice when applying X2Y components with traces and vias on the PCB.




Source: Source: NEW - X2Y EMI Filter Evaluation & Design Guide for comprehensive information





Via Layouts, Bypass / Decoupling

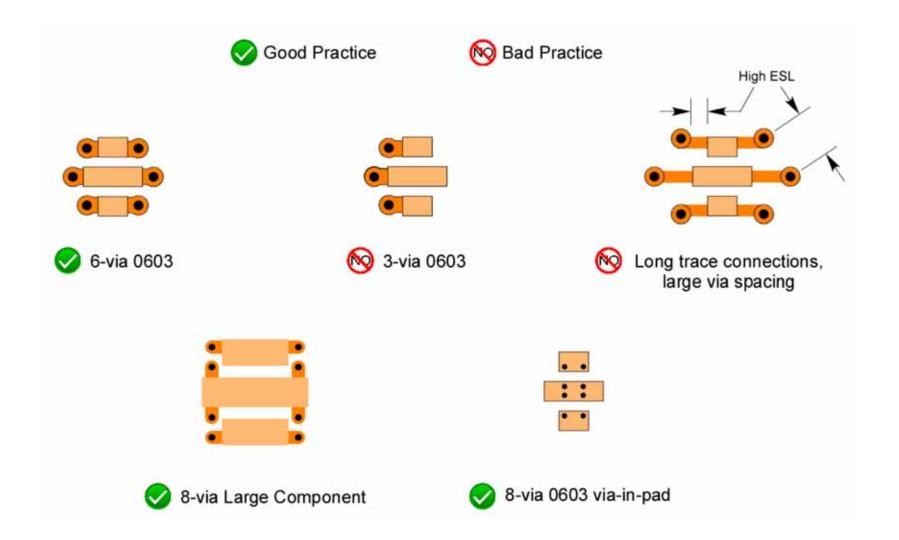The following are key elements of Good Mounting Practice when applying X2Y components with vias on the PCB.








Trace - Via Layout Summary

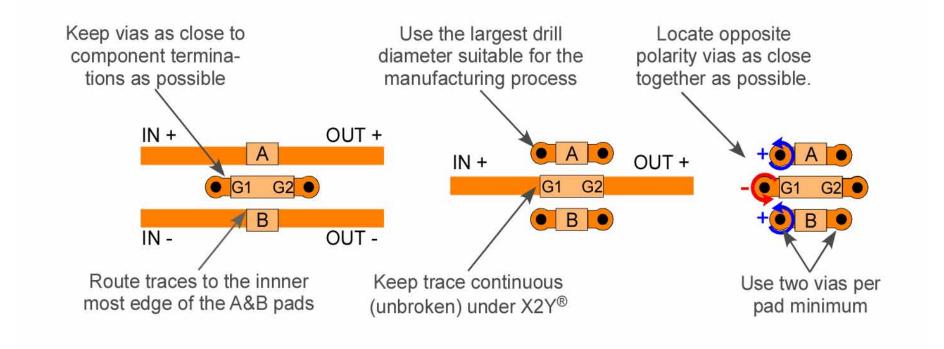The following are key elements of Good Mounting Practice when applying X2Y components with traces and vias on the PCB.



5/19/15


X2Y Component & Pad Sizes

PHYSICAL DIMENSIONS		0402 (X07)		0603 (X14)		0805 (X15)		1206 (X18)		1210 (X41)		1410 (X44)		1812 (X43)	
		IN	mm	IN	mm	IN	mm	IN	mm	IN	mm	IN	mm	IN	mm
CHIP	L	0.045 ±.003	1.143 ±.076	0.064 ±.005	1.626 ±.127	0.080 ±.008	2.032 ±.203	0.124 ±.010	3.150 ±.254	0.125 ±.010	3.175 ±.254	0.140 ±.010	3.556 ±.254	0.174 ±.010	4.420 ±.254
	w	0.025 ±.003	0.635 ±.076	0.035 ±.005	0.889 ±.127	0.050 ±.008	1.270 ±.203	0.063 ±.010	1.600 ±.254	0.098 ±.010	2.489 ±.254	0.098 ±.010	2.490 ±.254	0.125 ±.010	3.175 ±.254
	Т	0.020 max.	0.508 max.	0.026 max.	0.660 max.	0.040 max.	1.016 max.	0.050 max.	1.270 max.	0.070 max.	1.778 max.	0.070 max.	1.778 max.	0.090 max.	2.286 max.
	EB	0.008 ±.003	0.203 ±.076	0.010 ±.006	0.254 ±.152	0.012 ±.008	0.305 ±.203	0.016 ±.010	0.406 ±.254	0.018 ±.010	0.457 ±.254	0.018 ±.010	0.457 ±.254	0.022 ±.012	0.559 ±.305
	СВ	0.012 ±.003	0.305 ±.076	0.018 ±.004	0.457 ±.102	0.022 ±.005	0.559 ±.127	0.040 ±.005	1.016 ±.127	0.045 ±.005	1.143 ±.127	0.045 ±.005	1.143 ±.127	0.045 ±.005	1.143 ±.127
SOLDER PAD	Х	0.020	0.51	0.035	0.89	0.050	1.27	0.065	1.65	0.100	2.54	0.100	2.54	0.125	3.18
	Υ	0.020	0.51	0.025	0.64	0.035	0.89	0.040	1.02	0.040	1.02	0.040	1.02	0.040	1.02
	G	0.024	0.61	0.040	1.02	0.050	1.27	0.080	2.03	0.080	2.03	0.100	2.54	0.130	3.30
	٧	0.015	0.38	0.020	0.51	0.022	0.56	0.040	1.02	0.045	1.14	0.045	1.14	0.045	1.14
	U	0.039	0.99	0.060	1.52	0.080	2.03	0.120	3.05	0.160	4.06	0.160	4.06	0.190	4.83
	Z	0.064	1.63	0.090	2.29	0.120	3.05	0.160	4.06	0.160	4.06	0.180	4.57	0.210	5.33
X U V V V V V V V V V V V V V V V V V V					Solder mask beneath component should be avoided or minimized to reduce flux & contaminant entrapment.										

5/19/15

© X2Y Attenuators, LLC

Examples 1, 2: Dual-Line EMI Filtering

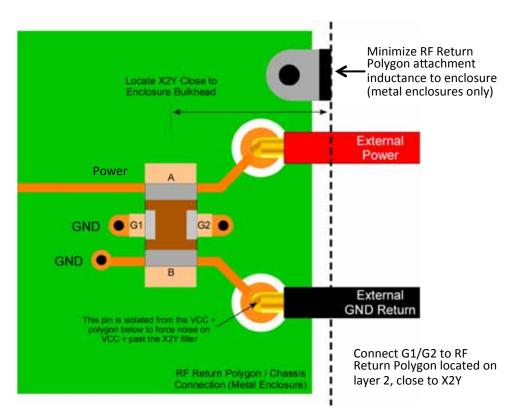

Internal
Signal A

A

External
Signal B

External
Signal B

RF Return Polygon / Chassis
Connection (Metal Enclosure)


1) Dual-Line EMI filtering of two conductor power feed.

2) Dual-Line EMI filtering of two conductor signal feed.


Note: Read X2Y® Capacitors vs. Common Mode Filters (sldes 75-78)



Dual-Line EMI Filtering Example 3

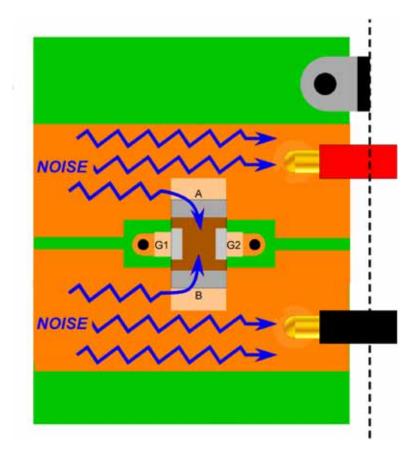





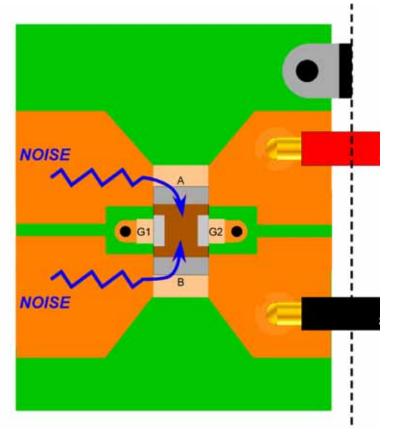



This design focuses the RF noise energy to X2Y filter

Examples 4,5: Dual Line EMI Filtering

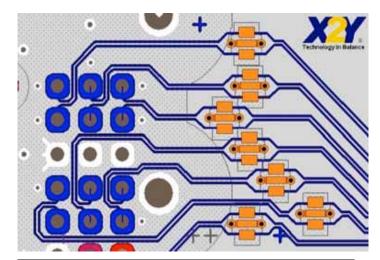

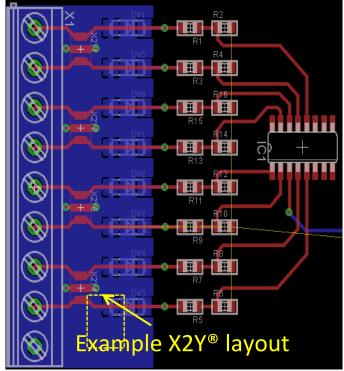


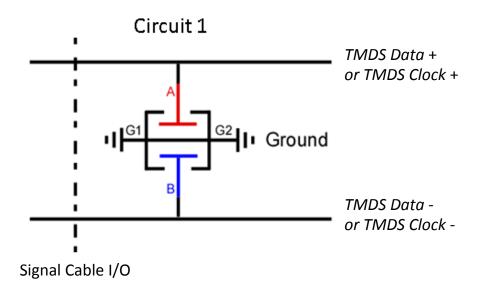


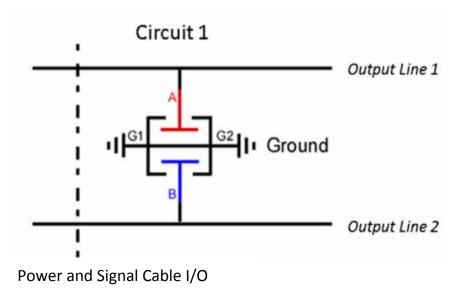



Example 6: EMI Filter & Pwr Bypass

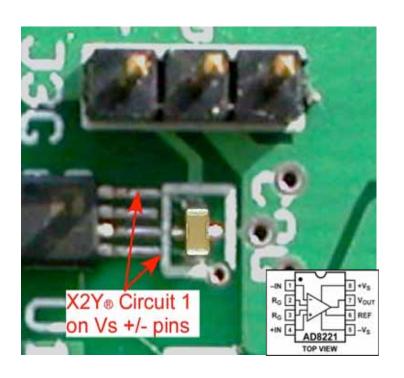


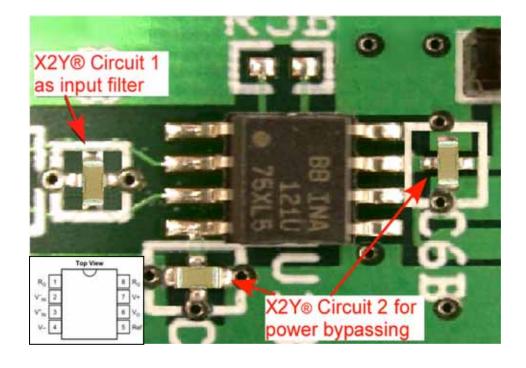


IC +/- power pins on same side: Single X2Y replaces 4 MLCCs, bypassing both the power rails. X2Y applied as dual-line input filter. IC +/power pins on opposite sides, X2Y is
applied in bypass on each power rail.

IC Power Bypass: Inner Planes Attachment

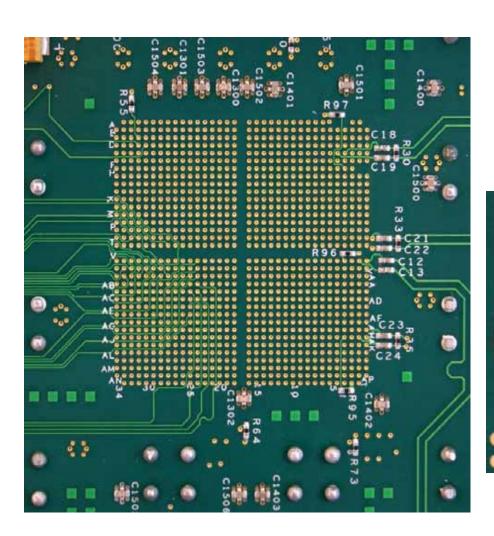
Multiple X2Y components are attached between the inner Vcc an GND planes on this PCB for FPGA power bypassing.



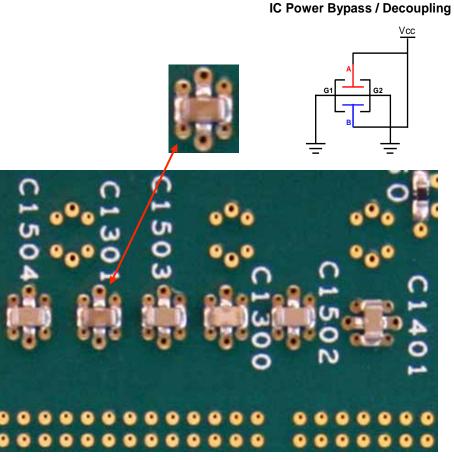


5/19/15


IC & Connector Pin Placement

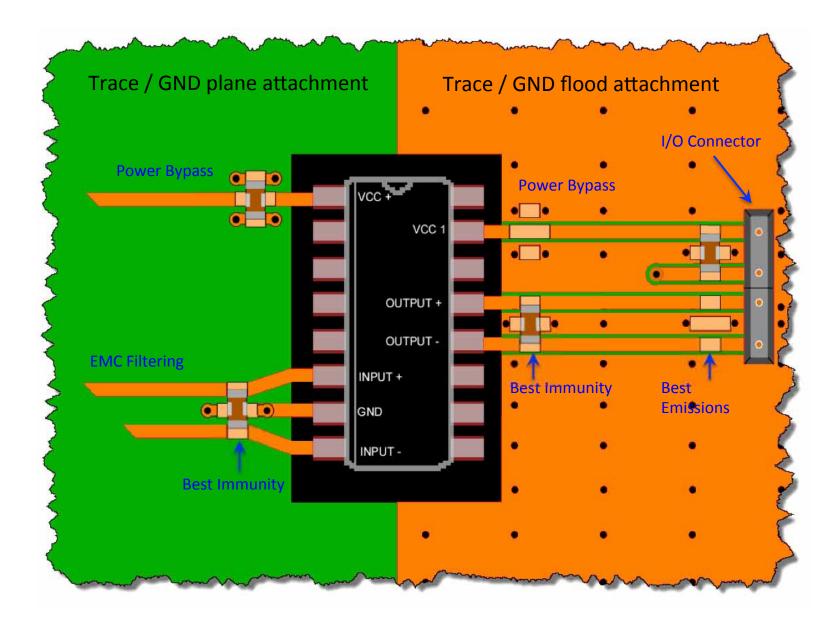



IC Power Bypass: Reduced EMC

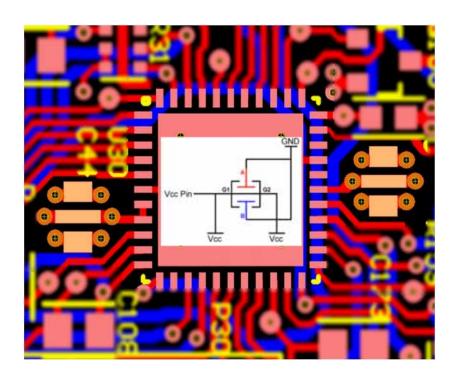

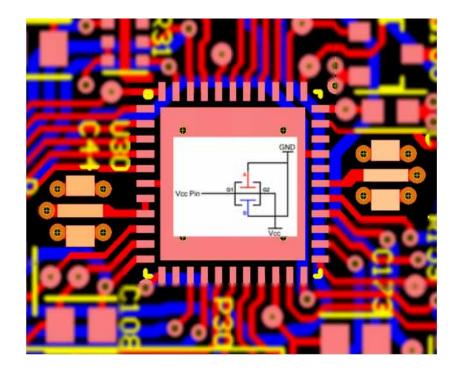


Using 6-vias and a continuous trace under the X2Y results in the **lowest PDN impedance** to GND

Using **5-vias**, removing via between the IC pin and X2Y, maximizes **RF noise immunity**. All noise must first go through the X2Y filter before reaching the IC power pin.

IC Power Bypass: BGA Layout with X2Y

0402 Size X2Y, 1 mm pitch

0603 Size X2Y, 1mm pitch

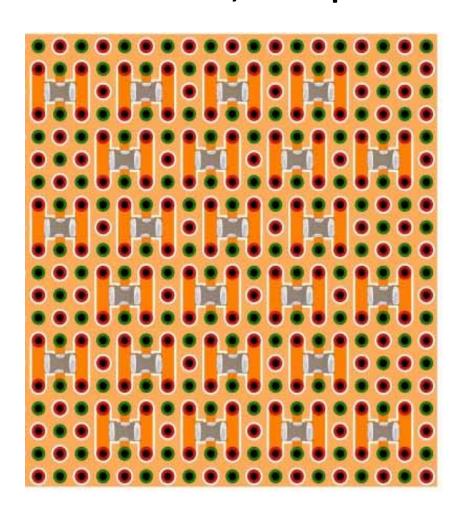

Source: X2Y® Capacitors in IC Back-Side Mounting Applications



5/19/15

We're here to help

Johanson provides first time adopters with application engineering assistance including part selection, schematic design review and PCB layout review.

Contact your local field sales representative for more information.

Thank You for your interest in the X2Y® Solution



Steve Cole Sr. FAE & BDM X2Y Components

Tel: (603) 433-6328

Email: scole@johansondielectrics.com Website: http://www.johansondielectrics.com



