


Biasing networks

- Biasing networks are needed to set appropriate operating conditions for active devices

There are two types:


- Passive biasing (or self-biasing)
 - resistive networks
 - drawback: poor temperature stability
- Active biasing
 - additional active components (thermally coupled)
 - drawback: complexity, added power consumption

Passive biasing

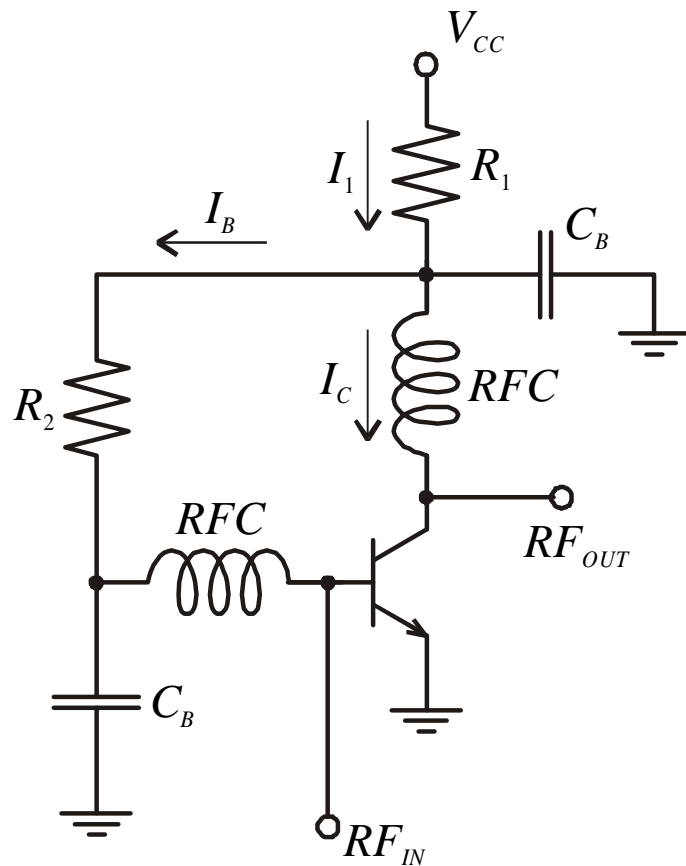

- Simple two element biasing
- blocking capacitors C_B and RFCs to isolate RF path
- Very sensitive to collector current variations


Passive biasing

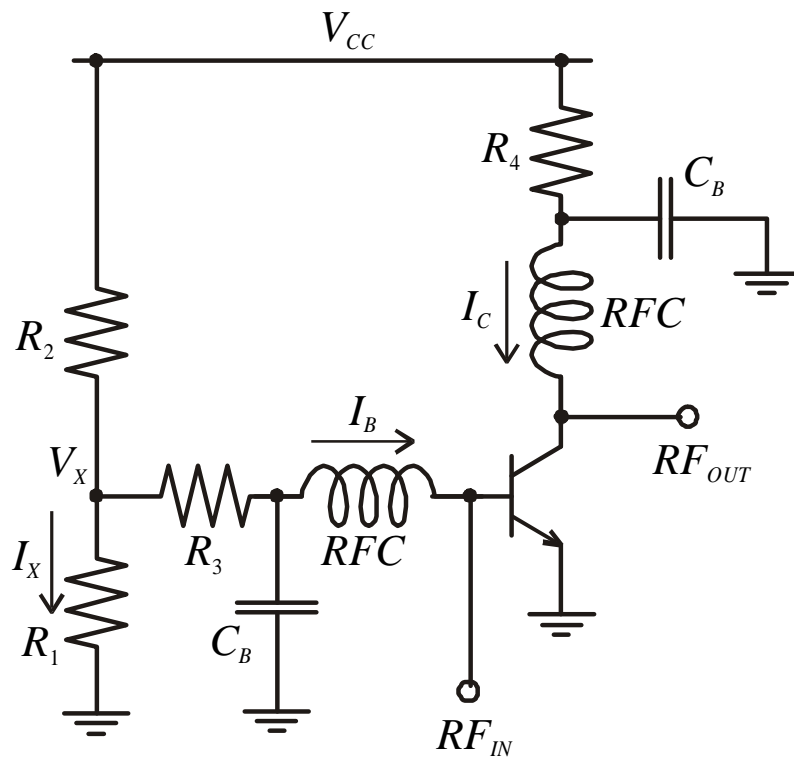

$$I_B \sim 10 I_X$$


- Voltage divider to stabilize V_{BE}
- Freedom to choose suitable voltage and current settings (V_X , I_X)
- Higher component count, more noise susceptibility

Active biasing

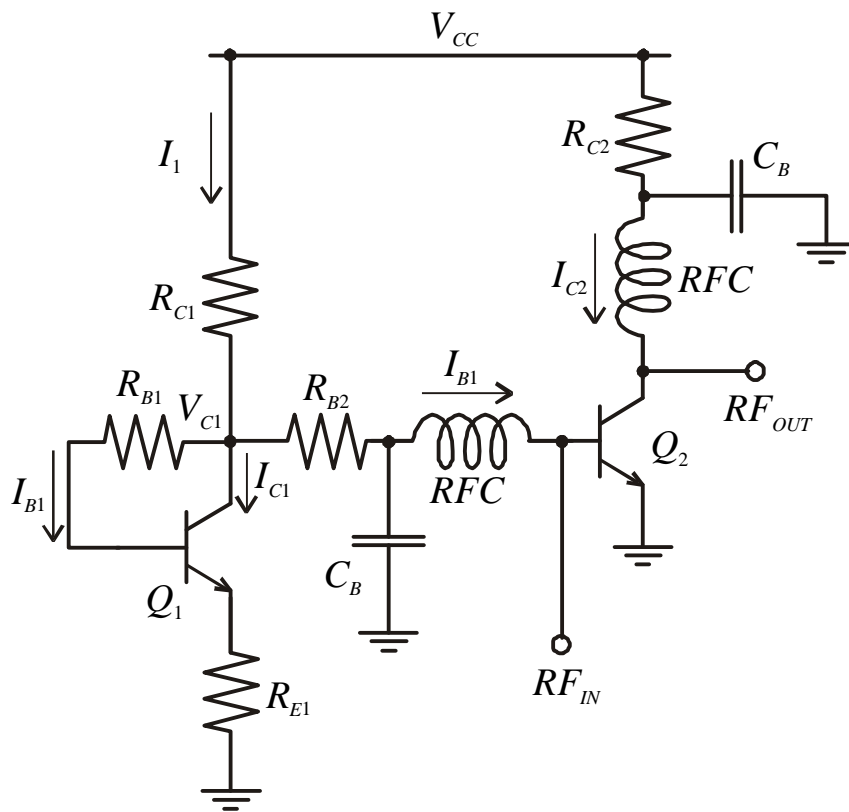


- Base current of RF BJT (Q_2) is provided by low-frequency BJT Q_1
- Excellent temperature stability (shared heat sink)
- high component count, more complex layout

Active biasing in common base

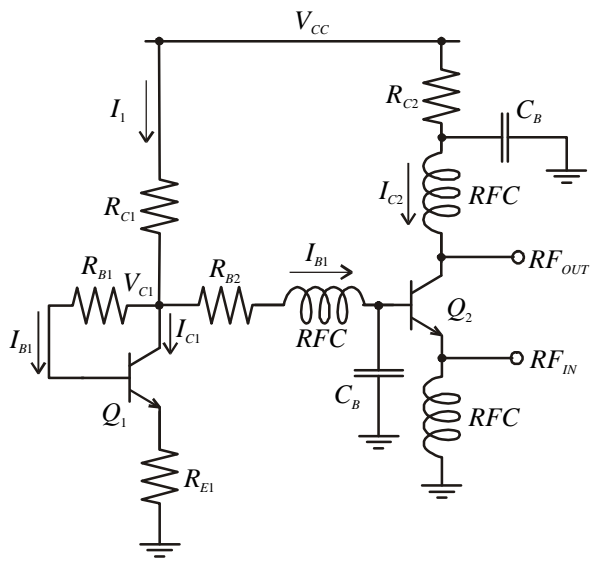


DC path

RF path

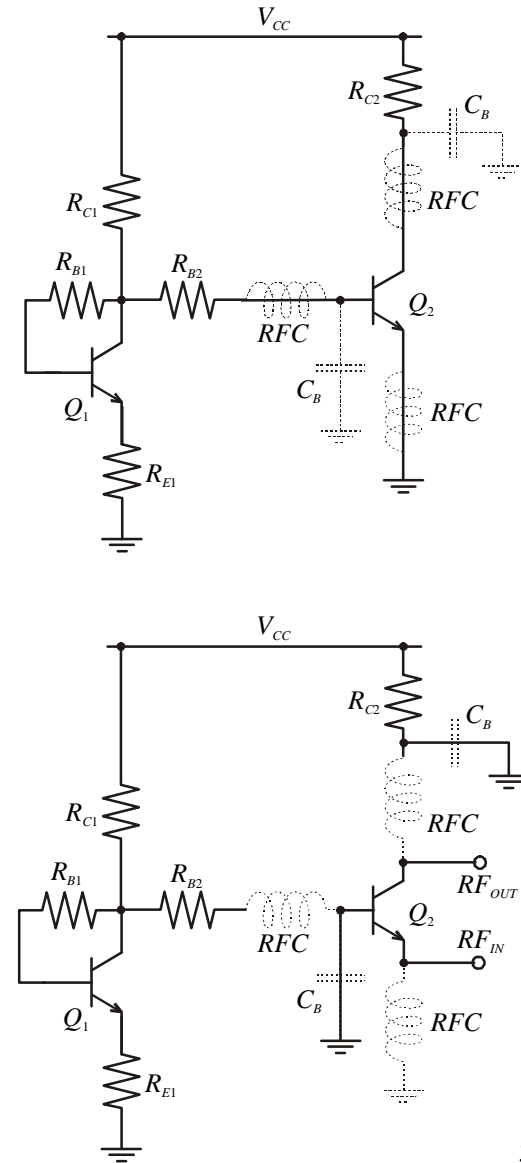



FET biasing

Bi-polar power supply

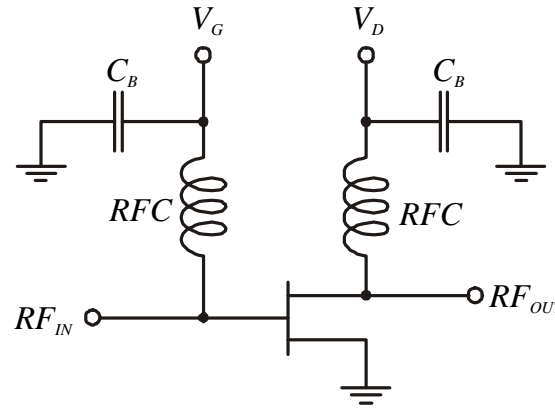


$V_G < 0$ and $V_D > 0$

Uni-polar power supply

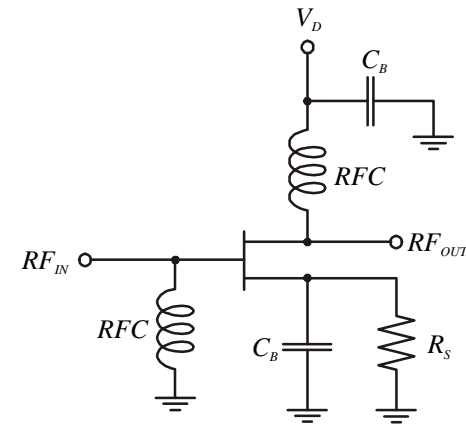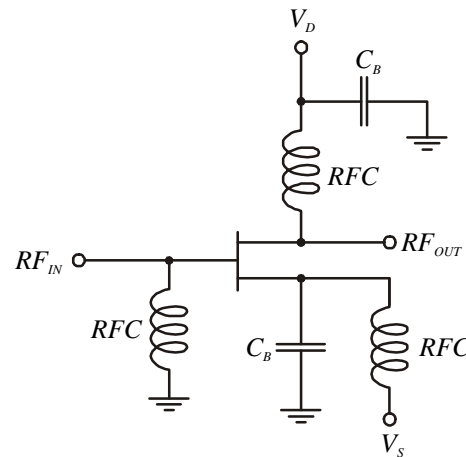


Matching to Self-Biased BJT Amp

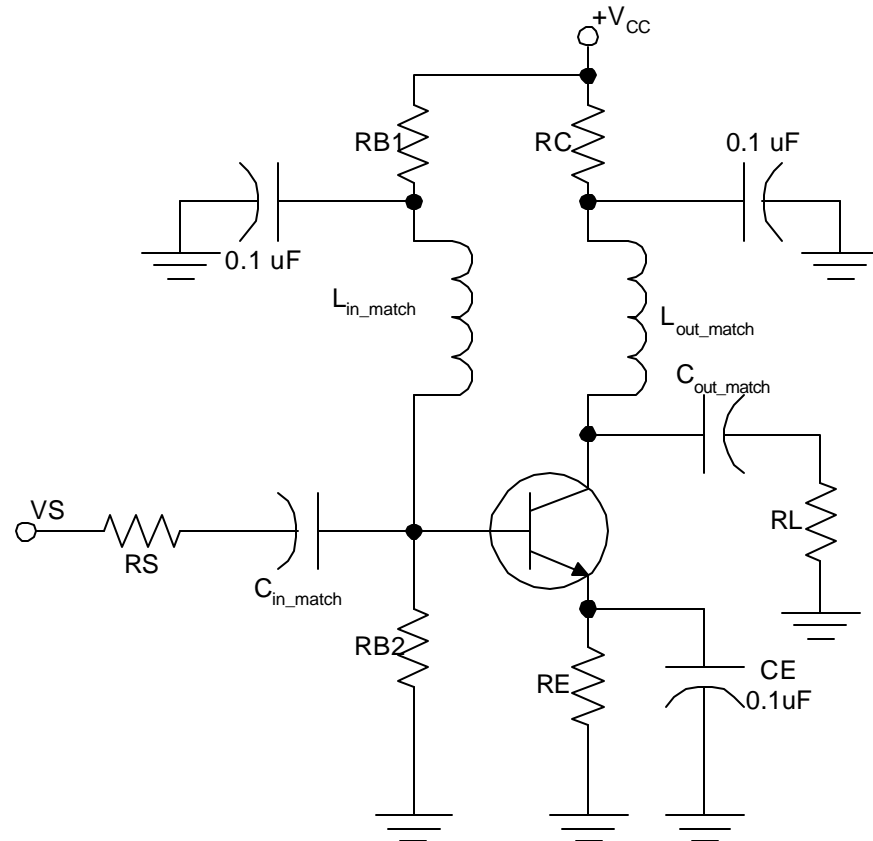- Design self-bias circuit as usual
- Design input and output matches to S_{11} and S_{22} respectively




Equivalent RF Model of BJT Amp

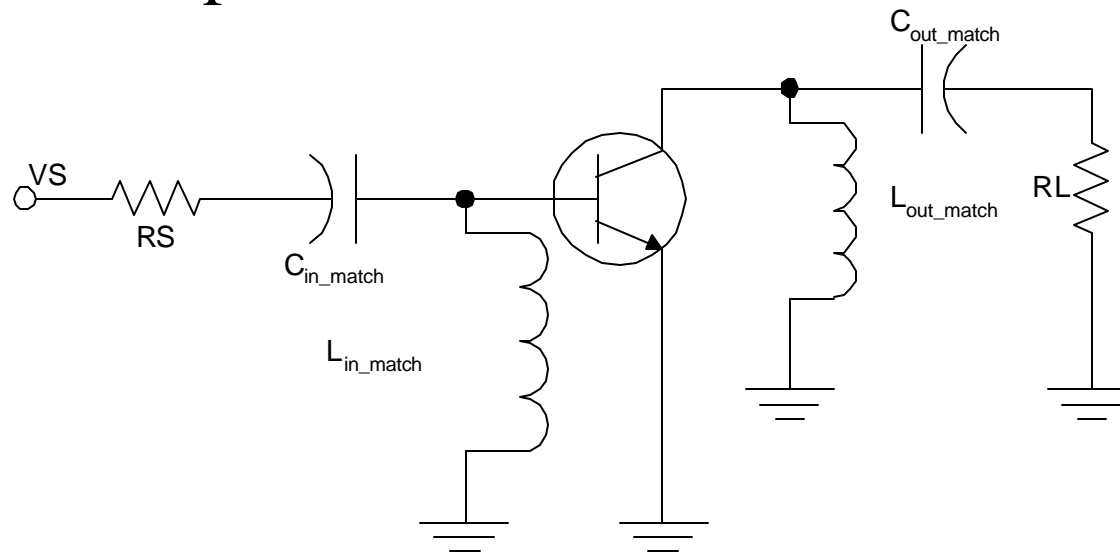- The equivalent RF model of the self-biased BJT amp is shown. Note that bias resistors do not affect RF performance




Matching to Self-Biased JFET Amp

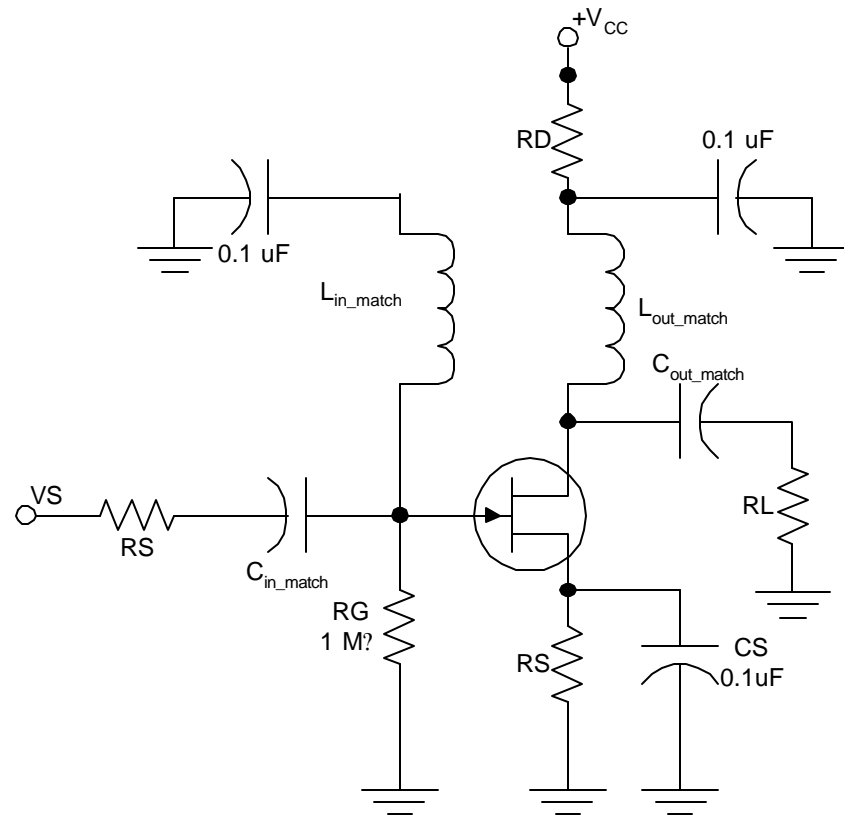- Design self-bias circuit as usual
- Design input and output matches to S_{11} and S_{22} respectively



Equivalent RF Model of JFET Amp

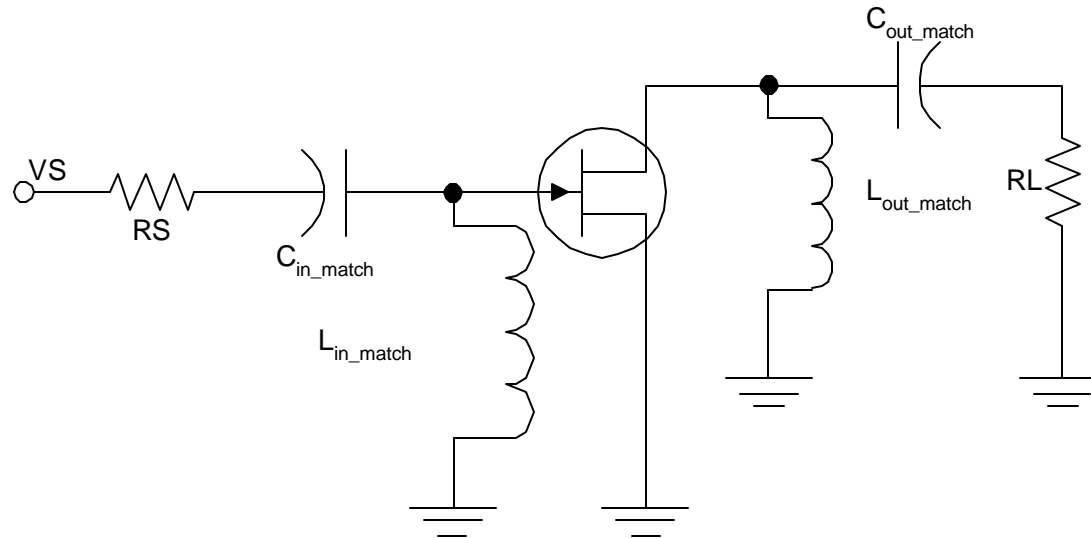- The equivalent RF model of the self-biased JFET amp is shown. Note that bias resistors do not affect RF performance



Matching Networks for Amplifiers

- Conjugate matching must be used for maximum power transfer
- Standard impedance matching using either two element L-C, Pi- or Tee-type network, or microstripline matching.
- Use Smith Charts with associated Node Quality Factor Q_n to determine network

Stub Tuner Matching for RF BJT Amp

- Can implement impedance matching network with microstriplines
- Shown is single stub tuner with shorted stub

